

ECE/ENGRD 2300
Digital Logic & Computer Organization
Spring 2025

Boolean Algebra



Cornell University

Announcements





- **Course staff email <ece2300-staff-L@cornell.edu> is active now**
- **HW 1 will be released on CMS today**
- **Labs and office hours start next week**
 - **More logistics will be posted on Ed soon**

Review: Digital Abstraction

- Typically digital implies a *binary system* (base 2)
 - Only 2 recognized values (logic levels)
 - High / Low
 - True / False
 - On / Off
 - ...
- Logic levels are particular voltage ranges
 - Don't allow "0" to be easily mistaken for a "1" or vice versa

Fun Facts: Number Bases

- Digital computers represent numbers in binary
- We count in 10
- Mayans used positional notation based on 20


0	1	2	3	4
	•	••	•••	••••
5	6	7	8	9
	•	••	•••	••••
10	11	12	13	14
	•	••	•••	••••
15	16	17	18	19
	•	••	•••	••••

Maya numerals



Review: Logic Gates

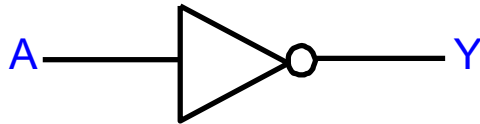
- Logic gates are functions: take one or more binary inputs and produce a binary output
 - Note that the input values are not constants



NOT Gate


A'	
A	Y
0	1
1	0

Truth Table

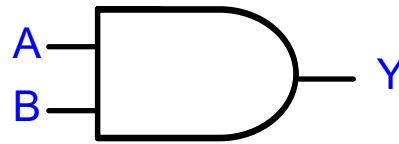

AND Gate

$A \cdot B$		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

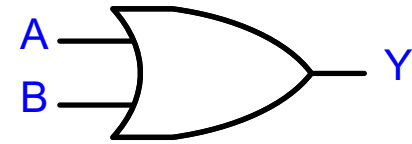

OR Gate

$A + B$		
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Exercise: Truth Table

- Write down the truth table for a three-input function $F = f(A,B,C)$ that outputs
 - $F = 1$ if $(A \cdot B)$ is equal to $(B + C')$
 - $F = 0$ otherwise
- Fill out the blank entries

ABC	F
000	0
001	1
010	0
011	0
100	
101	1
110	
111	1

Boolean Algebra

- **Mathematical foundation for analyzing and simplifying digital circuits**
- **Boolean algebra (George Boole, 1854)**
 - **Two-valued algebraic system**
 - **Used to formulate true or false postulations**
- **Switching algebra (Claude Shannon, 1938)**
 - **Adopted Boolean algebra for digital circuits in his master's thesis "A Symbolic Analysis of Relay and Switching Circuits"**
 - **Terms "Boolean algebra" and "switching algebra" are often used interchangeably**

Basic “Ingredients”

- **Variables that have values of either 1 or 0 (True or False)**
- **Basic operators are AND, OR, and NOT**

Some Important Definitions

- **Literal**: a single variable or its complement
 - e.g., A (positive literal), A' (negative literal)
- **Product term**: AND of (more than one) literals
 - e.g., $A' \cdot B$
- **Sum term**: OR of literals
 - e.g., $A + B + C'$

Operator Precedence

- What does $D \cdot A' + B \cdot C$ mean?
- Operator precedence rules
 1. NOT (highest priority)
 2. AND
 3. OR (lowest)

Some More Definitions

- **Normal term**: Product or sum term in which every variable appears, and exactly once
- **Minterm**: Normal product
 - e.g., $(A \cdot B' \cdot C)$ for a 3-input Boolean function
- **Maxterm**: Normal sum
 - e.g., $(A' + B + C')$

Minterms & Maxterms

ABC	Minterm	name	Maxterm	name
000	$A' \cdot B' \cdot C'$	m_0	$A+B+C$	M_0
001	$A' \cdot B' \cdot C$	m_1	$A+B+C'$	M_1
010	$A' \cdot B \cdot C'$	m_2	$A+B'+C$	M_2
011	$A' \cdot B \cdot C$	m_3	$A+B'+C'$	M_3
100	$A \cdot B' \cdot C'$	m_4	$A'+B+C$	M_4
101	$A \cdot B' \cdot C$	m_5	$A'+B+C'$	M_5
110	$A \cdot B \cdot C'$	m_6	$A'+B'+C$	M_6
111	$A \cdot B \cdot C$	m_7	$A'+B'+C'$	M_7

Each input combination corresponds to a unique minterm/maxterm

Input 0 corresponds to a negative literal in a minterm, 1 to a positive;

The opposite applies to maxterms

Canonical Form of a Boolean Function

- **A canonical form is a distinct representation for a Boolean function, ensuring that**
 - with a fixed ordering of input variables, two equivalent functions have the same form
- **Truth table is a canonical form**
 - e.g., $(A'+B')$ and $(A \cdot B)'$ have the same truth table
 - 2^n rows required for an n-input function
- **Other canonical representations**
 - **Canonical sum**, i.e., canonical sum of products (SOP)
 - **Canonical product**, i.e., canonical product of sums (POS)
 - Other (more) compact forms exist (outside the scope of 2300)

Canonical Sum of a Boolean Function

- Sum of minterms that correspond to the on-set of a function

– **On-set**: the set of input combinations for which the function produces an output of 1

$F = 1$ if one of the input combinations from on-set is selected; Otherwise, $F=0$

(Intuition: $F=1$ when input “hits” the onset)

$$\begin{aligned} F &= A' \cdot B' \cdot C' + A' \cdot B \cdot C + A \cdot B' \cdot C' + A \cdot B \cdot C \\ &= m_0 + m_3 + m_4 + m_7 \\ &= \Sigma_{A,B,C}(0,3,4,7) \end{aligned}$$



ABC	F
000	1
001	0
010	0
011	1
100	1
101	0
110	0
111	1

Canonical Product of a Boolean Function

- Product of maxterms that correspond to the off-set of a function
 - **Off-set**: the set of input combinations for which the function produces an output of 0

$F = 1$ if none of the input combinations from off-set is selected; Otherwise, $F=0$
(Intuition: $F=1$ when input “escapes” the offset)

$$\begin{aligned} F &= (A+B+C') \cdot (A+B'+C) \cdot (A'+B+C') \cdot (A'+B'+C) \\ &= M_1 \cdot M_2 \cdot M_5 \cdot M_6 \\ &= \prod_{A,B,C} (1,2,5,6) \end{aligned}$$

ABC	F
000	1
001	0
010	0
011	1
100	1
101	0
110	0
111	1



Different Forms, Same Function

- The canonical sum and canonical product are distinct (canonical) forms, representing the same function

$$F = \Sigma_{A,B,C}(0,3,4,7) = \Pi_{A,B,C}(1,2,5,6)$$

ABC	F
000	1
001	0
010	0
011	1
100	1
101	0
110	0
111	1

Exercise: Canonical Forms

- Write down the canonical sum & product forms for basic operators NOT, AND, OR

A	F
0	1
1	0

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

Axioms of Boolean Algebra

- **Statements that are assumed true**
- **Obey the principle of duality**
 - **Many axioms come in pairs**
 - **Interchange 1 and 0, AND and OR, still correct**

Axioms of Boolean Algebra

- **Binary**

(A1) $X = 0$ if $X \neq 1$ (A1') $X = 1$ if $X \neq 0$

- **Complement**

(A2) If $X = 0$, then $X' = 1$ (A2') If $X = 1$, then $X' = 0$

Axioms of Boolean Algebra

- AND and OR

$$(A3) \quad 0 \cdot 0 = 0$$

$$(A3') \quad 1 + 1 = 1$$

$$(A4) \quad 1 \cdot 1 = 1$$

$$(A4') \quad 0 + 0 = 0$$

$$(A5) \quad 0 \cdot 1 = 1 \cdot 0 = 0$$

$$(A5') \quad 1 + 0 = 0 + 1 = 1$$

- A1-A5 completely define Boolean algebra
 - Everything else derived from these axioms

Single Variable Theorems

- Identity: (T1) $X \cdot 1 = X$ (T1') $X + 0 = X$
- Null Element: (T2) $X \cdot 0 = 0$ (T2') $X + 1 = 1$
- Idempotency: (T3) $X \cdot X = X$ (T3') $X + X = X$
- Involution: (T4) $(X')' = X$
- Complements: (T5) $X \cdot X' = 0$ (T5') $X + X' = 1$
- Can prove by *perfect induction*
 - Show that all possible inputs meet the theorem

Exercise: Proof by Perfect Induction

$$(T3) \quad X \cdot X = X$$

$$X=0 \rightarrow 0 \cdot 0 = 0$$

$$X=1 \rightarrow 1 \cdot 1 = 1$$

$$(T3') \quad X + X = X$$

$$X=0 \rightarrow 0 + 0 = 0$$

$$X=1 \rightarrow 1 + 1 = 1$$

$$(T5) \quad X \cdot X' = 0$$

$$(T5') \quad X + X' = 1$$

Two and Three Variable Theorems

- **Commutativity**

(T6) $X \cdot Y = Y \cdot X$

(T6') $X + Y = Y + X$

- **Associativity**

(T7) $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

(T7') $(X + Y) + Z = X + (Y + Z)$

- **Distributivity**

(T8) $X \cdot Y + X \cdot Z = X \cdot (Y + Z)$

(T8') $(X + Y) \cdot (X + Z) = X + (Y \cdot Z)$

AND distributes over OR

OR distributes over AND

Two and Three Variable Theorems

- **Covering**

$$(T9) \quad X \cdot (X + Y) = X$$

$$(T9') \quad X + X \cdot Y = X$$

- **Combining**

$$(T10) \quad X \cdot Y + X \cdot Y' = X$$

$$(T10') \quad (X + Y) \cdot (X + Y') = X$$

- **Consensus**

$$(T11) \quad X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$$

$$(T11') \quad (X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$$

Exercise

- Prove algebraically: (T9') $X + X \cdot Y = X$

Exercise

- Prove algebraically: (T9') $X + X \cdot Y = X$

- Solution

$$\begin{aligned} - X + X \cdot Y &\stackrel{\text{T1}}{=} X \cdot 1 + X \cdot Y \stackrel{\text{T8}}{=} X \cdot (1 + Y) \stackrel{\text{T2}'_{(\text{null elements})}}{=} X \cdot 1 \stackrel{\text{T1}}{=} X \end{aligned}$$

(identity) (distributivity) (identity)

De Morgan's Theorem

- Very important, also known as De Morgan's *Law*

$$(T12) \quad (X1 \cdot X2 \cdot \dots \cdot Xn)' = X1' + X2' + \dots + Xn'$$

$$(T12') \quad (X1 + X2 + \dots + Xn)' = X1' \cdot X2' \cdot \dots \cdot Xn'$$

De Morgan Example

- By DeMorgan's Law

$$(X \cdot Y \cdot Z)' = X' + Y' + Z'$$

- Proof by perfect induction

XYZ	$(X \cdot Y \cdot Z)'$	$X' + Y' + Z'$
000	1	1
001	1	1
010	1	1
011	1	1
100	1	1
101	1	1
110	1	1
111	0	0

Next Class

**Combinational Logic Minimization
(H&H 2.4-2.7)**