

ECE 2300
Digital Logic & Computer Organization
Spring 2025

Combinational Building Blocks




Cornell University


Announcements

- Lab 1 released
- HW 1 due tomorrow
- HW 2 will be posted soon

NAND Logic Gate

 

 Using De Morgan's Law: $(X \cdot Y)' = X' + Y'$




We can build circuits from NAND only!

NAND is a Universal Gate


- NOT
- AND
- OR

We can build circuits from NAND only!

NOR Logic Gate

 


 Using De Morgan's Law: $(X+Y)' = X' \cdot Y'$




NOR is also a universal gate
We can build circuits from NOR only!

Sum-of-Products Revisited

 


AND-OR

 


NAND-NAND

Product-of-Sums Revisited

 


OR-AND

 

NOR-NOR

Multi-Level Logic

 - So far we have primarily focused on two-level representations for combinational logic
- Multi-level logic is typically more compact (i.e., cost-efficient) in practice




Combinational Building Blocks

- **More complex functions built from basic gates**
 - Comparators
 - Multiplexers
 - Decoders
 - Encoders
 - ...
- **Typically tens to hundreds of transistors**
 - *Used to be* called Medium Scale Integration (MSI)
- **Common building blocks for digital systems**


XOR Gate

X	Y	$X \oplus Y$	$(X \oplus Y)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

 

- **XOR:** $F = X \cdot Y' + X' \cdot Y$
 - Similar to OR gate, except when inputs are 1
 - Used for comparisons, error checking, etc.
- **XNOR:** $F = X' \cdot Y' + X \cdot Y$
 - Complemented version of XOR

Equality Comparators Using XOR



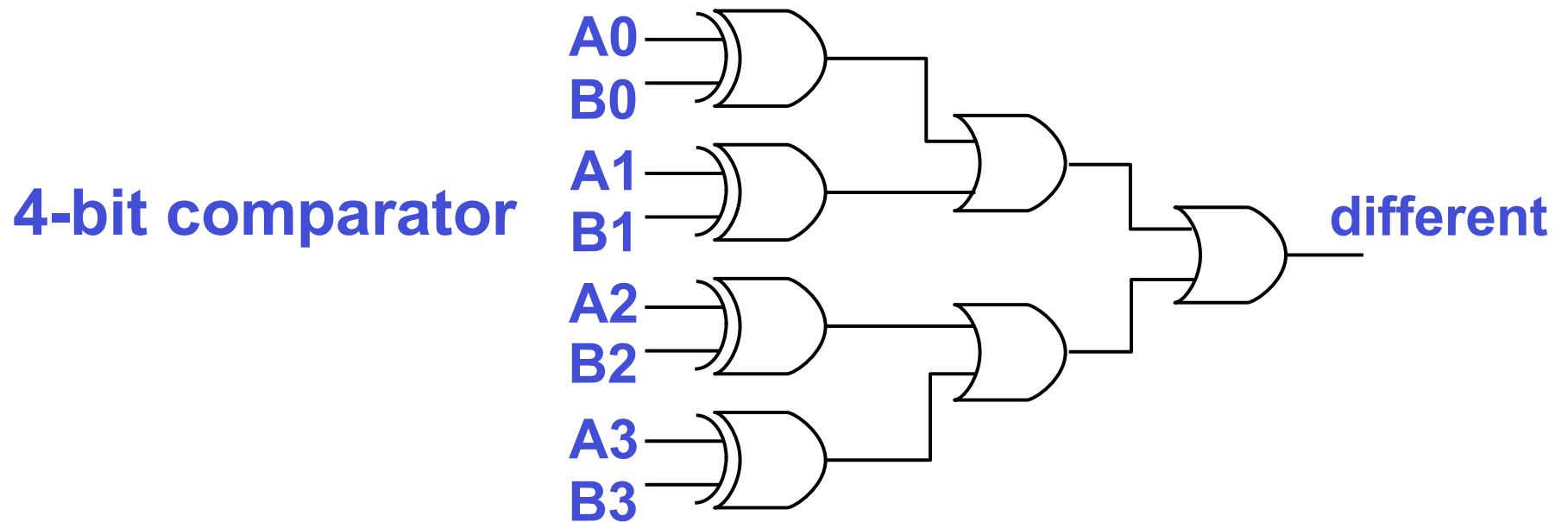


Multiplexer (“mux”)

- **Connects one of n inputs to the output**
 - ***select* control signals pick one of the n sources**
 - $\lceil \log_2 n \rceil$ ***select* bits**
- **Useful when multiple data sources need to be routed to a single destination**
 - **Often arises from resource sharing**
 - **Example: select 1-of- n *data* inputs to an adder**

2-to-1 Mux

  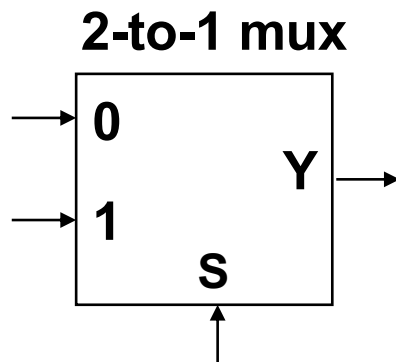
- **Selects one of two inputs to appear at the output**
 - Two data inputs (I_0 , I_1) and one control input (S)
 - Output is I_0 if $S = 0$ and I_1 if $S = 1$





$$Y = S' \cdot I_0 + S \cdot I_1$$

4-to-1 Mux

 - Selects one of four inputs to appear at the output



  
$$Y = S1' \cdot S0' \cdot I0 + S1' \cdot S0 \cdot I1 + S1 \cdot S0' \cdot I2 + S1 \cdot S0 \cdot I3$$



Cascading Multiplexers


 
- Large multiplexers can be implemented by cascading smaller ones



Logic Functions Using Muxes

- Any function of n variables can be implemented with a $2^n:1$ multiplexer
 - Input variables connected to *select* inputs
 - Data inputs tied to 0 or 1 according to truth table

ABC	Y
000	0
001	0
010	0
011	1
100	0
101	1
110	1
111	1

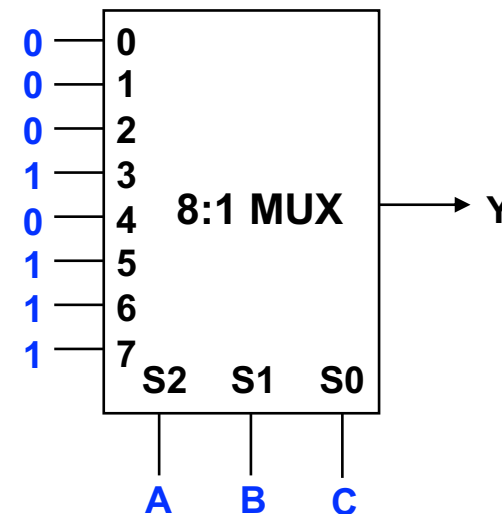
 


Getting Away with a Smaller Mux

- Can use $2^{n-1}:1$ multiplexer and at most one inverter

- Connect $n-1$ input variables to *select* inputs
- Data inputs tied to 0, 1, n^{th} variable, or inverted n^{th} variable

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

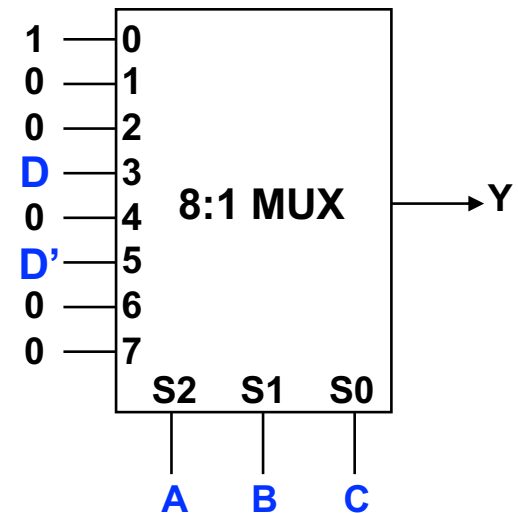 

Decoder

- **Binary decoders**


- n inputs, 2^n outputs
- Each output corresponds to a unique input value
- Only one output is asserted (true) at a time, also known as the *one-hot* scheme

- **Example: A 1-to-2 decoder**

A	Y_1	Y_0
0	0	1
1	1	0

$$Y_0 = A'$$
$$Y_1 = A$$

2-to-4 Decoder

 


A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$Y_0 = A_1' \cdot A_0'$$

$$Y_1 = A_1' \cdot A_0$$


$$Y_2 = A_1 \cdot A_0'$$

$$Y_3 = A_1 \cdot A_0$$

 

Logic Functions Using Decoders

 - **$n:2^n$ decoder can be used to implement any function of n variables**
 - Connect variables to inputs
 - Appropriate minterms summed using extra gates to form the function




Logic Functions Using Decoders

$$F1 = A'B'C'D' + AB'CD' + ABC'D'$$


$$F2 = A'B'C' + A'B'CD$$

$$= A'B'C'D' + A'B'C'D + A'B'CD$$

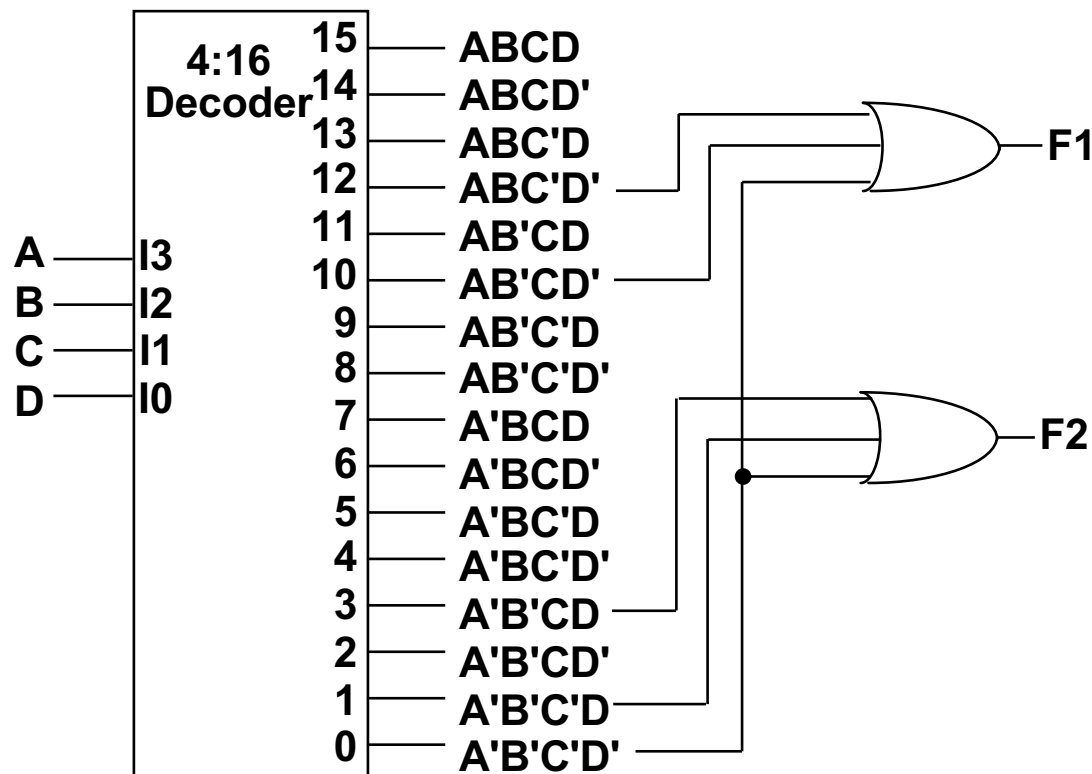

Decoder with Enable

 - Converts an n inputs into a one-hot 2^n outputs, but *only when the enable signal is active*
- Example: A 1-to-2 decoder with enable



$$Y_3 = A_1 \cdot A_0 \cdot E$$

$$Y_2 = A_1 \cdot A_0' \cdot E$$

$$Y_1 = A_1' \cdot A_0 \cdot E$$


$$Y_0 = A_1' \cdot A_0' \cdot E$$

E	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

X: don't care input

Here 0XX covers four input combinations
000, 001, 010, 011

Decoder with Enable (2)

 


$$Y_3 = A_1 \cdot A_0 \cdot E$$

$$Y_2 = A_1 \cdot A_0' \cdot E$$


$$Y_1 = A_1' \cdot A_0 \cdot E$$

$$Y_0 = A_1' \cdot A_0' \cdot E$$

 


Encoders

 - Opposite of decoders
- Binary encoders: 2^n inputs and n outputs



Binary code =>
(One-hot) positional code


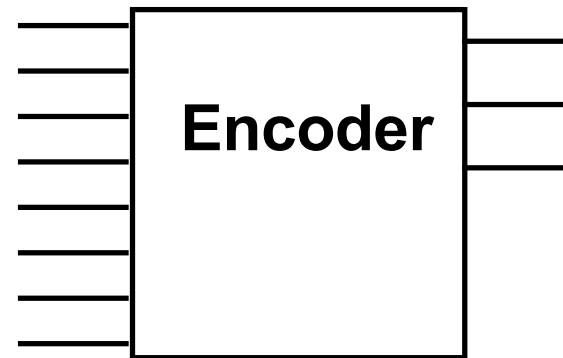


(One-hot) positional code =>
Binary code

4-to-2 Encoder

Exactly one input is asserted at any given time (one-hot inputs)



I3	I2	I1	I0	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

  

4-to-2 Encoder

Exactly one input is asserted at any given time (one-hot inputs)

I3	I2	I1	I0	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

  

		I3 I2				
			00	01	11	10
I1 I0						
00		d	1	d	1	
01		0	d	d	d	
11		d	d	d	d	
10		0	d	d	d	

Next Class

CMOS Logic
(H&H 1.7)