

**ECE 2300**  
**Digital Logic & Computer Organization**  
**Spring 2025**

**More Timing Analysis**  
**Binary Arithmetic**





Cornell University

# Announcements

- **Lab 3 released; Form groups on CMS by Wed**
- **Lab 2b due tomorrow**


# Review: Important Timing Parameters

  

# Timing Analysis Discussion (1)

- To achieve a *higher clock frequency* (i.e., smaller cycle time), would you prefer
  - 1) A smaller or larger combinational delay?
  - 2) A wider or narrower setup time window?
  - 3) A wider or narrower hold time window?
  - 4) A positive or negative clock skew?

# Review: Positive Clock Skew

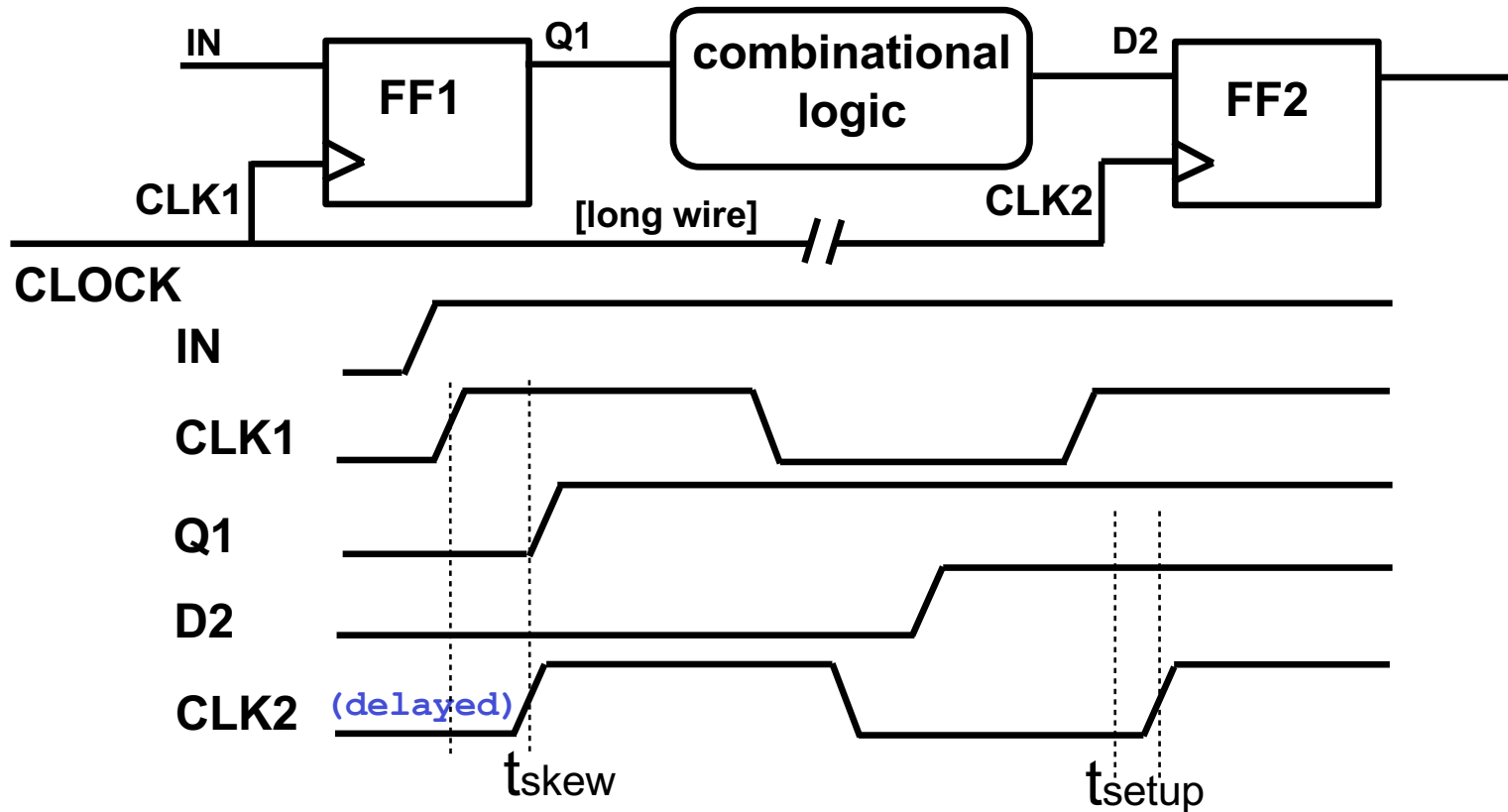



Receiving FF receives clock later than sending FF

$$t_{ffpd(max)} + t_{comb(max)} + t_{setup} \leq t_{clk} + t_{skew(min)}$$

$$\rightarrow t_{ffpd(max)} + t_{comb(max)} + (t_{setup} - t_{skew(min)}) \leq t_{clk}$$

(beneficial skew: setup time window effectively narrowed)

# Review: Negative Clock Skew

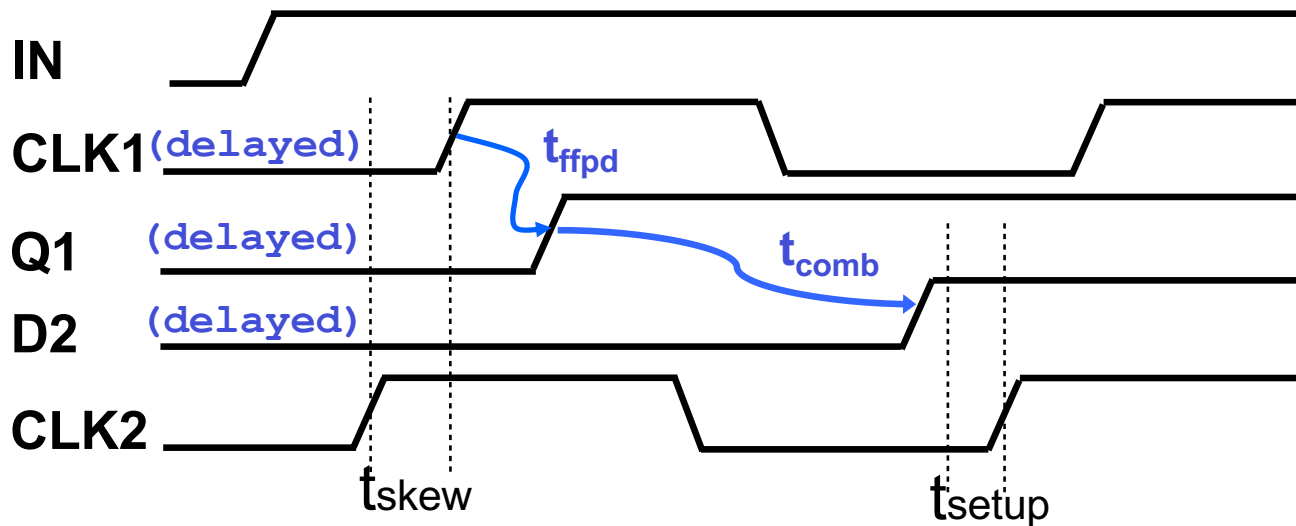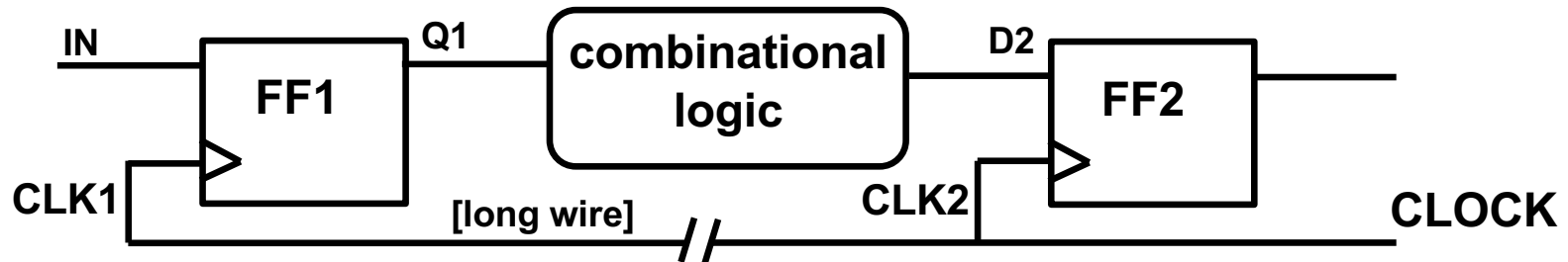


Receiving FF receives clock sooner than sending FF

$$t_{ffpd(max)} + t_{comb(max)} + t_{setup} \leq t_{clk} - t_{skew(max)}$$

$$\rightarrow t_{ffpd(max)} + t_{comb(max)} + (t_{setup} + t_{skew(max)}) \leq t_{clk}$$

(**harmful skew**: setup time window effectively widened)


# Recap: Avoiding Hold Time Violation

 

- FF input must remain stable after the triggering edge by at least  $t_{\text{hold}}$  amount of time
  - Otherwise, the receiving flip-flop may be contaminated with an unexpected value
- Need to consider minimum propagation delays (the shortest timing path) for hold time calculations

$$t_{\text{ffpd}(\text{min})} + t_{\text{comb}(\text{min})} \geq t_{\text{hold}}$$

# Example: Hold Time Constraint

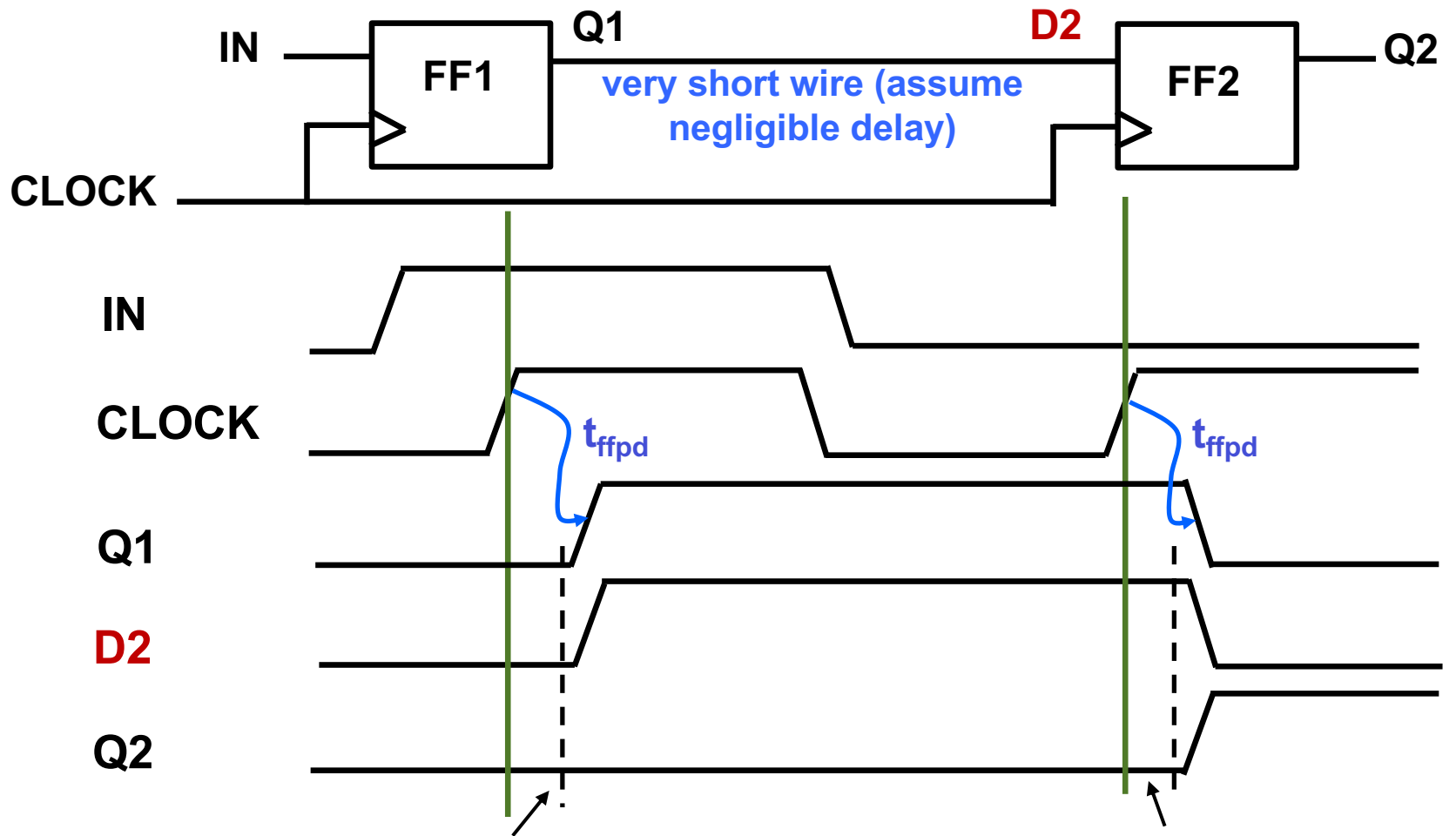


Hold time window ( $t_{\text{hold}}$ ): D2 must remain stable and not change too quickly

Same requirement every clock cycle

$$t_{\text{ffpd}(\text{min})} + t_{\text{comb}(\text{min})} = t_{\text{ffpd}(\text{min})} + 0 \geq t_{\text{hold}}$$



# Example: Hold Time Calculations

 



	<i>Prop Delay (ns)</i>		<b>Setup Time (ns)</b>	<b>Hold Time (ns)</b>
	<b>min</b>	<b>max</b>		
<b>FF</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>2</b>
<b>Comb</b>	<b>2</b>	<b>7</b>	<b>-</b>	<b>-</b>

- **Hold time at FF2 met?**

# Timing Analysis Discussion (2)

- To *avoid hold time violation*, would you prefer
  - 1) A smaller or larger combinational delay?
  - 2) A wider or narrower setup time window?
  - 3) A wider or narrower hold time window?
  - 4) A positive or negative clock skew?

# Hold Time With Positive Clock Skew

 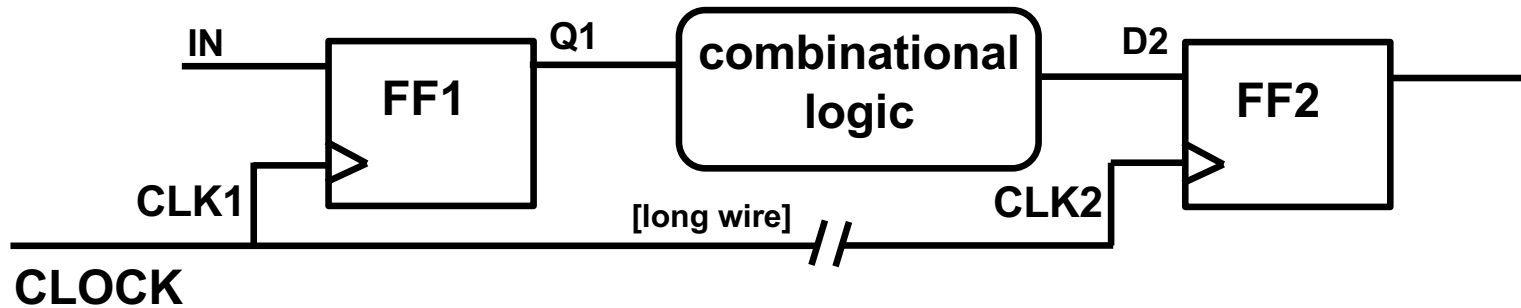


Receiving FF receives clock later than sending FF

$$t_{ffpd(\min)} + t_{comb(\min)} \geq t_{hold} + t_{skew(\max)}$$

(hold time window effectively widened)

**Harmful skew for meeting hold time constraint**

# Hold Time With Negative Clock Skew

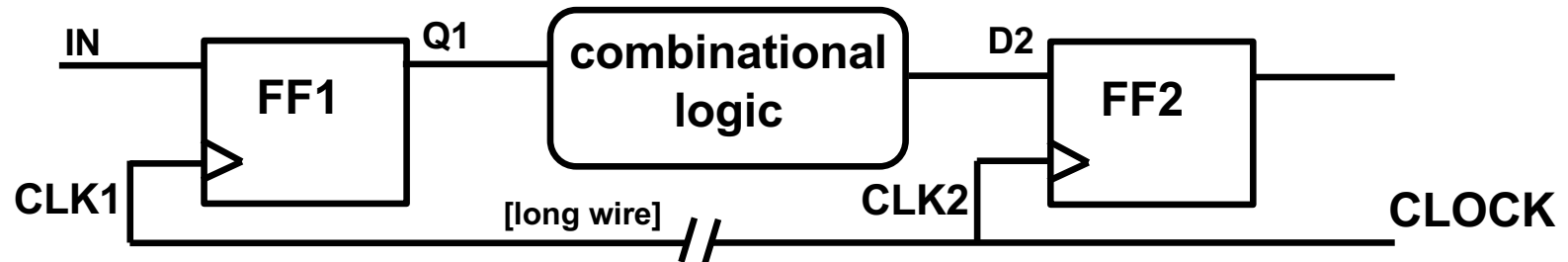


What if receiving FF receives clock sooner than sending FF?

$$t_{\text{ffpd}(\text{min})} + t_{\text{comb}(\text{min})} \geq t_{\text{hold}} - t_{\text{skew}(\text{min})}$$

(hold time window  
effectively narrowed)

**Beneficial skew for meeting hold time constraint**
 
# Example: Hold Time Analysis with Clock Skew




Clock may arrive at FF2 up to 2ns later than FF1

	<i>Prop Delay (ns)</i>		<b>Setup Time (ns)</b>	<b>Hold Time (ns)</b>
	<b>min</b>	<b>max</b>		
<b>FF</b>	<b>1</b>	<b>3</b>	<b>3</b>	<b>2</b>
<b>Comb</b>	<b>3</b>	<b>7</b>	<b>-</b>	<b>-</b>

- **Hold time at FF2 met?**
 
# Example: Hold Time Analysis with Clock Skew



Clock may arrive at FF2 up to 2ns later than FF1

	<i>Prop Delay (ns)</i>		<b>Setup Time (ns)</b>	<b>Hold Time (ns)</b>
	<b>min</b>	<b>max</b>		
<b>FF</b>	<b>1</b>	<b>3</b>	<b>3</b>	<b>2</b>
<b>Comb</b>	<b>3</b>	<b>7</b>	<b>-</b>	<b>-</b>

- **Hold time at FF2 met?**

$$t_{ffpd(\min)} + t_{comb(\min)} \geq t_{hold} + t_{skew(\max)}$$

$$1 + 3 \geq 2 + 2$$

The hold time constraint is met

# Course Content

- **Binary numbers and logic gates**
  - **Boolean algebra and combinational logic**
  - **Sequential logic and state machines**
  - **Clocking and timing analysis**
- 

- **Binary arithmetic**
- **Memories**
  
- **Instruction set architecture**
- **Processor organization**
- **Caches and virtual memory**
- **Input/output**

# Unsigned Binary Integers

- An  $n$ -bit unsigned number represents  $2^n$  integer values
  - Range is from 0 to  $2^n-1$
- For the unsigned binary number  $b_{n-1}b_{n-2}\dots b_1b_0$ , the decimal number is

$$D = \sum_{i=0}^{n-1} b_i \cdot 2^i$$

$2^2$	$2^1$	$2^0$	value
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7



# Unsigned Binary Addition

- **Just like base-10**

- Add from right to left, propagating carry


$\begin{array}{r} 10010 \\ + 01001 \\ \hline 10010 \end{array}$	$\begin{array}{r} \text{carry} \\ \curvearrowright \\ 10010 \\ + 01011 \\ \hline \end{array}$	$\begin{array}{r} \curvearrowright \curvearrowright \curvearrowright \curvearrowright \\ 01111 \\ + 00011 \\ \hline \end{array}$
$(18)$	$(18)$	$(15)$
$(9)$	$(11)$	$(3)$
$(27)$	$(29)$	$(18)$

# Signed Magnitude Representation

- **Most significant bit is used as a sign bit**
  - Sign bit of 0 for positive (001 = 1)
  - Sign bit of 1 for negative (101 = -1)
- **Range is from  $-(2^{n-1}-1)$  to  $(2^{n-1}-1)$  for an n-bit number**
- **Two representations for zero (+0 and -0)**
- **Does ordinary binary addition still work?**

$$\begin{array}{r} \mathbf{001} \quad (1) \\ + \mathbf{101} \quad (-1) \\ \hline \mathbf{110} \quad (\text{not } 0) \end{array}$$
 
# Another Way to Encode Signed Binary Numbers



# Two's Complement Representation (2's C)

- A (slightly) different positional encoding: **MSB has weight  $-2^{n-1}$** 
  - n is the bitwidth
  - For the 2's C binary number  $b_{n-1}b_{n-2}\dots b_1b_0$ , the decimal is
 
$$D = -b_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} b_i \cdot 2^i$$
- Range of an n-bit number:  **$-2^{n-1}$  through  $2^{n-1}-1$** 
  - Positive numbers and zero are same as unsigned binary representation
  - **Most negative number (namely,  $-2^{n-1}$ ) has no positive counterpart**

$-2^2$	$2^1$	$2^0$	
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	-4
1	0	1	-3
1	1	0	-2
1	1	1	-1



# Two's Complement Addition

- Procedure for addition is the same as unsigned addition regardless of the signs of the numbers

$$\begin{array}{r} 001 \quad (1) \\ + \underline{111} \quad (-1) \\ \hline 000 \quad (0) \end{array}$$

# Negating a 2'C Number

- To get two's complement negative notation of an integer
  - Flip every bit first
  - Then add one

	<b>001</b>	(1)		<b>01001</b>	(9)
	<b>110</b>	(1's comp)		<b>10110</b>	(1's comp)
<b>+</b>	<u>    <b>1</b></u>		<b>+</b>	<u>    <b>1</b></u>	
	<b>111</b>	(-1)		<b>10111</b>	(-9)

$$-X = (X' + 1)$$

# 2's C Negation Shortcut

- **To get -X**
  - Copy bits from right to left up to and including the first “1”
  - Flip remaining bits to the left


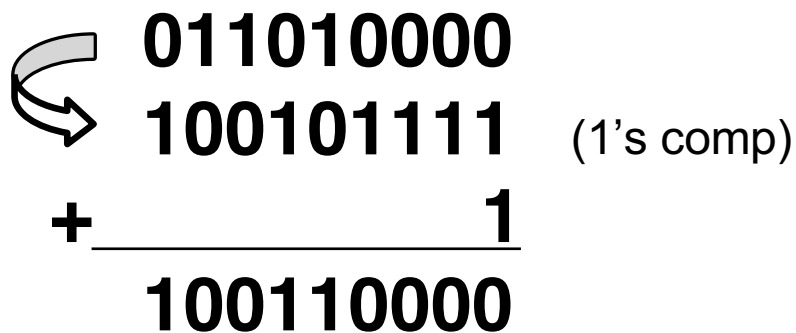


Diagram illustrating the addition of 1 to the 1's complement of a number to get its 2's complement:
 
$$\begin{array}{r} \text{011010000} \\ \text{100101111} \quad (\text{1's comp}) \\ + \quad \quad \quad \text{1} \\ \hline \text{100110000} \end{array}$$



# Converting Binary (2's C) to Decimal

1. If MSB = 1, take two's complement to get a positive number
2. Add powers of 2 for bit positions that have a "1"
3. If original number was negative, add a minus sign

$X$	$= 11100110_{\text{two}}$
$-X$	$= 00011010$
	$= 2^4 + 2^3 + 2^1 = 16 + 8 + 2$
	$= 26_{\text{ten}}$
$X$	$= -26_{\text{ten}}$

$n$	$2^n$
0	1
1	2
2	4
3	8
4	16
5	32
6	64
7	128
8	256
9	512
10	1024

*Assuming 8-bit 2's complement numbers*



# Converting Decimal to Binary (2's C)

## First Method: *Division*

1. Change to nonnegative decimal number
2. Divide by two – remainder is least significant bit
3. Keep dividing by two until answer is zero, recording remainders from right (LSB) to left
4. Append a zero as the MSB;  
if original number X was negative, return X'+1

$$X = 104_{\text{ten}}$$

$104/2 = 52$	r0	$bit\ 0 = 0$
$52/2 = 26$	r0	$bit\ 1 = 0$
$26/2 = 13$	r0	$bit\ 2 = 0$
$13/2 = 6$	r1	$bit\ 3 = 1$
$6/2 = 3$	r0	$bit\ 4 = 0$
$3/2 = 1$	r1	$bit\ 5 = 1$
$1/2 = 0$	r1	$bit\ 6 = 1$

$$X = 01101000_{\text{two}}$$

# Converting Decimal to Binary (2's C)

## Second Method: *Subtract Powers of Two*

1. Change to nonnegative decimal number
2. Subtract largest power of two less than or equal to number
3. Put a one in the corresponding bit position
4. Keep subtracting until result is zero
5. Append a zero as MSB;  
if original was X negative, return X'+1

<i>n</i>	$2^n$
0	1
1	2
2	4
3	8
4	16
5	32
6	64
7	128
8	256
9	512
10	1024

$X = 104_{\text{ten}}$	$104 - 64 = 40$	<i>bit 6 = 1</i>
	$40 - 32 = 8$	<i>bit 5 = 1</i>
	$8 - 8 = 0$	<i>bit 3 = 1</i>
$X = 01101000_{\text{two}}$		

# Fixed Size Representation

- Microprocessors usually represent numbers as fixed size n-bit values
- Result of adding two n-bit integers is stored as n bits
- Integers are typically 32 or 64 bits (*words*)
  - 4 or 8 *bytes* (1 *byte* = 8 bits)

# Fixed Size Addition

- Examples with  $n = 4$

$$\begin{array}{r} 2 \quad 0010 \\ + 3 \quad 0011 \\ \hline 5 \quad 0101 \end{array}$$

$$\begin{array}{r} 2 \quad 0010 \\ + -3 \quad 1101 \\ \hline -1 \quad 1111 \end{array}$$

$$\begin{array}{r} -2 \quad 1110 \\ + 6 \quad 0110 \\ \hline 4 \quad 0100 \end{array}$$

$$\begin{array}{r} -2 \quad 1110 \\ + -6 \quad 1010 \\ \hline -8 \quad 1000 \end{array}$$

$$\begin{array}{r} 7 \quad 0111 \\ + 6 \quad 0110 \\ \hline -3 \quad 1101 \end{array}$$

$$\begin{array}{r} -7 \quad 1001 \\ + -4 \quad 1100 \\ \hline 5 \quad 0101 \end{array}$$

Something went wrong!

# Overflow

- If operands are too big, sum cannot be represented as  $n$ -bit 2's complement number

<b>01000</b>	(8)	<b>11000</b>	(-8)
<b>+ 01001</b>	(9)	<b>+ 10111</b>	(-9)
<b>10001</b>	(-15)	<b>01111</b>	(+15)

- **Overflow occurs if**
  - Signs of both operands are the same, and
  - Sign of sum is different
- **Another test (easy to do in hardware)**
  - Carry into MSB does not equal carry out

# Exercise: Would Overflow Occur?

$$\begin{array}{r} 011100 \\ + 010101 \\ \hline \end{array}$$

# Next Class

**More Binary Arithmetic**  
**ALU**  
**(H&H 5.1-5.2.4)**