

ECE 2300
Digital Logic & Computer Organization
Spring 2025

More Binary Arithmetic
ALU



Cornell University

Announcements

- **Supplementary notes on timing analysis posted on course web**

Thu 3/6	11: Timing Analysis [slides] [supplementary notes]
---------	---

- **HW 4 due tomorrow**
- **HW 5 will be released soon**

Review: Overflow in 2's C

- **When performing fixed-size addition in 2's C, overflow occurs if**
 - Signs of both operands are the same, and
 - Sign of sum is different
- **Another test (easy to do in hardware)**
 - Carry into MSB does not equal carry out

Did Overflow Occur?

$$\begin{array}{r} \text{carries} \rightarrow 111 \\ 011100 \\ + 010101 \\ \hline 110001 \end{array}$$

YES


$$\begin{array}{r} \text{carries} \rightarrow 1111 \\ 111101 \\ + 010100 \\ \hline 010001 \end{array}$$

NO




Full Adder (1 bit Adder with Carry)

- Inputs: A, B and C_{in} (carry-in)
- Outputs: S (sum) and C_{out} (carry-out)


A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Full-Adder Circuit Symbol

   

OR

 

Building a Multi-Bit Binary Adder


carries →

$$\begin{array}{r} \begin{array}{cccccccc} & 1 & 1 & 1 & 0 & 0 & 0 & 0 \\ & \swarrow & \swarrow & \swarrow & \swarrow & \swarrow & \swarrow & \swarrow \\ & 0 & 1 & 1 & 0 & 1 & 0 & 0 & 0 & 0 \\ & & 0 & 1 & 1 & 0 & 1 & 0 & 0 & 0 \end{array} \\ + \underline{\quad 11110000} \\ \hline 01011000 \end{array} \begin{array}{l} \text{(A)} \\ \text{(B)} \\ \text{(S)} \end{array}$$

- **Inputs & outputs for the i^{th} bit position**
 - Inputs: A_i , B_i and C_i (carry-in)
 - Outputs: S_i (sum) and C_{i+1} (carry-out)
- **Carry-out of a bit position is the carry-in for next bit position**

Four Bit Adder
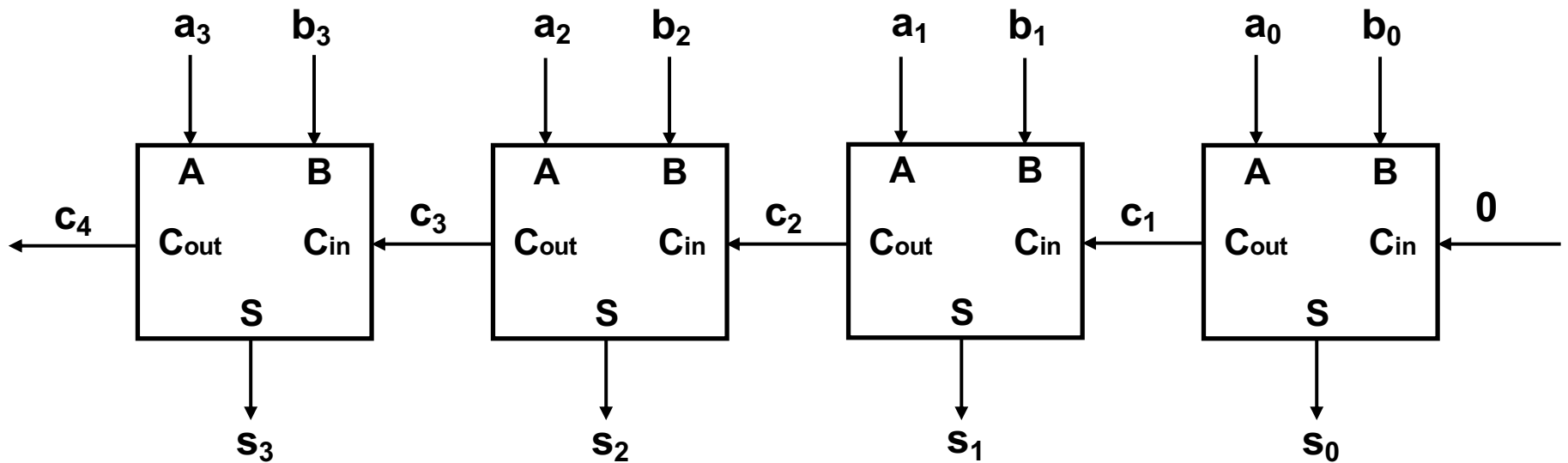
$$\begin{array}{r} 11000 \\ \text{---} \\ 1100 \\ + 0110 \\ \hline 0010 \end{array}$$



Ripple Carry Adder (RCA)

Two's Complement Subtraction

- Negate second operand and add

$$\begin{array}{r} 01101000 \quad (104) \\ - \underline{00010001} \quad (17) \end{array}$$





$$\begin{array}{r} 01101000 \quad (104) \\ + \underline{11101111} \quad (-17) \\ \hline 01010111 \quad (87) \end{array}$$


Four Bit Subtractor

negating the
second operand

$$-b = (b'+1)$$

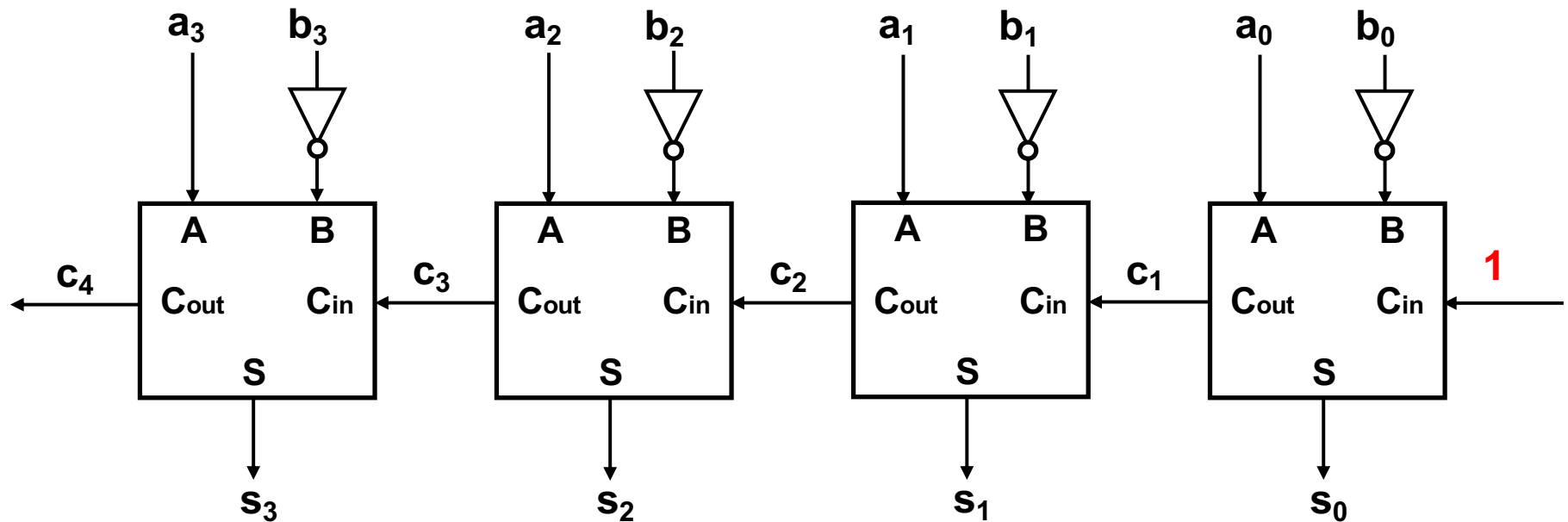 

Four Bit Adder / Subtractor

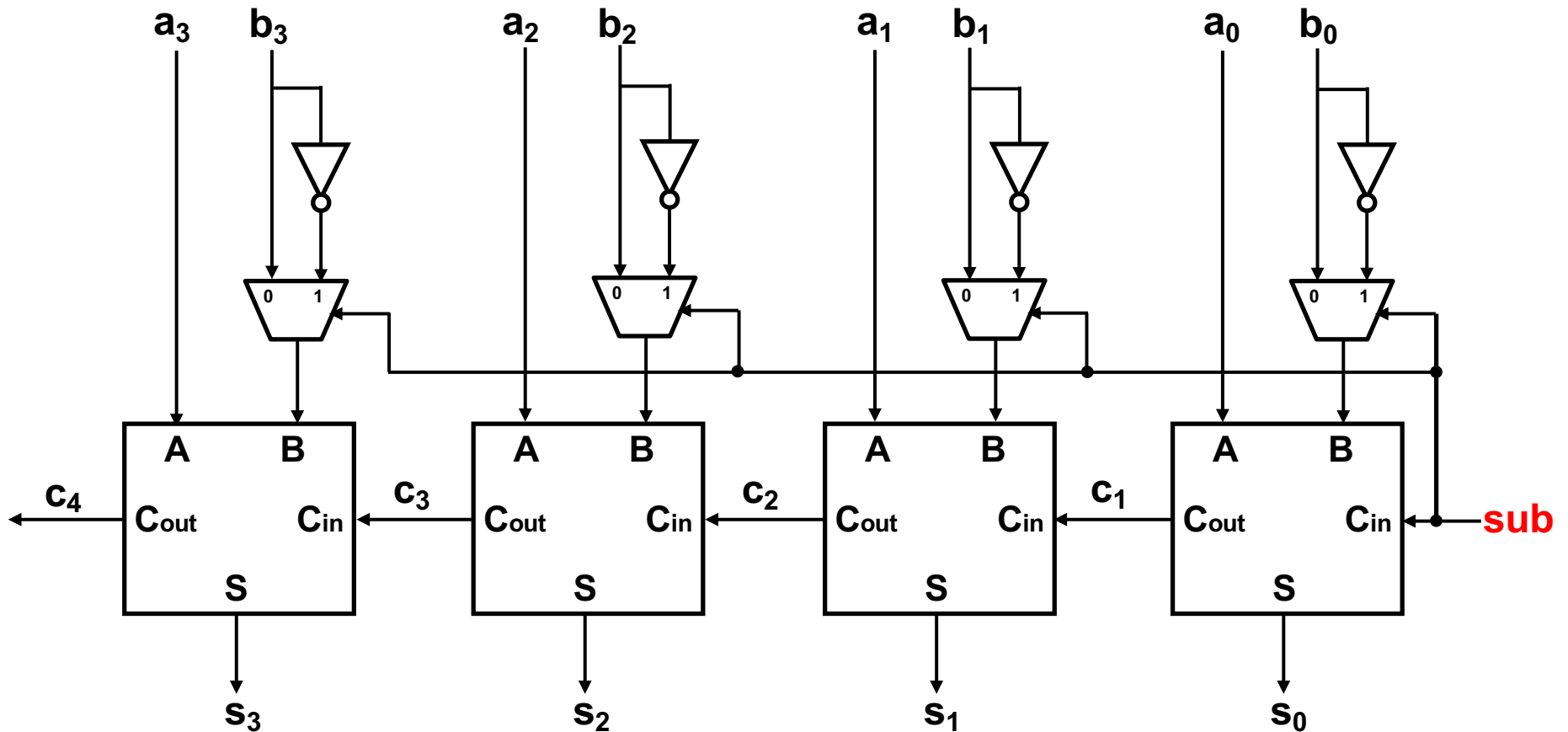

“sub” is a 1-bit control signal that selects the operation mode of the adder/subtractor

Adder Implementations

- Many different adder implementations exist, which differ in speed and circuit complexity
- Ripple carry adder is simple but slow
 - Each 1-bit full adder must wait for the carry bit to be calculated from the previous full adder
- Common techniques to speed up carry propagation
 - Carry lookahead
 - Carry select
 - Carry save
 - etc.

Carry Lookahead Adder (CLA)

- **Calculation of carry out of MSB is slow for large RCAs**
 - Carry has to propagate from LSB to the MSB, which forms the longest path (critical path)
- **CLA adder calculates groups of carries in parallel**

Carry Generation and Propagation

$$\begin{array}{r} 01010010 \\ + 00010011 \\ \hline 01100101 \end{array}$$

generated generated

$$\begin{array}{r} 11000110 \\ + 00101011 \\ \hline 11110001 \end{array}$$

propagated generated

- $C_{out} = 1$ from a bit position happens for 2 reasons
 - Carry is generated from this bit position
 - Carry in to this position is propagated to the next

Carry Generation and Propagation

- **Carry from i^{th} position: c_{i+1}**
 - namely, the carry into $(i+1)^{\text{th}}$ position
- **Carry generation function for the i^{th} position**
$$G_i = a_i \cdot b_i \quad (\text{if position } i \text{ generates a carry})$$
- **Carry propagation function for the i^{th} position**
$$P_i = a_i + b_i \quad (\text{if position } i \text{ can propagate a carry})$$
- **Carry out of the i^{th} position**
$$c_{i+1} = G_i + P_i \cdot c_i$$

Carry Out Equations for 4-bit Adder

$$c_1 = G_0 + P_0 \cdot c_0$$

$$c_2 = G_1 + P_1 \cdot c_1 \\ = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot c_0$$

$$c_3 = G_2 + P_2 \cdot c_2 \\ = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot c_0$$

$$c_4 = G_3 + P_3 \cdot c_3 \\ = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot c_0$$

generate carry from this position

propagate carry generated in position 2

propagate carry generated in position 1

propagate carry generated in position 0

propagate carry in to position 0


$$G_i = a_i \cdot b_i \\ P_i = a_i + b_i$$

Carry Out Logic for 4-bit Adder


$$G_i = a_i \cdot b_i$$

$$P_i = a_i + b_i$$

$$\begin{aligned}
 c_4 &= G_3 + P_3 \cdot c_3 \\
 &= G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot c_0 \\
 &= \underbrace{G_3 + P_3 \cdot (G_2 + P_2 \cdot (G_1 + P_1 \cdot G_0))}_{G_{3:0} - \text{Carry generation from bits 3-0}} + \underbrace{(P_3 \cdot P_2 \cdot P_1 \cdot P_0)}_{P_{3:0} - \text{Carry propagation through bits 3-0}} \cdot c_0
 \end{aligned}$$


 


32-bit CLA with 4-bit RCAs

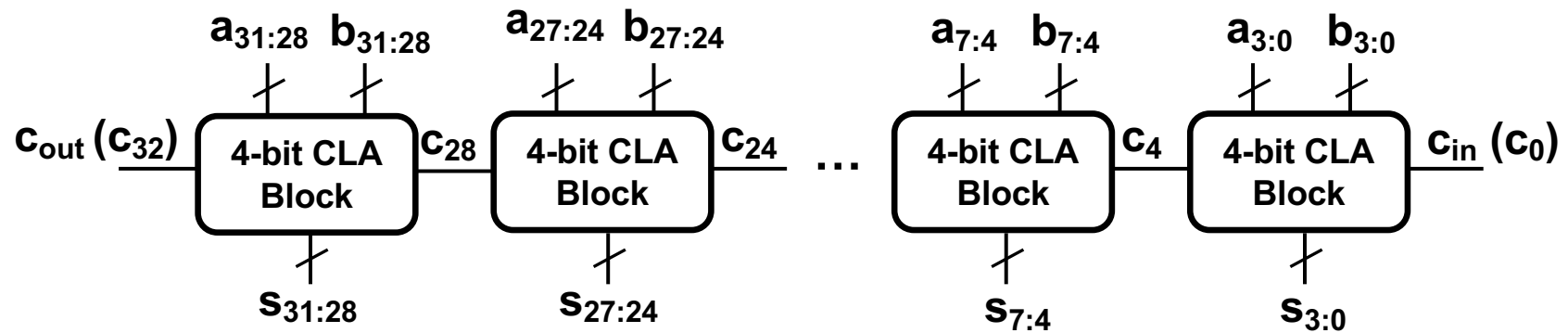

- Carry out logic gets more complicated beyond 4 bits
- CLAs are often implemented as 4-bit modules and instantiated in a hierarchical way to realize wider adders



32-bit CLA with 4-bit RCAs

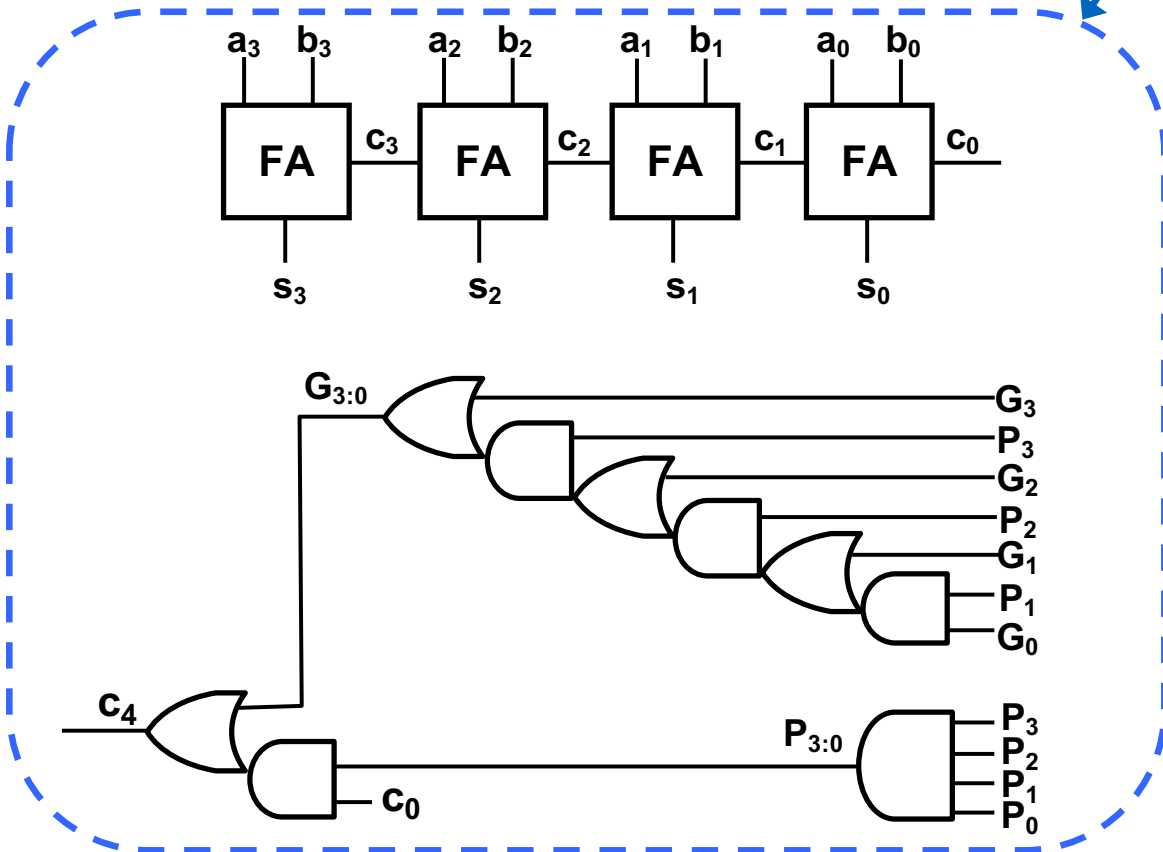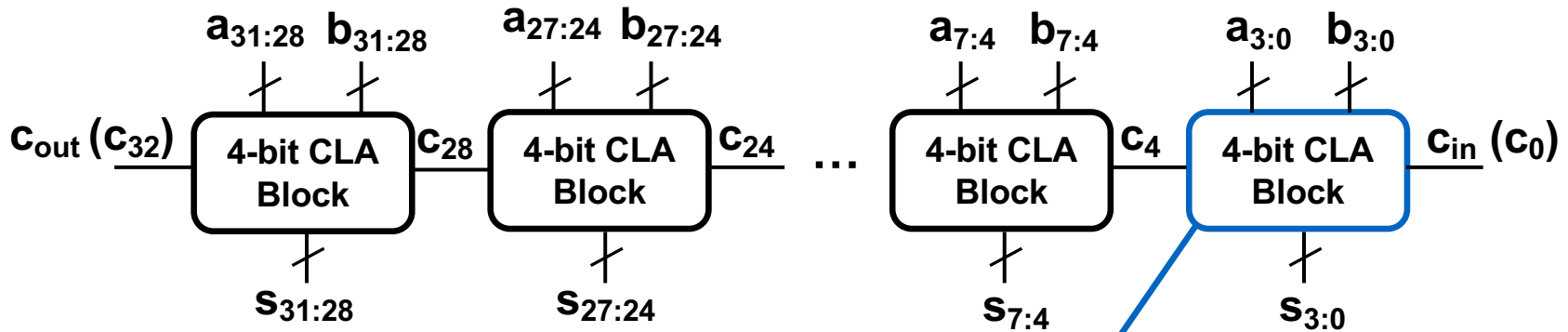

Sum bits ($s_0 \sim s_3$) generated by 4-bit RCA

Carry-out (c_4) to next CLA block generated separately using P's and G's

32-bit CLA with 4-bit RCAs

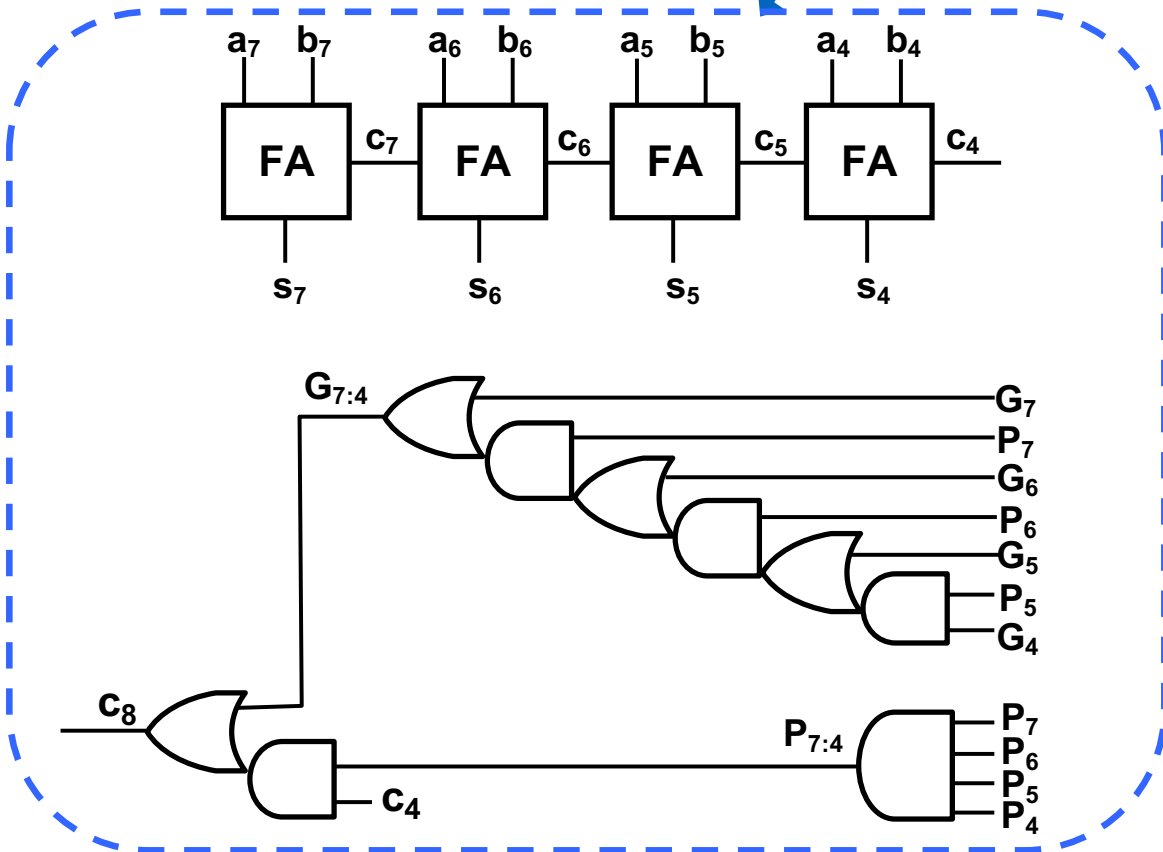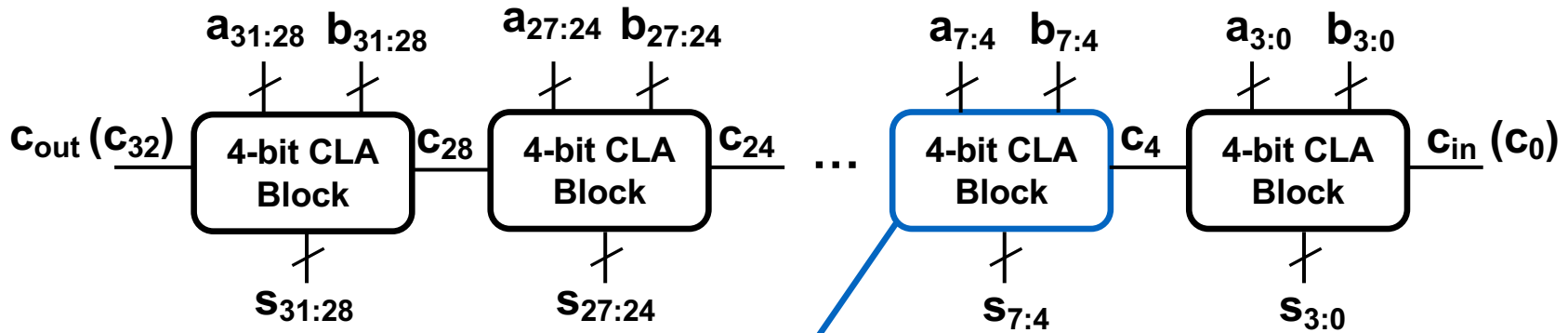


Sum bits ($s_4 \sim s_7$) generated by 4-bit RCA


Carry-out (c_8) to next CLA block generated separately using P's and G's

Discussion: Delay of a 4-bit CLA Block

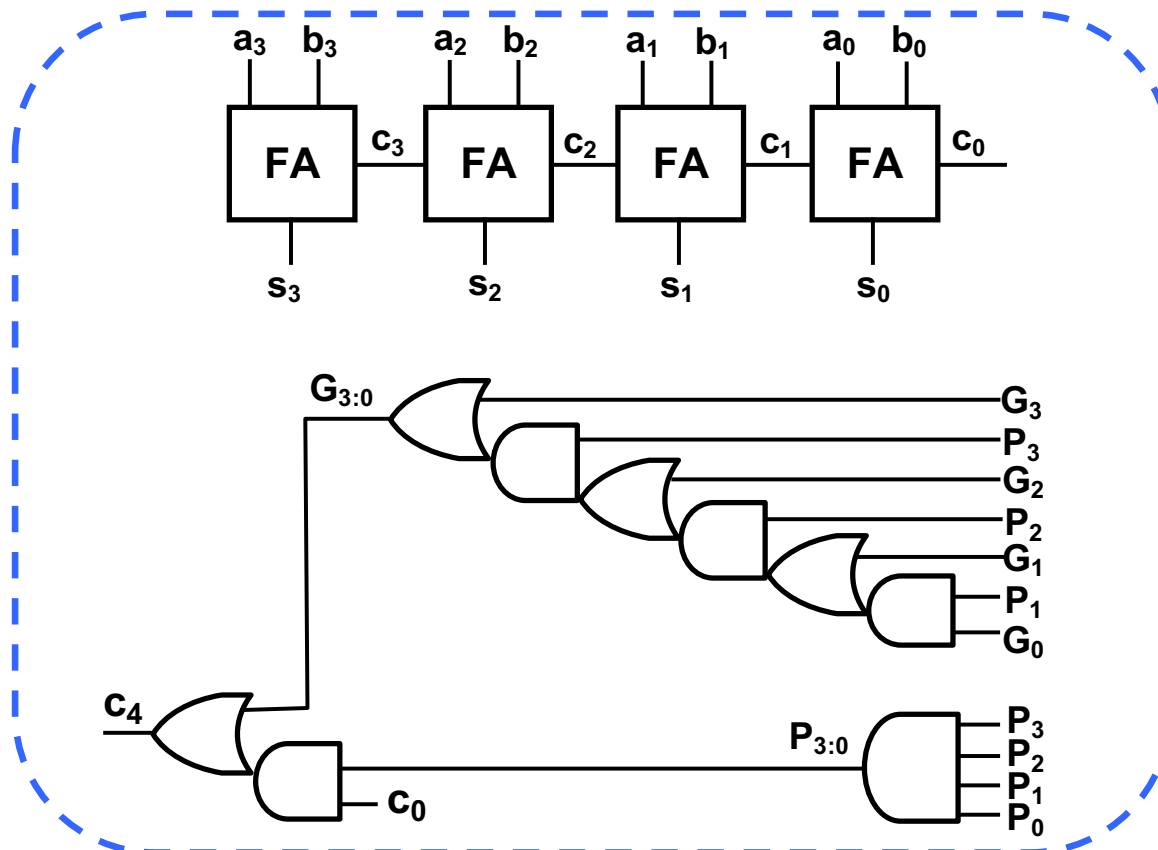- Assumptions: Each logic gate has a delay of 1ns, and each full adder (FA) takes 3ns. Calculating Gs and Ps requires 1ns.
- Analyze the longest path delays for outputs s_3 and c_4 , respectively.



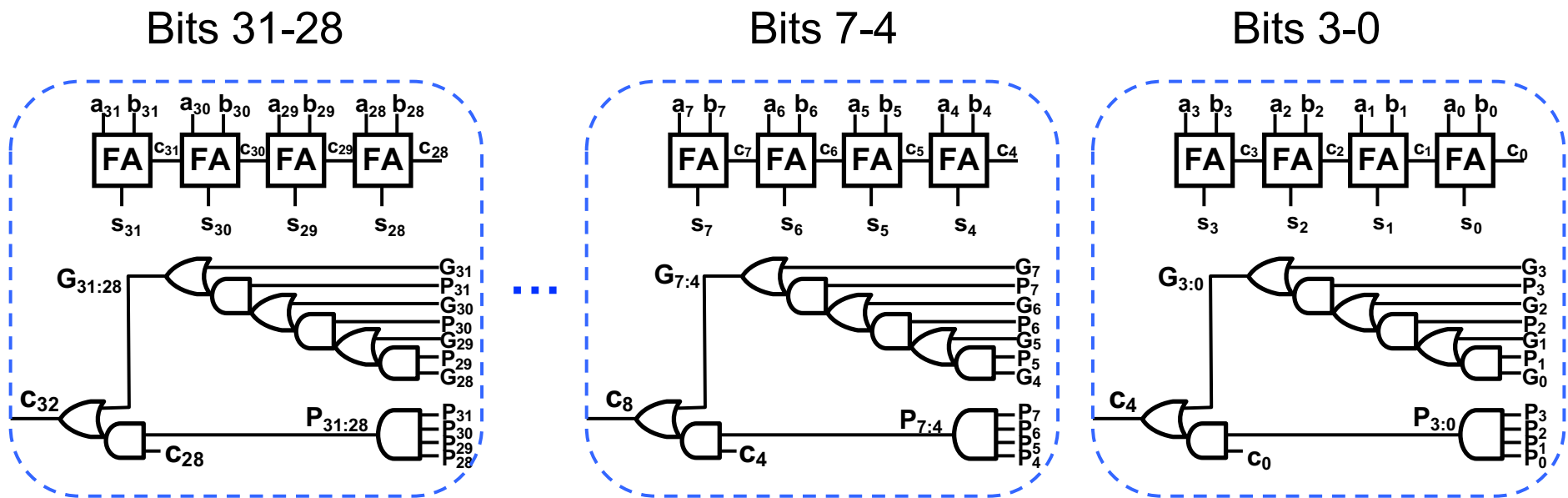Analyzing the Critical Path (Longest Delay)




Carry generation and propagation functions (e.g., $G_{7:4}$, $P_{7:4}$) in a 4-bit CLA block do not depend on results from other CLA blocks



P 's and G 's for all CLA blocks are generated *in parallel*

Critical Path of 32-bit CLA

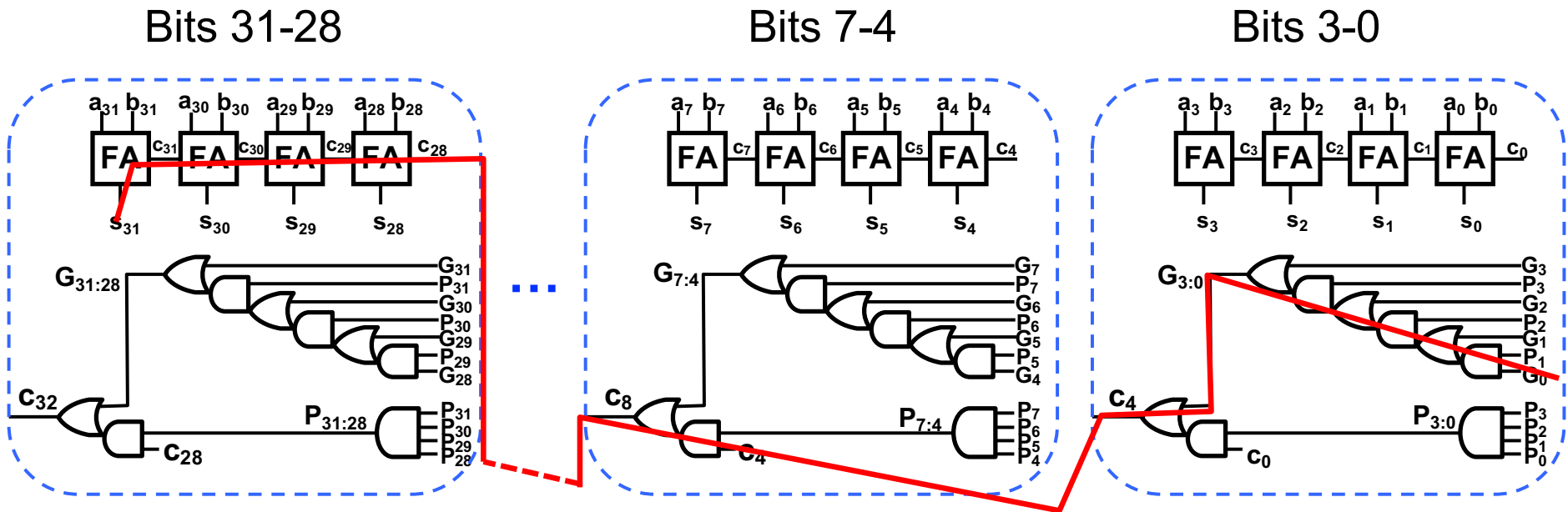


Carry generation and propagation functions (e.g., $G_{7:4}$, $P_{7:4}$) in a 4-bit CLA block do not depend on results from other CLA blocks



P 's and G 's for all CLA blocks are generated *in parallel*

Discussion: Critical Path Delay of 32-bit CLA

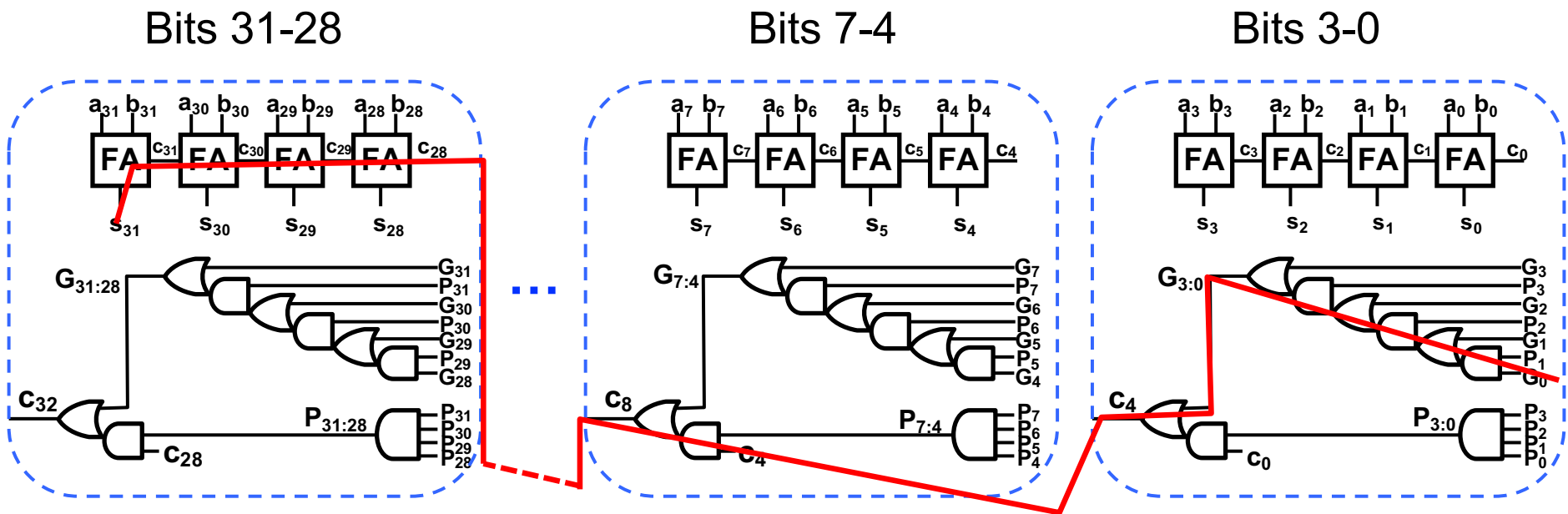- Assumptions: Each logic gate has a delay of 1ns, and each full adder (FA) takes 3ns. Calculating Gs and Ps requires 1ns.




c_4 stabilizes at 8ns, c_8 at $8+2$, c_{12} at $8+2*2$, c_{16} at $8+2*3$, ...

→ c_{28} stabilizes at $8 + 2*6 = 20$ ns

→ s_{31} depends on c_{28} ; it stabilizes at $20 + 4*Delay_{FA} = 20 + 4*3 = 32$ ns

Our Microprocessor is Built to Compute

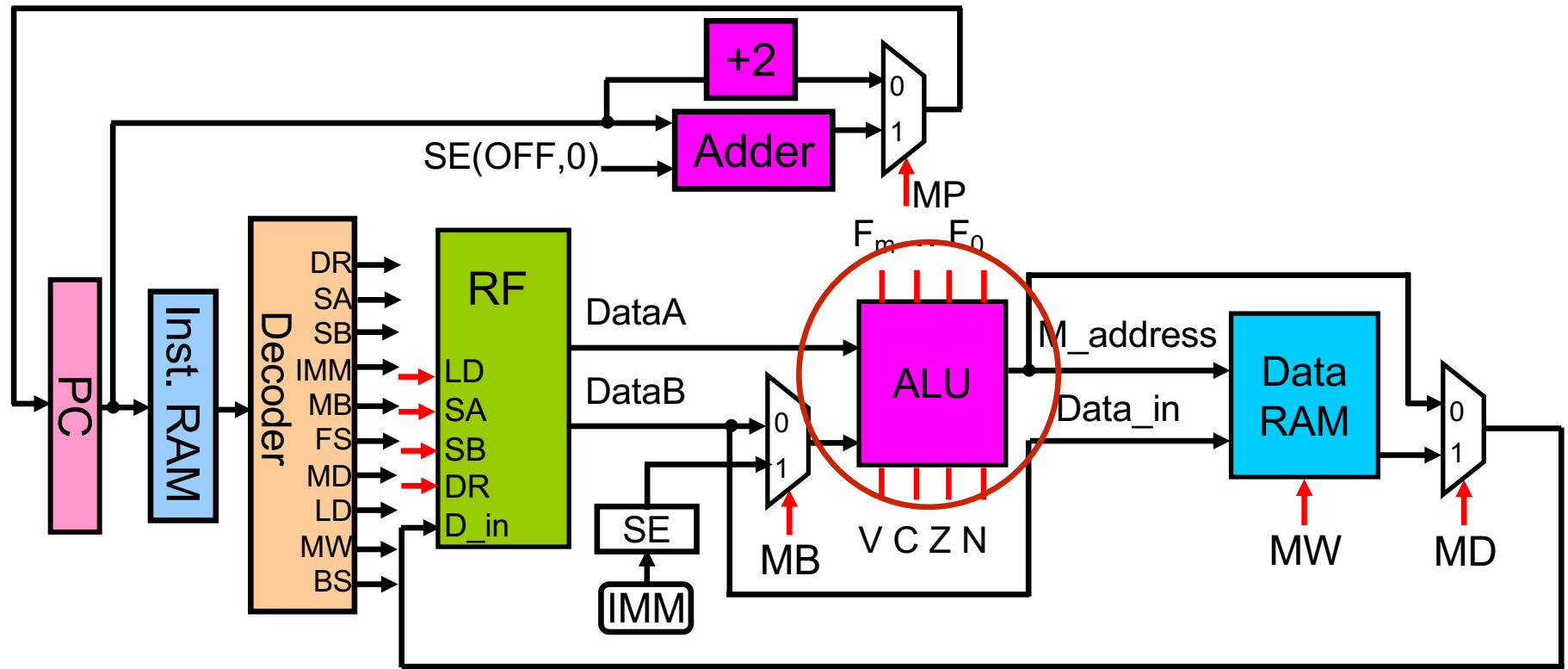


ALU is the computing core of a processor

What is an ALU?

- **Arithmetic Logic Unit (ALU):** Combinational logic circuit that combines a variety of operations into a single unit
- **Common operations may include**
 - **Addition and subtraction**
 - **Logical (OR, AND)**
 - **Shift**
 - **Comparisons**

A Simple 8-Bit ALU

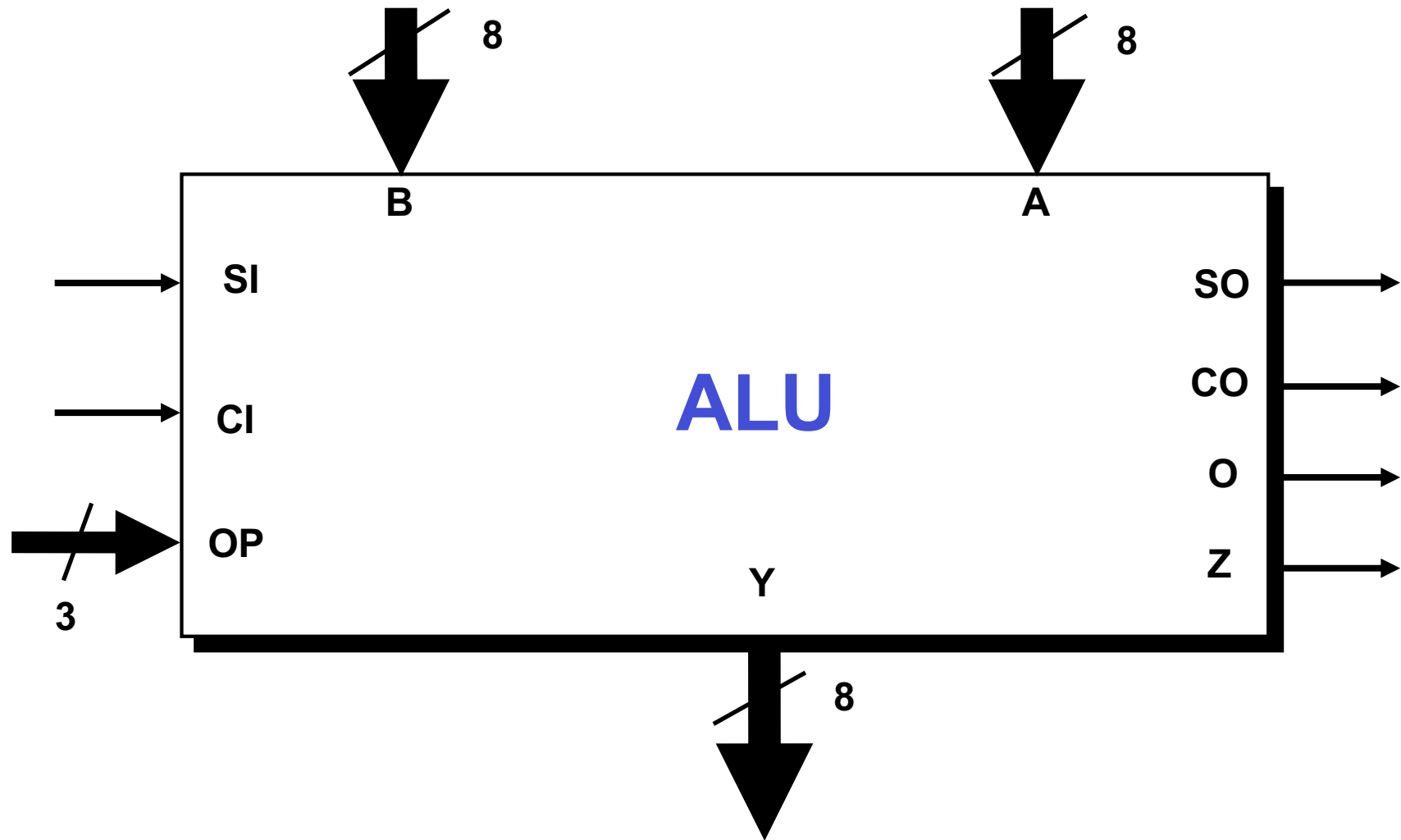

ALU Operations, Inputs & Outputs

- **Operations**

- **Addition and Subtraction** (and Comparison)
- **Bitwise AND and OR**
- **Left Shift and Right Shift**

- **Inputs**


- **A, B, Carry In (CI)**
- **Shift In (SI)**
- **Code indicating operation to be performed (OP)**

- **Outputs**

- **Y, Carry Out (CO)**
- **Shift Out (SO)**
- **Flags regarding the result of the operation**
 - **Overflow flag (O), Zero flag (Z)**


Shift Operations

 - **Left Shift: shifts each bit left by 1 position**




- MSB shifted into **SO**, **SI** shifted into LSB

 - **Right Shift: shifts each bit right by 1 position**



- LSB shifted into **SO**, **SI** shifted into MSB

ALU Block Diagram

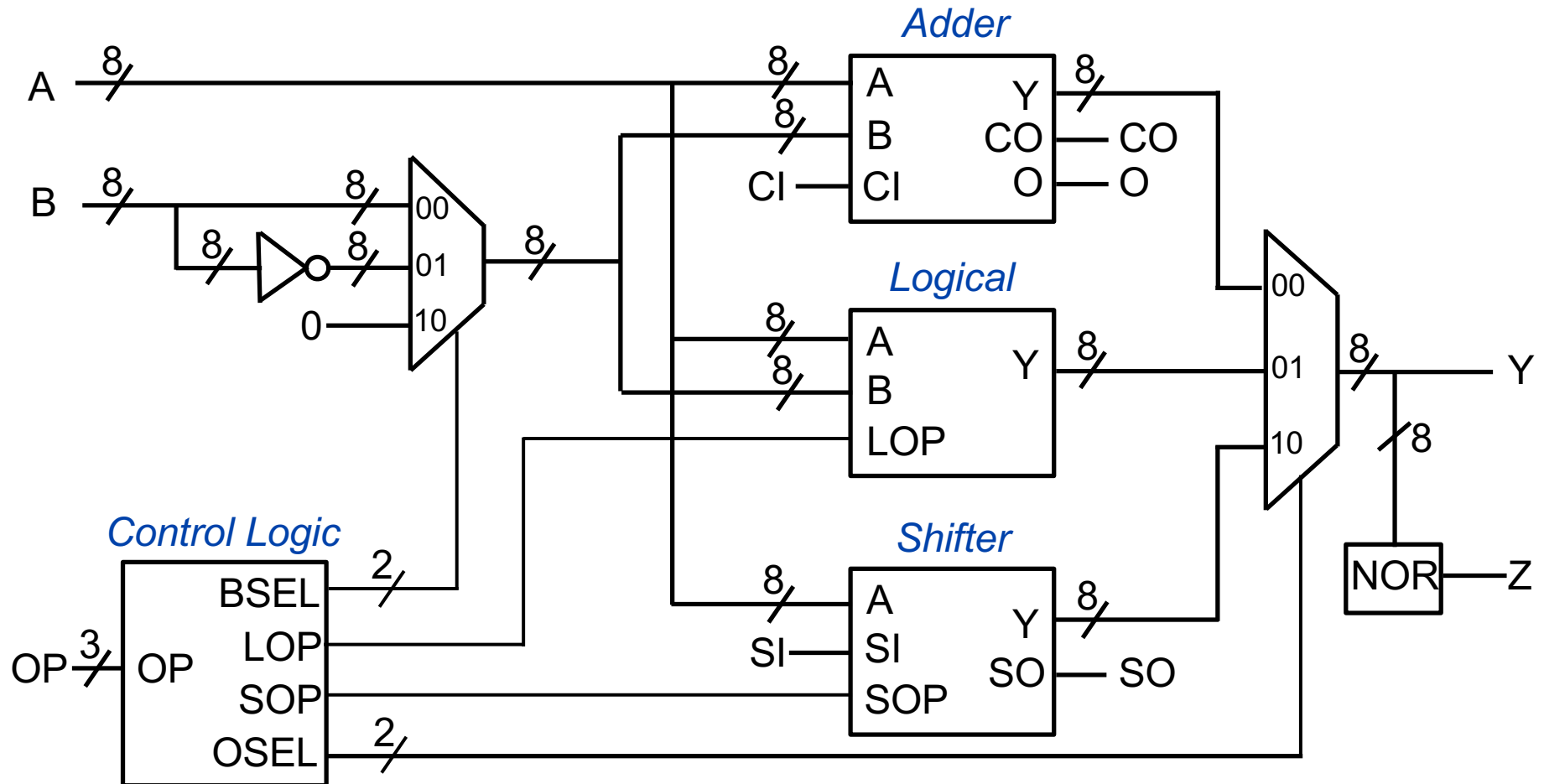


Control logic outputs

- **BSEL:** B input mux select
- **LOP:** Logical unit opcode
- **SOP:** Shifter opcode
- **OSEL:** Output mux select


ALU Operation Encodings

OP Name	OP	BSEL	CI	LOP	SOP	OSEL	Operation
ADD	000	00	0	-	-	00	$Y = A + B + CI$
SUB	001	01	1	-	-	00	$Y = A + B' + 1$
AND	011	00	-	0	-	01	$Y = A \text{ AND } B$
OR	100	00	-	1	-	01	$Y = A \text{ OR } B$
SHL	101	-	-	-	0	10	$Y = A[6..0], SI$
SHR	110	-	-	-	1	10	$Y = SI, A[7..1]$
PASS A	111	10	0	-	-	00	$Y = A$

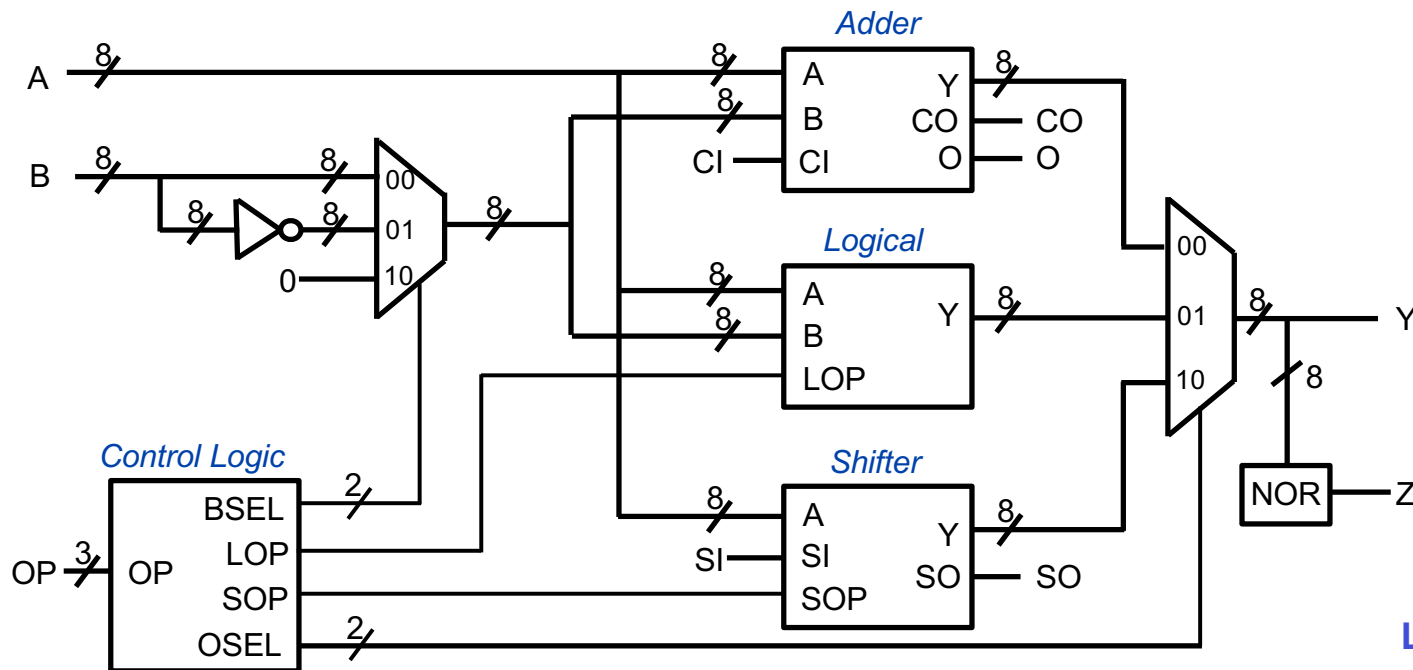

Comparison Operations (Byproduct of SUB)

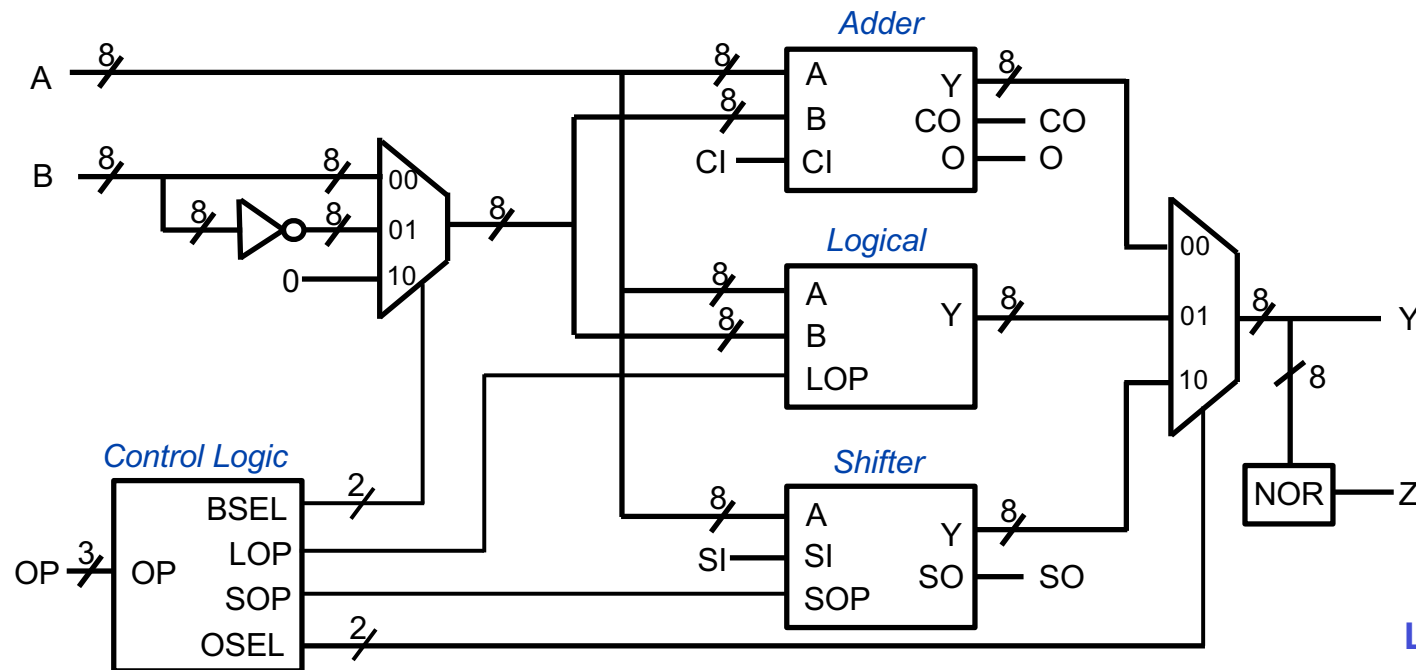- **To compare A and B, perform $A - B$**
 - If the result is 0, then $A = B$
 - Z flag set to 1 whenever ALU result is 0
 - 8-input NOR returns 1 only if all 8 input bits are 0
 - Can check for $A \geq B$ and $A < B$ by observing the MSB of the result of $A - B$



Next Class

**Memories
(H&H 5.5)**