


# **ECE 2300 Digital Logic and Computer Organization Fall 2025**

## **Topic 2: Combinational Logic**

School of Electrical and Computer Engineering  
Cornell University

revision: 2025-09-04-10-50


<b>1</b>	<b>From Voltages to Bits</b>	<b>3</b>
<b>2</b>	<b>From Digital Circuits to Truth Tables</b>	<b>4</b>
<b>3</b>	<b>From Truth Tables to Combinational Logic Gates</b>	<b>9</b>
3.1.	Primitive Gate Sets . . . . .	13
<b>4</b>	<b>Combinational Gate-Level Networks</b>	<b>16</b>
<b>5</b>	<b>Combinational Logic Timing Analysis</b>	<b>20</b>
5.1.	Combinational Logic Gates Timing . . . . .	21
5.2.	Combinational Gate-Level Network Timing . . . . .	23
5.3.	Combinational Gate-Level Network Timing . . . . .	24
<b>6</b>	<b>Verilog Modeling of Combinational Logic</b>	<b>27</b>
6.1.	Modeling Logic Gates in Verilog . . . . .	28
6.2.	Modeling Gates-Level Netlists in Verilog . . . . .	29
6.3.	Modeling Delays in Verilog . . . . .	32
<b>7</b>	<b>Summary of Abstractions</b>	<b>33</b>

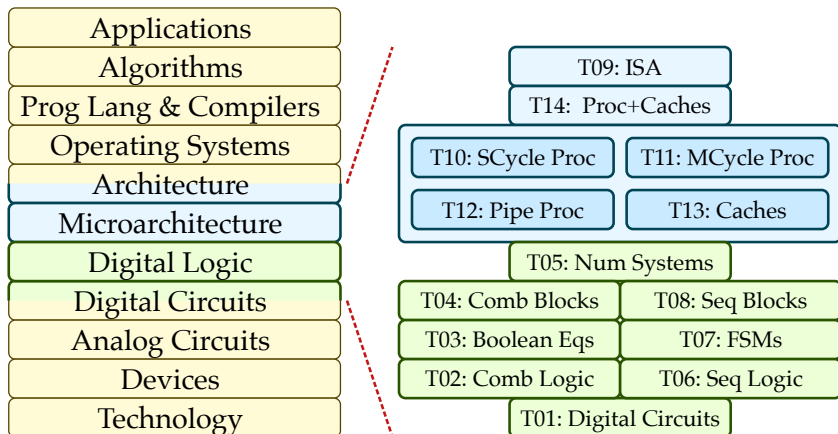

Copyright © 2025 Christopher Batten. All rights reserved. This handout was prepared by Prof. Christopher Batten at Cornell University for ECE 2300 / ENGRD 2300 Digital Logic and Computer Organization. Download and use of this handout is permitted for individual educational non-commercial purposes only. Redistribution either in part or in whole via both commercial or non-commercial means requires written permission.

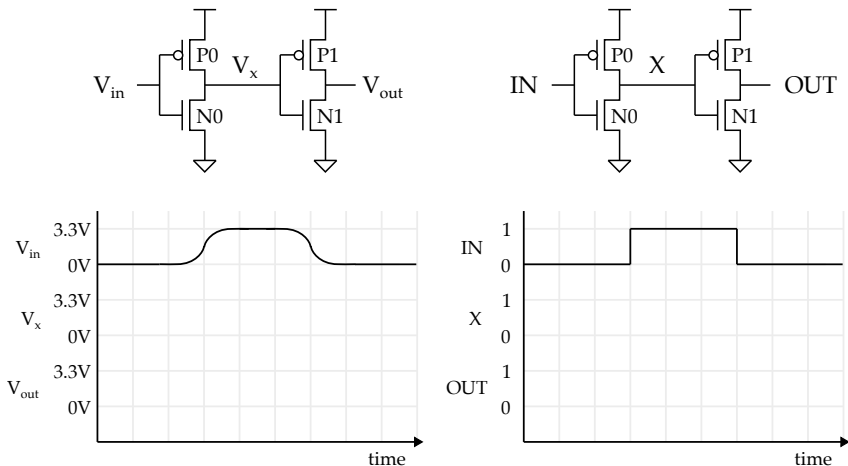
## 1. From Voltages to Bits

- Abstract 3.3V to be logic 1, and abstract 0V to be logic 0
- Enables ignoring specific voltage levels at higher abstraction levels
- Can now interpret wires as representing *binary digits* (bits)
- Include noise margins to make our circuits more robust




Output of First Inverter

Input of Second Inverter

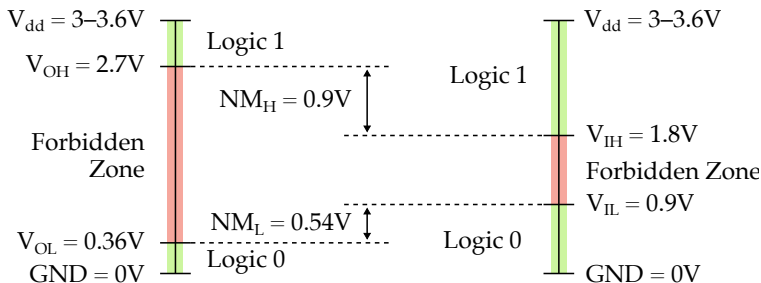

 
## 2. From Digital Circuits to Truth Tables

- A *truth table* specifies the output values for specific input values, with one row for every possible combination of input values
- Let's start by deriving truth tables from digital circuits




$V_a$	$V_y$
0V	
3.3V	

A	Y
0	
1	

 


$V_a$	$V_b$	$V_y$
0V	0V	
0V	3.3V	
3.3V	0V	
3.3V	3.3V	

A	B	Y
0	0	
0	1	
1	0	
1	1	

 


A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 


A	B	X	Y
0	0		
0	1		
1	0		
1	1		

 - Now let's derive digital circuits from truth tables



A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0


A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0



  
### 3. From Truth Tables to Combinational Logic Gates




A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


NOT

  



NAND2

  



NOR2

 



NAND3

  



NOR3

 
 


#### AND2

  



#### OR2

  

  

**Derive the truth table for the above gate-level network. Verify it matches the truth table for an XOR gate.**

A	B	X	W	Z	Y
0	0				
0	1				
1	0				
1	1				

  


### 3.1. Primitive Gate Sets

- Can implement a logic gate using other logic gates which can then be implemented again using more logic gates (e.g., XNOR)
- Can implement a logic gate using many different combinations of other logic gates
- \_\_\_\_\_ = lowest level “atomic” logic gates which are not implemented in terms of any other logic gates but are instead implemented using digital circuits
 
#### Incomplete Primitive Gate Sets

- Consider a primitive gate set with just an AND2 gate



- This is an *incomplete* primitive gate set since it is not possible to use this gate set to implement any other logic gate

## Universal Primitive Gate Sets

- Consider a primitive gate set with just a NAND2 gate

- This is an *universal* primitive gate set since it is possible to use this gate set to implement any other logic gate
- A primitive gate set with just a NOR2 is also a universal
- It is inefficient (both in terms of area and timing) to implement all other logic gates just using NAND2 or NOR2 gates

## Maximal Primitive Gate Sets


- Consider a primitive gate set with the following
  - NOT gate
  - n-input AND, n-input NAND gate
  - n-input OR, n-input NOR gate
  - n-input XOR, n-input XNOR gate
  - AOI21, AOI22 gate (and-or-inverting)
  - OAI12, OAI22 gate (or-and-inverting)
  - Multiplexors, half-adders, full-adders
  - Flip-flops, latches
- It is very efficient (both in terms of area and timing) to use a large primitive gate set
- It is difficult to understand how more complex gates work if we treat them as a block box implemented using digital circuits

## ECE 2300 Primitive Gate Set

- The course will use a primitive gate set with the following
  - NOT gate
  - n-input AND, n-input NAND gate
  - n-input OR, n-input NOR gate
  - n-input XOR, n-input XNOR gate
 
## 4. Combinational Gate-Level Networks


- A *gate-level network* is a collection of logic gates connected by wires
- Let's start by deriving truth tables from gate-level networks




**Truth Table**

A	B	C	X	Y
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 **Timing Diagram** (assume zero delay model)






 

**Truth Table**


A	B	C	X	Y
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 **Timing Diagram** (assume zero delay model)



- Now let's derive gate-level networks from truth tables


**Gate-Level Network**

 

**Truth Table**


A	B	Y
0	0	1
0	1	0
1	0	1
1	1	1

**Gate-Level Network**

 

**Truth Table**


A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 **Gate-Level Network****Truth Table**

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1
 
## 5. Combinational Logic Timing Analysis



- Use abstract time units ( $\tau$ ) instead of picoseconds (ps)



- Recall from previous topic that many delay models are possible
  - Zero delay models
  - Constant delay models
  - Input-dependent constant delay models
  - Transition- and input-dependent constant delay models
  - Load-, transition-, and input-dependent linear delay models
  - Slew-, load-, transition-, and input-dependent linear delay models
  - Non-linear delay models


## 5.1. Combinational Logic Gates Timing

### • Zero Delay Model

  


$t =$

### • Constant Delay Model

 

$t =$

 
### • Input-Dependent Constant Delay Model



$t_{A \rightarrow Y} =$

$t_{B \rightarrow Y} =$
 
### • Transition- and Input-Dependent Constant Delay Model



$t_{A \rightarrow Y, hl} =$


$t_{A \rightarrow Y, lh} =$

$t_{B \rightarrow Y, hl} =$


$t_{B \rightarrow Y, lh} =$
 
## Propagation and Contamination Delay Modeling

- We want to improve the accuracy of the constant delay model but without the more complex of delay models
- \_\_\_\_\_ ( $t_{pd}$ ) = maximum time from when input changes until the output reaches final value
- \_\_\_\_\_ ( $t_{cd}$ ) = minimum time from when input changes until any output changes its value (might not be final value)



 
- Constant Delay Model  
(with propagation and contamination delays)



$$t_{pd} =$$

$$t_{cd} =$$

 - Input-Dependent Constant Delay Model  
(with propagation and contamination delays)



$$t_{pd,A \rightarrow Y} =$$

$$t_{cd,A \rightarrow Y} =$$



$$t_{pd,B \rightarrow Y} =$$

$$t_{cd,B \rightarrow Y} =$$

- Propagation and contamination delay modeling is conservative but simplifies our analysis
  
## Complete the timing diagrams for a NAND gate.


- Constant Delay Model  
(with propagation and contamination delays)



$$t_{pd} = 2\tau$$

$$t_{cd} = 1\tau$$

 - Input-Dependent Constant Delay Model  
(with propagation and contamination delays)



$$t_{pd,A \rightarrow Y} = 2\tau$$

$$t_{cd,A \rightarrow Y} = 1\tau$$


$$t_{pd,B \rightarrow Y} = 1.5\tau$$

$$t_{cd,B \rightarrow Y} = 1\tau$$


## 5.2. Combinational Gate-Level Network Timing

- Apply our delay model to all gates in a gate-level network
- Analyze all paths from every input to every output in network
- \_\_\_\_\_ = longest path through a gate-level network (only consider propagation delays!)
- \_\_\_\_\_ = shortest path through a gate-level network (only consider contamination delays!)

 
### 5.3. Combinational Gate-Level Network Timing



Gate	$t_{pd}$	$t_{cd}$
NOT	$1\tau$	$1\tau$
NAND2	$2\tau$	$1\tau$
NOR2	$3\tau$	$1\tau$

 



 


Gate	$t_{pd}$	$t_{cd}$
NOT	$1\tau$	$1\tau$
NAND2	$2\tau$	$1\tau$
NOR2	$3\tau$	$1\tau$


Path	Propagation Delay	Contamination Delay
A → NOT → NAND2 → NOR2 → Y		
B → NAND2 → NOR2 → Y		
C → NOT → NOR2 → Y		

- Which path is the critical path?
- Which path is the short path?

 Complete the timing diagram and table for given gate-level network.



Gate	$t_{pd}$	$t_{cd}$
NOT	$1\tau$	$1\tau$
NAND2	$2\tau$	$1\tau$
NOR2	$3\tau$	$1\tau$

 

Path	Propagation Delay	Contamination Delay

## 6. Verilog Modeling of Combinational Logic

- Verilog is not a programming language (PL), it is a hardware description language (HDL)
- \_\_\_\_\_ = portion of the language that models real hardware
- \_\_\_\_\_ = portion of the language that does not model real hardware but is instead used to test hardware
- We will *simulate* designs implemented in Verilog to verify their functionality
- We will *synthesize* designs implemented in Verilog to map them to real hardware in the lab using a field programmable gate array


### Verilog Datatypes

- All signals in Verilog can have one of four values:
  - Logic 1
  - Logic 2
  - X (undefined value or don't care about specific value)
  - Z (floating)


It is critical to always keep in mind the  
*real hardware* you are trying to model using Verilog!
 
## 6.1. Modeling Logic Gates in Verilog


- Declare wires using `wire`
- Instantiate logic gate primitives (e.g., `not`, `and`)
- List wires to connect them to inputs and outputs, output is first
- Logic gates with more than two inputs are allowed



 
```
1 wire a;
2 wire y;
3 not( y, a );
```



 
```
1 wire a;
2 wire b;
3 wire y;
4 and( y, a, b );
```



 
```
1 wire a;
2 wire b;
3 wire y;
4 nand( y, a, b );
```



 
```
1 wire a;
2 wire b;
3 wire y;
4 or( y, a, b );
```


 
```
1 wire a;
2 wire b;
3 wire y;
4 nor( y, a, b );
```


 
```
1 wire a;
2 wire b;
3 wire y;
4 xor( y, a, b );
```




```
1 wire a;
2 wire b;
3 wire y;
4 xnor( y, a, b );
```

- What if one of the inputs is X?
- Consider an AND gate

A	B	Y
0	X	
1	X	
X	0	
X	1	
X	X	
 
## 6.2. Modeling Gates-Level Netlists in Verilog




```

1 wire a;
2 wire b;
3 wire c;
4 wire x;
5 wire y;
6
7 and( x, a, b );
8 or ( y, x, c );

```

### Defining Hardware Modules in Verilog

 


```

1 module AndOr
2 (
3     input wire a,
4     input wire b,
5     input wire c,
6     output wire y
7 );
8
9     wire x;
10
11     and( x, a, b );
12     or ( y, x, c );
13
14 endmodule

```

<https://www.edaplayground.com/x/KjwN>
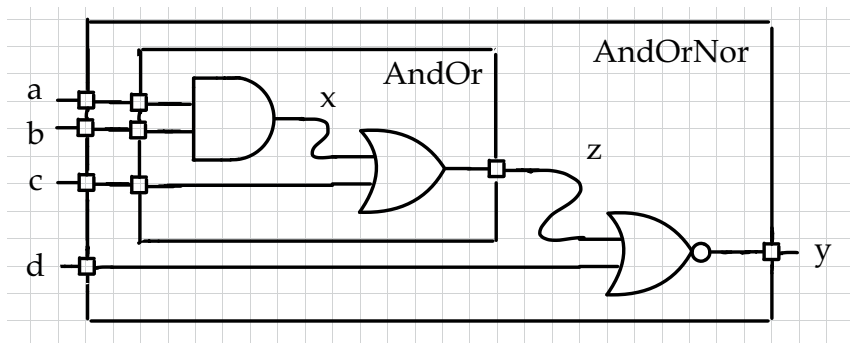
## Instantiating Hardware Modules in Verilog




```


1 module AndOrNor
2 (
3     input wire a,
4     input wire b,
5     input wire c,
6     input wire d,
7     output wire y
8 );
9
10 wire z;
11
12 AndOr and_or
13 (
14     .a (a),
15     .b (b),
16     .c (c),
17     .y (z)
18 );
19
20 or( y, z, d );
21
22 endmodule

```

 **Implement the following gate-level network in Verilog.** Match the coding style from the previous examples.



## 6.3. Modeling Delays in Verilog

 

Gate	$t_{pd}$	$t_{cd}$
NOT	$1\tau$	$1\tau$
NAND2	$2\tau$	$1\tau$
NOR2	$3\tau$	$1\tau$

```

1 module NorNand
2 (
3     input wire a,
4     input wire b,
5     output wire y
6 );
7
8     wire x;
9
10    nor #(3) ( x, a, b );
11    nand #(2) ( y, x, b );
12
13 endmodule

```

<https://www.edaplayground.com/x/Hpjf>



## 7. Summary of Abstractions

