 



2. Finite-State Machines



- *Finite state machines* (FSM) are abstractions for sequential gate-level networks
 - Finite number of inputs (A)
 - Finite number of outputs (Y)
 - Finite number of states (S)
 - Designated reset state
 - FSM next-state equation ($S_{next}(S, A)$)
 - FSM output equation ($Y(S)$ or $Y(S, A)$)
- Two kinds of FSMs
 - Moore FSMs: Outputs only depend on current state ($Y(S)$)
 - Mealy FSMs: Outputs depend on current state and inputs ($Y(S, A)$)
- FSMs can be represented using:
 - FSM diagrams
 - FSM next state and output tables (i.e., truth tables)
 - FSM next state and output equations

2.1. FSM Abstraction Triangle

Diagrams

 

Next State & Output Tables

S_1	S_0	$S_{1,next}$	$S_{0,next}$	Y
0	0	0	1	0
0	1	1	0	0
1	0	1	1	0
1	1	0	0	1


Next State & Output Equations

$$S_{0,next} = \overline{S_1} \overline{S_0} + S_1 \overline{S_0}$$

$$S_{1,next} = \overline{S_1} S_0 + S_1 \overline{S_0}$$


$$Y = S_1 S_0$$

Gate-Level Networks

 

2.2. Moore FSMs

FSM Diagram

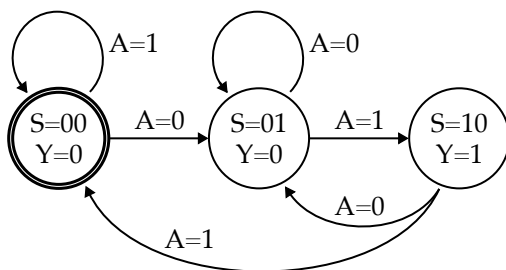

FSM Next State and Output Table

S_1	S_0	A	$S_{1,next}$	$S_{0,next}$	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			

FSM Implicit-Clock Simulation Table


cycle	S	A	S_{next}	Y
0	00	0	01	0
1		0		
2		1		
3		0		
4		0		
5		0		
6		1		
7		1		
8		0		
9		1		
10		0		

FSM Next State and Output Equations


		S_1S_0			
		00	01	11	10
A	0				
	1				

		S_1S_0			
		00	01	11	10
A	0				
	1				


		S_1S_0			
		00	01	11	10
A	0				
	1				

 

FSM Sequential Gate-Level Network

 

 Implement the following FSM at the gate level.



What does this FSM do?

S_1	S_0	A	$S_{1,next}$	$S_{0,next}$	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			


$A \backslash S_1 S_0$	00	01	11	10
0				
1				

$A \backslash S_1 S_0$	00	01	11	10
0				
1				

$A \backslash S_1 S_0$	00	01	11	10
0				
1				

2.3. Mealy FSMs

FSM Diagram

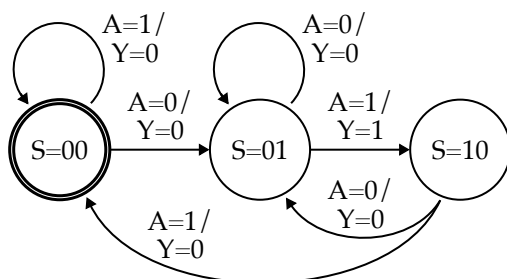

FSM Next State and Output Table

S_1	S_0	A	$S_{1,next}$	$S_{0,next}$	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			

FSM Implicit-Clock Simulation Table


cycle	S	A	S_{next}	Y
0	00	0	01	0
1		0		
2		1		
3		0		
4		0		
5		0		
6		1		
7		1		
8		0		
9		1		
10		0		

FSM Next State and Output Equations

A \ S_1S_0	00	01	11	10
	0			
1				

A \ S_1S_0	00	01	11	10
	0			
1				


A \ S_1S_0	00	01	11	10
	0			
1				

 FSM Sequential
Gate-Level Network

Optimized FSM Diagram

 2.4. FSM State Encoding

- Often there is freedom in choosing how to encode the states
- Different encodings result in different FSM next state and output equations (and thus produce different gate-level implementations)
- Two common FSM encodings
 - *Binary encoding* uses a binary to encode each state
 - *One-hot encoding* uses a separate bit to encode each state




S_2	S_1	S_0	A	$S_{1,next}$	$S_{1,next}$	$S_{0,next}$	Y
0	0	1	0				
0	0	1	1				
0	1	0	0				
0	1	0	1				
1	0	0	0				
1	0	0	1				

2.5. Designing FSMs

- Step 1. Understand problem statement, determine inputs/outputs
- Step 2. Choose Moore vs. Mealy, identify states, create state diagram
- Step 3. Determine state encoding
- Step 4. Create FSM next state and output tables
- Step 5. Determine FSM next state and output equations



Design an FSM with one input (A) and two outputs (Y, Z) which monitors the input and sets Y to one when it has seen two or more consecutive ones and sets Z to one when it has seen three or more consecutive ones.

 Step 1. Understand problem statement, determine inputs/outputs



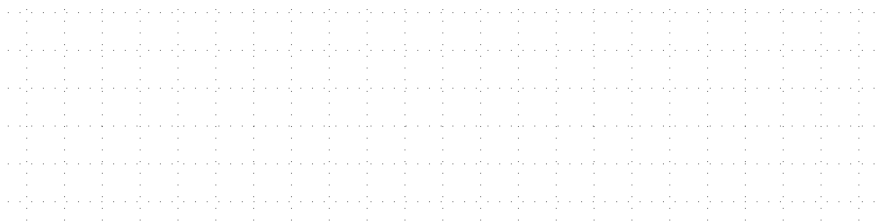 
Step 2. Choose Moore vs. Mealy, identify states, create state diagram




Step 3. Determine state encoding**Step 4. Create FSM next state and output tables****Step 3. Determine FSM next state and output equations**

 2.6. Factoring FSMs


- Design a FSM for a traffic light controller
- Four-way intersection with traffic lights
- Opposing lanes sequence together
 - Turn on green light for 20 seconds
 - Turn on yellow light for 5 seconds
 - Turn on red light for 25 seconds
- Four scenarios
 - E/W green and N/S red for 20 seconds
 - E/W yellow and N/S red for 5 seconds
 - E/W red and N/S green for 20 seconds
 - E/W red and N/S yellow for 5 seconds




- Requires an FSM with 10 states
 - E/W green and N/S red1 for 5 seconds
 - E/W green and N/S red2 for 5 seconds
 - E/W green and N/S red3 for 5 seconds
 - E/W green and N/S red4 for 5 seconds
 - E/W yellow and N/S red for 5 seconds
 - E/W red and N/S green1 for 5 seconds
 - E/W red and N/S green2 for 5 seconds
 - E/W red and N/S green3 for 5 seconds
 - E/W red and N/S green4 for 5 seconds
 - E/W red and N/S yellow for 5 seconds

 

 
- Factoring FSMs involves breaking an FSM into multiple communicating FSMs
 - Simplifies large FSMs
 - May result in fewer states
- **Light Controller (LC) FSM has 4 states**
 - **G/R, Y/R, R/G, R/Y**
- **Timer FSM controls when the LC FSM advances to the next state**
 - **Keeps LC in Green states for 4 clock cycles**



Light Controller (LC) FSM

 

Timer FSM

 


3. Verilog Modeling

3.1. Gate-Level Modeling of FSMs


```

1 module MooreDetect01_GL
2 (
3   input wire clk,
4   input wire rst,
5   input wire a,
6   output wire y
7 );
8   // Sequential: state flip-flops
9
10  wire s0, s0_next;
11
12  DFFR_GL s0_dffr
13  (
14    .clk (clk),
15    .rst (rst),
16    .d   (s0_next),
17    .q   (s0)
18  );
19
20  wire s1, s1_next;
21
22  DFFR_GL s1_dffr
23  (
24    .clk (clk),
25    .rst (rst),
26    .d   (s1_next),
27    .q   (s1)
28  );
29
30  // Combinational: next state logic
31
32  not( s0_next, s0 );
33  and( s1_next, s0, a );
34
35  // Combinational: output logic
36
37  assign y = s1;
38
39 endmodule

```

 
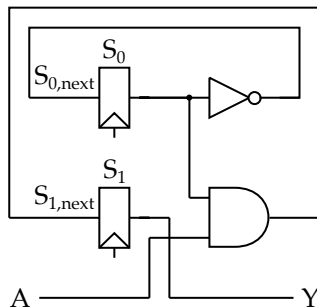
$$\begin{aligned}
 S_{1,next} &= S_0 A \\
 S_{0,next} &= \overline{A} \\
 Y &= S_1
 \end{aligned}$$




Implement 00/11 detector in Verilog using gate-level modeling.

```

1 module MooreDetect00or11_GL
2 (
3   input wire clk,
4   input wire rst,
5   input wire a,
6   output wire y
7 );
8   // Sequential: state flip-flops
9
10  wire s0, s0_next;
11  DFFR_GL s0_dffr( .clk(clk), .rst(rst), .d(s0_next), .q(s0) );
12
13  wire s1, s1_next;
14  DFFR_GL s1_dffr( .clk(clk), .rst(rst), .d(s1_next), .q(s1) );

```

 

```

1 endmodule


```

3.2. RTL Modeling of FSMs

```

1 module MooreDetect01_RTL
2 (
3   input logic clk,
4   input logic rst,
5   input logic a,
6   output logic y
7 );
8   localparam STATE_S0 = 2'b00;
9   localparam STATE_S1 = 2'b01;
10  localparam STATE_S2 = 2'b10;
11
12  // Sequential: state register
13  logic [1:0] state, state_next;
14  Register_2b_RTL state_reg
15  (
16    .clk (clk),
17    .rst (rst),
18    .d   (state_next),
19    .q   (state)
20  );
21
22  // Combinational: next state logic
23  always_comb begin
24    case ( state )
25      STATE_S0 : state_next = ( a ) ? STATE_S0 : STATE_S1;
26      STATE_S1 : state_next = ( a ) ? STATE_S2 : STATE_S1;
27      STATE_S2 : state_next = ( a ) ? STATE_S1 : STATE_S0;
28      default  : state_next = 'x;
29    endcase
30  end
31
32  // Combinational: output logic
33  always_comb begin
34    case ( state )
35      STATE_S0 : begin y = 0; end
36      STATE_S1 : begin y = 0; end
37      STATE_S2 : begin y = 1; end
38      default  : state_next = 'x;
39    endcase
40  end
41
42 endmodule

```

 


Implement 00/11 detector in Verilog using RTL modeling.

```

1 module MooreDetect00or11_RTL
2 (
3   input logic clk, input logic rst,
4   input logic a, output logic y
5 );
6 // Sequential: state register
7 localparam STATE_S0 = 2'b00;
8 localparam STATE_S1 = 2'b01;
9 localparam STATE_S2 = 2'b10;
10 localparam STATE_S3 = 2'b11;
11 logic [1:0] state, state_next;
12 Register_2b_RTL state_reg( .clk(clk), .rst(rst),
13                           .d(state_next), .q(state) );

```

 

```

1 endmodule

```