

ECE 2300
Digital Logic & Computer Organization
Spring 2025

CMOS Logic



Cornell University

Announcements

- **Links to lecture recordings & previous quiz questions are in the pinned post on Ed**


A Little Bit of History

- **Transistors**

- Invented by John Bardeen, Walter Brattain, and William Shockley at Bell Labs in 1947

- **Integrated circuits (IC)**

 - Independently developed by Jack Kilby (at TI) and Robert Noyce (at Fairchild) in the 1950s
- Robert Noyce and Gordon Moore founded Intel in 1968




Technology scaling of CMOS transistors

<https://www.tsmc.com/english/dedicatedFoundry/technology/logic>

MOS Transistors

- **Metal-Oxide Semiconductor Field-Effect Transistors (MOSFETs)**


– **MOS for short**

 

A 3-terminal device that changes its conductance (or resistance) based on the voltage applied to the gate terminal

- **Extreme changes in resistance (0 to ∞) make transistors act like switches**

MOSFET

 

(cross-section view of a MOSFET)

MOS: three materials needed to make a transistor


- Metal: strong conductor of current
- Oxide: insulator (does not conduct)
- Semiconductor: conduction can be controlled

FET: Field Effect Transistor


- Acts as a voltage-controlled switch: gate voltage creates electric field that turns on/off connection between source and drain
 - Two types of switches: active low and active high
(active = connection is on)

NOT Gate Using Switches

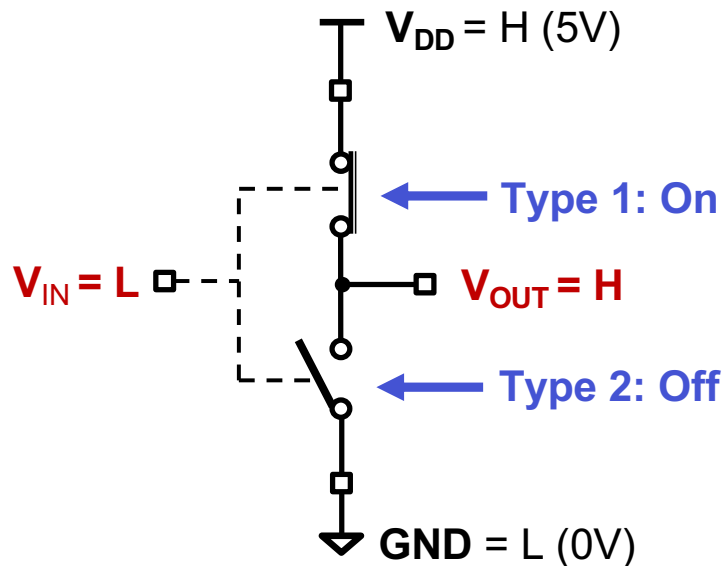- Can build an inverter using two types of complementary switches
 - Type 1 (active low): ON when input = 0, OFF when input = 1
 - Type 2 (active high): ON when input = 1, OFF when input = 0



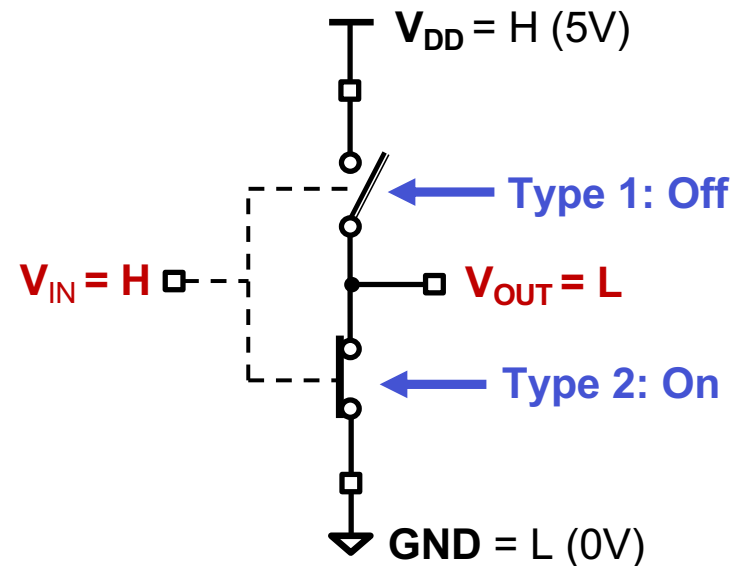
When input voltage is low, output is connected to voltage supply (V_{DD})




When input voltage is high, output is connected to ground (GND)

Two Types of MOS Transistors

 - PMOS: Type 1 switch; NMOS: Type 2 switch
- Current flows when ON (*conducting*)
- No current flows when OFF (*not conducting*)



Type 1 (active low)

 

Type 2 (active high)


G: Gate S: Source D: Drain

○ Bubble indicates active low

Two Types of MOS Transistors


- **PMOS**

 - Closed when input is low ^[1]
- Open when input is high
- Passes a good one
(but a poor zero) ^[2]



- **NMOS**

 - Closed when input is high ^[1]
- Open when input is low
- Passes a good zero
(but a poor one) ^[2]




PMOS and NMOS
have
complementary
properties

[1] In both cases, the voltage difference between gate and source must exceed a certain threshold voltage before the the transistor starts having any effect.



[2] Optional reading: vlsimsee.blogspot.com/2013/05/why-cant-nmos-pass-1-and-pmos-pass-0.html

CMOS Logic Gates

 - **Complementary MOS (CMOS)**
 - CMOS dominates the digital IC market
- **Uses both NMOS and PMOS devices such that there is no direct supply-ground path**
 - Dissipates little power when the inputs don't change
- **Our focus: Static CMOS gates**
 - Other types exist as well (pseudo-NMOS, domino, ...)



CMOS Inverter

  


A is high
Q1 is on
Q2 is off
Z is low

A is low
Q1 is off
Q2 is on
Z is high

→

A	Z
L	H
H	L


CMOS NAND Gate

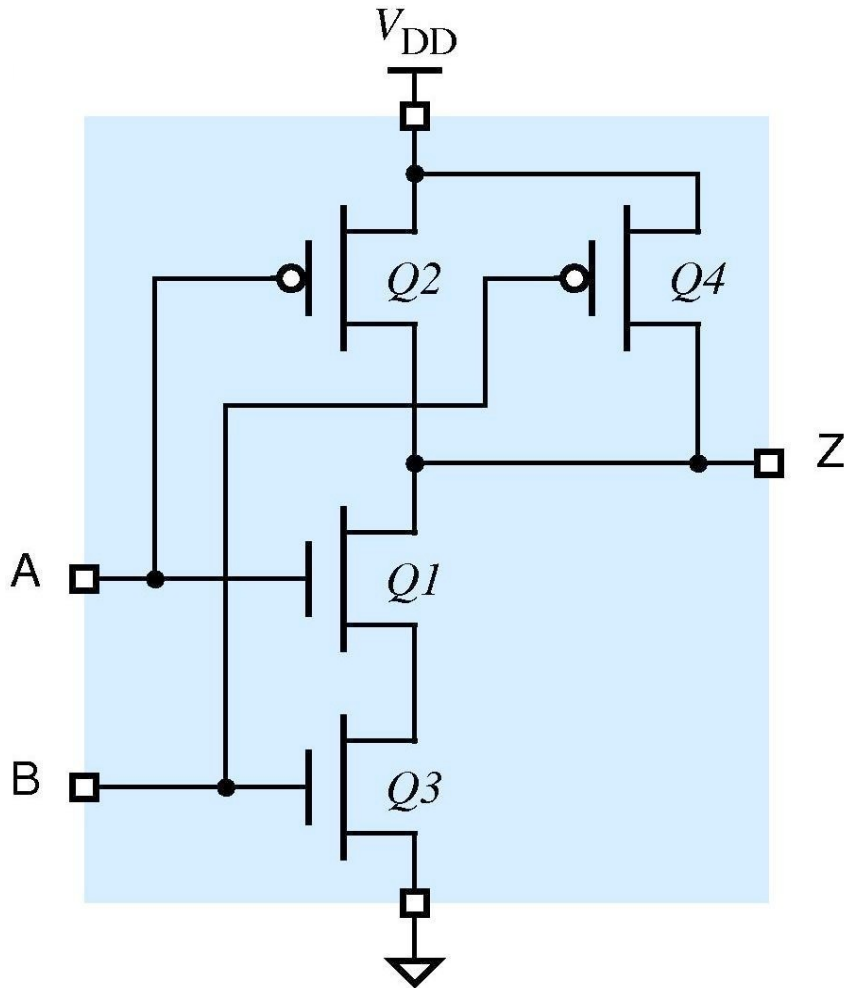


A	B	<i>Q1</i>	<i>Q2</i>	<i>Q3</i>	<i>Q4</i>	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	H
H	L	on	off	off	on	H
H	H	on	off	on	off	L



3 Input CMOS NAND Gate

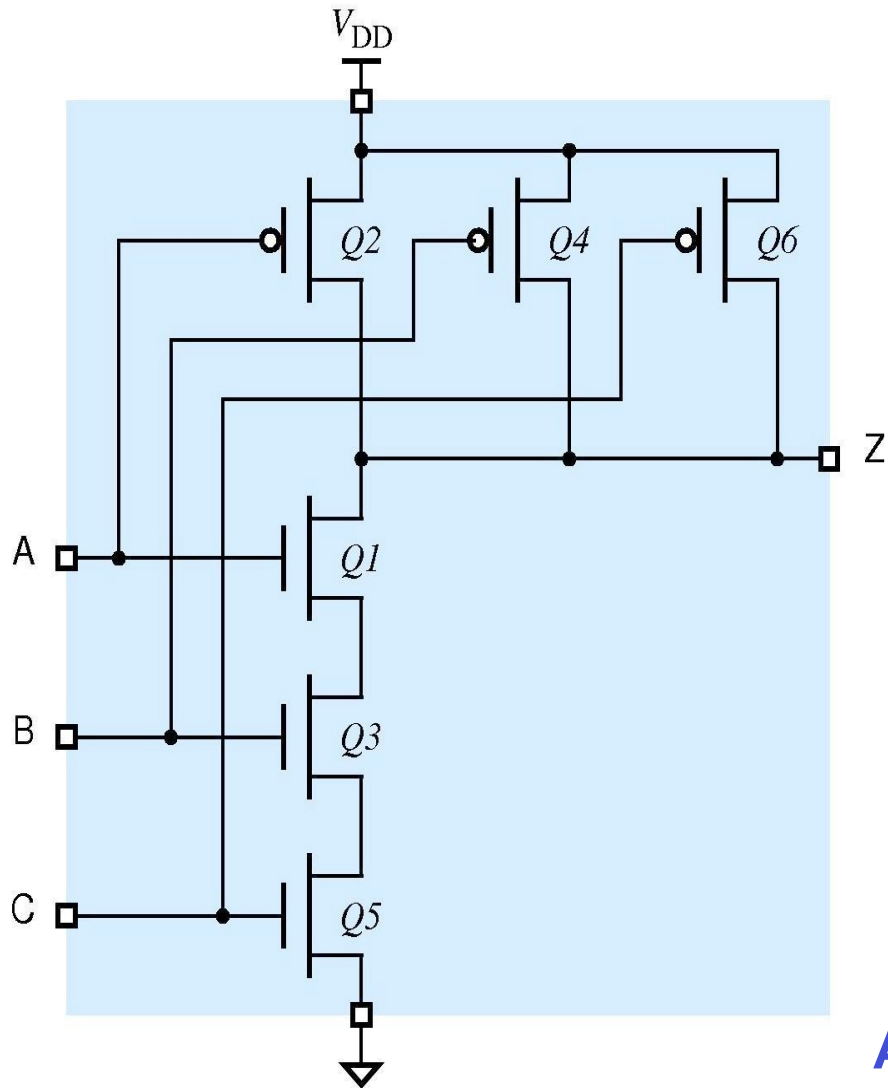


A	B	C	Q1	Q2	Q3	Q4	Q5	Q6	Z
L	L	L	off	on	off	on	off	on	H
L	L	H	off	on	off	on	on	off	H
L	H	L	off	on	on	off	off	on	H
L	H	H	off	on	on	off	on	off	H
H	L	L	on	off	off	on	off	on	H
H	L	H	on	off	off	on	on	off	H
H	H	L	on	off	on	off	off	on	H
H	H	H	on	off	on	off	on	off	L

 


An n -input NAND uses $2n$ transistors

Another “Mystery” Gate

 

2-Input AND Gate in CMOS

 - CMOS gates produce inherent inversion
- Need to invert to the output of NAND to implement an AND gate




A	B	Q1	Q2	Q3	Q4	Q5	Q6	Z
L	L	off	on	off	on	on	off	L
L	H	off	on	on	off	on	off	L
H	L	on	off	off	on	on	off	L
H	H	on	off	on	off	off	on	H




Structure of Transistor Networks

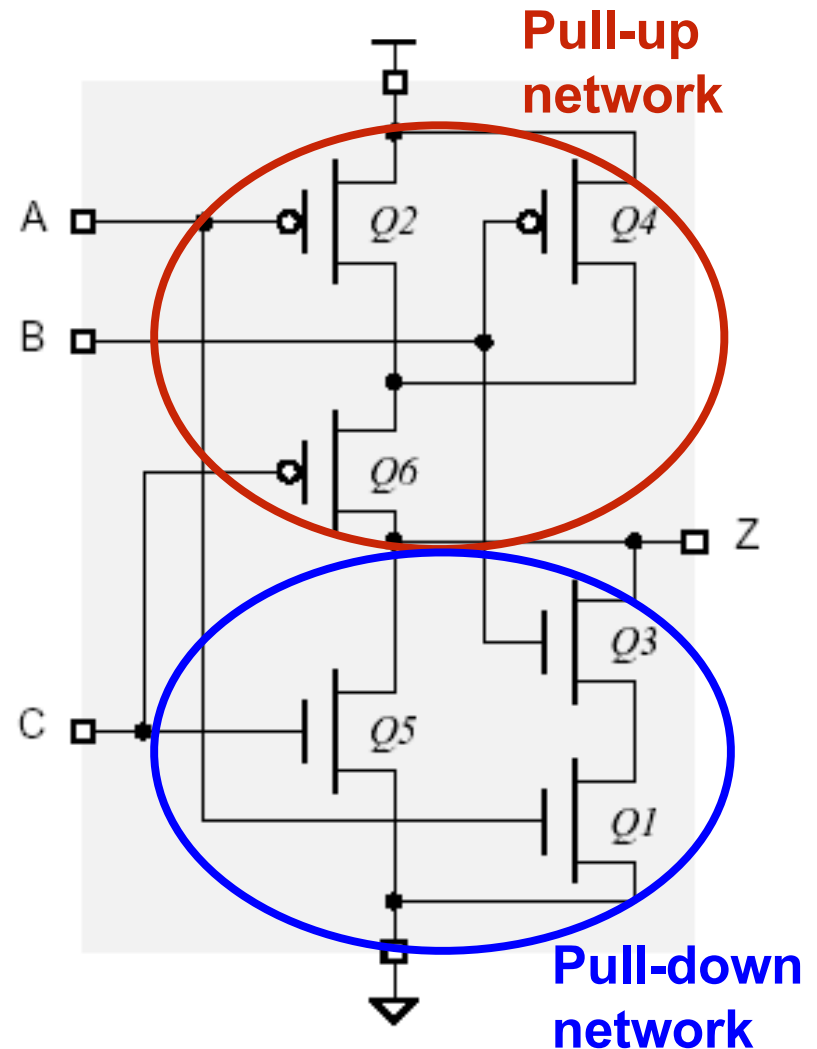- **Two complementary networks**
 - A pull-up network composed of PMOS, with sources tied to voltage supply
 - A pull-down network composed of NMOS, with sources tied to ground
 - Equal number of NMOS and PMOS transistors



Structure of Transistor Networks

 
- The pull-up and pull-down networks are always duals
- To construct the dual of a network:
 - Exchange NMOS for PMOS (and vice versa)
 - Exchange series subnets for parallel subnets (and vice versa)
 - This transformation applies to hierarchical structures



Series and Parallel Subnets


- **Parallel**

 - *At least one* input must be 0 (p-type) or 1 (n-type) to make the connection




- **Series**

 
- *All* inputs must be 0 (p-type) or 1 (n-type) to make the connection



Duality of Parallel/Series Subnets

 


=

 


p-type parallel subnet
F pulls up to 1 when
A or B is low =>
 $F = A' + B' = (A \cdot B)'$

 n-type series subnet
F pulls down to 0 when
A and B are high =>
 $F = (A \cdot B)'$



=

 


n-type parallel subnet
F pulls down to 0 when
A or B is high =>
 $F = (A + B)'$

p-type series subnet
F pulls up to 1 when
A and B are low =>
 $F = A' \cdot B' = (A + B)'$

Analysis of Transistor Networks

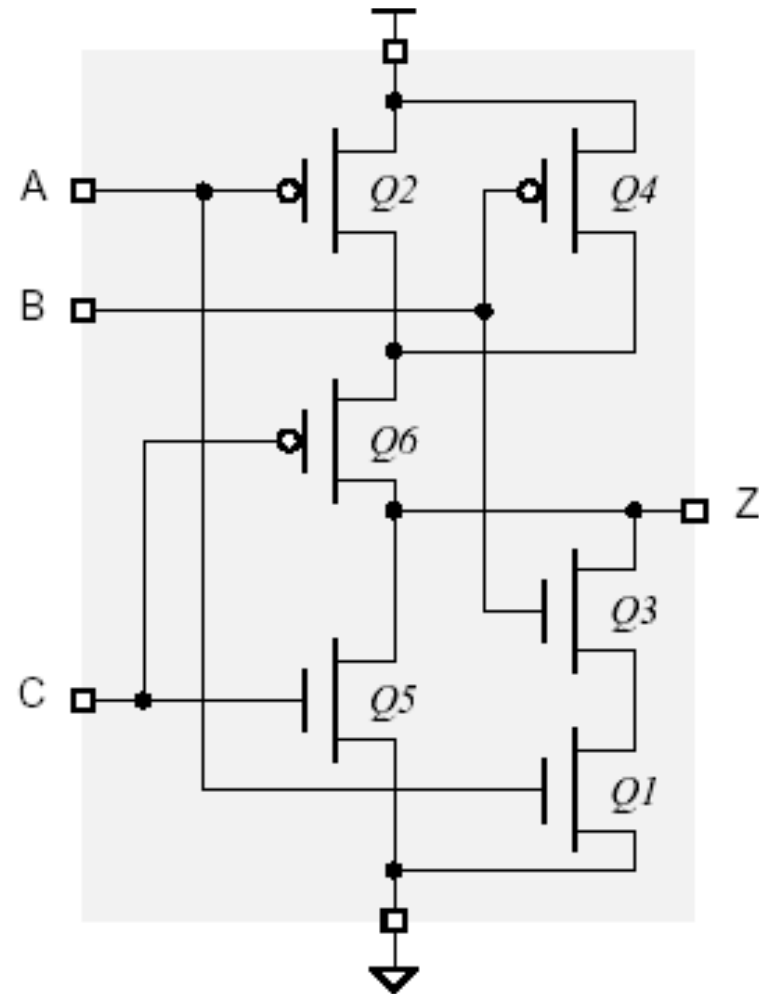
- **Transistor states**
 - Determine all possible input combinations
 - Figure out the state of each transistor
 - Determine final output
- **or by inspection**
 - Figure out what input combinations cause a 1 (or a 0) output



Analysis of Transistor Networks

- **By inspection**

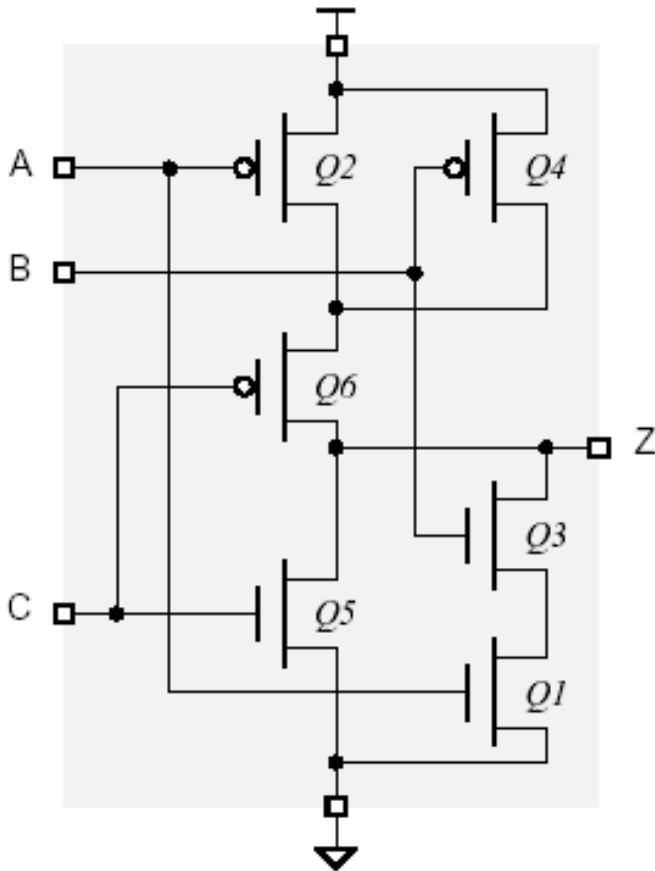- Inspect *either* pull-up (PMOS) or pull-down (NMOS) network
- Translate the series (parallel) subnets into product (sum) terms
- For pull-down network, negate the combined expression




Pull-up: $(A'+B')C'$


||

Pull-down: $(A \cdot B + C)'$

A More Complicated Circuit

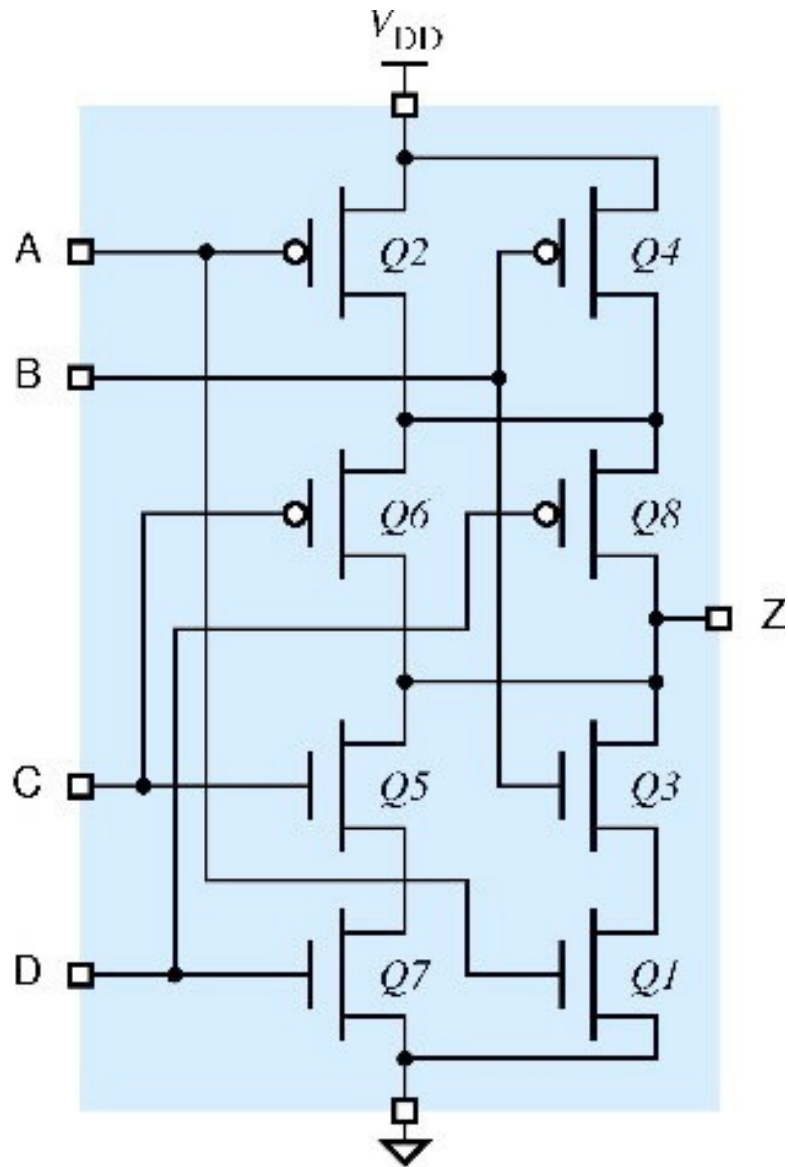

A More Complicated Circuit

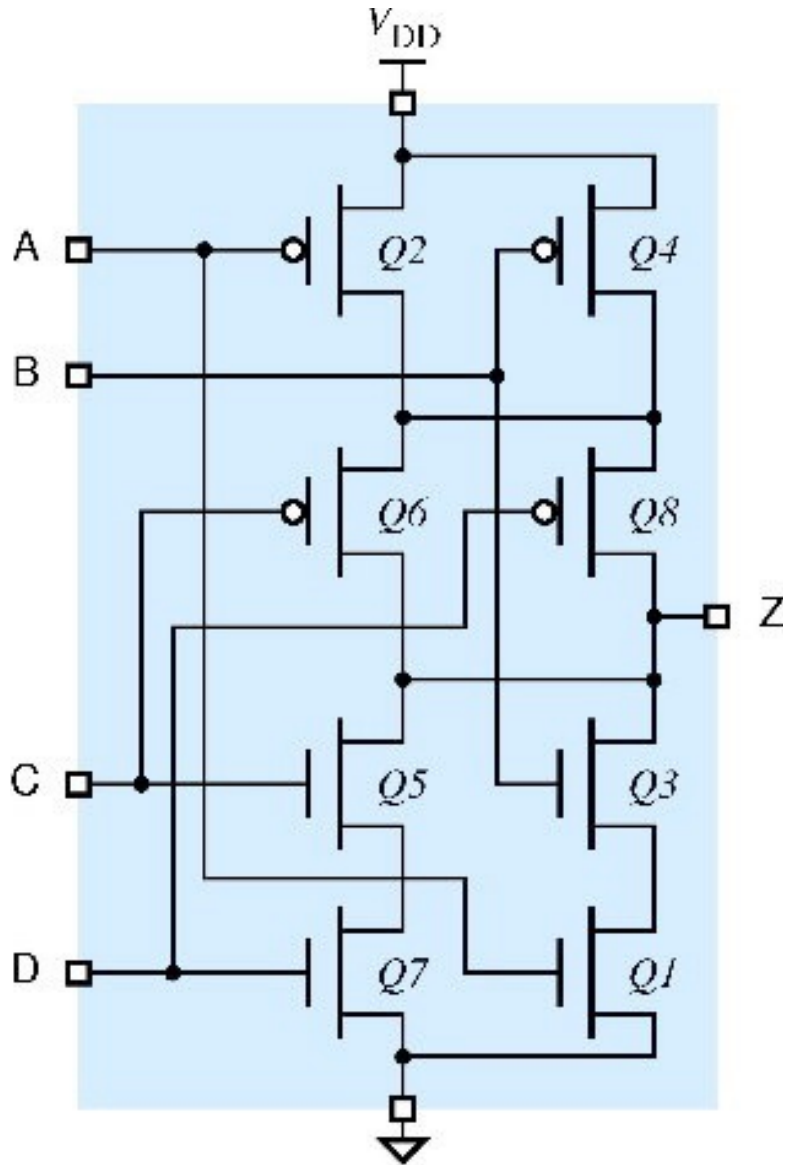


Pull-up: $(A'+B') \cdot (C'+D')$

Pull-down: $(A \cdot B + C \cdot D)'$


Constructing CMOS Gate from Boolean Expression

 Example: $F = (A \cdot (B + C))'$


Step 1. Figure out pull-down network that does what you want (e.g., what combination of inputs generates a low output)



 Step 2. Walk the hierarchy replacing NMOS with PMOS, series subnets with parallel subnets, and parallel subnets with series subnets




 Step 3. Combine PMOS pull-up network (from Step 2) with NMOS pull-down network (from Step 1) to form a fully-complementary CMOS gate



CMOS Sanity Checks

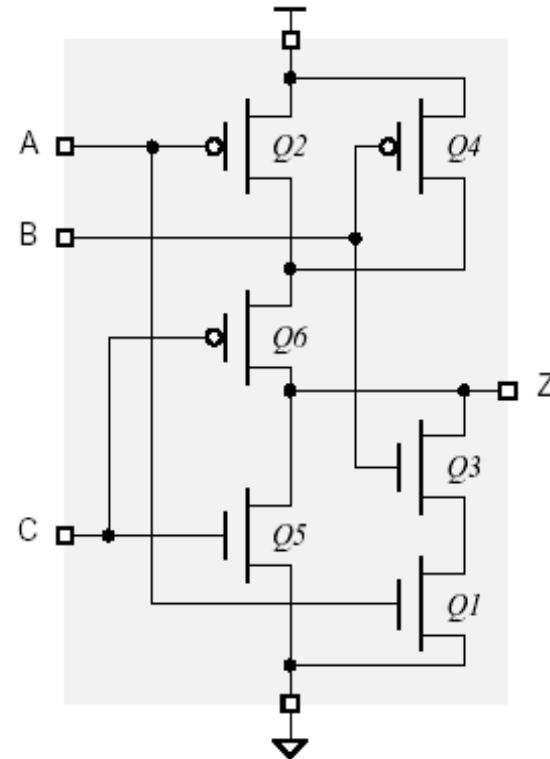- Equal number of NMOS and PMOS
- NMOS sources tied to ground or to drain of another NMOS
- PMOS sources tied to Vdd or drain of another PMOS
- Inputs tied to pairs of PMOS and NMOS transistors



Next Class

**Sequential Logic: Clocks,
Latches, Flip-Flops
(H&H 3.1-3.2)**