

ECE 2300
Digital Logic & Computer Organization
Spring 2025

Sequential Logic:
Clocks
Latches
Flip-Flops



Cornell University



Announcements

- HW 2 due tomorrow
- HW 3 will be posted today

CMOS Logic: True or False?

1. NMOS is an active low switch
2. PMOS (pull-up) network passes a poor zero
3. NMOS and PMOS networks can be ON at the same time
4. A CMOS gate consists of an even number of transistors
5. A 2-input NOR requires 2 transistors

2-Input NOR Gate in CMOS

 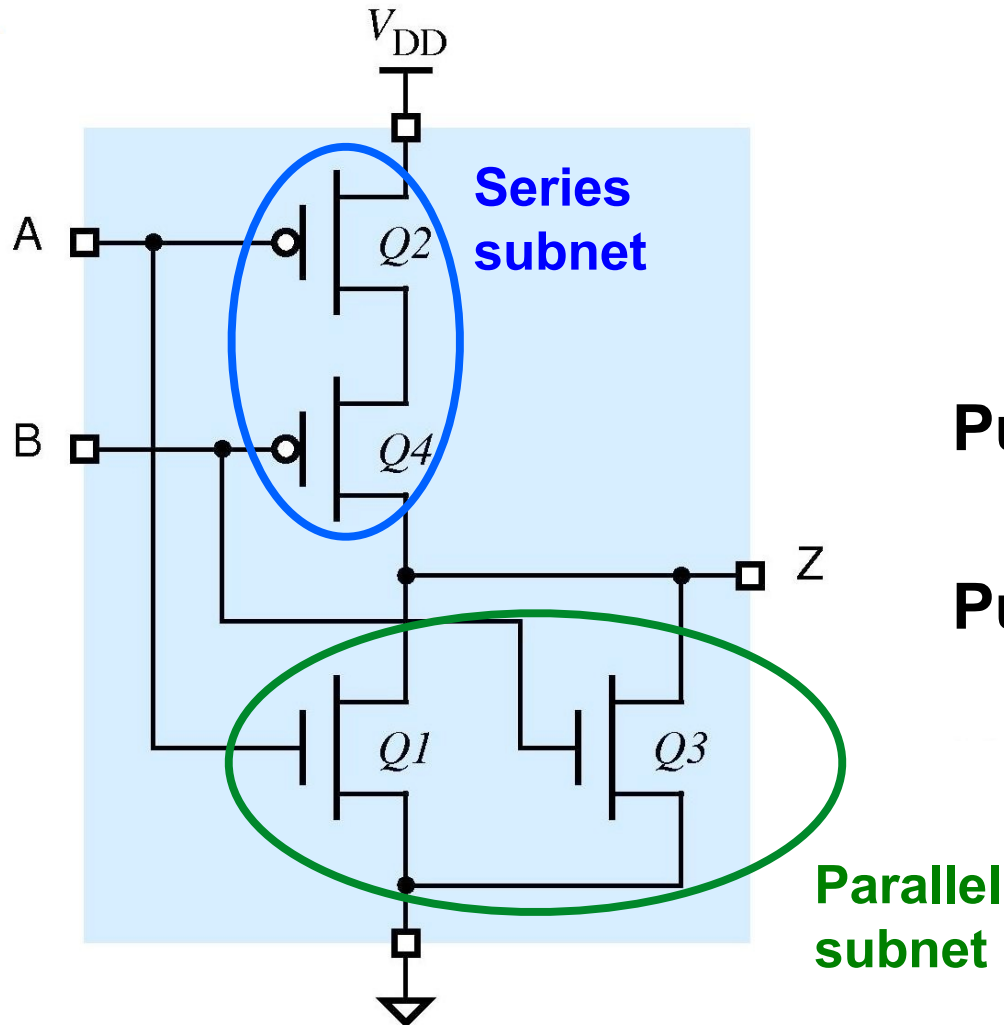

Pull-up: $A' \cdot B'$


Pull-down: $(A+B)'$

Combinational vs. Sequential Circuits

Combinational Circuit



Sequential Circuit

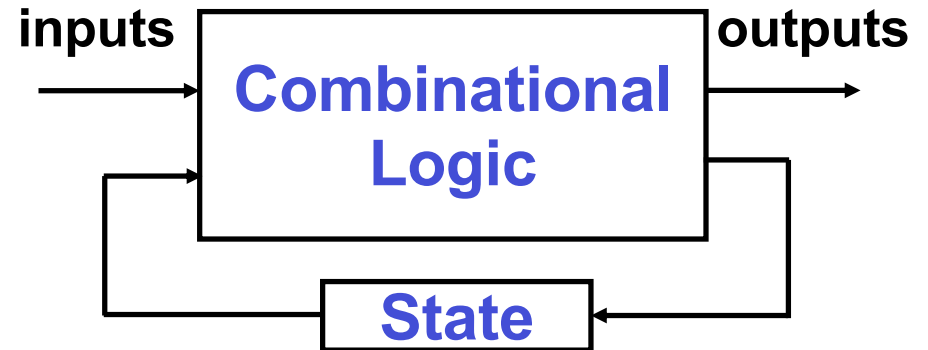

- **Combinational**

- Output depends only on current inputs

- **Sequential**

- Output depends on current inputs plus *state* (past history)
- Requires memory


Sequential Circuits

- **Outputs depend on inputs and state variables**
- **The state variables embody the past history of the circuit**
 - **Storage elements hold the state variables**
- **A clock periodically advances the circuit**

Basic Storage Element

Bistable Element


 
- Basic storage element
- Inverters with outputs connected to inputs



- What does the circuit do?

Bistable = Two Stable States

  
- Two inverters with outputs connected to inputs
- Bistable element stores a “given” value indefinitely (as long as powered)




How can we change the stored value?
(Extra inputs are required)

Revisit 2-input NOR

- NOR can implement an inverter

 


- NOR has a **null element**

 

A NOR gate outputs 0 when one of the inputs is 1, regardless of the value of the other input

S-R Latch (Set-Reset Latch)

 

Q_{next} is new state of Q
when R or S changes

Set (S) and Reset (R) inputs
allow (re)setting stored value

Hold: both NORs act as inverters,
forming a bi-stable element

Reset/Set: the null element of
NOR ("1") is in effect


Hold state

Reset

Set

S	R	Q_{next}
0	0	
0	1	
1	0	
1	1	

S-R Latch (Set-Reset Latch)

 

Boolean expression for Q_{next} in terms of R, S, Q:


$$\begin{aligned}
 Q_{next} &= (R + QN)' \\
 &= (R + (S + Q)')' \\
 &= R' \cdot (S + Q) \\
 &= R' \cdot S + R' \cdot Q
 \end{aligned}$$

S	R	$R' \cdot S$	$R' \cdot Q$	Q_{next}
0	0	0	Q	(Last) Q
0	1	0	0	0
1	0	1	Q	1
1	1	0	0	0

When $SR=00$, it holds (*latches*) the previous state

Avoid $SR = 11$

Exercise: S-R Latch

 

- Suppose the S-R latch is initialized with $Q=0$, write down the next state given the following input sequence


$$S=1, R=0 \rightarrow Q = ?$$

$$S=0, R=0 \rightarrow Q = ?$$

$$S=0, R=1 \rightarrow Q = ?$$


Instability (**Avoid SR=11**)

- **SR=11 may cause instability of the internal state**
 1. When **SR=11** \rightarrow **Q=QN=0**
 2. If inputs subsequently change to **SR=00**, output may be undefined

 


Revisit 2-input NAND

- **NAND can implement an inverter**

 


- **NAND has a null element**

 

A NAND gate outputs 1 when one of the inputs is 0, regardless of the value of the other input

\overline{S} - \overline{R} Latch

 - *S-bar-R-bar latch*: Built from NAND gates




D Latch

- **D latch: builds on S-R latch where S and R cannot be both 1**
 - **Output “follows” input**
- **D latch captures input data (what to set) when certain condition holds (when to set)**
- **Operates in two modes**
 - **Open (or enabled): input flows through to output**
 - **Closed (or disabled): output does not change**

D Latch

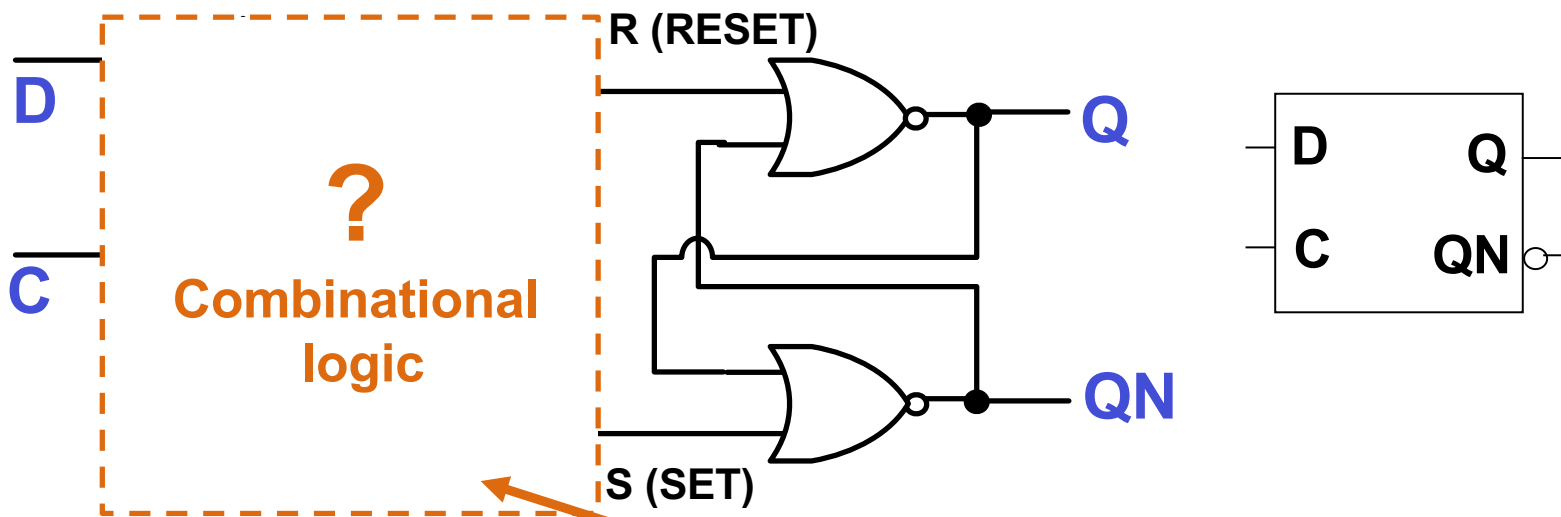- When C is enabled, Q output follows D input
- When C is disabled, Q output retains last state





Can we build a D latch using an SR latch as a building block?

C	D	R	S	Q _{next}
1	0			0
1	1			1
0	X			(Last) Q

D Latch

 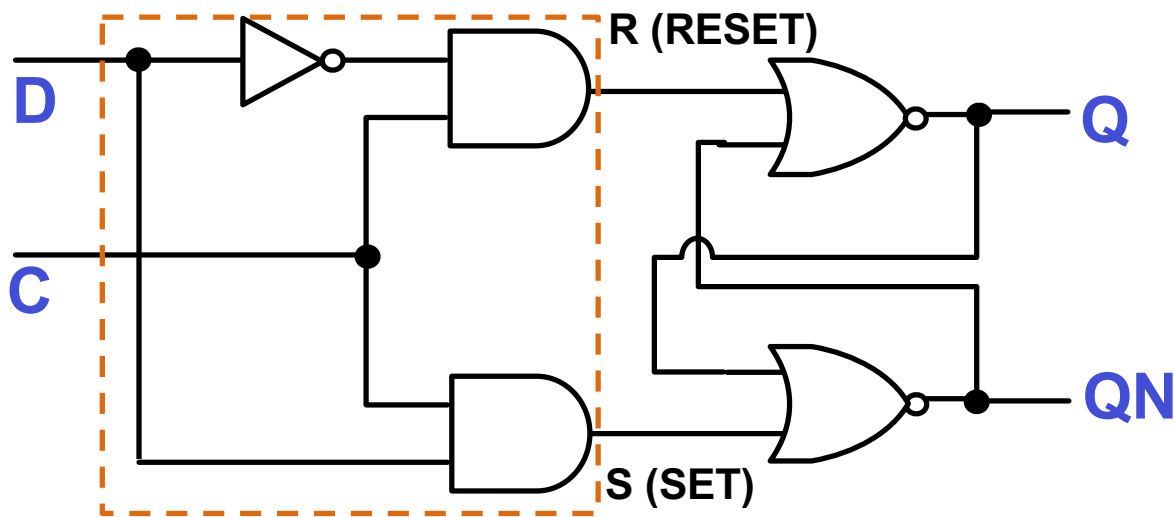- When C is enabled, Q output follows D input
- When C is disabled, Q output retains last state




$$R = C \cdot D'$$
$$S = C \cdot D$$

C	D	R	S	Q _{next}
1	0	1	0	0
1	1	0	1	1
0	X	0	0	(Last) Q


Multi-Bit Latch

 - Simultaneously latches multiple bits
- “Latch” may refer to 1 bit latch or multi-bit one



Clock

 
- An input to a sequential circuit that changes output and state values at a predetermined rate





- Triggering edge: Transition of the clock that captures input data
 - By default, we use positive rising edge (L→H) as the triggering edge in this course
 - Clock tick: Occurrence of a triggering edge

Clock Period and Frequency

 - **Clock Period (cycle time):** Time between successive transitions in the same direction (e.g., L→H)
 - e.g., 1ms, 2ns, 500ps
- **Clock Frequency: 1/period**
 - e.g., 1kHz, 500MHz, 2GHz



D Latch Timing

  


- **D latch is level sensitive**
 - Captures input D when the latch is enabled (i.e., latch open when clock is high)
 - Holds the previous state otherwise (i.e., latch closed when clock is low)


Flip-Flop

- An edge-sensitive storage element
- D flip-flop (FF): Two D latches back-to-back
 - Inputs: D (Data) and Clock
 - Output: Q
- Captures input (copy D to Q) on *triggering edge* of clock
 - Otherwise (when clock steady at 0 or 1) it retains its value

D Flip-Flop


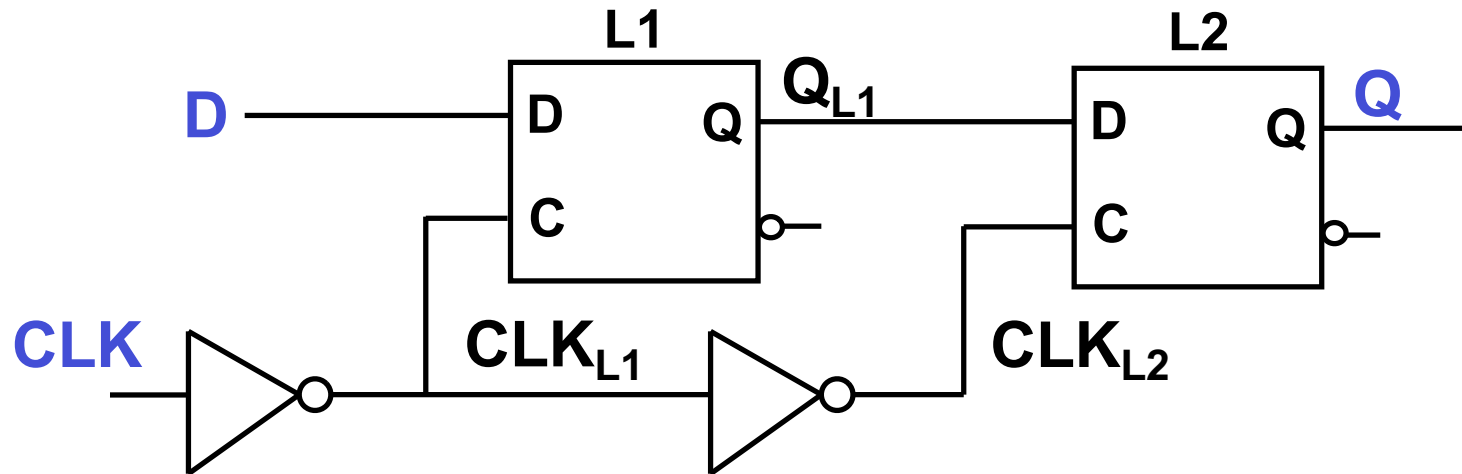


D	CLK	Q_{next}
0		0
1		1
X	0	(Last) Q
X	1	(Last) Q

 

Q_{next} is new state of Q after a triggering clock edge occurs (rising edge in this case)


D Flip-Flop Timing

 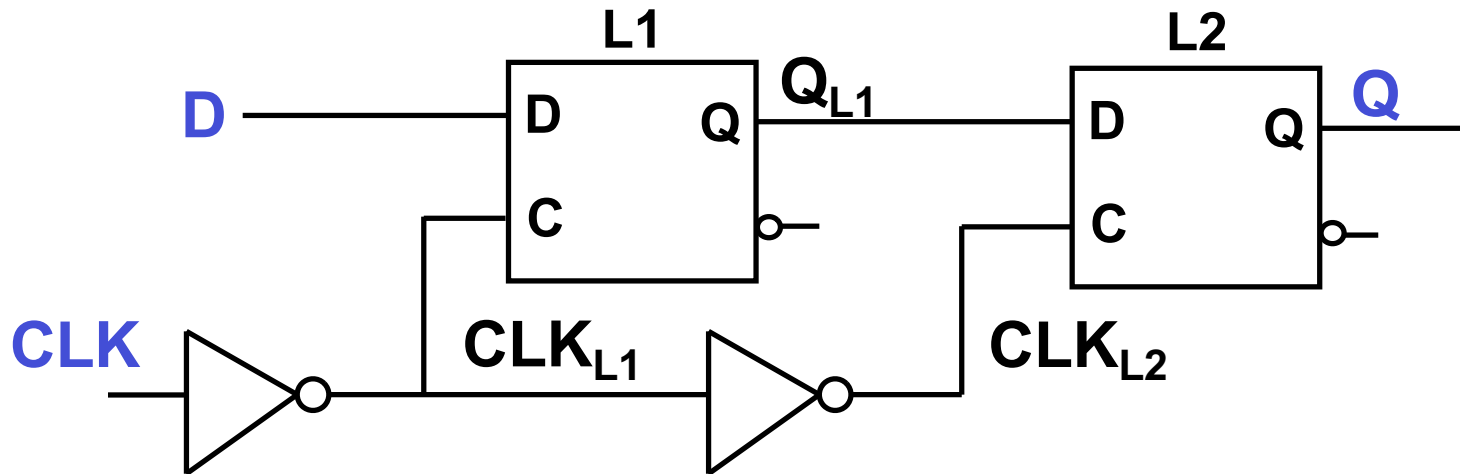

Input D copied to Q on the rising edge of the clock

Register

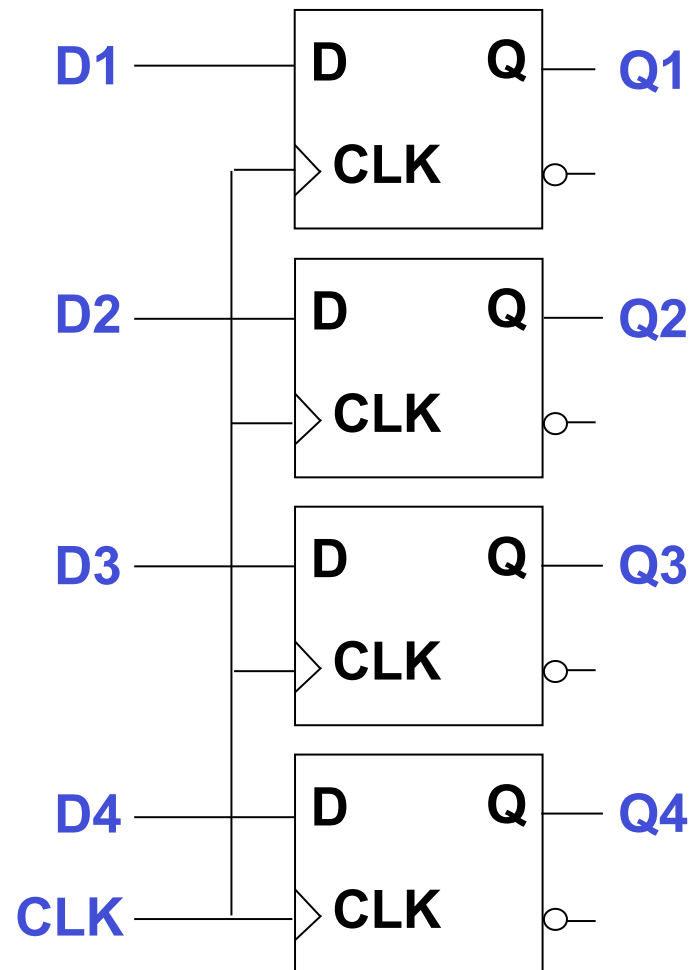- Collection of FFs operating off common clock
- A single D flip-flop is a 1-bit register



Next Class

**More Sequential Logic
Verilog**

H&H 4.1-4.5 (skip VHDL parts), 5.4