

**ECE 2300**  
**Digital Logic & Computer Organization**  
**Spring 2025**

**More Sequential Logic**  
**Verilog**



Cornell University

# Announcements

- Lab 1 due tomorrow
- Lab 2 will be released today


# Sequential Logic: True or False

- 4 transistors are required to build an S-bar-R-bar latch
- A rising clock edge is also called a positive edge
- D latch changes its state when input changes
- D Flip-Flop is edge sensitive

 
# $\overline{S}$ - $\overline{R}$ Latch

- *S-bar-R-bar latch*

- Built from NAND gates
- Inputs are active low rather than active high
- **When both inputs are 0,  $Q = \overline{Q} = 1$  (avoid!)**




S	R	Q	$\overline{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Last Q	Last $\overline{Q}$

 

 
# D Latch and Flip-Flop



- **D Latch: level sensitive**
  - Captures the input when enable signal asserted



 - **D Flip-Flop (DFF): edge sensitive**
  - Captures the input at the triggering clock edges (e.g., L→H)
  - A single FF is also called a one-bit register




# Recap: DFF Timing

 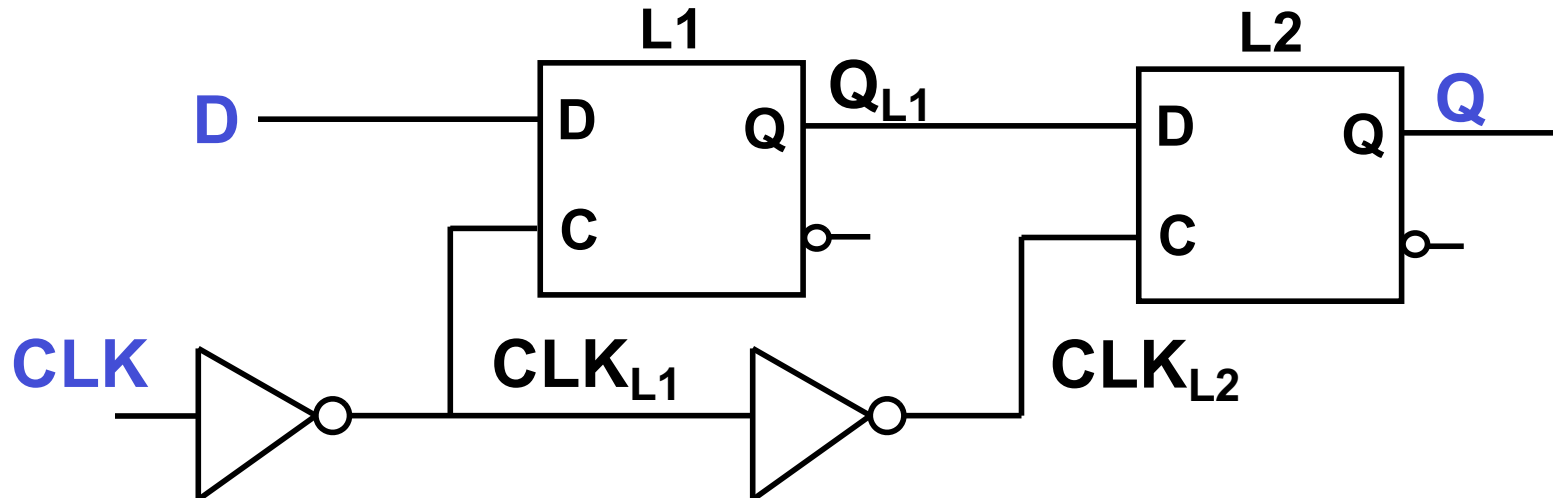

**Input D copied to Q on the rising edge of the clock**


# Another DFF Timing Example

Circuit diagram

 


Waveform

(assume both DFFs hold 0s initially)

 


# Yet Another DFF Timing Example

## Circuit diagram

 

## Waveform<sup>1</sup>

(assume both DFFs hold 0s initially)

 


<sup>1</sup> A DFF is often termed a “delay element” because it introduces a delay in data propagation. This delay results from updating the DFF state/output only on a clock edge. Beyond its important role as a storage element for holding states, the delay introduced by a DFF is also crucial for timing control and sequencing in digital systems.


 
# T (*Toggle*) Flip-Flop

- Output toggles only if  $T=1$
- Output does not change if  $T=0$
- Useful for building counters




(when  $T=1$ )  
**Q: 0, 1, 0, 1, 0, 1, 0, ...**

**Can we build a T flip-flop using a DFF as the building block?**

# T (*Toggle*) Flip-Flop

- Output toggles only if T=1
- Output does not change if T=0
- Useful for building counters

T	Q	Q <sub>next</sub>
0	0	0
0	1	1
1	0	1
1	1	0

 

(when T=1)

Q: 0, 1, 0, 1, 0, 1, 0, ...

$$Q_{\text{next}} = T \cdot Q' + T' \cdot Q$$

# Binary Counters

- Counts in binary in a particular sequence
- Advances at every tick of the clock
- Many types

		Divide-	
Up	Down	by-n	n-to-m
0 0 0	1 1 1	0 0 0	n
0 0 1	1 1 0	0 0 1	n+1
0 1 0	1 0 1	0 1 0	n+2
0 1 1	1 0 0	0 1 1	⋮
1 0 0	0 1 1	1 0 0	m-1
1 0 1	0 1 0	⋮	m
⋮	⋮	n-1	n
		0 0 0	n+1
		0 0 1	⋮

# Up Counter Sequence


0 0 0  
0 0 1  
0 1 0  
0 1 1  
1 0 0  
1 0 1  
1 1 0  
1 1 1

Toggles every clock tick  
that two right bits = 11

Toggles every clock tick

Toggles every clock tick  
that right bit = 1

# Building Binary Up Counter

 

**Q<sub>2</sub> Q<sub>1</sub> Q<sub>0</sub>**

**0 0 0**

**0 0 1**

**0 1 0**

**0 1 1**

**1 0 0**

**1 0 1**

**1 1 0**

**1 1 1**

**Q0 toggles at every rising edge**



**Q1 toggles at the rising edge when Q0=1**

**Q2 toggles at the rising edge when Q0=Q1=1**


**0 0 0**

**0 0 1**

# Up Counter Timing Diagram

  

# Evolution of Design Abstractions

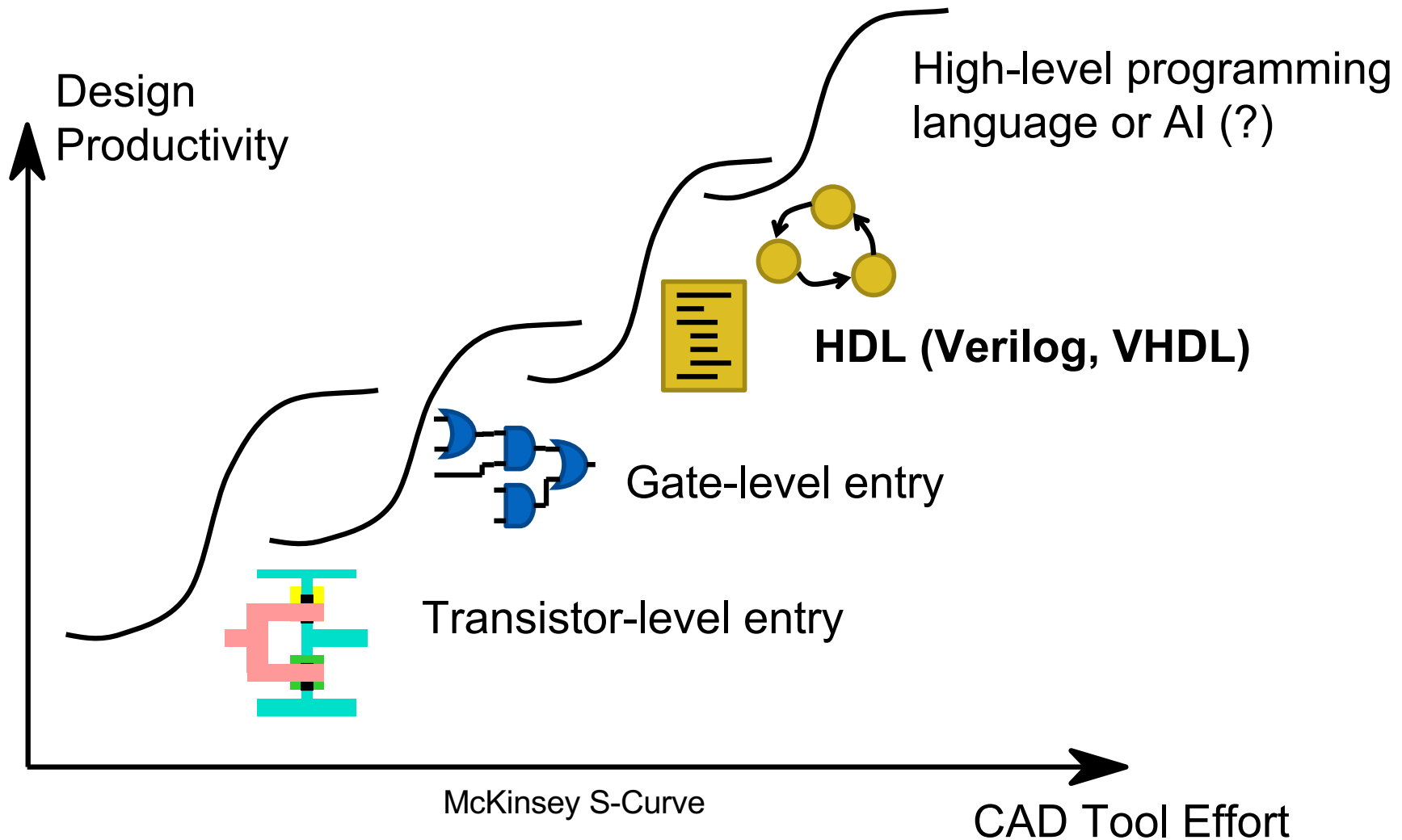

[Figure credit: Kurt Keutzer]

# Hardware Description Languages

- **Hardware Description Language (HDL):**  
a language for describing hardware
  - **Efficiently code large, complex designs**
    - Programming at a more abstract level than schematics
  - **CAD tools can automatically synthesize circuits**
- **Industry standards:**
  - **Verilog: We start using it from Lab 2**
  - **SystemVerilog: Successor to Verilog, gaining wide adoption**
  - **VHDL (Very High Speed Integrated Circuit HDL)**



# Verilog

- **Developed in the early 1980s by Gateway Design Automation (later bought by Cadence)**
- **Supports modeling, simulation, and synthesis**
  - **Simulation verifies the functionality of the design by executing the model (i.e., Verilog design) and testing its behavior over time**
  - **Synthesis converts the Verilog design into an optimized circuit for implementation on physical hardware**
  - **We will use a (synthesizable) subset of the language features**
- **Major language features (in contrast to software programming languages)**
  - **Structure and instantiation**
  - **Concurrency**
  - **Bit-level behavior**

# Values

- **Verilog signals can take 4 values** (for simulation purpose)
  - 0 Logical 0, or false**
  - 1 Logical 1, or true**
  - x Unknown logical value**
  - z High impedance (Hi-Z), floating/non-connected**

**x means unknown/uninitialized (could be 0, 1, z, or in transition) or don't cares**

# Bit Vectors

- Multi-bit values are represented by bit vectors (i.e., grouping of 1-bit signals)

- Right-most bit is always least significant

- Examples:

```
input a; /* 1-bit input */
```

```
input[7:0] a, b, c; /* three 8-bit inputs */
```

- Constants

**4'b1001**



Base format (b,d,h,o)

Decimal number representing bit width

- Binary Constants

- 8'b00000000

- 8'b0xx01xx1

- Decimal Constants

- 4'd10

- 32'd65536

# Operators

- **Bitwise Boolean operators**

- ~ NOT

- & AND

- ^ Exclusive OR

- | OR

- **Arithmetic operators**

- + Addition

- / Division

- << Shift left

- Subtraction


- % Modulus

- >> Shift right

- \* Multiplication

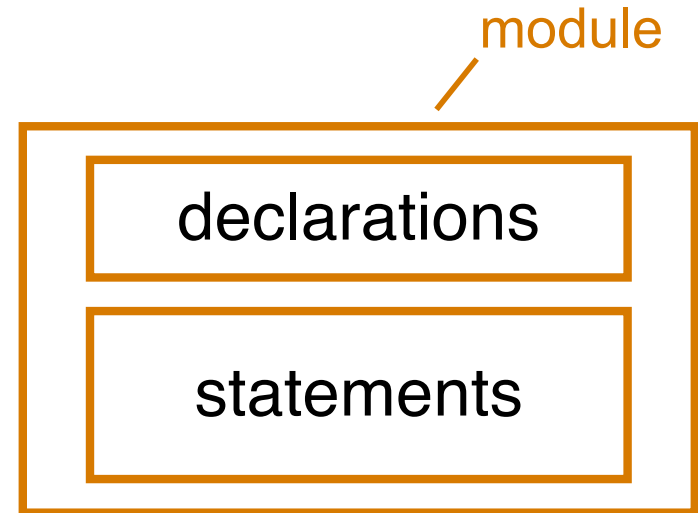
# Verilog Program Structure

- **System is a collection of *modules***
  - **Module represents a hardware component or a design unit**



- **Declarations**
  - **Describe names and types of inputs and outputs**
  - **Describe local signals, variables, constants, etc.**
- **Statements specify what the module does**

# Verilog Module Hierarchy

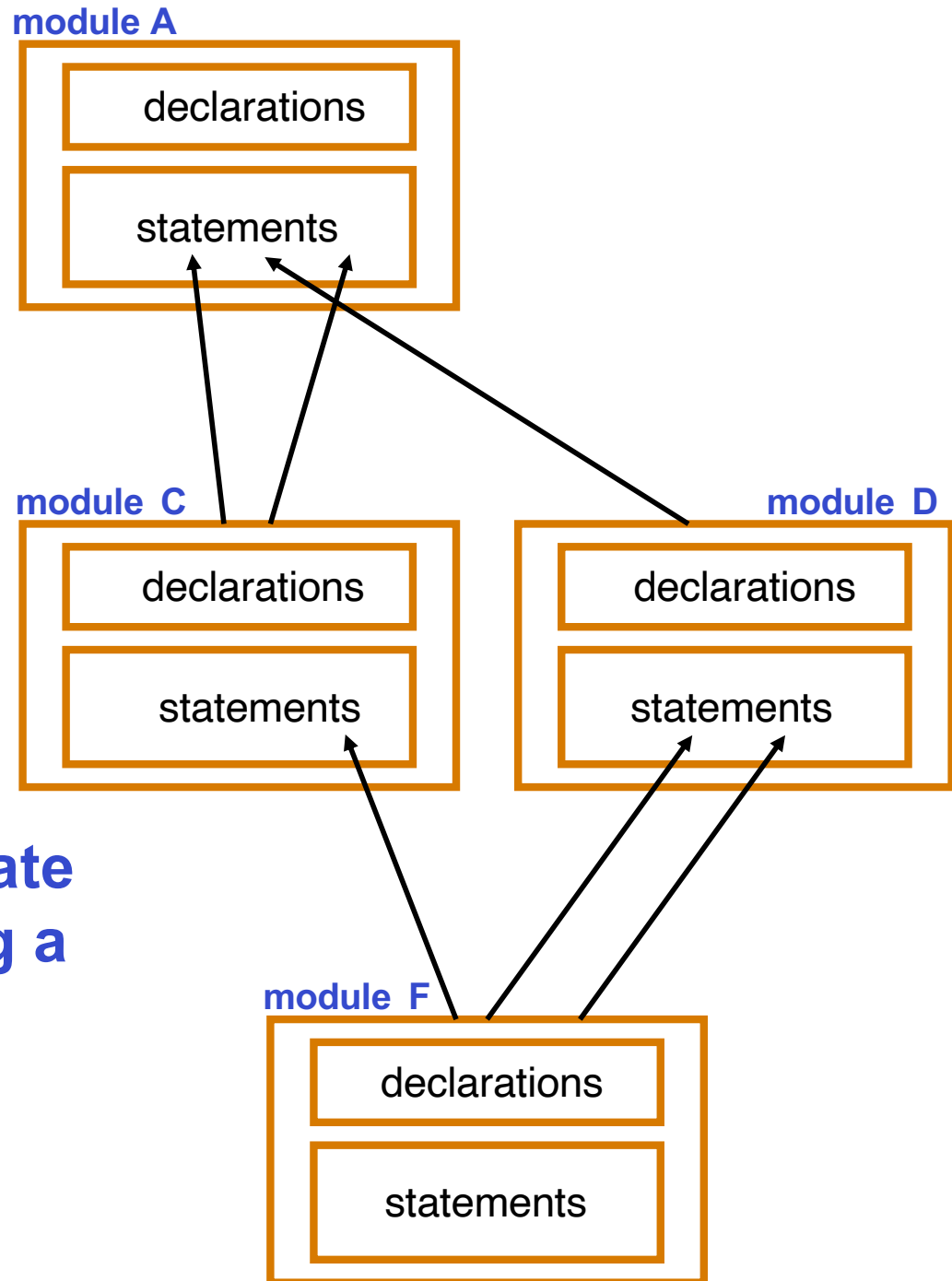

A module can instantiate other modules forming a module hierarchy

# Example: Verilog Program Structure

```
module M_2_1 (a, b, sel, Y);  
  input a, b;  
  input sel;  
  output Y;  
  wire ta, tb;
```

**Declarations**

```
  AND and0 (a, ~sel, ta);  
  AND and1 (b, sel, tb);  
  OR or0 (ta, tb, Y);
```

**Statements**

(instantiating two AND gates and one OR gate)

```
endmodule
```

# Verilog Programming Styles

- **Structural**

- Describe how a module is built from other modules and their interconnections via instance statements
- Textual equivalent of drawing a schematic

- **Behavioral**

- Specify what a module does in high-level constructs
- Use continuous assignments and/or procedural code (in always blocks) to indicate what actions to take

**We can mix the structural and behavioral styles  
in a Verilog design**



# Net and Variable Types

- **We will mainly use two data type classes**
  - **wire**: represents a physical connection (also called net) between hardware elements
    - A stateless way of connected two elements
    - Can only be used to model combinational logic
    - Cannot be used in the left-hand side (LHS) in an always block
  - **reg**: similar to wires, but can be used to store information (or state) like registers
    - This is used in the behavioral style only
    - *Can be used to model both combinational & sequential logic*
    - Cannot be used in the LHS of a continuous assignment statement

# Structural Style

```
module MUX_2_1 (a, b, sel, Y);  
  input a, b, sel; // here "input" is same with "input wire"  
  output Y; // here "output" is same with "output wire"
```


```
  wire ta, tb;
```

```
  AND and0 (a, ~sel, ta);
```

```
  AND and1 (b, sel, tb);
```

```
  OR or0 (ta, tb, Y);
```

```
endmodule
```

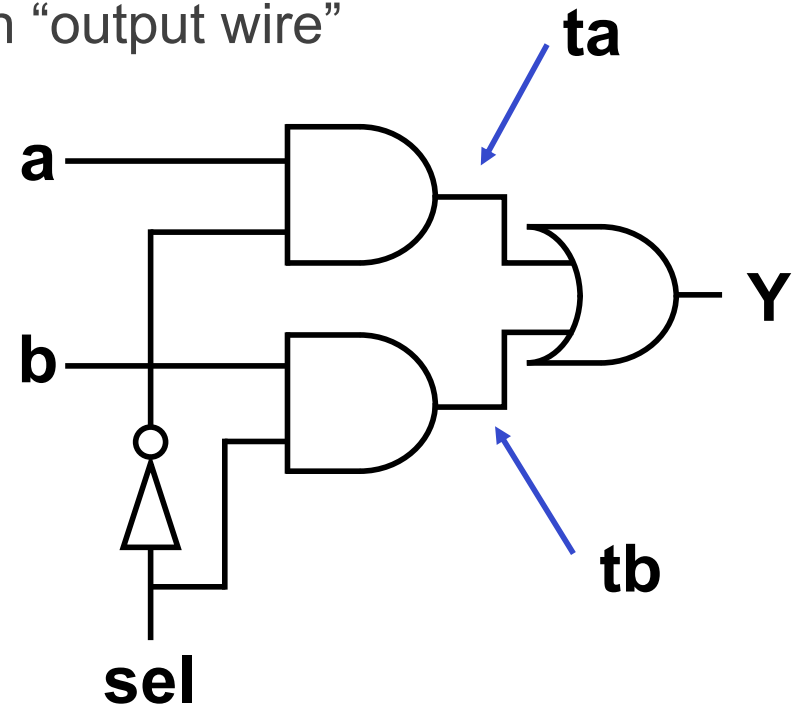

**The order of the module instantiation does not matter, essentially describing the schematic textually**

# Behavioral Style with Continuous Assignments

- An *assign* statement represents continuously executing combinational logic

```
module MUX_2_1 (a, b, sel, Y);  
  input a, b, sel;  
  output Y;
```

```
  assign Y = (~sel & a) | (sel & b);
```

```
endmodule
```

continuous assignment



- Multiple continuous assignments happen in parallel; the order does not matter

# Always Blocks

```
always @( <sensitivity_list> )  
begin  
    <procedural assignments>  
end
```

- An always block is a procedural construct that executes whenever there is a change in the specified sensitivity list
  - Can model either combinational or sequential logic
  - **Sequential logic can only be modeled using always blocks**
- Always blocks execute concurrently with other always blocks, instance statements, and continuous assignment statements in a module

# Procedural Statements in Always Block

- **Procedural statements are similar to conventional programming language statements**
  - **begin-end blocks**
    - *begin procedural-statement ... procedural-statement end*
  - **if**
    - *if ( condition ) procedural-statement else procedural-statement*
  - **case**
    - *case ( sel-expr ) choice : procedural-statement ... endcase*
  - **for**
    - *for(initial\_assignment; expression; step\_assignment) statement;*
  - **while**
    - *while ( logical-expression ) procedural-statement*
  - **repeat**
    - *repeat ( integer-expression ) procedural-statement*

Mostly used in test bench  
(simulation only, not synthesizable)

# (Behavioral Style) Combinational Logic with Always Blocks

```
module MUX_2_1 (a, b, sel, Y);  
  input a, b, sel;  
  output reg Y;  
  
  always @(a, b, sel)  
  begin  
    Y = (~sel & a) | (sel & b);  
  end  
endmodule
```

sensitivity list


procedural assignment

- An *always* block is activated whenever a signal in its sensitivity list changes
  - Formed by procedural assignment statements
  - The left-hand side of a procedural assignment must be declared as a “reg”
 
# Sequential Logic with Always Blocks


*Sequential logic can ONLY be modeled using always blocks*

```
reg Q;  
  
always @(clk, D)  
begin  
    if ( clk )  
        Q = D;  
end
```



 **D latch**

```
reg Q;  
  
always @(posedge clk)  
begin  
    Q = D;  
end
```



**DFF**

**Q is declared as a "reg" since it appears on the left-hand side of a procedural assignment**

# Next Class

**More Verilog  
Finite State Machines  
(H&H 3.4)**