

**ECE 2300**  
**Digital Logic & Computer Organization**  
**Spring 2025**

**More FSMs**  
**Timing**




Cornell University

# Announcements

- **HW4 will be released today**
- **Lab 2a due tomorrow**

# Review: FSM General Circuit Form

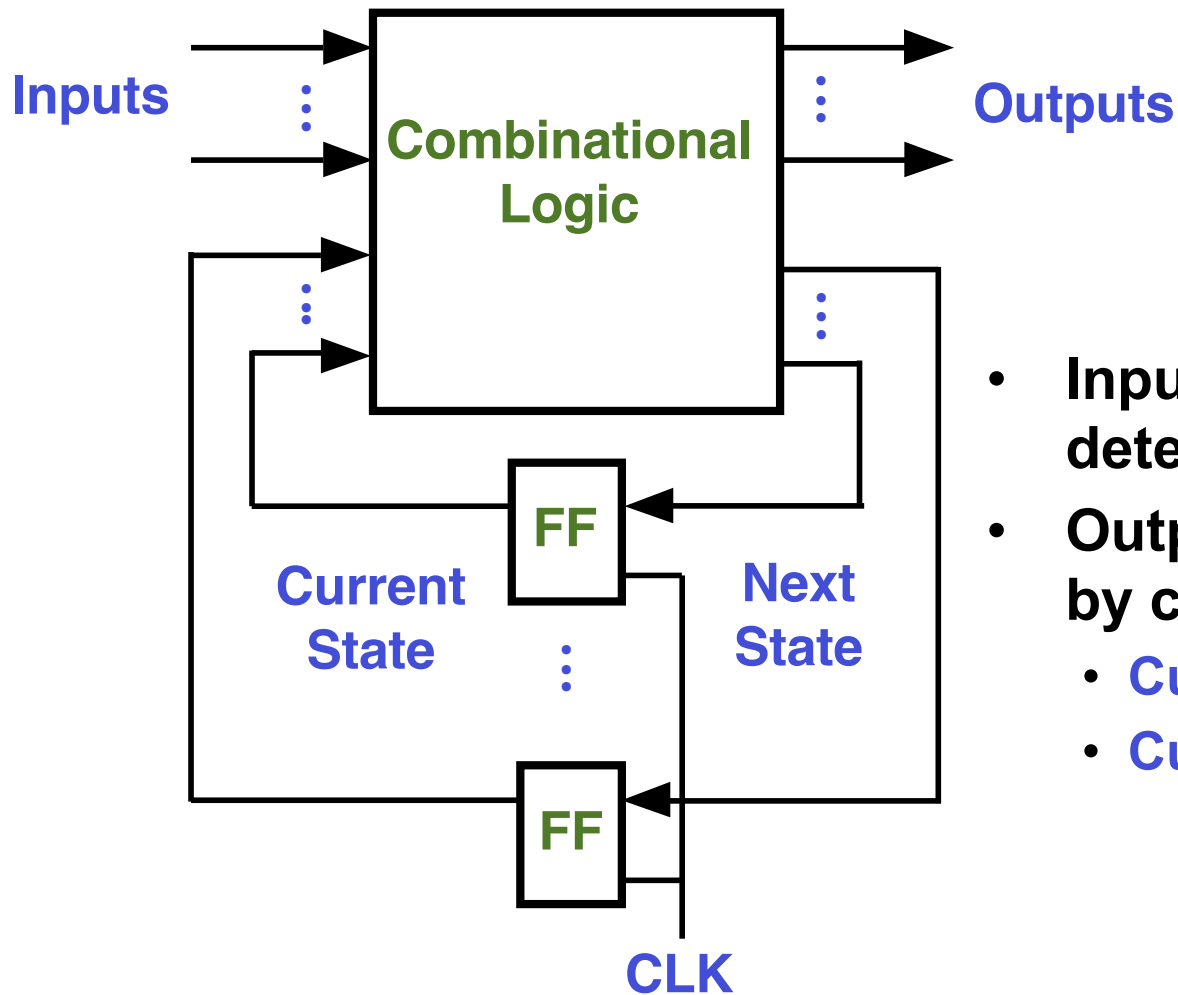



- Inputs and current state determine state transitions
- Output changes determined by changes in
  - Current state (Moore), or
  - Current state + inputs (Mealy)

# FSMs: True or False?

- The next state in Moore FSM only depends on its current state
- The output logic in Mealy FSM is sequential
- D flip-flop is a Moore machine

# Recap: Moore State Diagram for DFF

- Input: D
- Output: Q

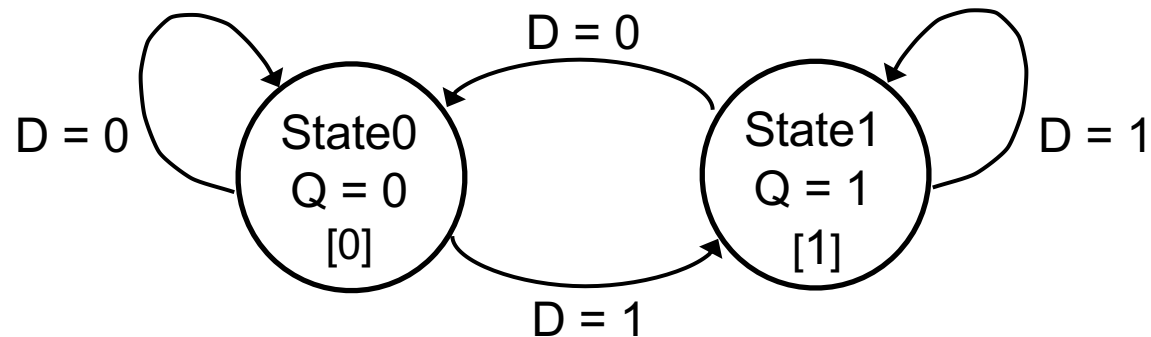 



S	S*		Q
	D = 0	D = 1	
0	0	1	0
1	0	1	1

$$S^* = D$$

$$Q = S$$

# Mealy State Diagram for DFF?


- Input: D
- Output: Q

  

S	S*, Q	
	D = 0	D = 1
0	0, 0	1, ?
1	0, ?	1, 1

 
# Traffic Light Controller

- **4-way intersection with traffic lights**
  - East-West (E & W), North-South (N & S)
- **Opposing lanes sequence together**
  - 20 seconds dwell on green
  - 5 seconds dwell on yellow
  - 25 seconds dwell on red


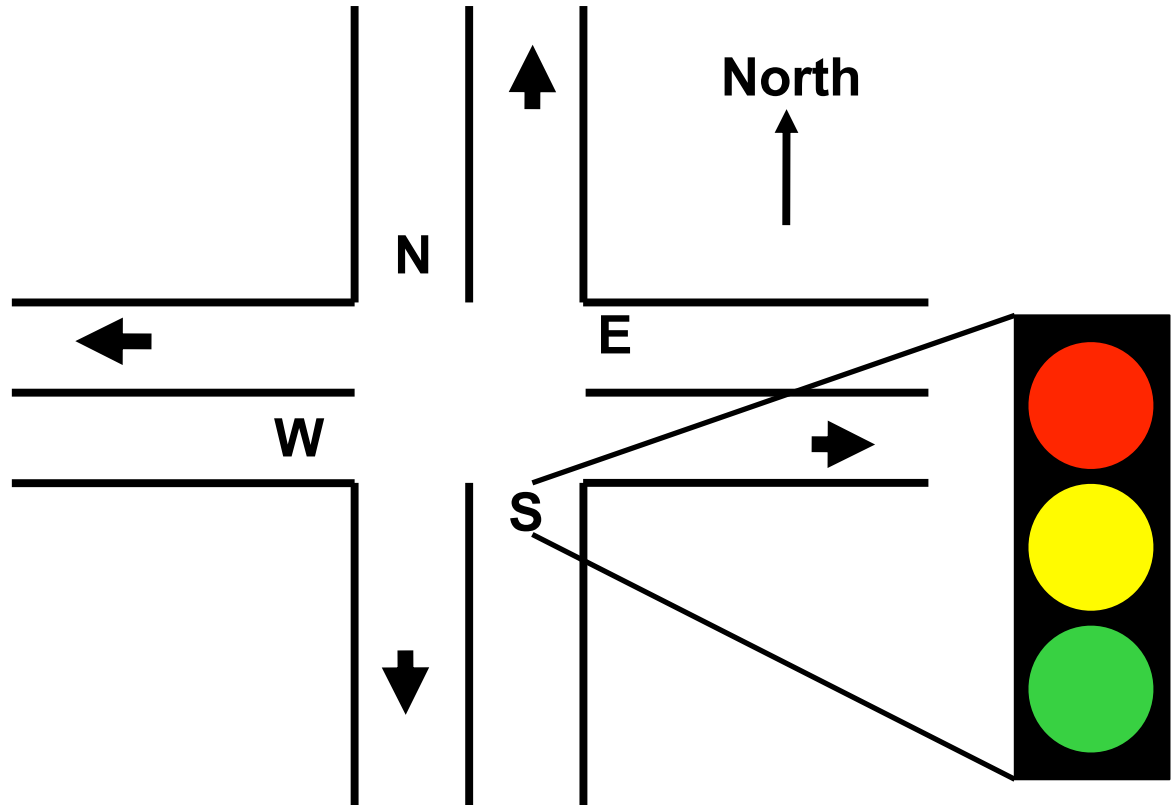
# Four Scenarios

- E & W Green / N & S Red for 20 seconds
- E & W Yellow / N & S Red for 5 seconds
- E & W Red / N & S Green for 20 seconds
- E & W Red / N & S Yellow for 5 seconds






# Traffic Light Controller States

- **10 states**

- E & W Green / N & S Red1 for 5 seconds
- E & W Green / N & S Red2 for 5 seconds
- E & W Green / N & S Red3 for 5 seconds
- E & W Green / N & S Red4 for 5 seconds
  
- E & W Yellow / N & S Red for 5 seconds
  
- E & W Red / N & S Green1 for 5 seconds
- E & W Red / N & S Green2 for 5 seconds
- E & W Red / N & S Green3 for 5 seconds
- E & W Red / N & S Green4 for 5 seconds
  
- E & W Red / N & S Yellow for 5 seconds


**Clock period is 5 seconds**

# Traffic Light Controller FSM

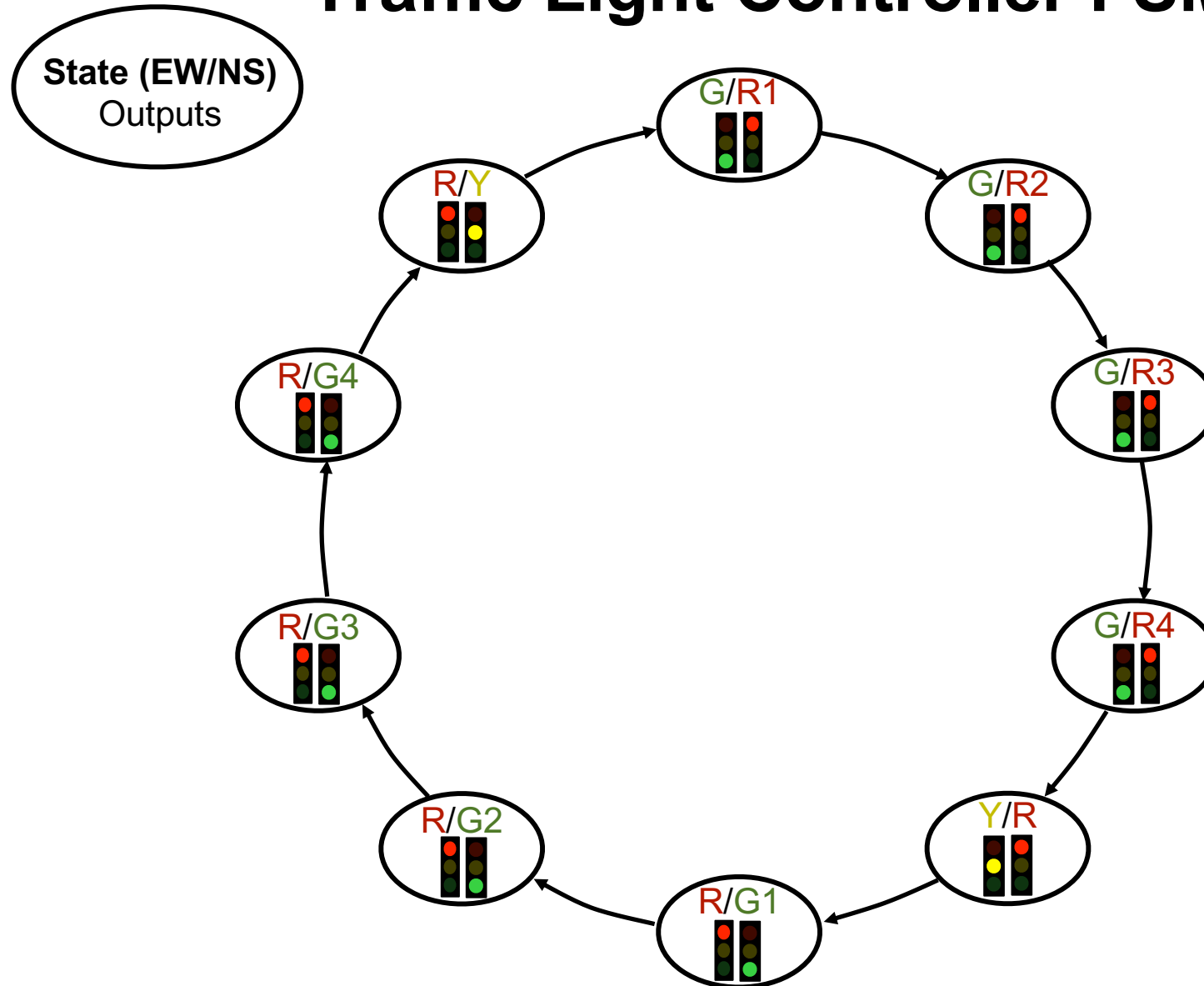

 
# Factoring FSMs

- Break FSM into multiple communicating FSMs
- Simplifies large FSMs
- May result in fewer states


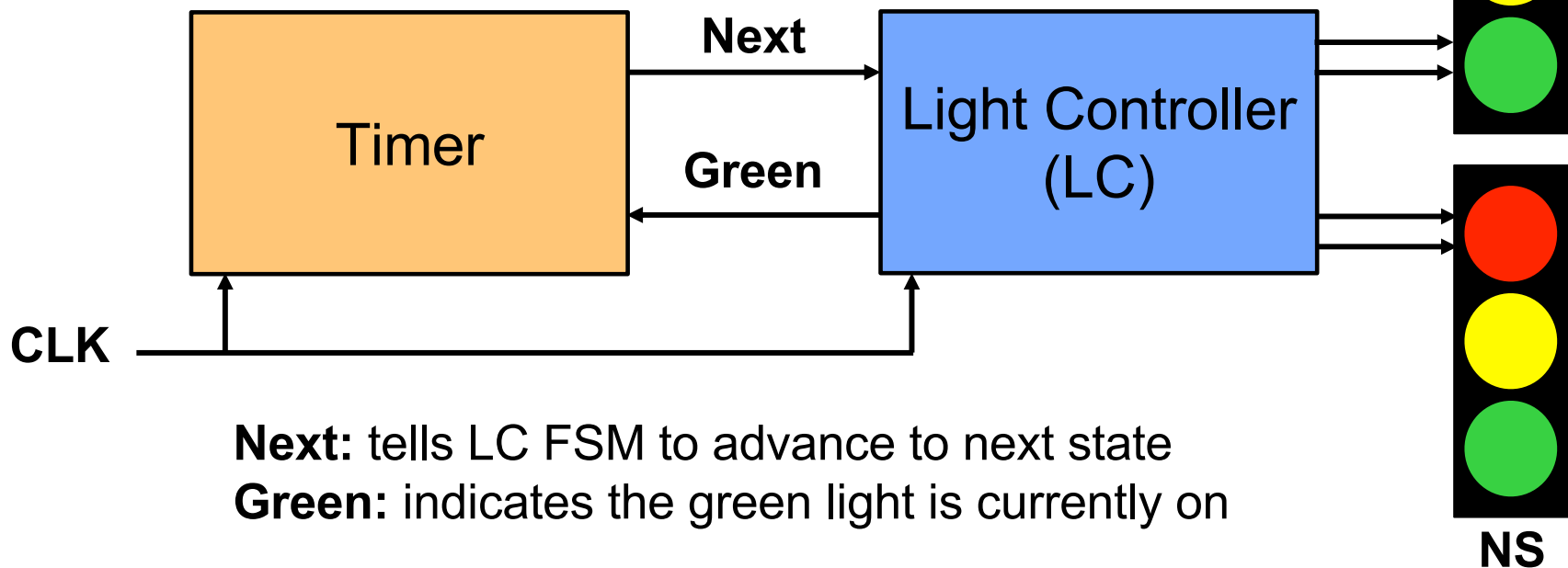
# Traffic Light Controller Using 2 FSMs



- **Light Controller (LC) FSM has 4 states**
  - G/R, Y/R, R/G, R/Y
- **Timer FSM controls when the LC FSM advances to the next state**
  - Keeps LC in *Green* states for 4 clock cycles



**Next:** tells LC FSM to advance to next state

**Green:** indicates the green light is currently on

# Light Controller (LC) FSM

 
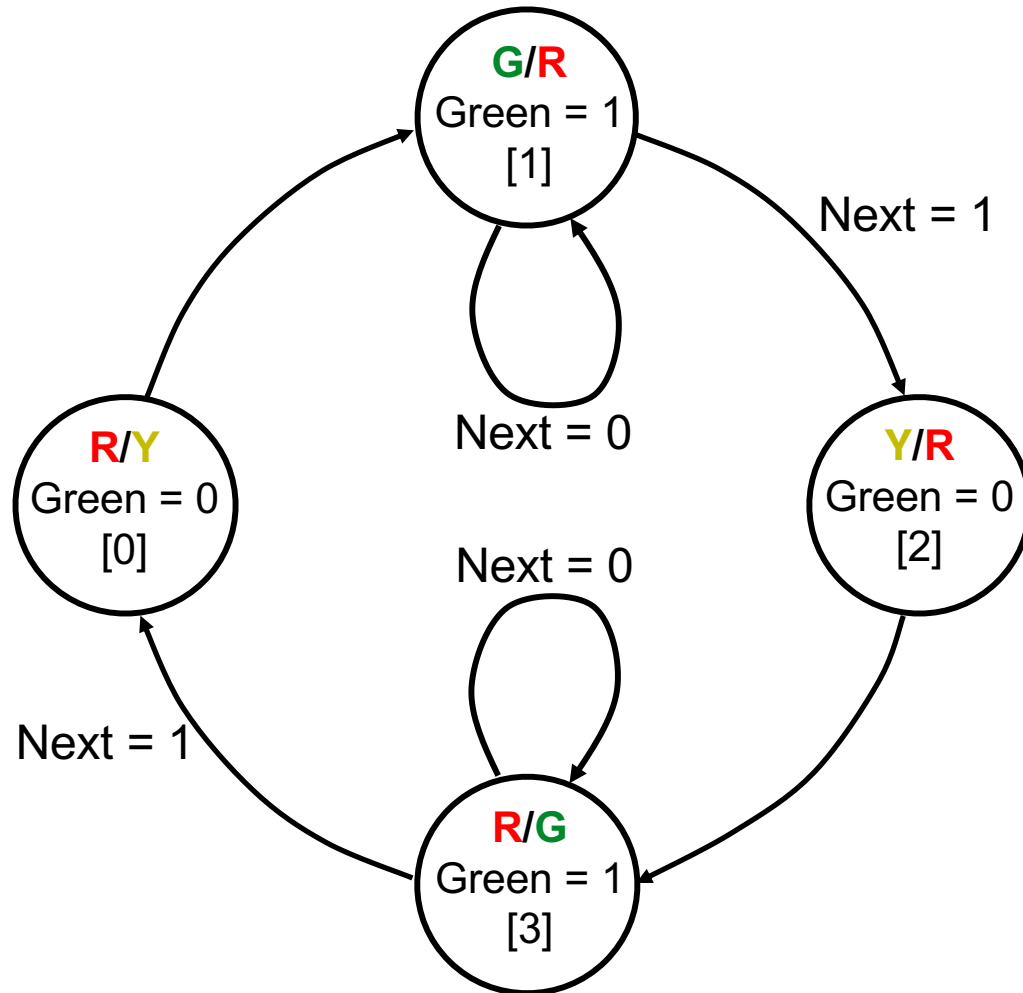


# Timer FSM


Timer stays in state **G4/NG** and outputs Next=1 for 2 consecutive cycles

**G4**: Last Green



**NG**: Not Green (yellow light is on)

 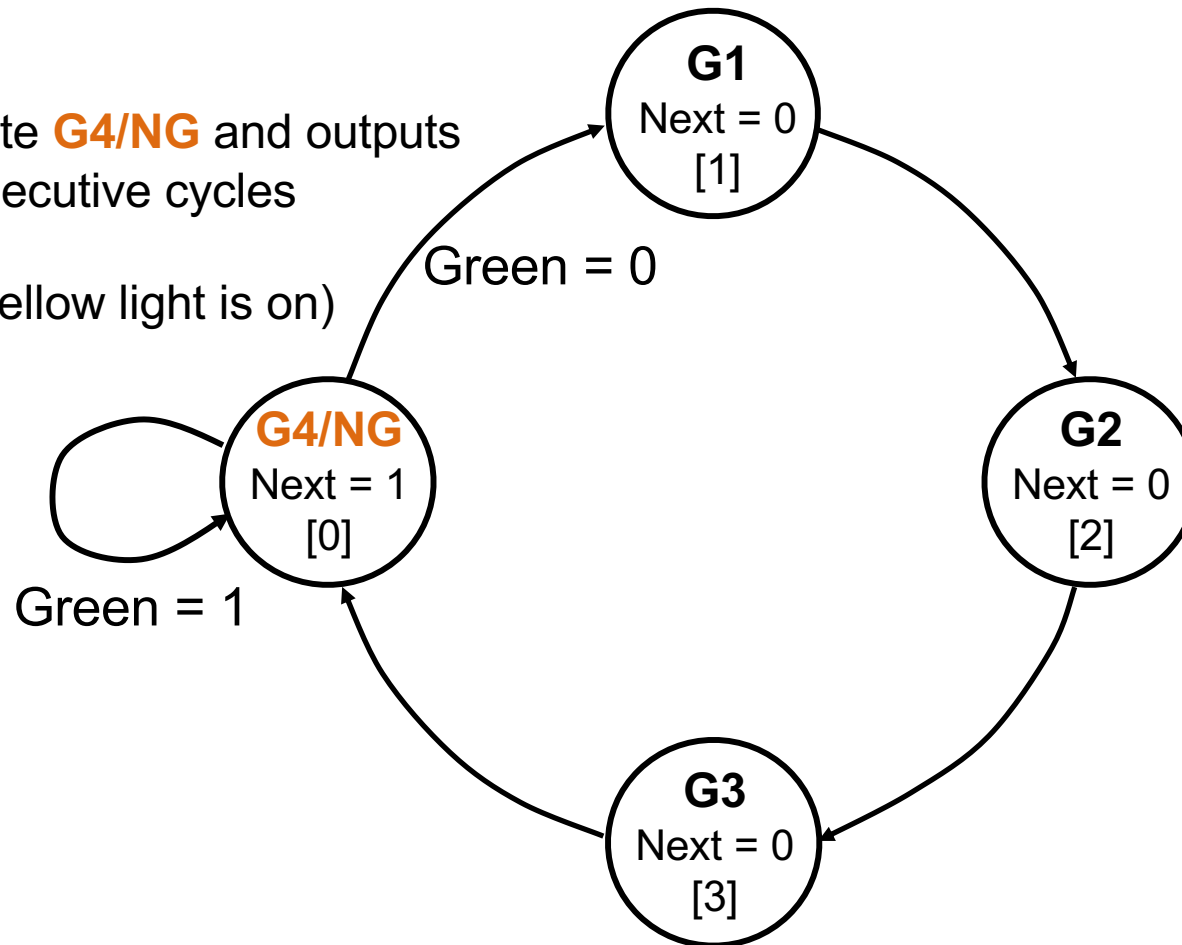


# Traffic Light Controller Operation

 

# Traffic Light Controller Operation

  



Light Controller FSM

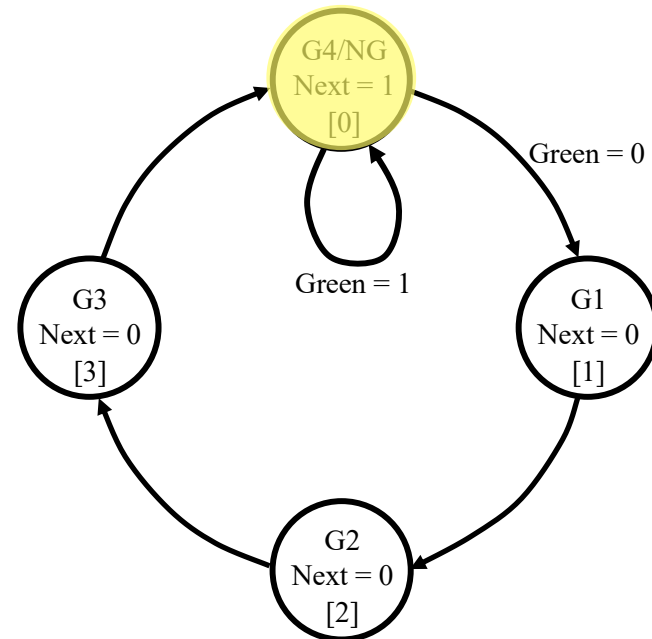


Timer FSM



# Traffic Light Controller Operation

 
 


Light Controller FSM

 


Timer FSM

# Traffic Light Controller Operation

 
 


Light Controller FSM

 


Timer FSM

# Traffic Light Controller Operation

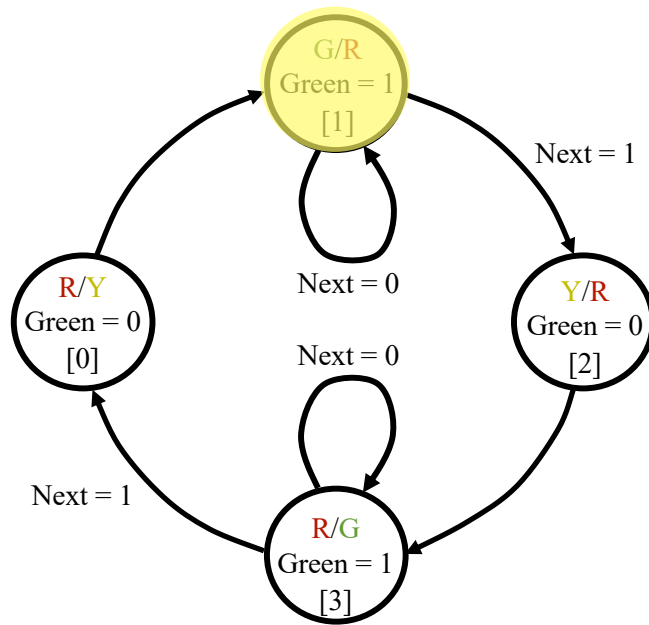
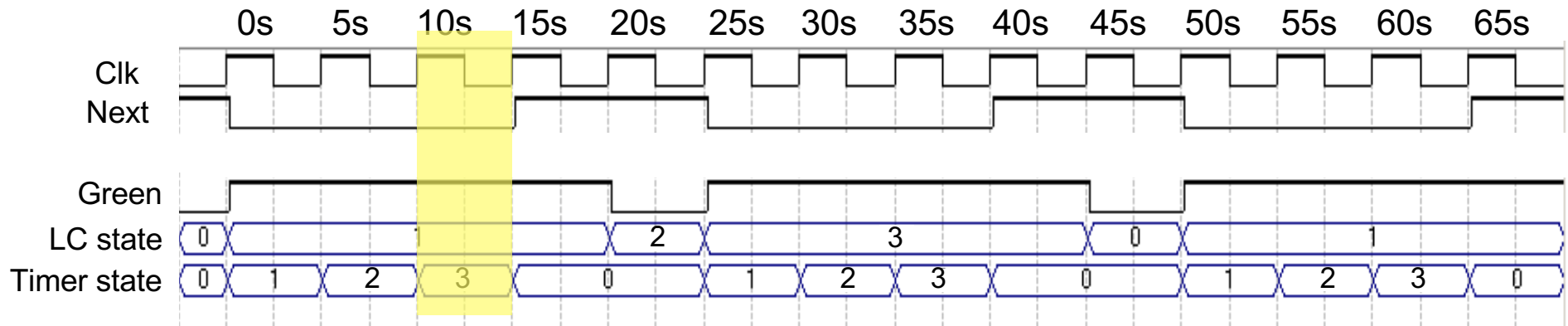


Light Controller FSM

 


Timer FSM

# Traffic Light Controller Operation

 
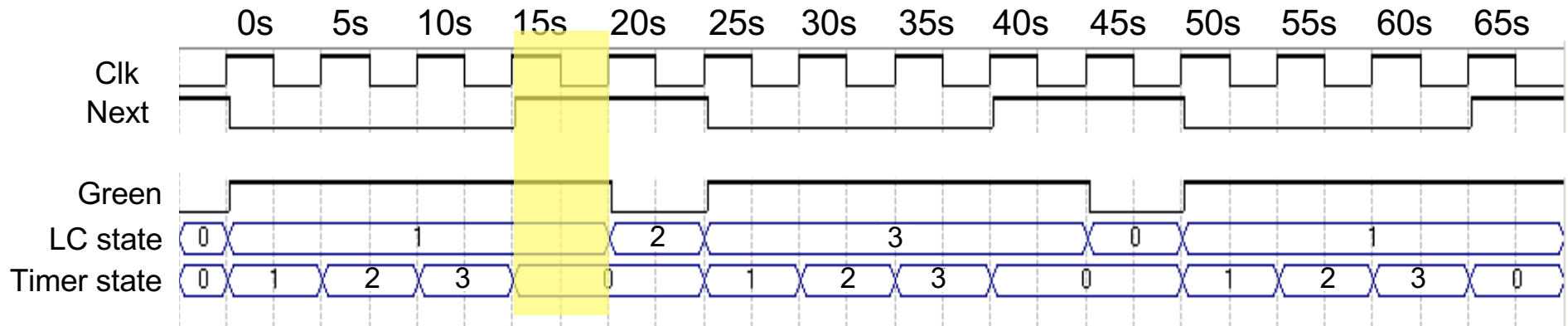


Light Controller FSM

 


Timer FSM

# Traffic Light Controller Operation

 
 


Light Controller FSM

 


Timer FSM

# Traffic Light Controller Operation

  


Light Controller FSM

 

Timer FSM
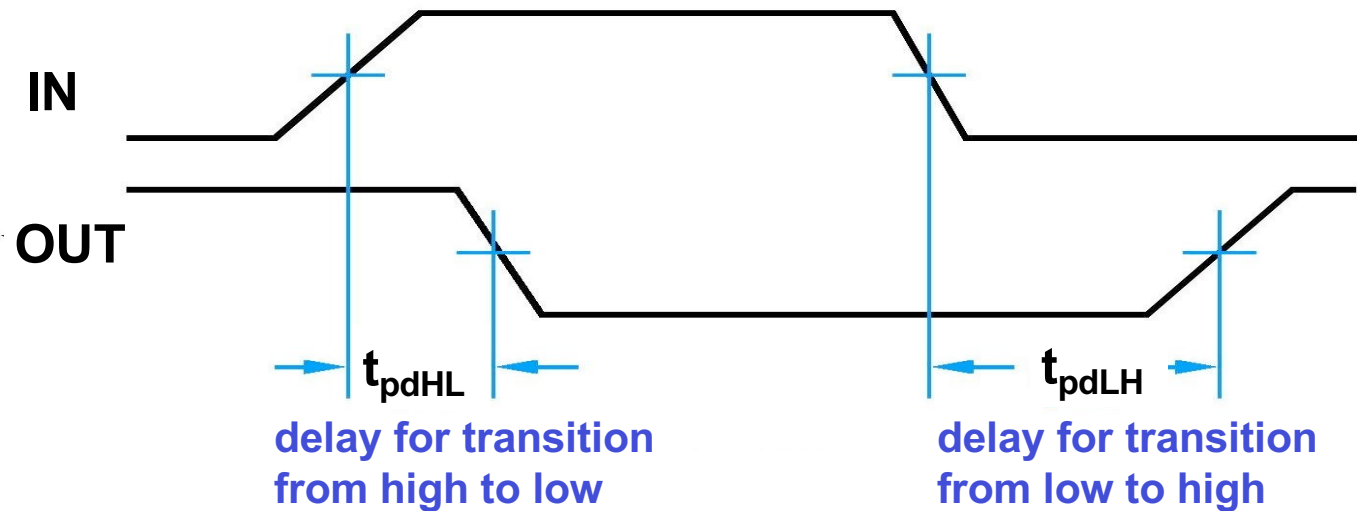
# Propagation Delay ( $t_{pd}$ )



- Time for change in input to change the output
  - Typically specified between 50% points



- Circuits have minimum and maximum propagation delays
  - Minimum sometimes called the *contamination delay* and maximum the *propagation delay*
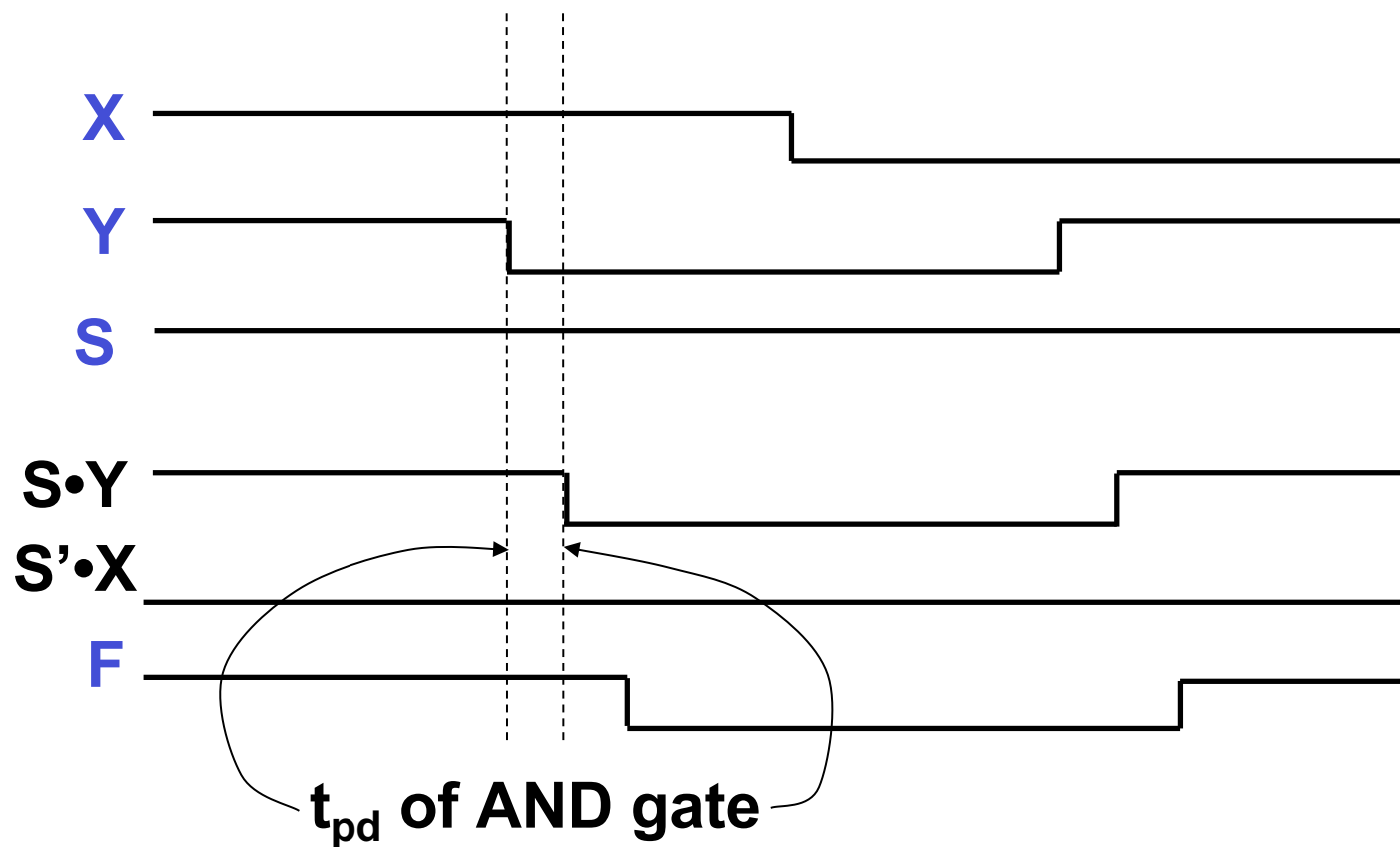 
# Timing Diagram

- Shows how outputs respond to changes in inputs over time






# Glitch (Hazard)


- **Unplanned momentary switching of an output**

- **Types of glitches**


 
- **Static 1-hazard: Input change causes output to go from 1 to 0 to 1 (should have stayed 1)**



 - **Static 0-hazard: Input change causes output to go from 0 to 1 to 0 (should have stayed 0)**



  - **Dynamic hazards: Input change causes a change from 0 to 1 to 0 to 1 or from 1 to 0 to 1 to 0 (there should be just one change)**




# Glitch Example

- Glitches are typically caused by unequal signal propagation delays through the circuit

Assume X and Y are 1



S changes from 1 → 0

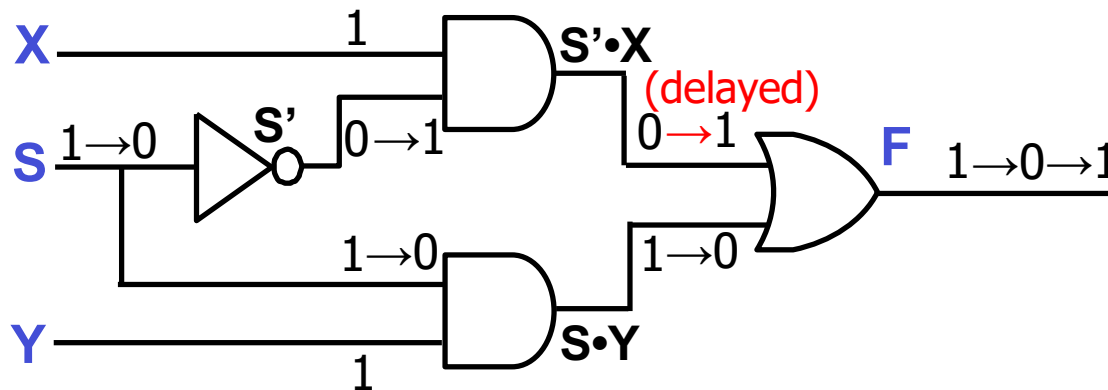**Expected behavior without considering delays:** This is a 2:1 mux. Both inputs are 1, so F should have remained 1 regardless of the S value




**Actual behavior:** Transition of S'·X is slower than that of S·Y because of the additional propagation delay on the top path → F shows a transient 0 value



# Timing Diagram Showing Glitch

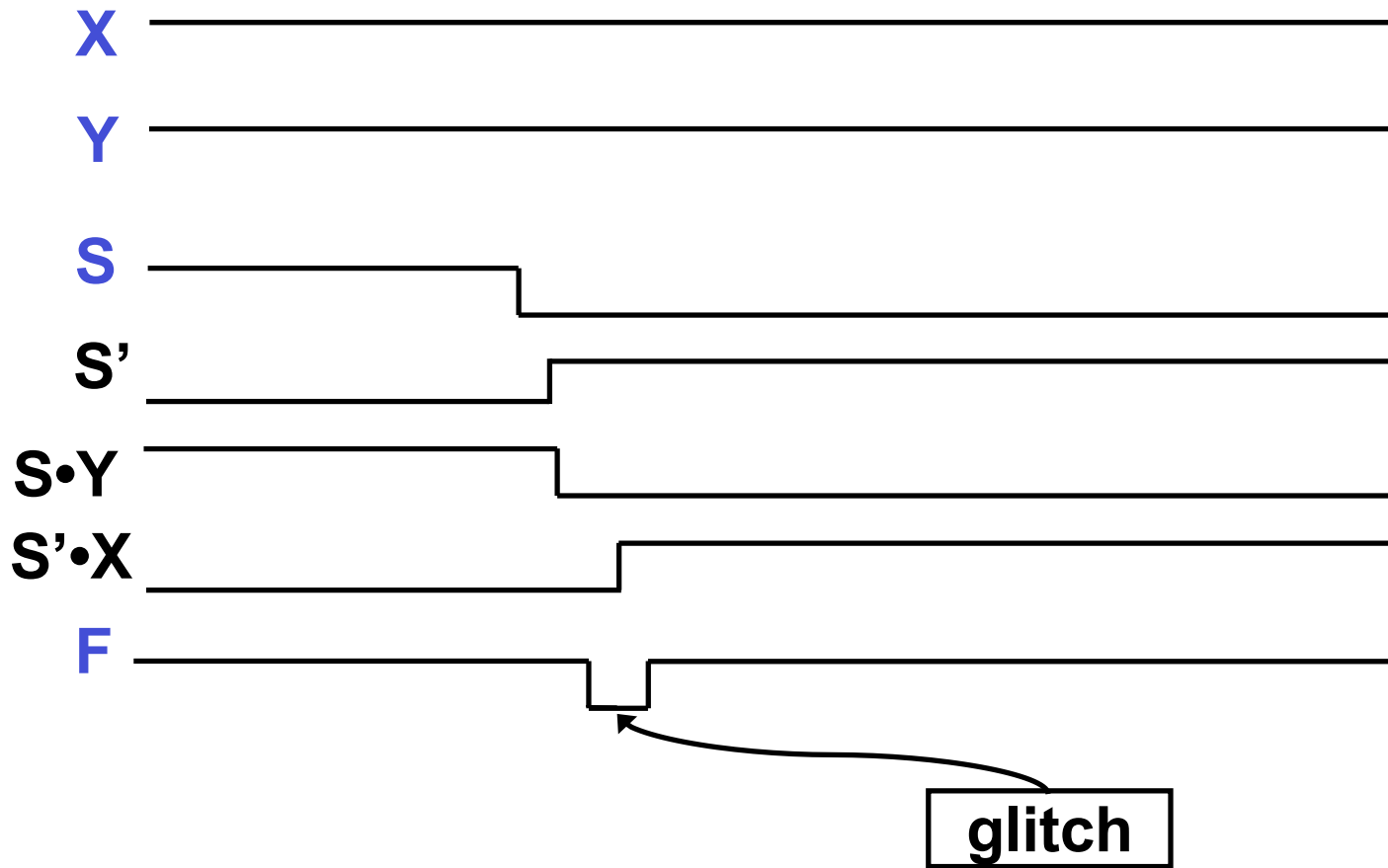 



# Do Glitches Matter?

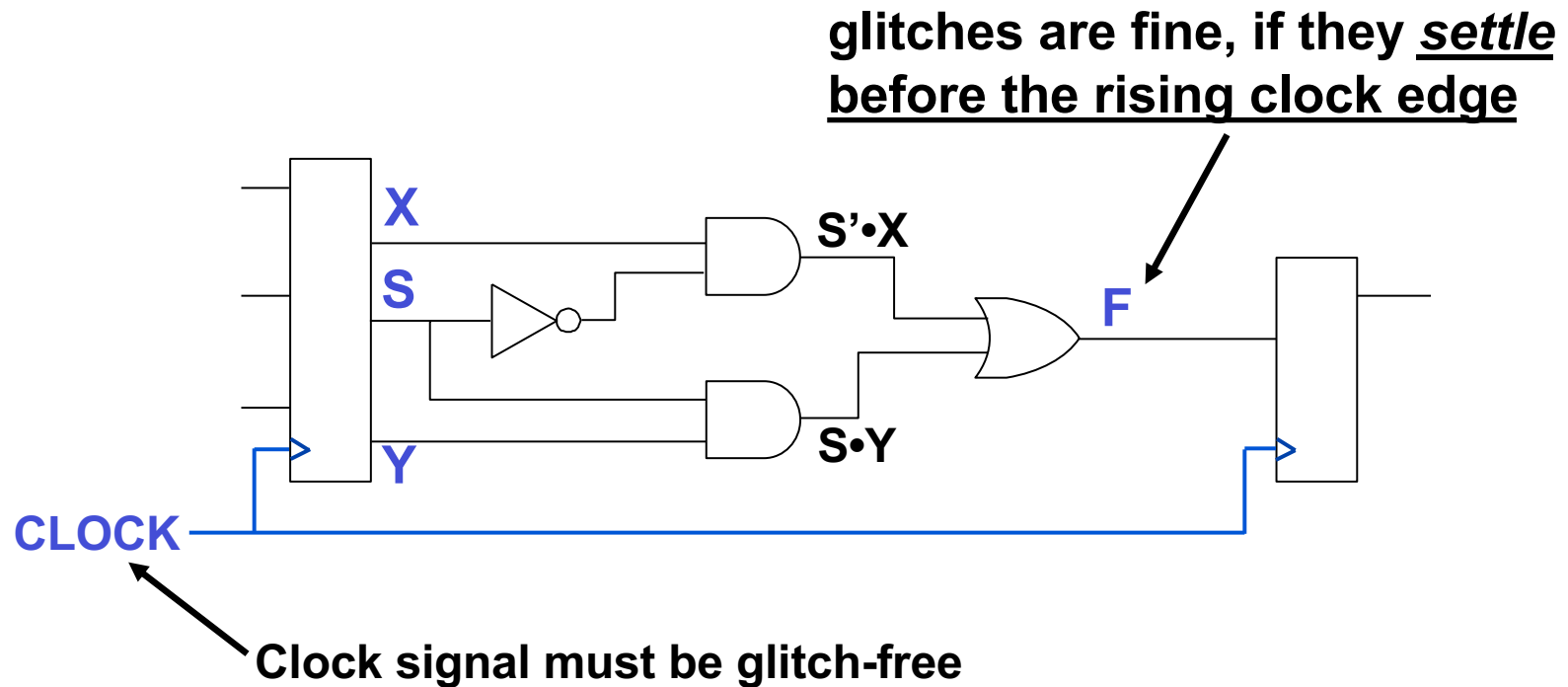


# Sequential Circuit Timing

  


# Glitch on F: No Problem

  

# But What About This Situation?

 

 Incorrect value captured; we'll go over how to prevent this in the next lecture



# Next Class

## Timing Analysis (H&H 3.5)