

ECE 2300
Digital Logic & Computer Organization
Spring 2025

Timing Analysis




Cornell University

Announcements


- **Prelim 1 graded**
 - **Mean: 39.2 (out of 50); Median: 40; High: 50**
- **Lab 3 teaming starts soon; complete it by next Wed to earn a bonus!**
- **Instructor OH today cancelled today**

Synchronous Circuits

 

- **The changes in the state of the memory elements are synchronized by a clock signal**
 - All flip-flops (FFs) are synchronized to capture the inputs *simultaneously* on the clock tick
- **Must ensure the output of the combinational logic has *settled* before the next clock tick**


Key Timing Parameters (1)

 

- **Clock cycle time (t_{clk}):** also known as the clock period or the clock pulse width
- **Combinational logic propagation delay (t_{comb}):** the time it takes for a signal to travel through a combinational logic block from input to output.

These are typically design specific


Key Timing Parameters (2)

 



- **Setup time (t_{setup}):** The minimum time before the (triggering) clock edge that the data input must be stable
- **Hold time (t_{hold}):** The minimum time after the clock edge that the data input must remain stable
- **Flip-flop propagation delay (t_{ffpd}):** the time it takes for the FF output to be stable after the clock edge

The above parameters are typically specified in datasheets by the manufacturer

Stable FF Situation

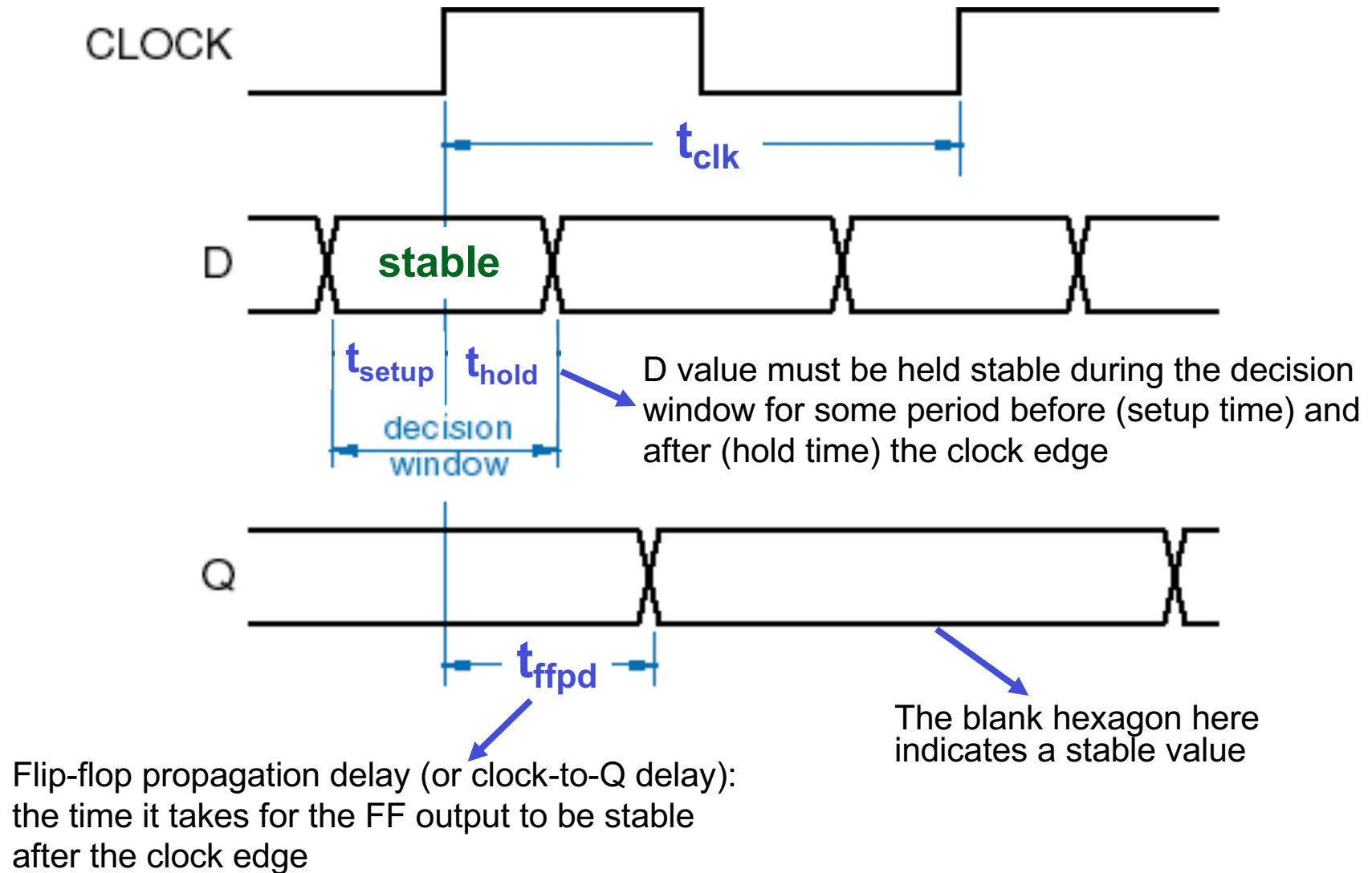


What if This Happens?

  


D2 input still transitioning (not stable)

FF may capture neither 0 nor 1


Metastable State

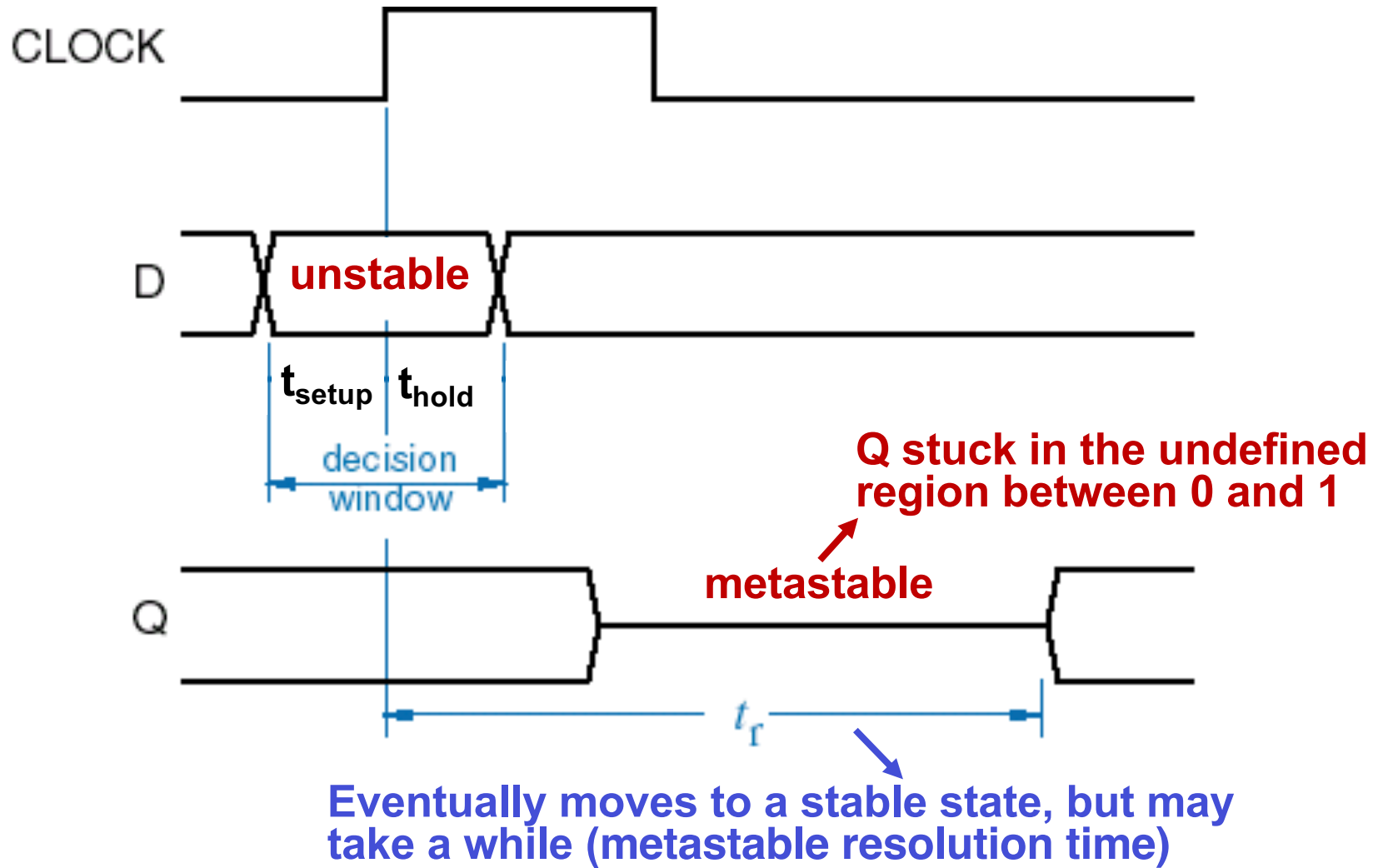

Recap: What About This Situation?

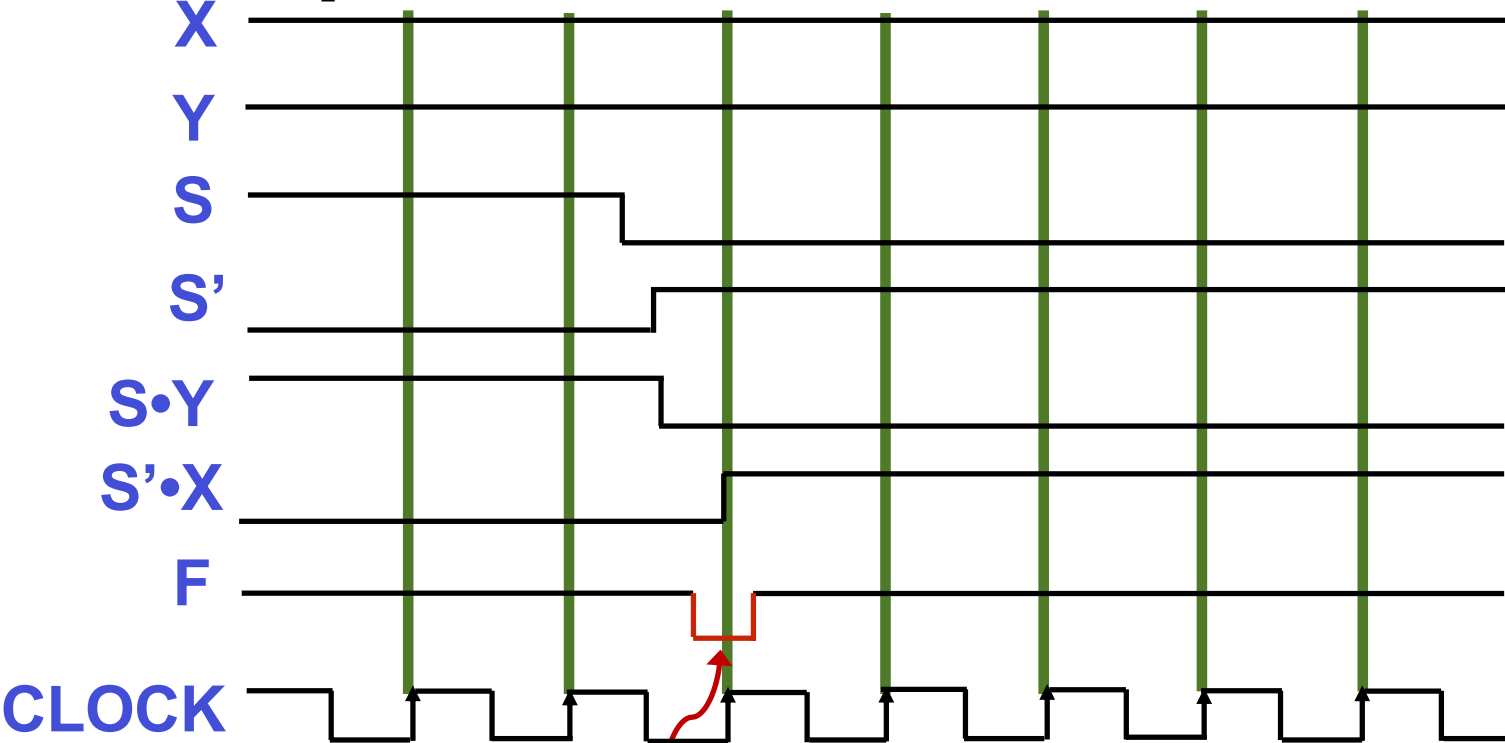

Wrong value captured

 



Avoiding Timing Failure

- **Possible causes of metastability and wrong value capture**
 - **Clock pulse that is too narrow**
 - **Input changes too soon before a clock edge**
 - **Input changes too soon after a clock edge**
- **Require timing analysis to ensure the design meets setup time, hold time, and minimum clock pulse width specifications**

Sequential Circuit Timing Analysis


- Timing analysis involves calculating the time delays between all FF pairs within the circuit
- To determine the maximum operating frequency and ensure that setup time requirements are met
 - **The clock cannot be too fast**
- To ensure that hold time requirements are met
 - The minimum propagation delay of the combinational logic (contamination delay) cannot be too small
 - **Independent of clock cycle time**

Important Timing Parameters

 
 


Setup Time Constraint

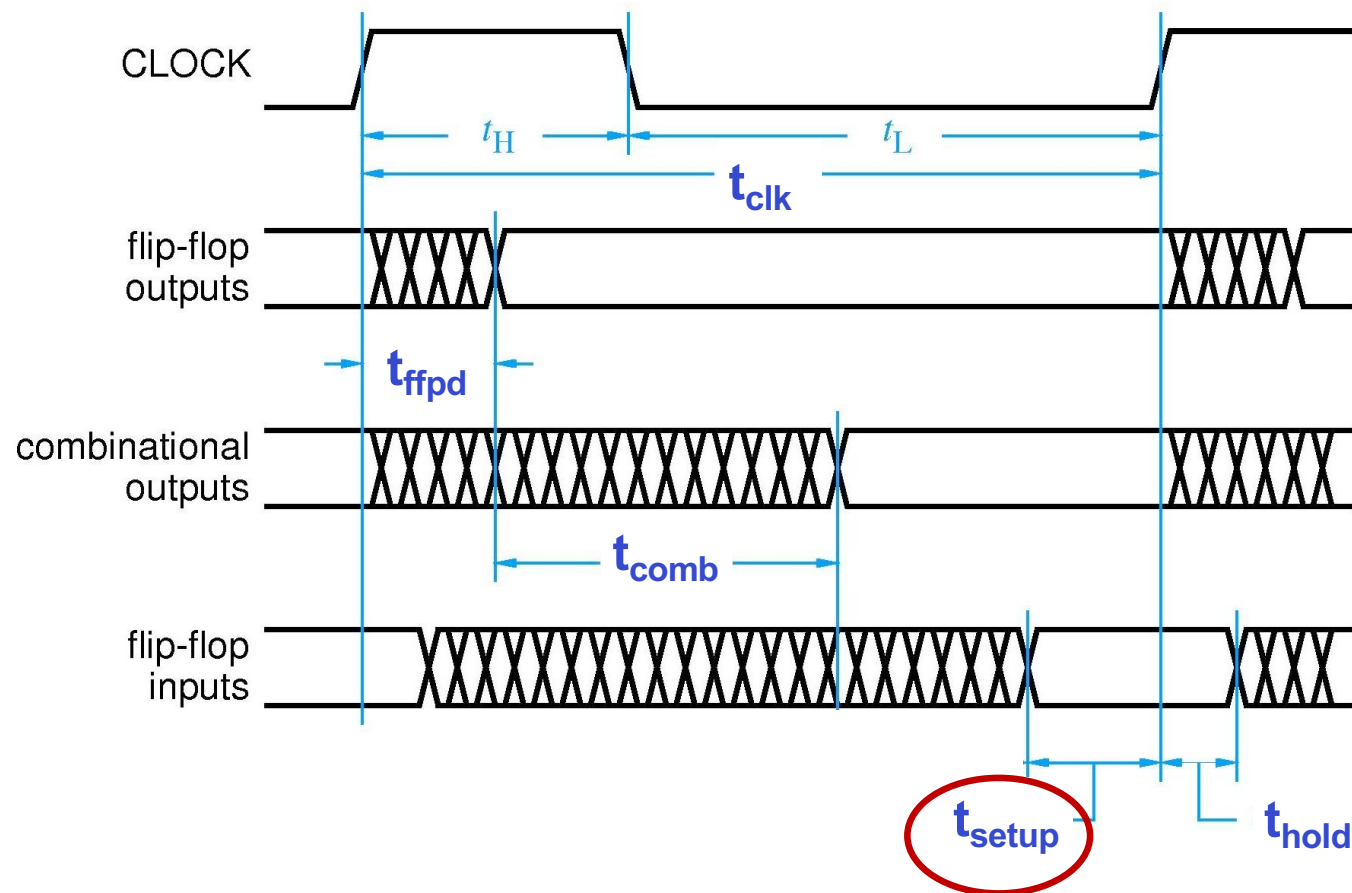- t_{setup} is the minimum amount of time before the triggering edge during which FF input must be stable



Meeting Setup Time Constraint

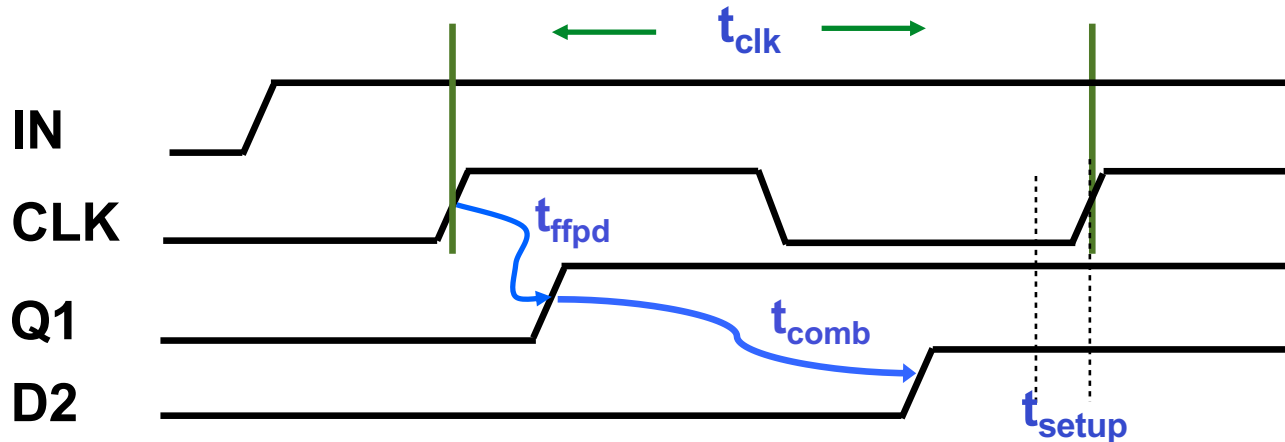 


D2 must stabilize before the t_{setup} window

$$t_{\text{clk}} - t_{\text{setup}} \geq t_{\text{ffpd}(\text{max})} + t_{\text{comb}(\text{max})}$$


We use the maximum delay here because it represents the worst-case scenario for meeting setup time. If the maximum propagation delay satisfies the inequality, the minimum delay case automatically holds, since $t_{\text{ffpd}(\text{max})} + t_{\text{comb}(\text{max})} \geq t_{\text{ffpd}(\text{min})} + t_{\text{comb}(\text{min})}$

Determining Clock Cycle Time

 

- $t_{\text{clk}} \geq t_{\text{ffpd(max)}} + t_{\text{comb(max)}} + t_{\text{setup}}$
Every circuit path between every pair of FFs must satisfy the above equation to run the circuit at a frequency of $1/t_{\text{clk}}$
- Consider maximum propagation delays (the longest timing path) to determine the maximum clock frequency
 - Worst case temperature and voltage
 - Worst case manufacturing variations


Example: Cycle Time Calculation

 

	<i>Prop Delay (ns)</i>		Setup Time (ns)	Hold Time (ns)
	min	max		
FF	1	2	3	1
Comb	3	7	-	-

What's the best achievable cycle time?


Example: Cycle Time Calculation

 

	<i>Prop Delay (ns)</i>		Setup Time (ns)	Hold Time (ns)
	min	max		
FF	1	2	3	1
Comb	3	7	-	-

$$t_{\text{clk}} \geq t_{\text{ffpd}(\text{max})} + t_{\text{comb}(\text{max})} + t_{\text{setup}} = 2 + 7 + 3 = 12\text{ns}$$

Exercise: Cycle Time Analysis

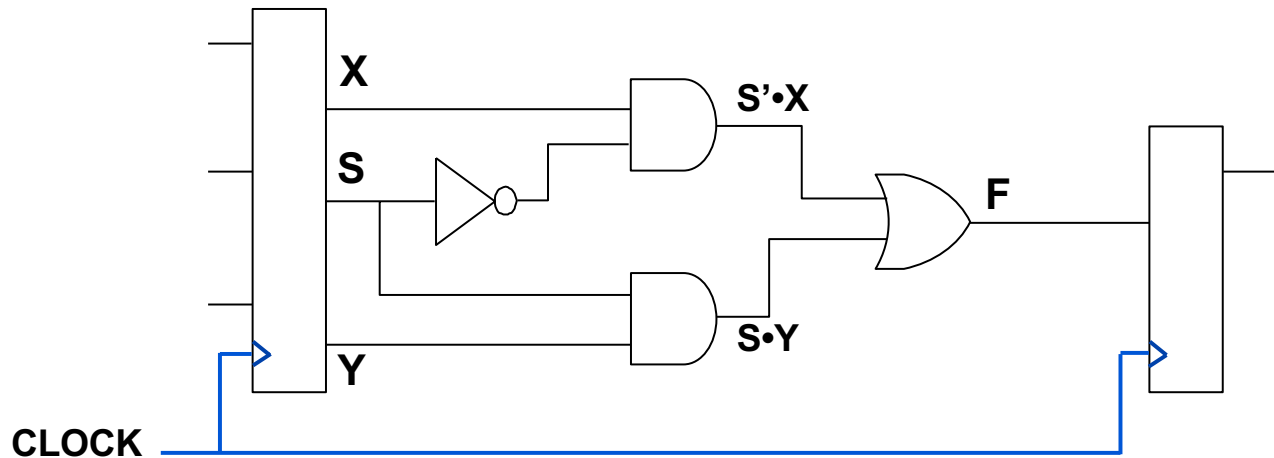



Assumptions:

- (1) FF propagation delay = 1ns
- (2) Uniform gate delay = 1ns
- (3) Setup time = 2ns, hold time = 2ns

What's the best achievable cycle time?

Clock Skew Complicates Matters Further

 
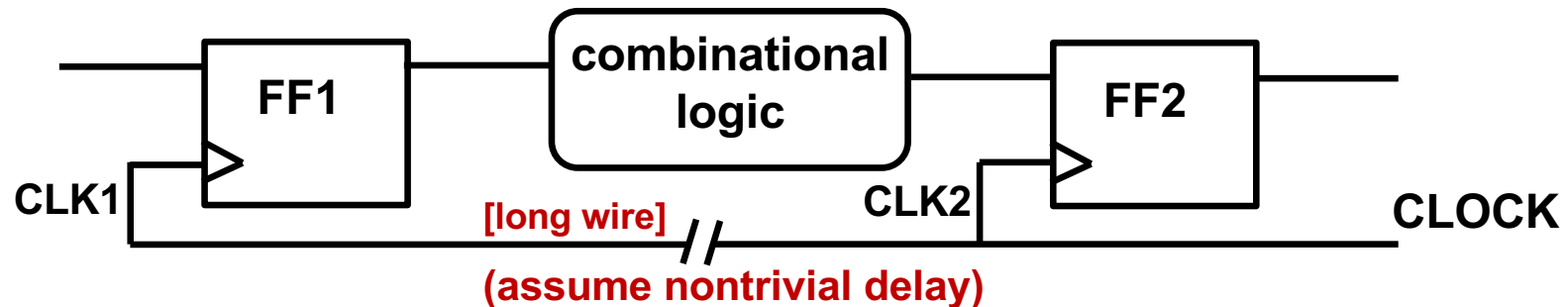
- Clock may not reach all flip-flops simultaneously





$t_{skew(max)}$: Maximum clock skew

$t_{skew(min)}$: Minimum clock skew

Setup Time Analysis With Clock Skew

 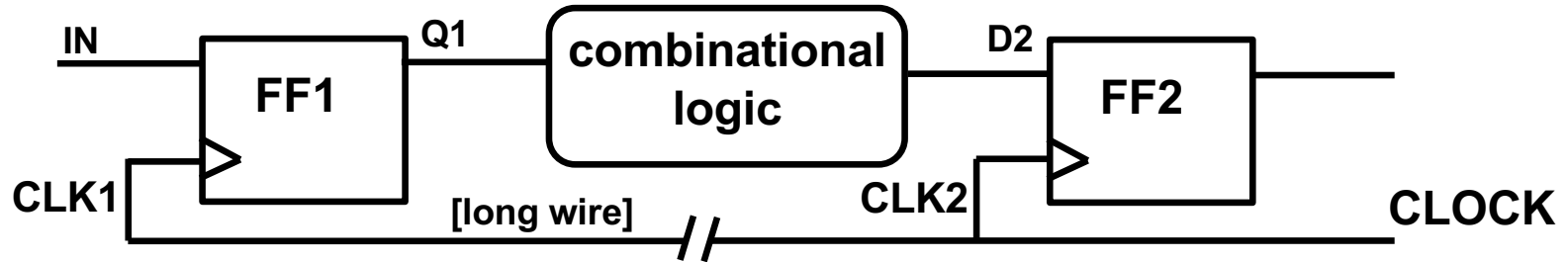

Negative Clock Skew

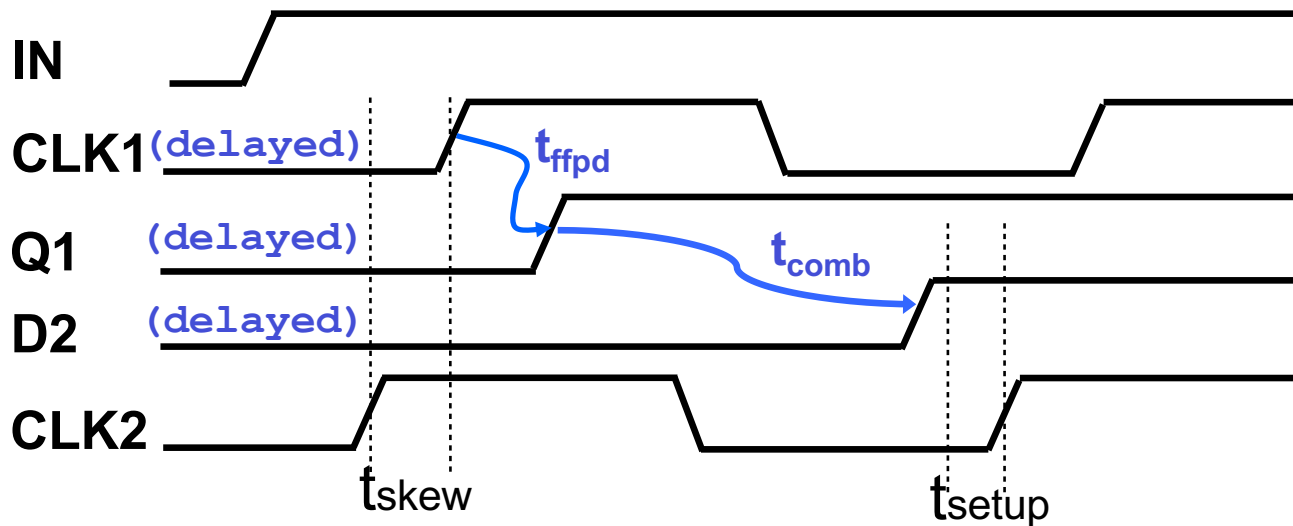
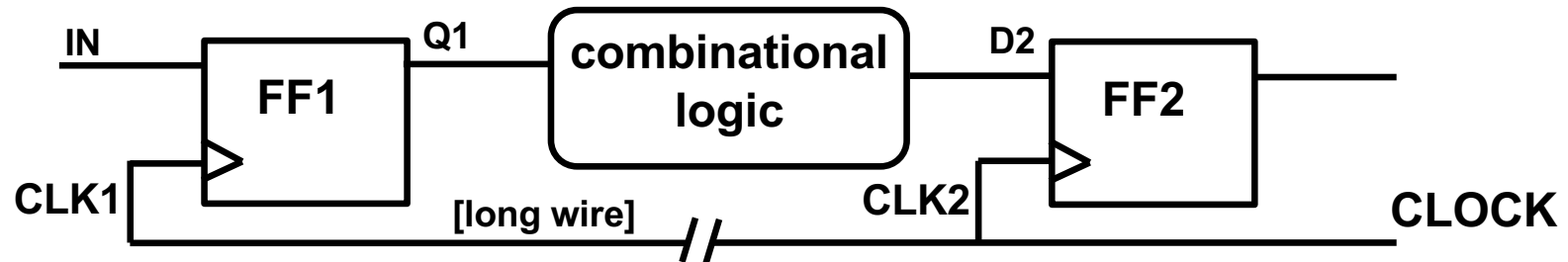


Sending FF receives clock later than receiving FF

$$t_{ffpd(max)} + t_{comb(max)} + t_{setup} \leq t_{clk} - t_{skew(max)}$$

Harmful skew for meeting setup time constraint

Positive Clock Skew

 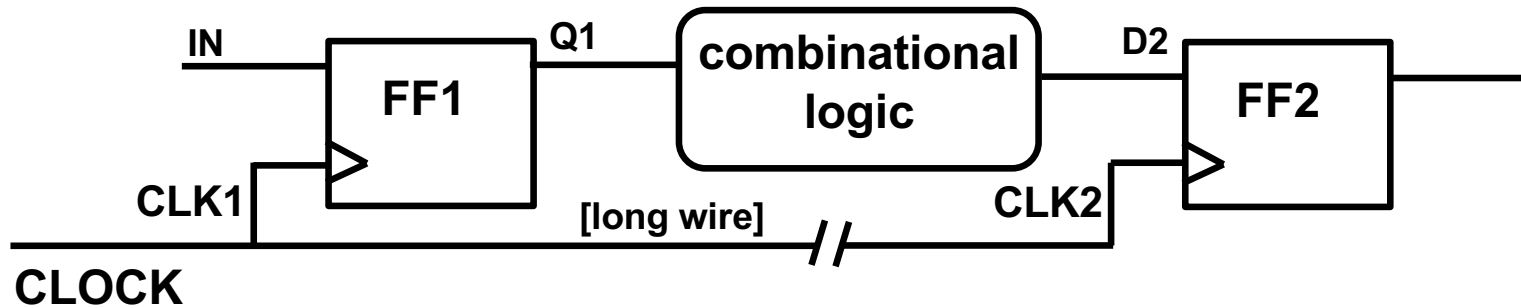


Sending FF receives clock sooner than receiving FF

$$t_{ffpd(max)} + t_{comb(max)} + t_{setup} \leq t_{clk} + t_{skew(min)}$$

Beneficial skew for meeting setup time constraint

Example: Setup Analysis with Clock Skew

 


Clock arrives at FF1 **at least 4ns** earlier than FF2

	<i>Prop Delay (ns)</i>		Setup Time (ns)	Hold Time (ns)
	min	max		
FF	1	2	3	1
Comb	3	7	-	-

- **What's the best achievable cycle time?**

Example: Setup Analysis with Clock Skew

 

Clock arrives at FF1 at least 4ns earlier than FF2

	<i>Prop Delay (ns)</i>		Setup Time (ns)	Hold Time (ns)
	min	max		
FF	1	2	3	1
Comb	3	7	-	-


- What's the best achievable cycle time?

$$t_{\text{ffpd}(\text{max})} + t_{\text{comb}(\text{max})} + t_{\text{setup}} \leq t_{\text{clk}} + t_{\text{skew}(\text{min})}$$


$$t_{\text{clk}} \geq 2 + 7 + 3 - 4 = 8\text{ns}$$

Hold Time Constraint

 - t_{hold} is the minimum amount of time after the triggering edge during which *FF input must remain stable*



Avoiding Hold Time Violation

 

- FF input must remain stable after the triggering edge by at least t_{hold} amount of time
 - Otherwise, the receiving flip-flop may be contaminated with an unexpected value
- Need to consider minimum propagation delays (the shortest timing path) for hold time calculations

$$t_{\text{ffpd}(\text{min})} + t_{\text{comb}(\text{min})} \geq t_{\text{hold}}$$

We'll discuss this next lecture

Next Class

More Timing Analysis
Binary Arithmetic
(H&H 1.4)