

ECE 2300
Digital Logic & Computer Organization
Spring 2025

Single Cycle Microprocessor




Cornell University


Announcements

- **HW 5 due tomorrow**
- **HW 6 will be posted today**
 - **Covers Lecture 16**
- **Prelim 2: Thursday April 10, 7:30pm, 90mins, GSH G76**
 - **Coverage: Lectures 8~16**
 - **FSMs, timing analysis, binary arithmetic, memories, single-cycle microprocessor (no Verilog)**
 - **A sample exam will be posted on CMS next week**
 - **TA-led review will be scheduled on Monday 4/7**
 - **Email the instructor asap if you have a conflict**

SRAM vs. DRAM

 

 
- **SRAM: usually on the same chip with CPU**
 - (+) Fast access
 - (-) Relatively high area & cost per bit (6T)



- **DRAM: typically off-chip & used for main memory**
 - (+) Single transistor bit cell (1T1C)
 - Lower area & lower cost per bit
 - (-) Slow: need periodic refresh

SRAM typically ranges from KB to MB, while DRAM is usually in GB.


Computer Memory Explained (by analogy)

 


Course Roadmap (Part 1)

- Boolean algebra
- Combinational logic and minimization
- Logic functions
- CMOS gates
- Binary arithmetic and ALUs
- Latches and flip-flops
- Counters
- Verilog
- Finite state machines
- Hazards, timing, clocking
- Memories


Part 2: Computer Organization

 

Let's Build a Microprocessor!

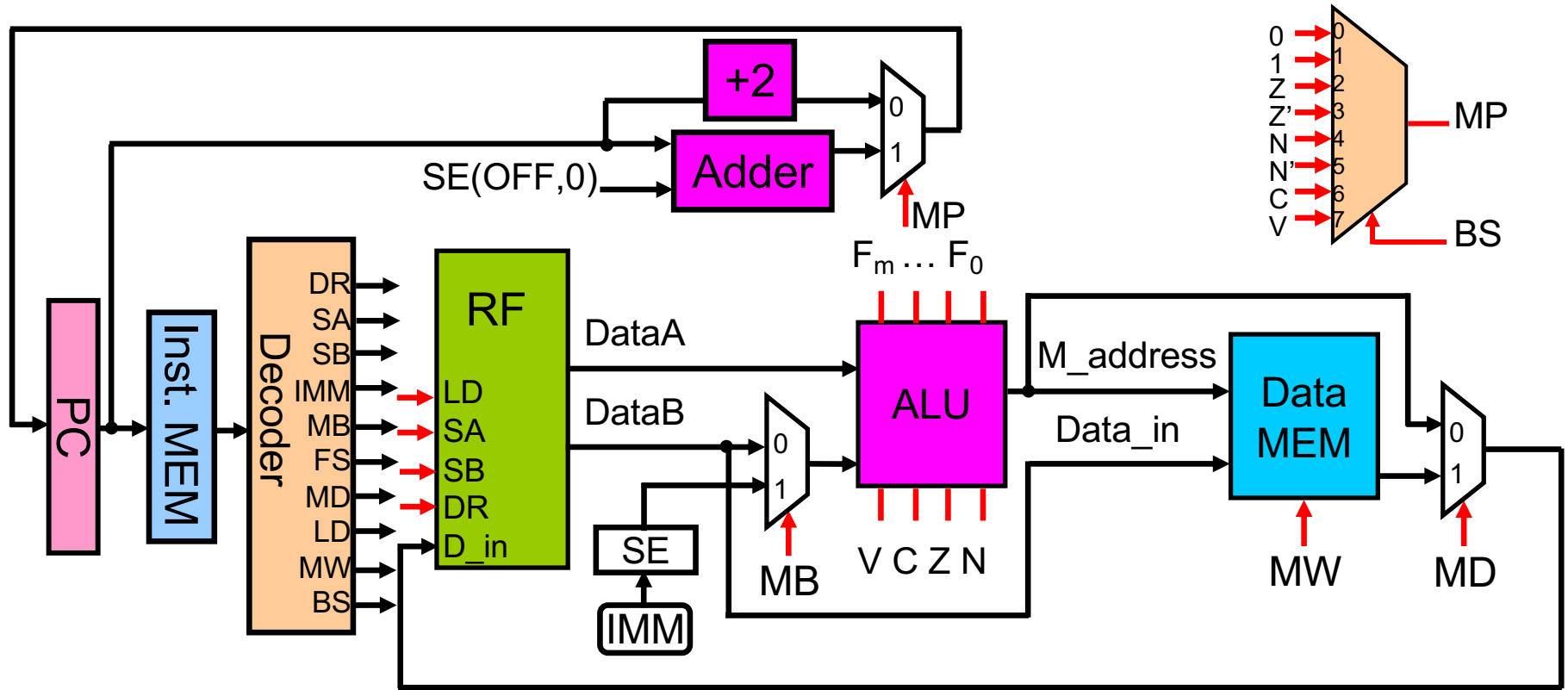


The Compute Core

 

- The processor has internal memory called the register file (RF), built with DFFs or SRAM, which are much faster to access than DRAM, but also a lot more expensive¹
- The ALU reads data from the RF, performs computations, and write back the result

¹ The RF is small, so data must be moved between main memory and RF using explicit load/store instructions (covered in later slides).

The Basic Processing Cycle

 

- Read data from two registers
- Perform an operation
- Place the result into a register
- All three steps performed in 1 clock cycle

Register File (RF)

- **Collection of 2^k n-bit registers**


- **Data outputs (two read ports)**

DataA – Output data A

DataB – Output data B

- **Data inputs (one write port)**

D_in – Input data

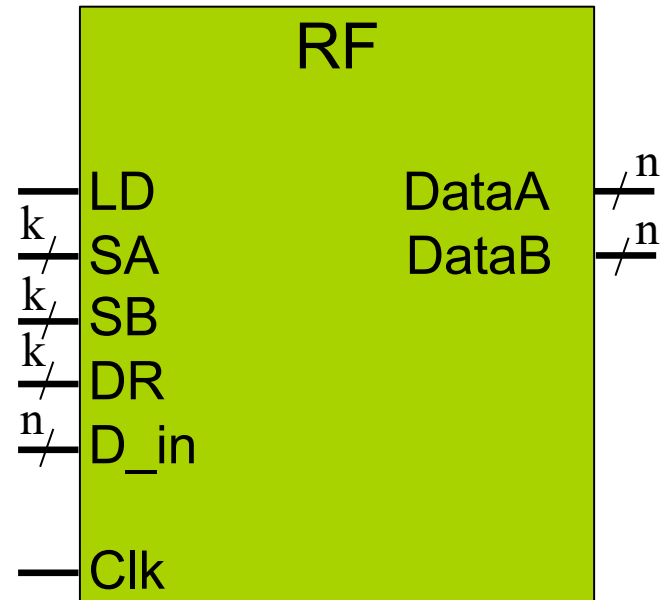

- **Control inputs**


SA – Address (or index) of source register A

SB – Address of source register B

DR – Address of destination register


LD (i.e., write enable) – Load D_in into destination register DR

Example RF Organization

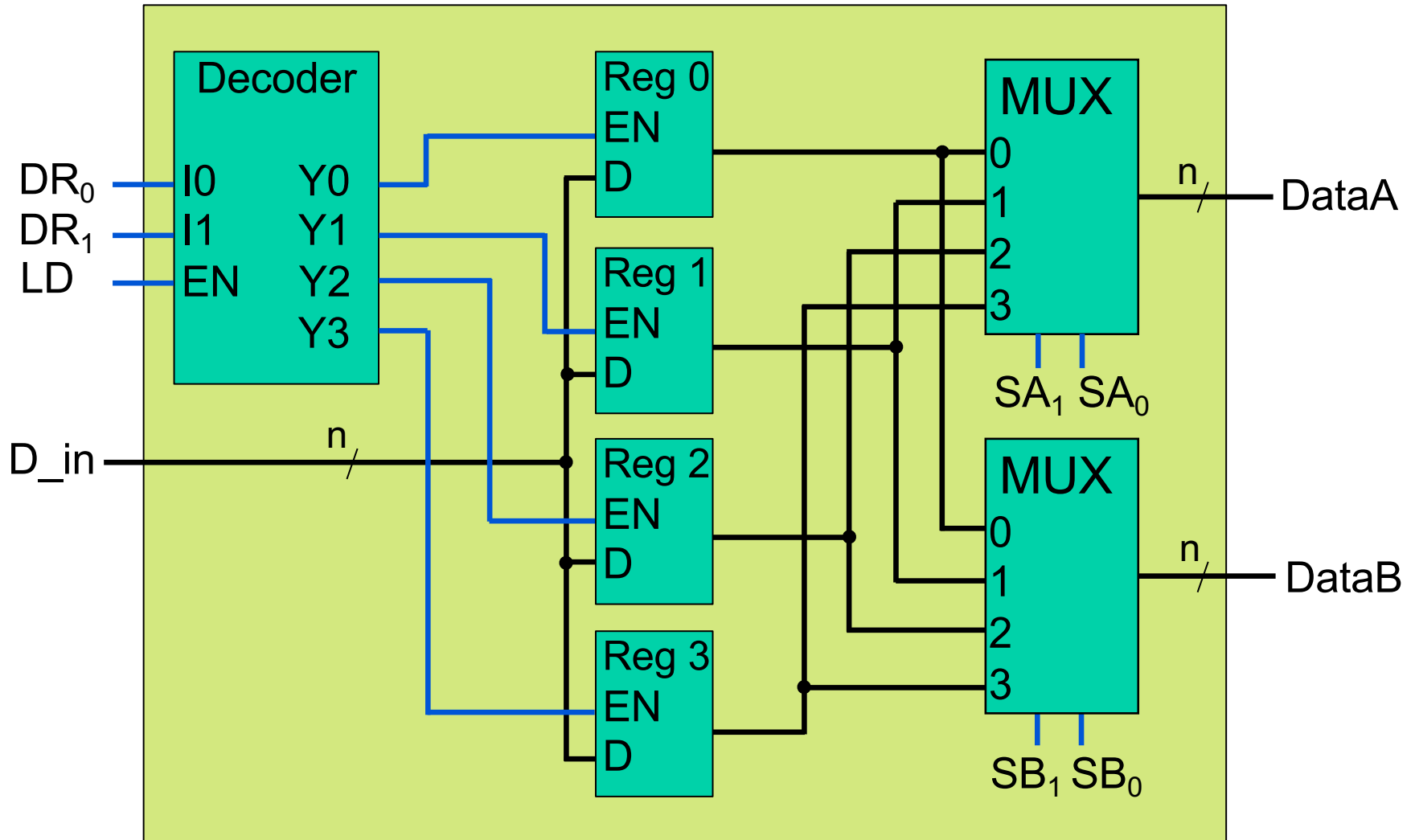

Example with 4 registers. Typically have 32 or more.


Instruction Execution

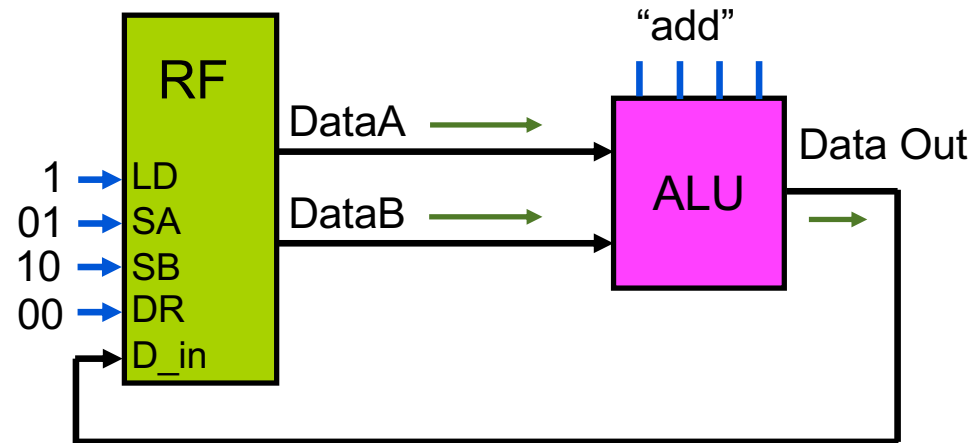


Example: **ADD R0, R1, R2** // R0 \leftarrow R1 + R2

operation \nearrow
destination register \nearrow
source registers \nearrow
(write to Reg 0) (read from Reg 1 & Reg 2)


Instruction Execution

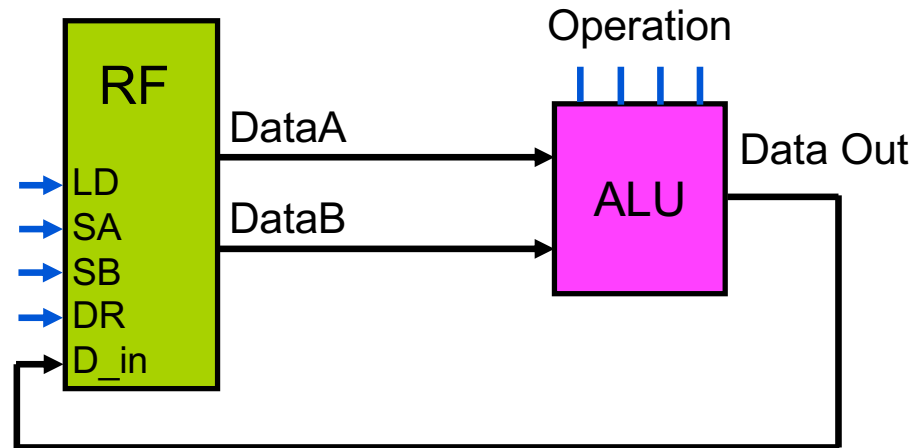


ADD R0, R1, R2

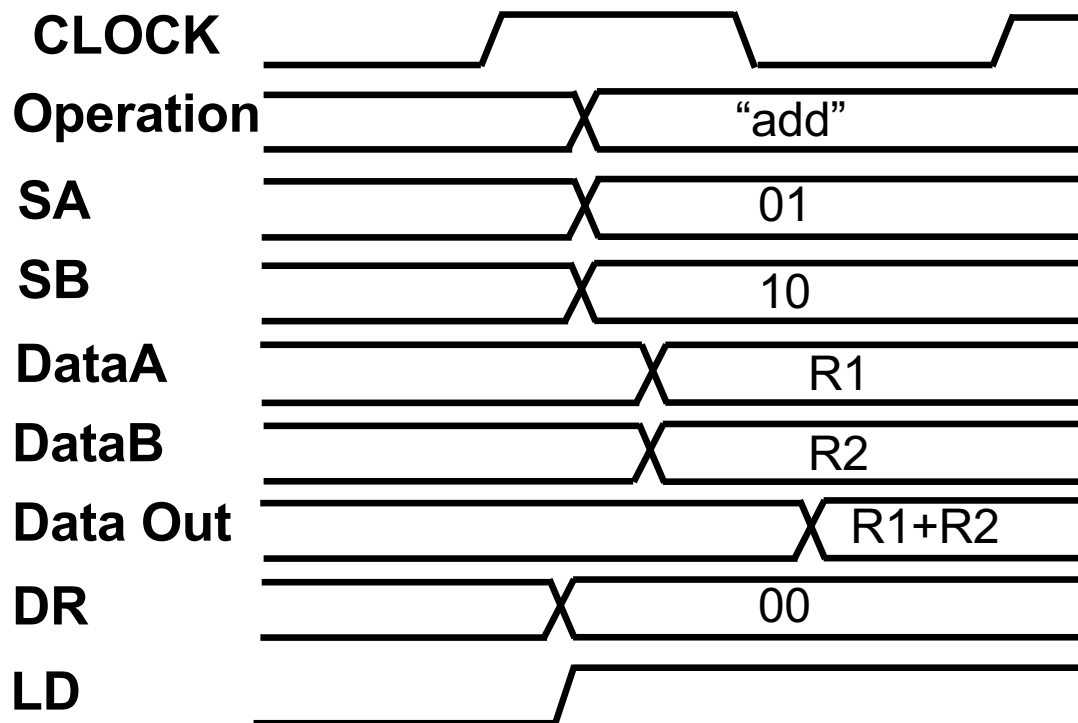


Instruction Execution

 

ADD R0, R1, R2
SUB R3, R2, R1

 

Operations With Constants

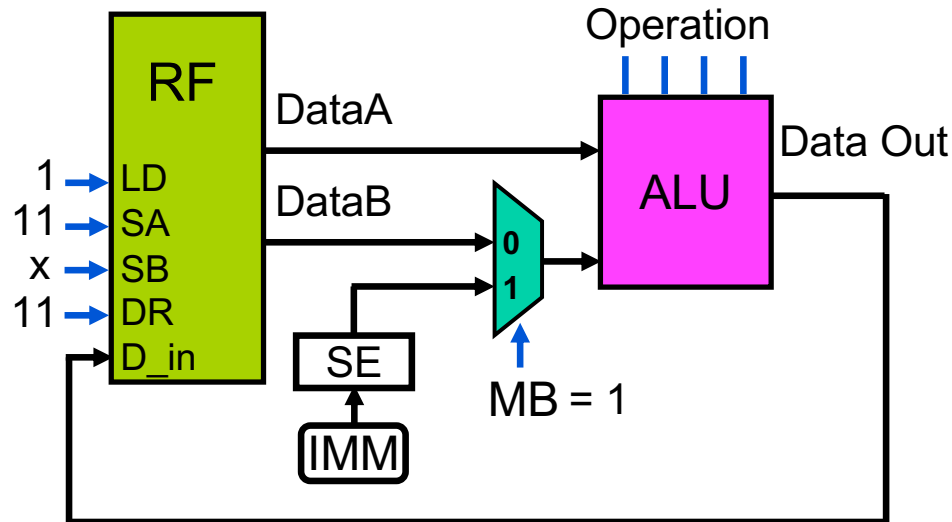

```
ADDI R3, R3, 1
// R3 <= R3 + 1
```

- Constants are called *immediate values* (IMM)
- Sign extend (SE) IMM to the width of DataA to perform correct two's complement operation
 - Why? not enough bits in instruction (explained later)
 - Assume IMM is 4 bits and DataA is 8 bits wide

```
0001 → 00000001
1110 → 11111110
```


Sign Extension

- Replicate the MSB (sign bit)

<u>4-bit</u>		→	<u>8-bit</u>	
0100	(4)		00000100	(still 4)
1100	(-4)		11111100	(still -4)


- Necessary for aligning two's complement numbers of different lengths before a fixed-size arithmetic operation

Reading and Writing Memory

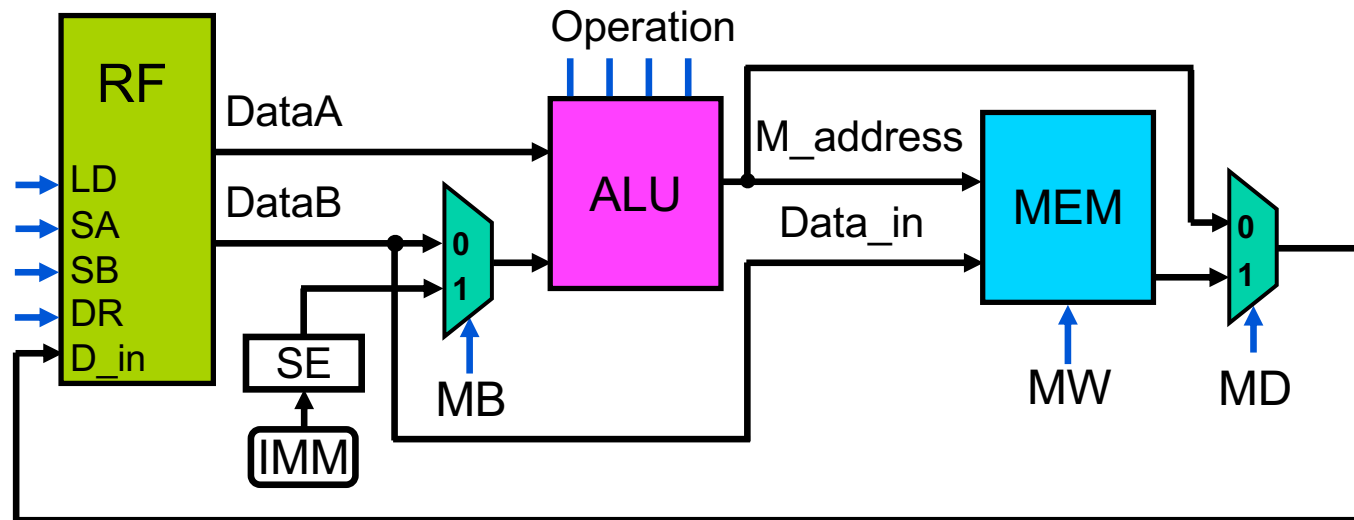

- Most data are held in main memory (MEM)
- Must be moved into registers for ALU to operate on them
- Data will also move out of registers into memory
 - To make room for other data
 - Or to later move it to permanent storage (e.g., disk)

Reading from Memory (“Load”)

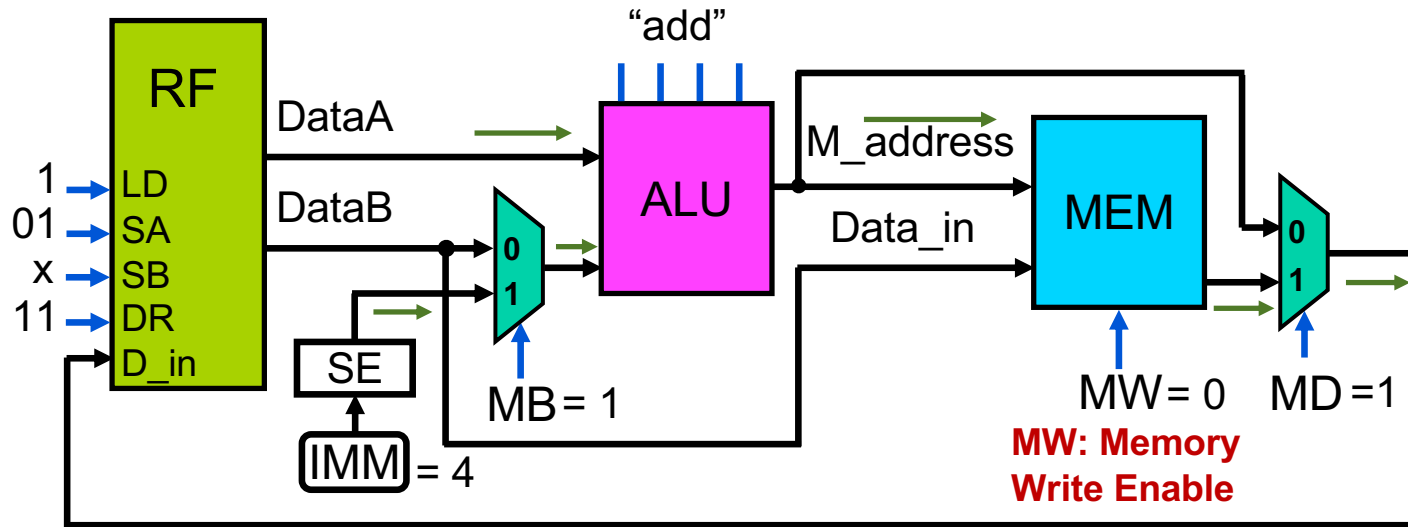


Example: **LOAD R3, 4(R1)** // $R3 \leftarrow M[R1 + 4]$

M means “Main Memory”

Step 1: Form the memory address by adding R1 (*base address*) with the immediate 4 (*offset*)

Step 2: Read the data at that address in RAM ($M[R1+4]$) and place it in R3

Writing to Memory (“Store”)

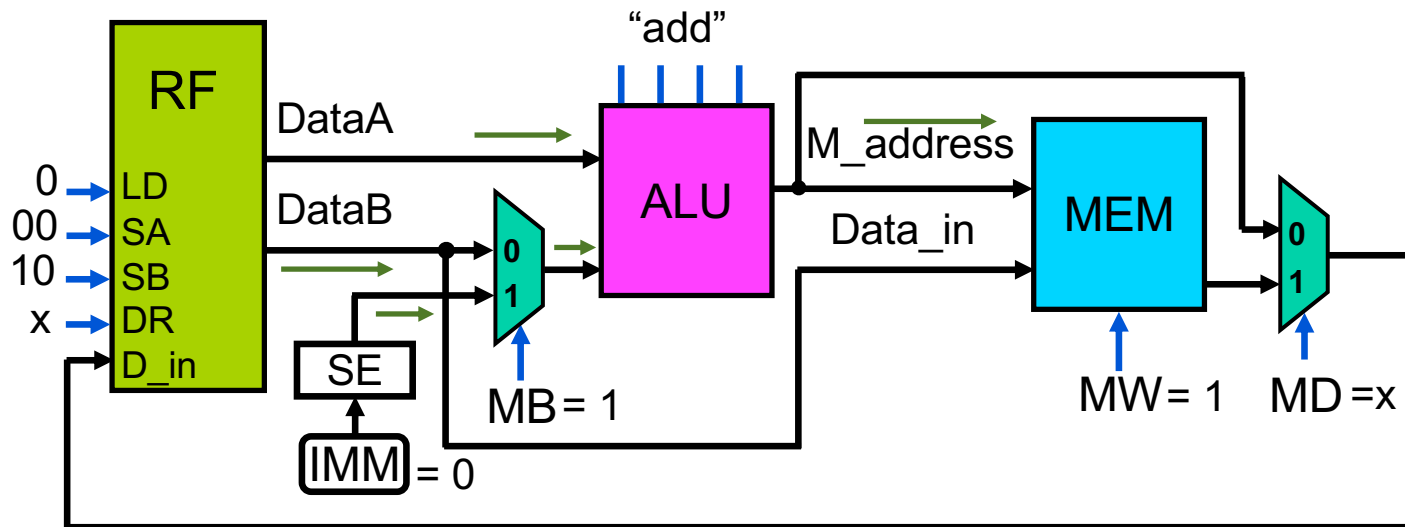

Example: **STORE R2, 0(R0)** // $M[R0] \leftarrow R2$



Step 1: Form the memory address by adding R0 (base) with the immediate 0 (offset)

Step 2: Write the data in R2 into the RAM at that address ($M[R0+0]$, i.e., $M[R0]$)

Control Unit (CU)


- **Regulates the interaction between data and operations on data (i.e., datapath)**
- **Series of *control words* control the datapath to perform a sequence of operations**
- **The sequence of operations performed by the CU may be affected by the *ALU Condition Codes***
 - **Z: Zero**
 - **N: Negative**
 - **Also V: Overflow and C: Carry out**

Datapath + Control Unit

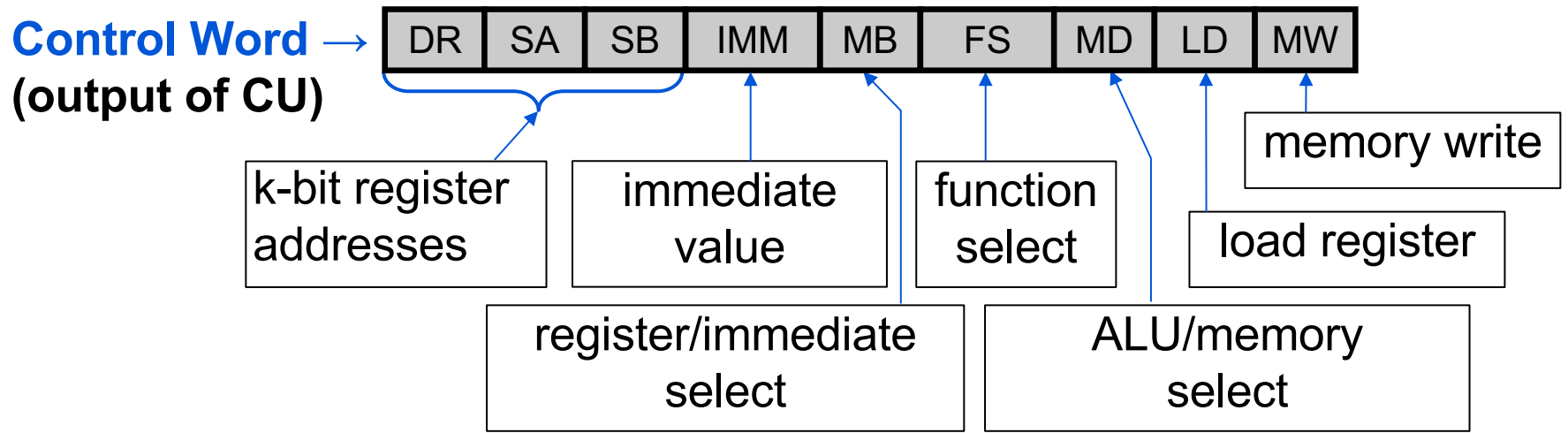 

Sequence of Operations

Assuming 8 registers in the RF

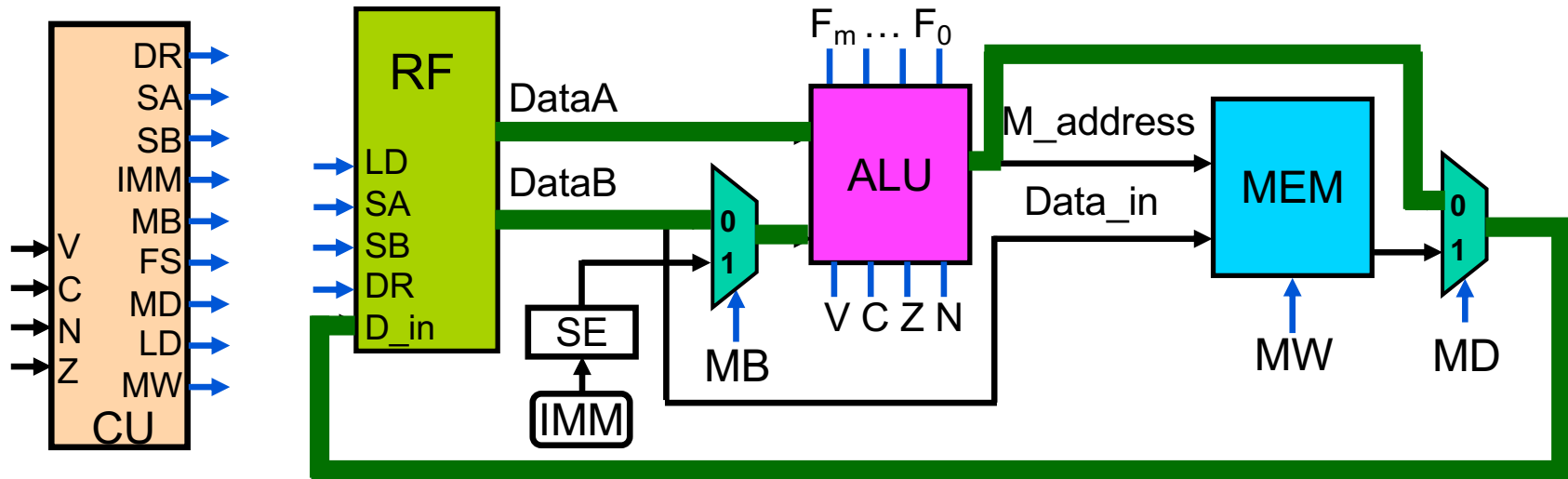


R2 <= R0 + R1

DR	SA	SB	IMM	MB	FS	MD	LD	MW
010	000	001	x	0	ADD	0	1	0

Sequence of Operations

Assuming 8 registers in the RF

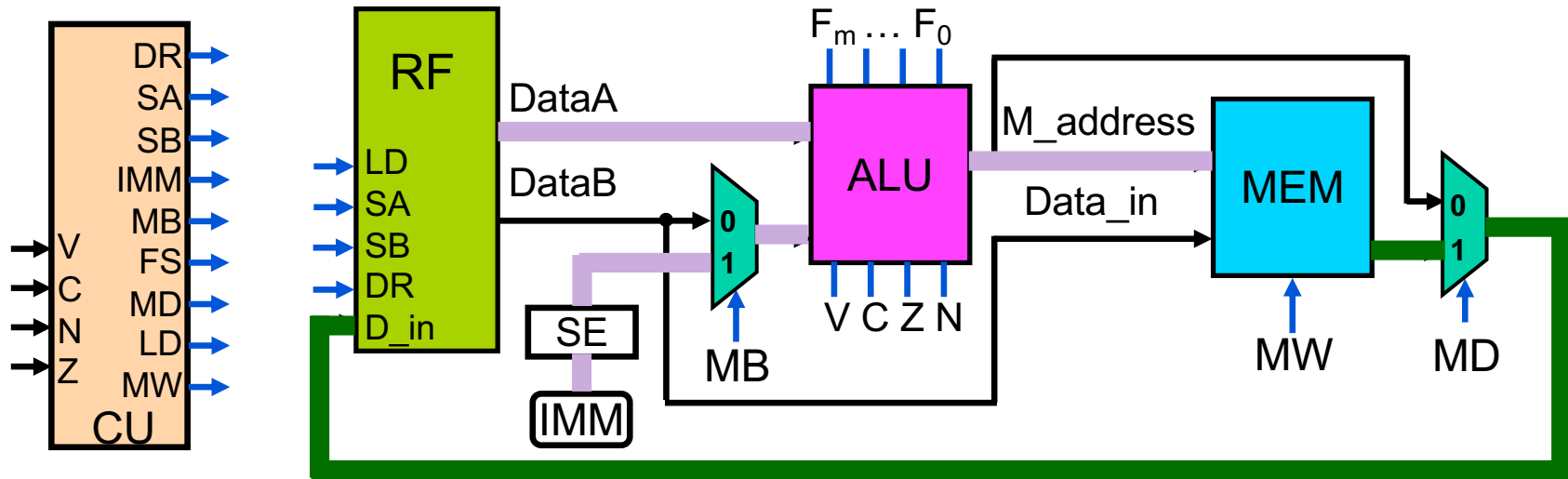


$R2 \leq R0 + R1$

$R1 \leq M[R2]$

DR	SA	SB	IMM	MB	FS	MD	LD	MW
010	000	001	x	0	ADD	0	1	0
001	010	x	0	1	ADD	1	1	0

Sequence of Operations

Assuming 8 registers in the RF

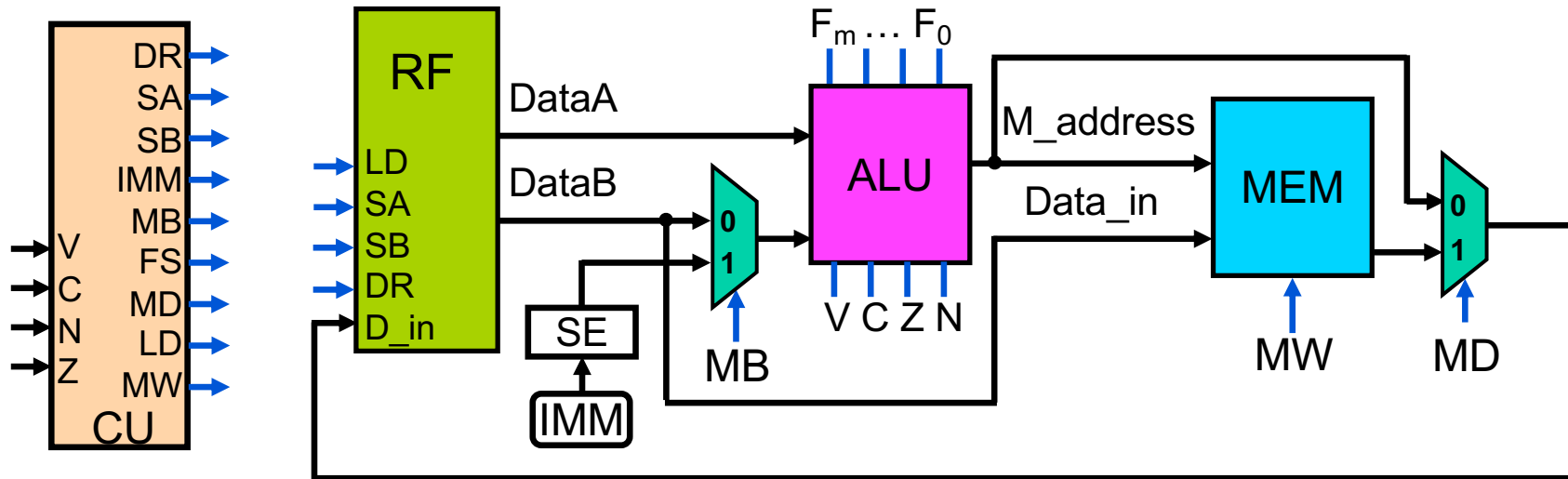

$$R2 \leq R0 + R1$$

$$R1 \leq M[R2]$$

$$R3 \leq R1 - 3$$

DR	SA	SB	IMM	MB	FS	MD	LD	MW
010	000	001	x	0	ADD	0	1	0
001	010	x	0	1	ADD	1	1	0
x	010	000	0	1	ADD	x	0	1
011	001		3		SUB			

Next Class

**More Single Cycle Microprocessor
(H&H 7.3)**