

**ECE 2300**  
**Digital Logic & Computer Organization**  
**Spring 2025**

**Instruction Set Architecture**  
**Pipelined Microprocessor**





Cornell University

Lecture 17: 1

# Announcements

- HW 6 due tomorrow
- Solutions to HW 5-6 and sample prelim 2 will be posted next week
- TA-led prelim 2 review is scheduled on Monday 4/7, 7:30pm

# Review: Branch

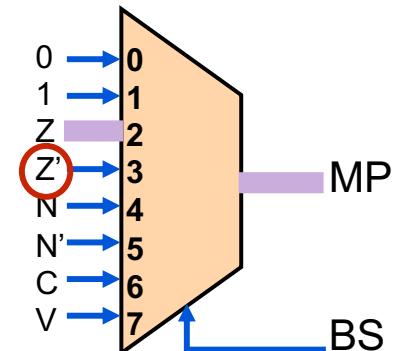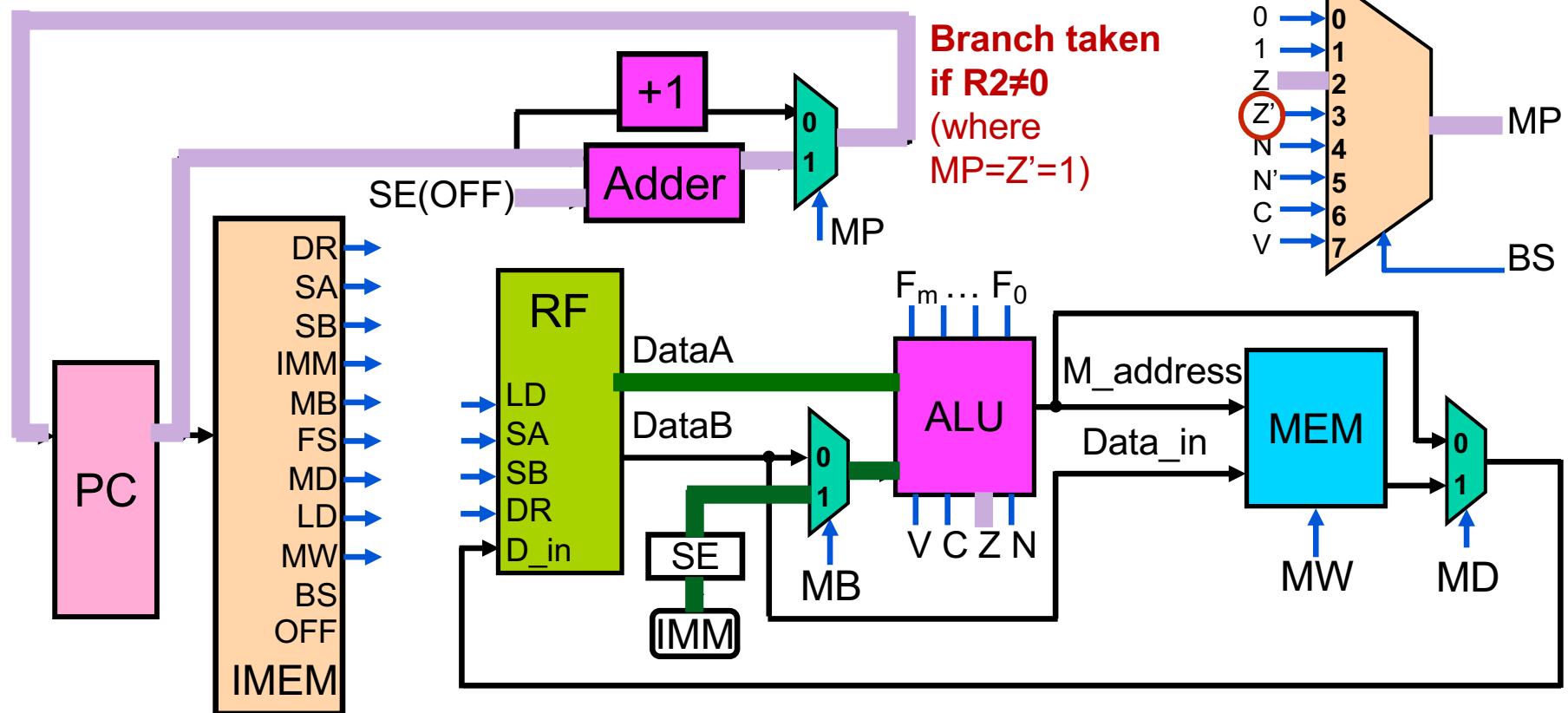

$R1 \leftarrow R1 \ll 1$   
**if ( $R2 \neq 0$ ) goto 4**  
 $M[R0+2] \leftarrow R3$


	DR	SA	SB	IMM	MB	FS	MD	LD	MW	BS	OFF
8:	001	001	x	x	x	SLL	0	1	0	000	x
9:	x	010	x	0	1	SUB	x	0	0	011	-5
10:	x	000	011	2	1	ADD	x	0	1	000	x

**Branch if non-zero**

Lecture 17: 3
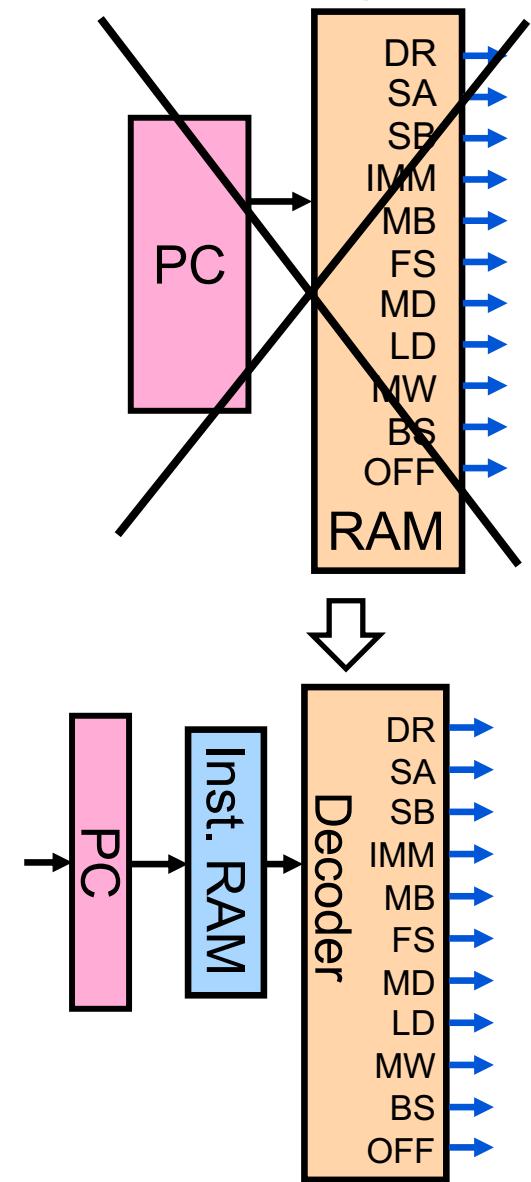
# Review: Providing Even More Flexibility

- Replace control words with instructions
  - More intuitive and not specific to particular hardware
  - Shorter than control words
  - Instruction decoder (hardwired logic) creates the control words from the instruction




# Instruction Set Architecture (ISA)


- The ISA describes a set of instructions supported by a family of machines
- The ISA specification informs hardware & software (compiler and operating system) developers about
  - Instruction formats
  - Operation of each instruction
  - Ways to form memory addresses
  - Data formats
  - Lots of other
- Examples: x86, ARM, MIPS, POWER, SPARC, RISC-V
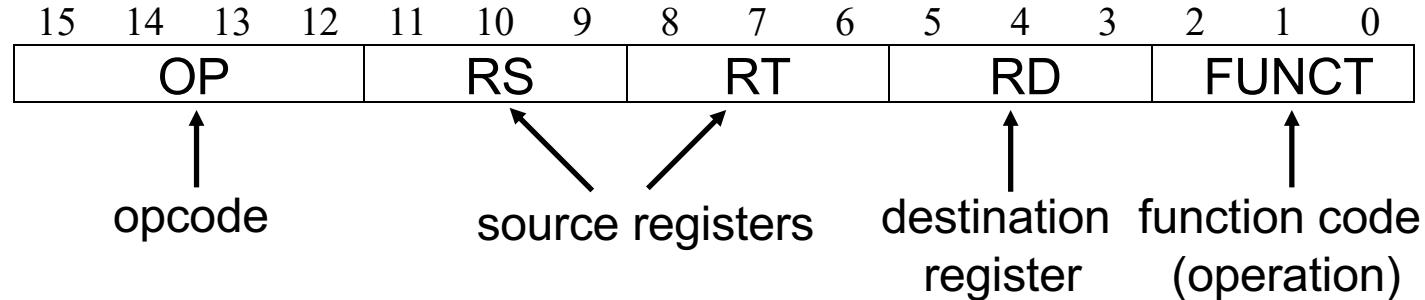
# Our 2300 Instruction Formats

Register to Register (*R*-Type): ALU operations with 2 source registers



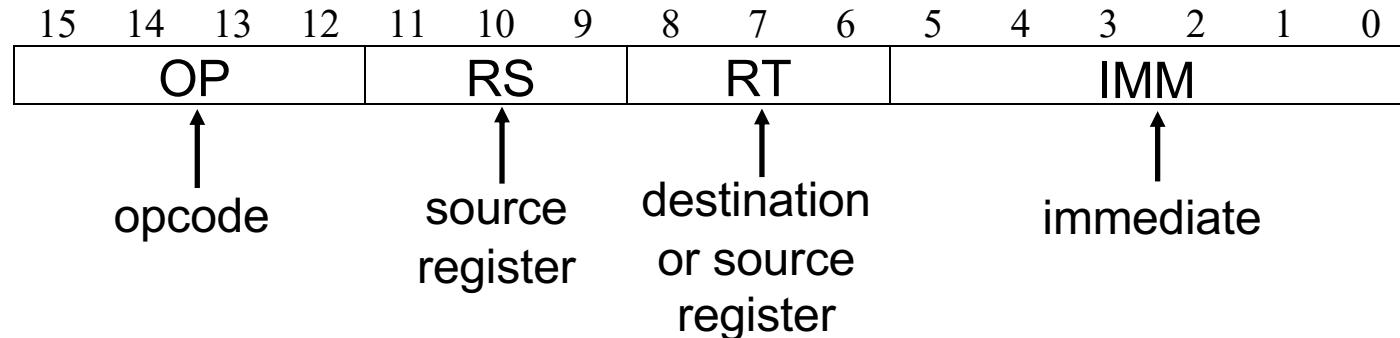Immediate (*I*-Type): ALU operations with immediate, load/store, branch




Our 2300 instructions are 2 bytes wide (16 bits)

Lecture 17: 6
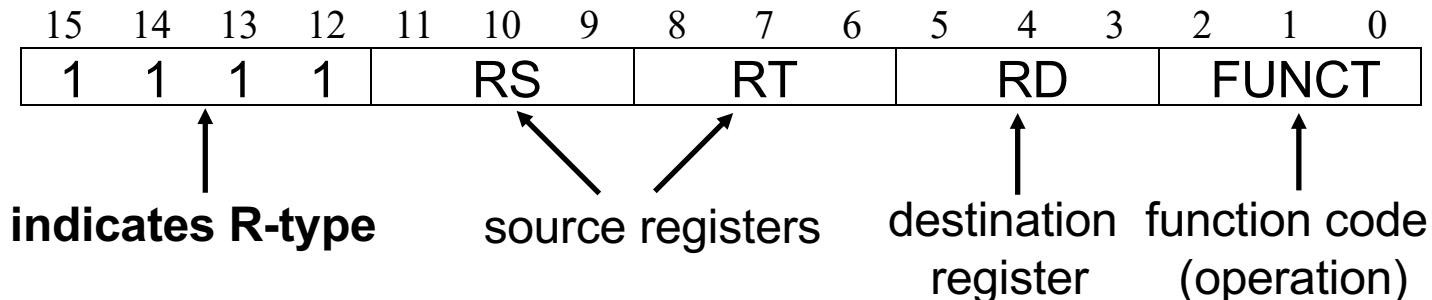
# R-Type Instructions

Register to Register (R-Type): ALU operations with 2 source registers



FUNCT	Instruction
000	ADD RD, RS, RT
001	SUB RD, RS, RT
010	SRA RD, RS
011	SRL RD, RS
100	SLL RD, RS
101	AND RD, RS, RT
110	OR RD, RS, RT
111	Unused

**Arithmetic Right Shift (SRA)** on RS by 1 bit; result is put into RD  
**(preserves sign bit)**

**Logical Right Shift (SRL)** on RS by 1 bit; result is put into RD  
**(0 shifted into MSB)**


**Logical Left Shift (SLL)** on RS by 1 bit; result is put into RD  
**(0 shifted into LSB)**

# Logical and Arithmetic Right Shift

- **Logical right shift (SRL)**
  - Shifts each bit right by 1 position; 0 shifted into MSB
    - Example: 10000000 after SRL => 01000000
- **Arithmetic right shift (SRA)**
  - Preserves the sign bit
    - Example: 10000000 after SRA => 11000000
  - Equivalent to signed division by 2 (for two's complement)
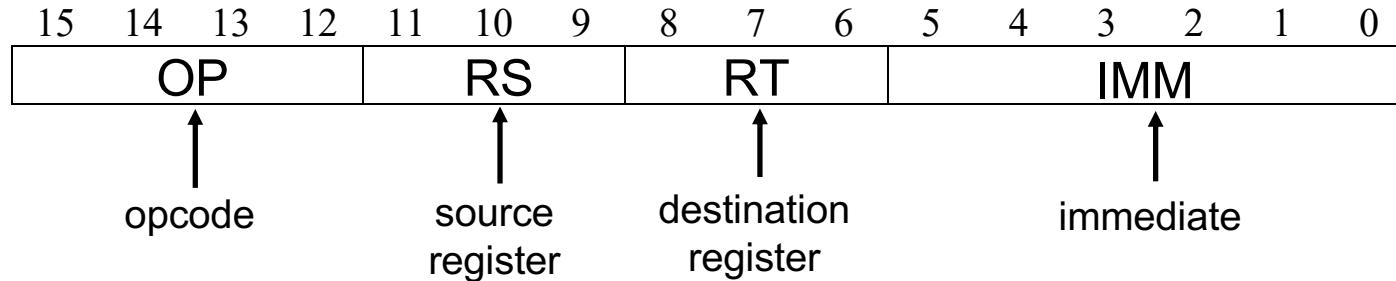
# I-Type: ALU with Immediate

Immediate (I-Type): ALU operations with immediate, load/store, branch




**ALU operations with immediate**

OP	Instruction
0101	ADDI RS, RT, IMM
0110	ANDI RS, RT, IMM
0111	ORI RS, RT, IMM
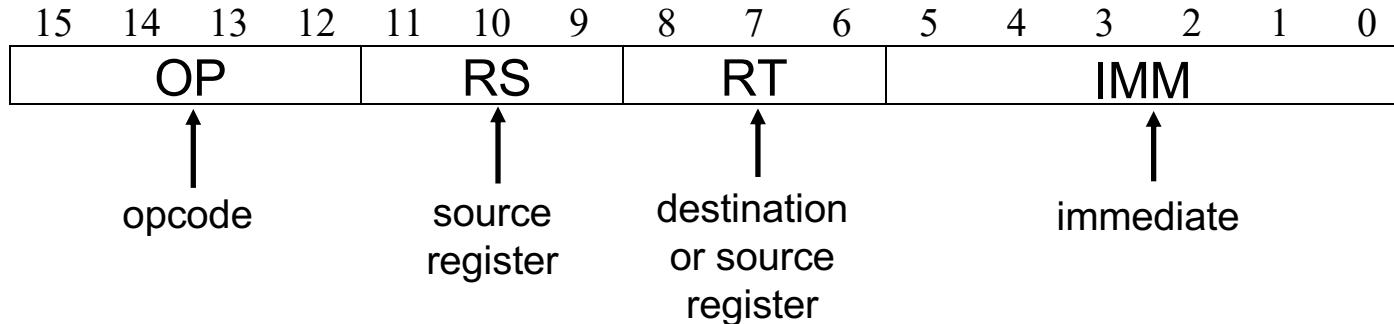
# I-Type: Load and Store

Immediate (I-Type): ALU operations with immediate, load/store, branch



## Load and Store Instructions

OP	Instruction
0001	LW RT, IMM(RS)
0010	LB RT, IMM(RS)
0011	SW RT, IMM(RS)
0100	SB RT, IMM(RS)

(Load Word)

(Load Byte)

(Store Word)

(Store Byte)


- **Important assumptions in our ISA**
  - Main memory is byte addressable
  - 2 bytes per word

# Memory Operations

- Like other modern computer architectures, our ISA assumes a byte addressable memory system
  - The smallest addressable quantity in the main memory system is a *byte* (8 bits)
  - Hence a memory address points to a byte
- LB: Load Byte
  - Reads the byte at this address
- LW: Load Word
  - reads a word this address, which in our case is 2 bytes
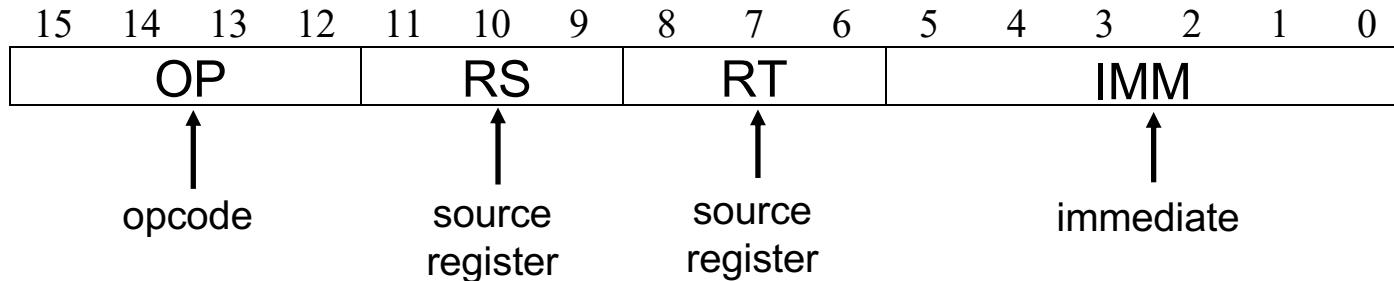
# I-Type: Branch

Immediate (I-Type): ALU operations with immediate, load/store, branch



## Branch Instructions

OP	Instruction
1000	BEQ RT, RS, target
1001	BNE RT, RS, target
1010	BGEZ RS, target
1011	BLTZ RS, target


(if  $RT = RS$ , goto target addr)  
(if  $RT \neq RS$ , goto target addr)  
(if  $RS \geq 0$ , goto target addr)  
(if  $RS < 0$ , goto target addr)

- **Condition**
  - Test two registers for equality (BEQ, BNE)
  - Test if a register is positive or negative (BGEZ, BLTZ)
- **Target address: Formed by adding the offset to the PC**
  - Where to jump in the program if the condition is true

# Forming the Branch Target Address

Instruction	Format	OP	Operation
<b>BEQ rt,rs,target</b>		<b>1000</b>	$\text{if}(R[\text{rs}] == R[\text{rt}]) \text{ PC} = \text{PC} + \text{sext}(\{\text{imm}, 1'b0\})$
<b>BNE rt,rs,target</b>		<b>1001</b>	$\text{if}(R[\text{rs}] \neq R[\text{rt}]) \text{ PC} = \text{PC} + \text{sext}(\{\text{imm}, 1'b0\})$
<b>BGEZ rs,target</b>		<b>1010</b>	$\text{if}(R[\text{rs}] \geq 0) \text{ PC} = \text{PC} + \text{sext}(\{\text{imm}, 1'b0\})$
<b>BLTZ rs,target</b>		<b>1011</b>	$\text{if}(R[\text{rs}] < 0) \text{ PC} = \text{PC} + \text{sext}(\{\text{imm}, 1'b0\})$

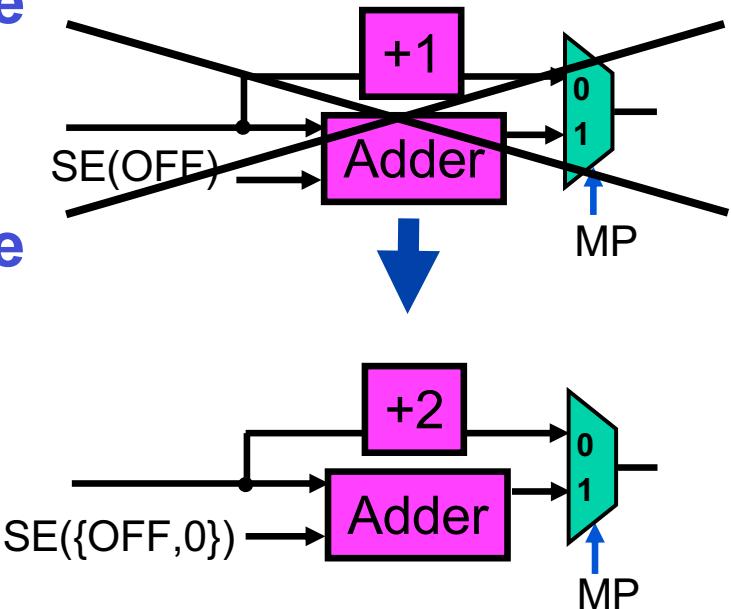- A memory address points to a byte location (byte addressable)
- Since instructions are 2 bytes wide
  - Instructions are located at even locations (0, 2, 4, ...)
  - The PC must be incremented by 2 ( $\text{PC}+2$ )
  - Since the offset refers to the number of *instructions* (not bytes) to jump, we append a 0 to LSB (i.e.,  $\{\text{imm}, 1'b0\}$ )



# Iterative Multiplication Revisited


- L0: SUB R0,R0,R0
- L1: LB R1,0(R0)
- L2: LB R2,1(R0)
- L3: SUB R3,R3,R3
- L4: ANDI R4,R2,1
- L5: BEQ R4,R0,L7
- L6: ADD R3,R3,R1
- L7: SRL R2,R2
- L8: SLL R1,R1
- L9: BNE R2,R0,L4
- L10: SW R3,2(R0)

OP	RS	RT	RD	FUNCT
1111	000	000	000	001
0010	000	001		000000
0010	000	010		000001
1111	011	011	011	001
0110	010	100		000001
1000	000	100		<u>000010</u>
1111	011	001	011	000
1111	010	xxx	010	011
1111	001	xxx	001	100
1001	000	010		<u>111011</u>
0011	000	010		000010
OP	RS	RT	IMM	

## Instruction Encoding

\* The branch offsets are usually automatically generated by assembler based on labels

# Programmable Single-Cycle Processor

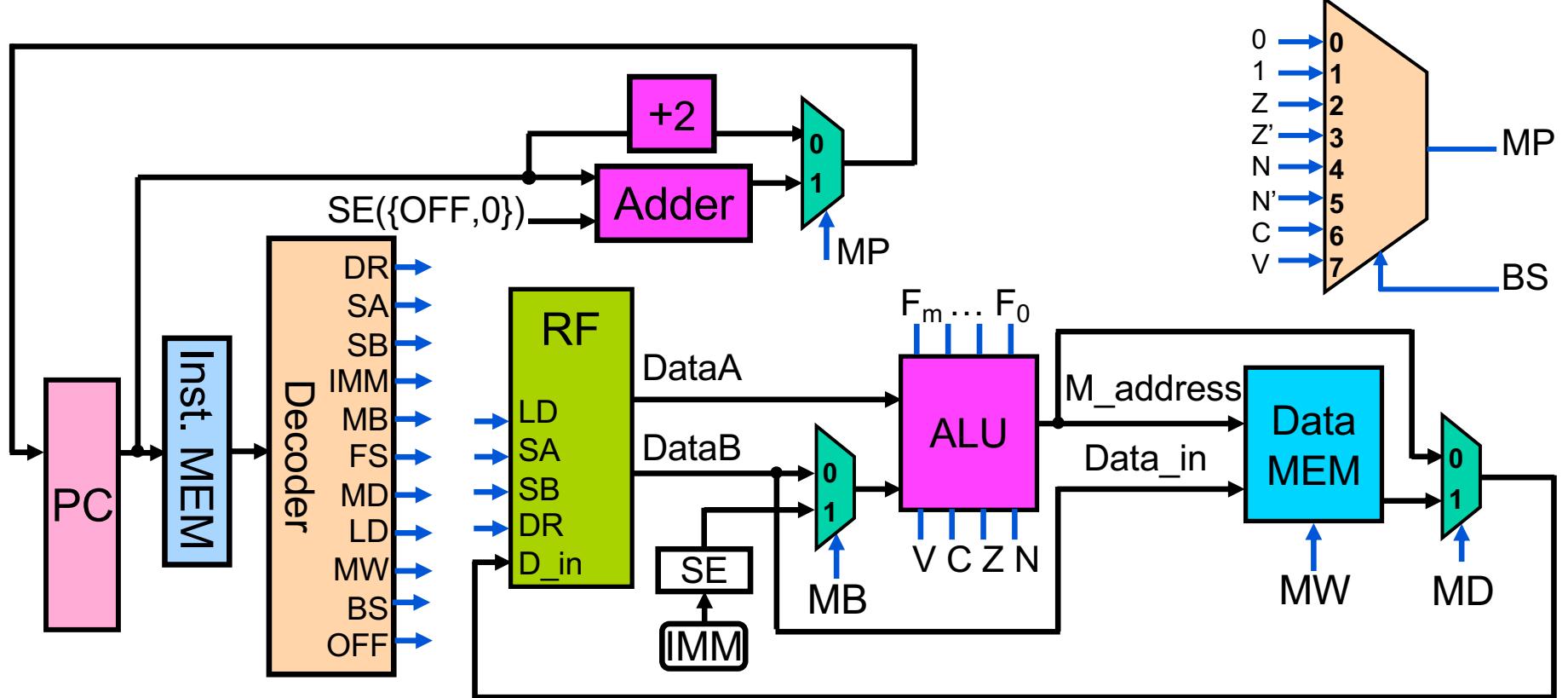

- **Instruction RAM holds the program to be run**
  - In 2300, each instruction is 2 bytes (16 bits)
- **Decoder derives control word from the instruction**


# Steps in Instruction Execution

- **Instruction Fetch (IF)**
  - Fetch instruction; Update PC
- **Instruction Decode (ID)**
  - Decode instruction; Read register file
- **Execute (EX)**
  - Perform ALU operation
- **Memory (MEM)**
  - Perform memory operation
- **Write Back (WB)**
  - Put result into register file
- **Clock period is limited by the longest path**
  - Suppose each step takes 1ns, clock period is 5ns

# Pipelining Intuition
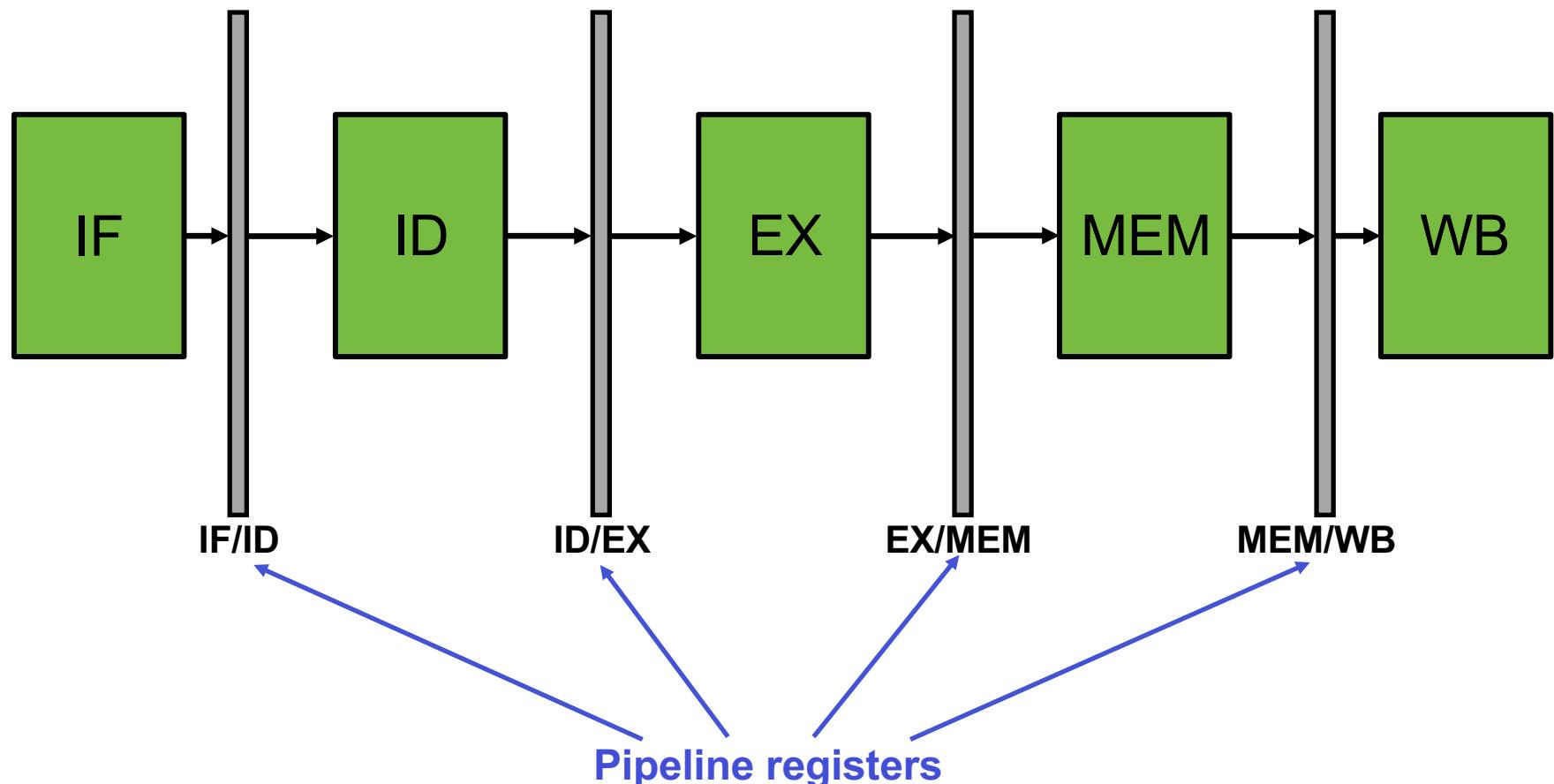
# Pipelining: Basic Idea


- Overlap instruction execution by performing each step in successive clock cycles




(hold intermediate data and control signals  
between pipeline stages)

# Pipelining: Overlapped Instructions

- **Single-cycle execution**

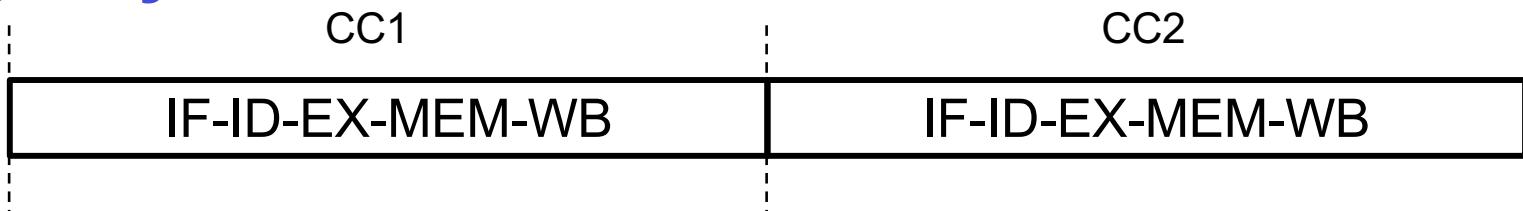


- **Pipelined execution**

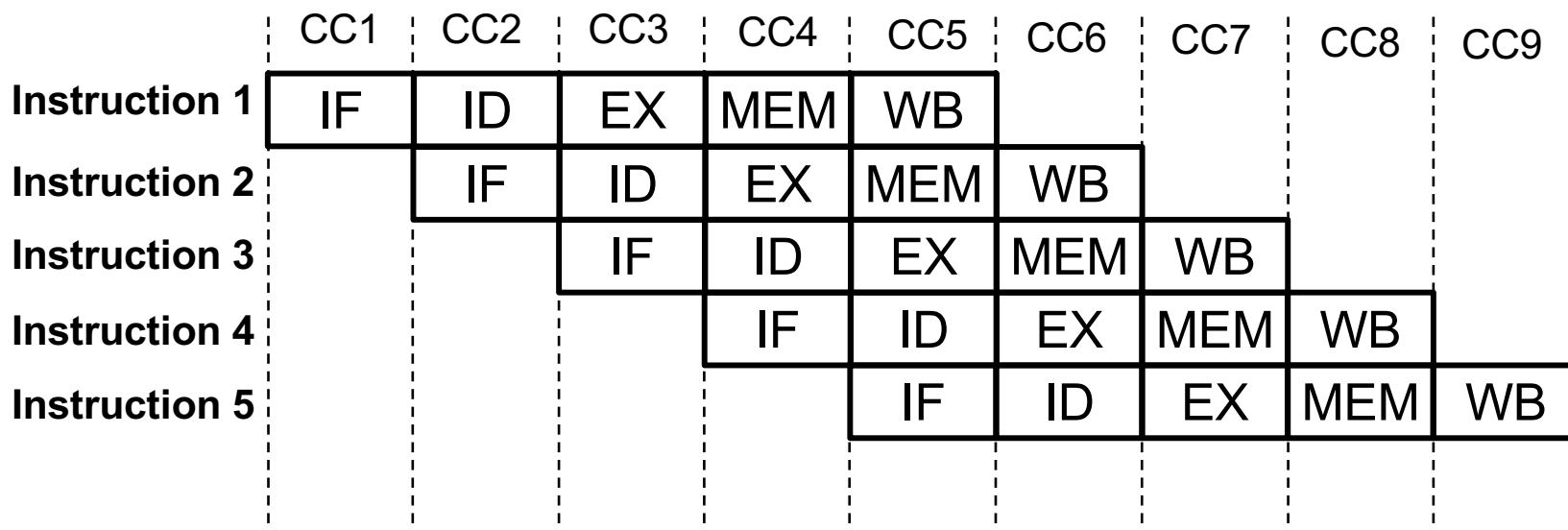
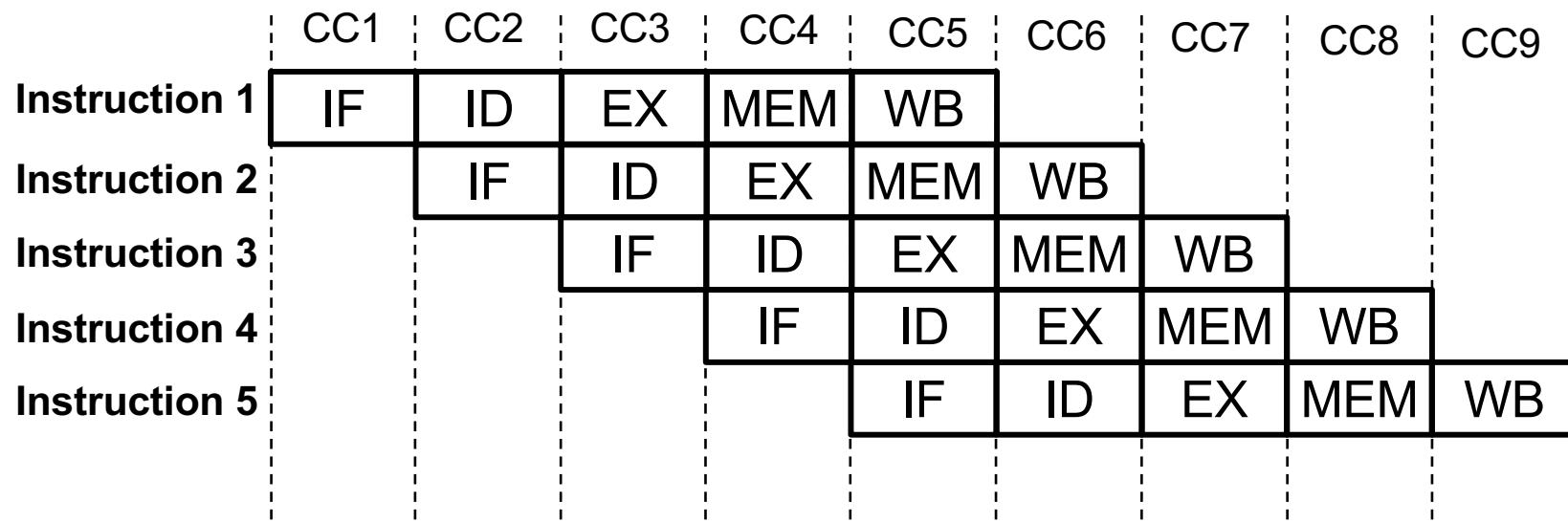
# Exercise: Pipelining Performance

In an ideal 5-stage pipeline, how many cycles are needed to complete the execution of 100 instructions?




# Pipelining: Performance


- Faster clock frequency than single cycle processor
- Each instruction takes 5 cycles
- Average number of cycles per instruction (CPI)

$$\frac{\text{Number of cycles for } N \text{ instructions}}{N} = \frac{N + 4}{N} \approx 1$$

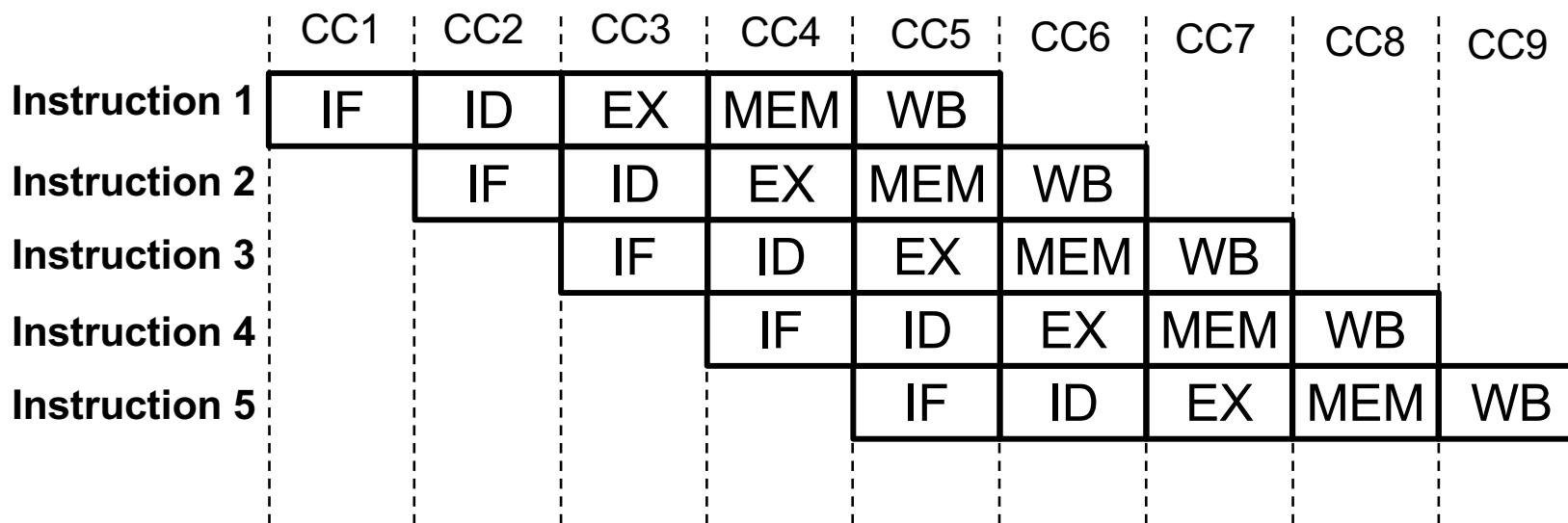- ~1 instruction completed every cycle (ideally)




# Instruction Fetch Stage (IF)

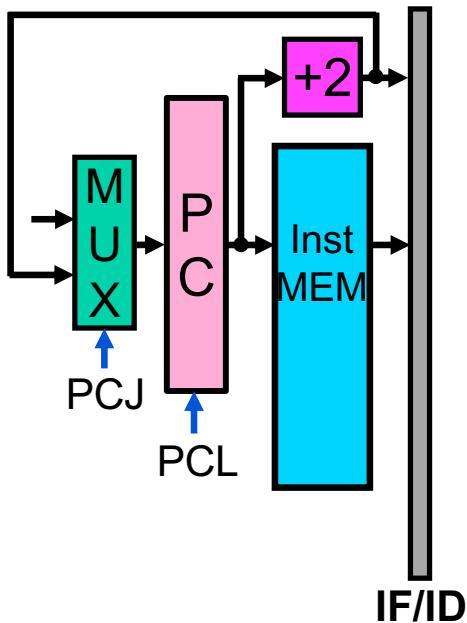


- **Fetch the instruction into IF/ID (based on current PC)**
- **Place PC+2 into IF/ID**
- **Update PC (PCL means PC write enable)**

# Instruction Decode Stage (ID)

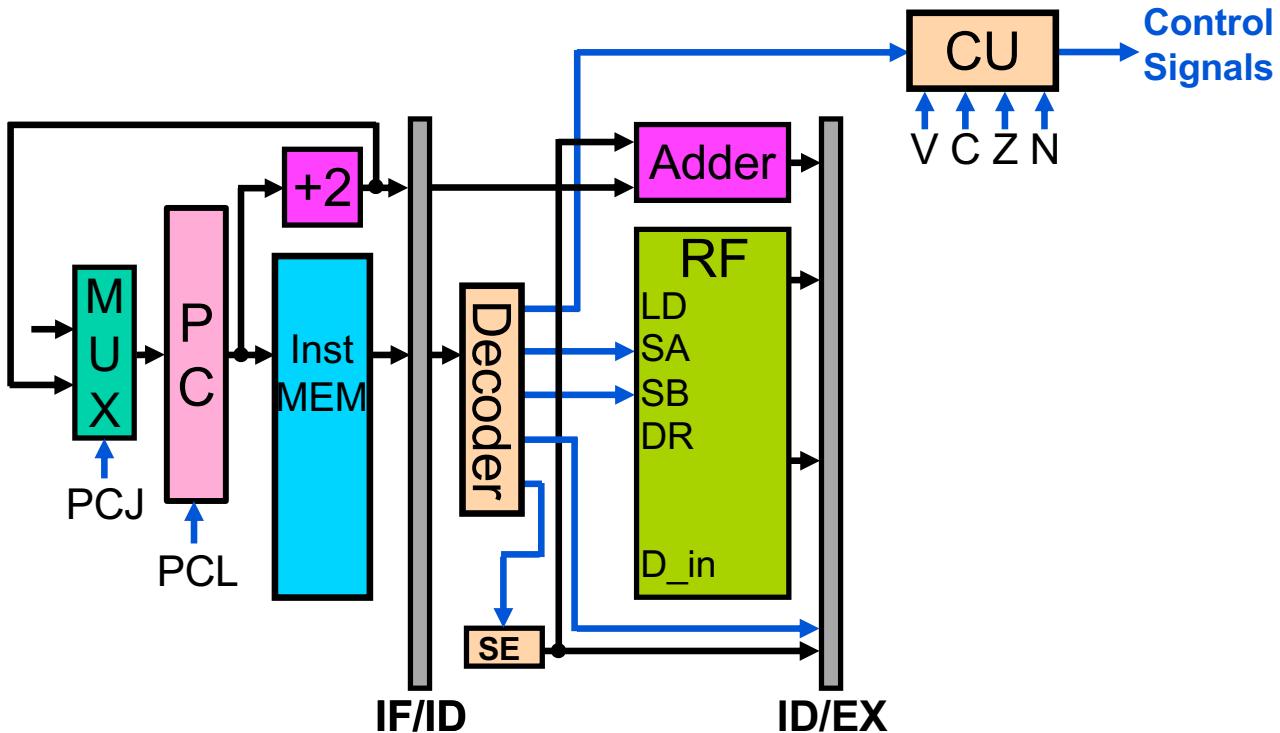


- **Read source operands from RF into ID/EX**
- **Place SE(IMM) into ID/EX**
- **Place SE(IMM)+(PC+2) into ID/EX**
- **Place DR & LD into ID/EX**

# Execute Stage (EX)

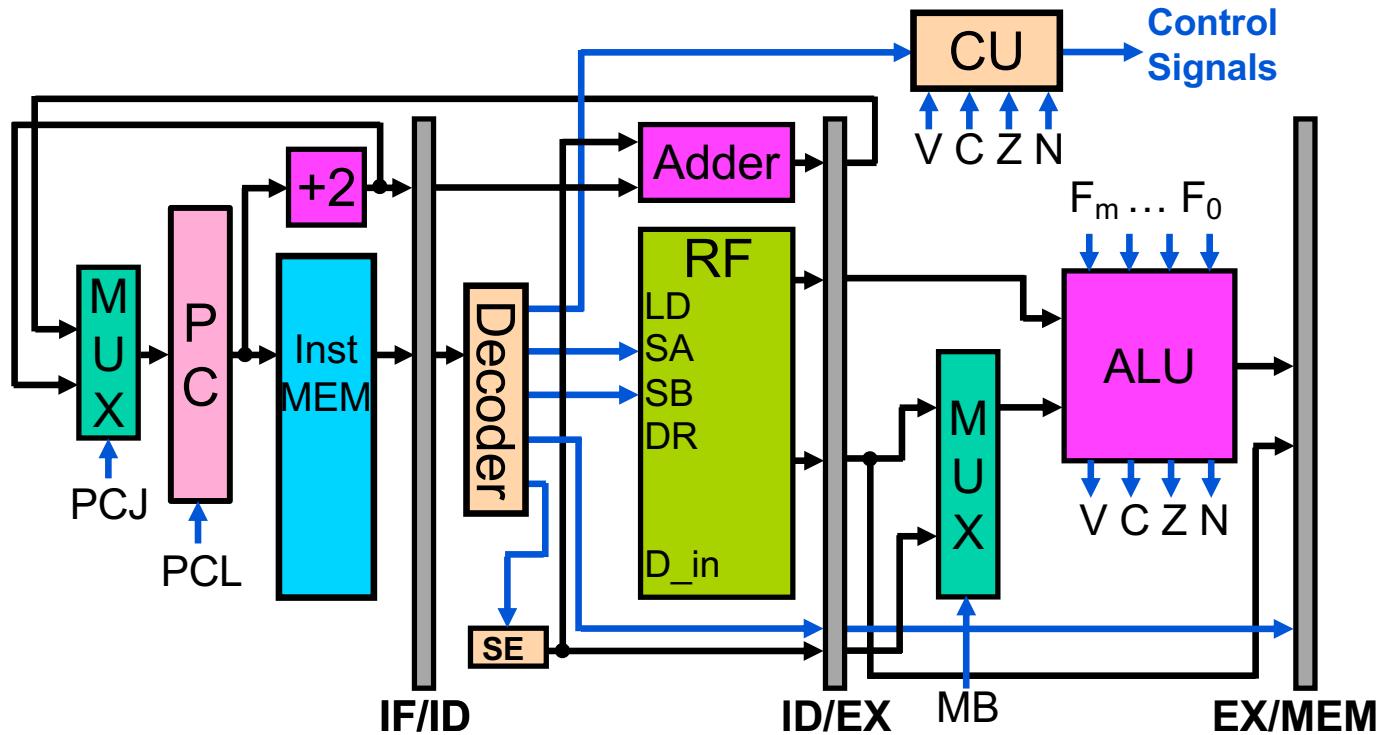


- Perform **ALU operation and place result into EX/MEM**
- Pass DataB from the RF to EX/MEM
- Pass DR & LD to EX/MEM
- If taken branch, update PC (**Is it too late?**)

# Memory Stage (MEM)

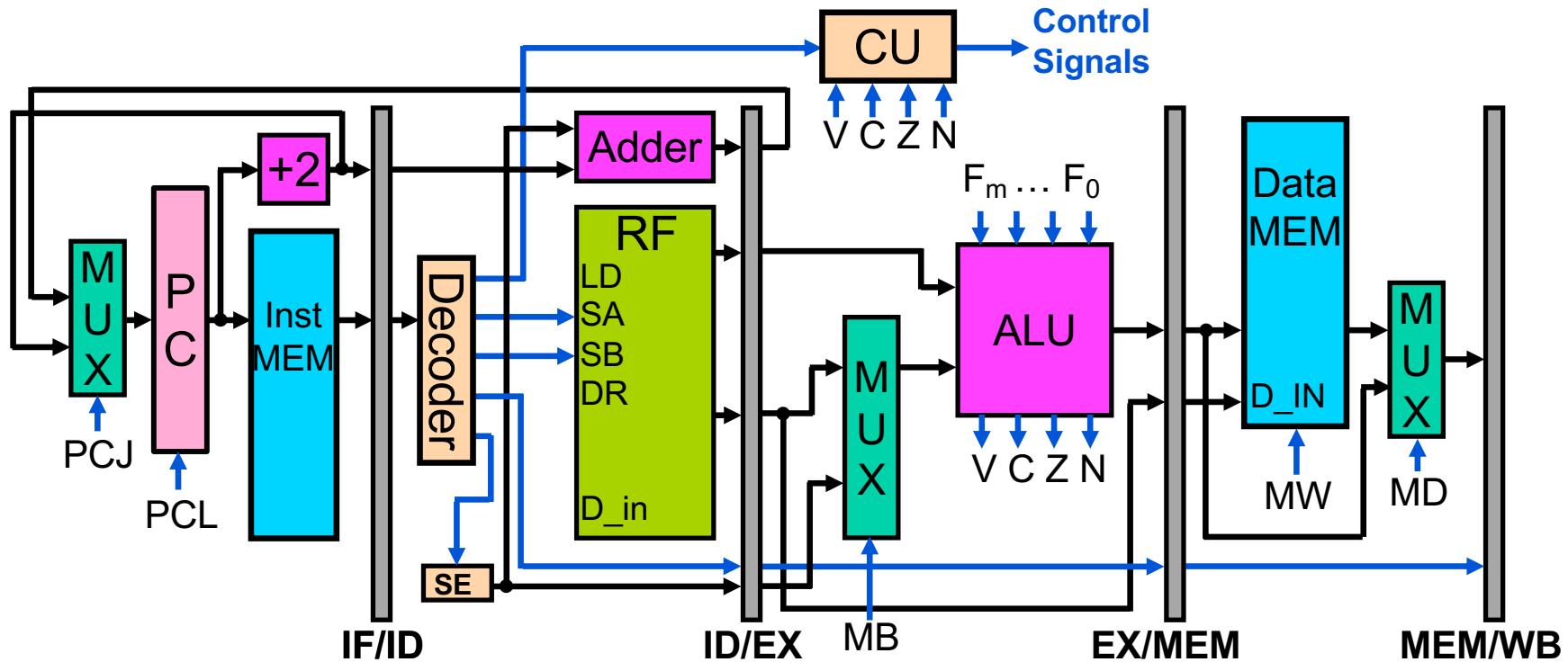


- Store: Write DataB into RAM
- Load: Read data from RAM into MEM/WB
- ALU operation: pass ALU result from EX/MEM to MEM/WB
- Pass DR & LD to MEM/WB

# Writeback Stage (WB)

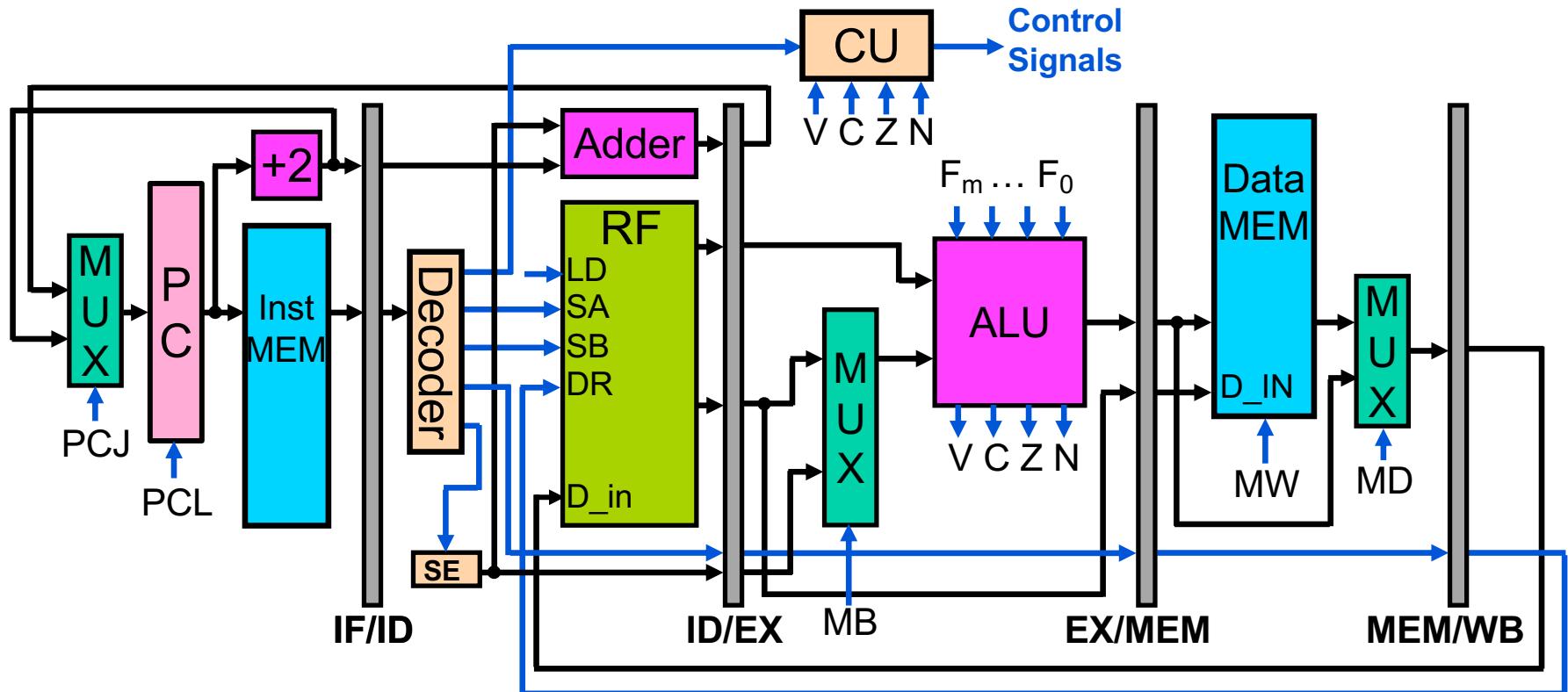


- Load or ALU operation: Write to register file if (LD=1)

# Pipelined Microprocessor

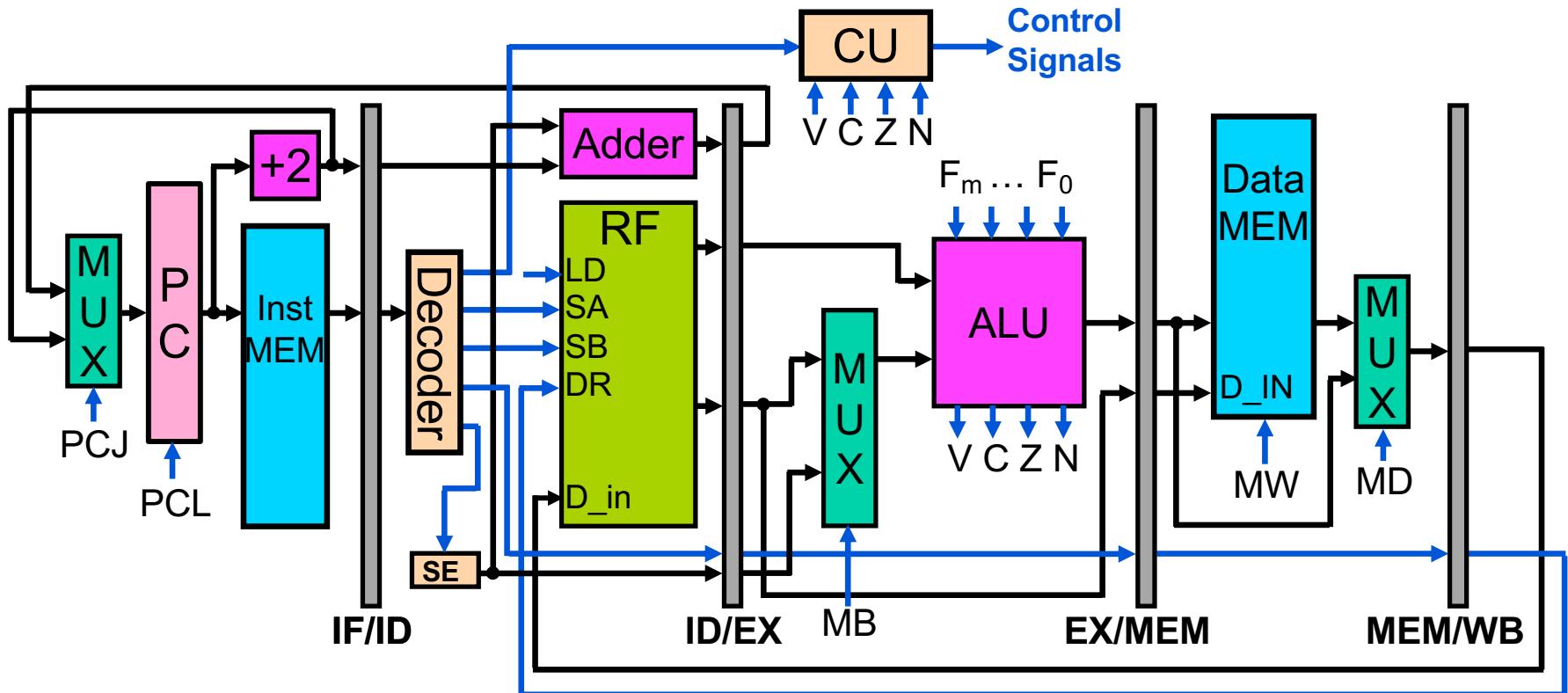


- Faster clock frequency than single cycle processor
- In the ideal case, ~1 instruction completed every cycle, where all pipeline stages are busy all the time

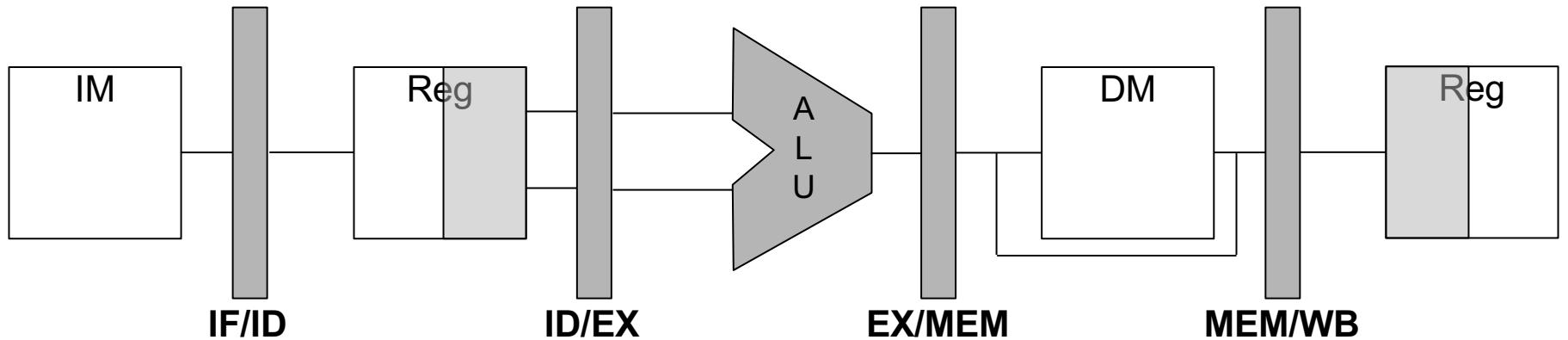
# Abstract Representation of Pipelined Processor



# Example Instruction Sequence

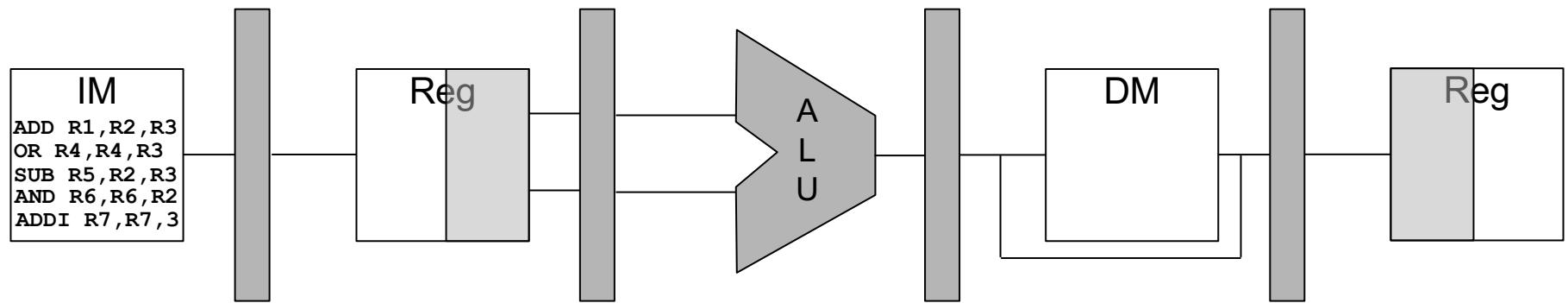


# Example Instruction Sequence

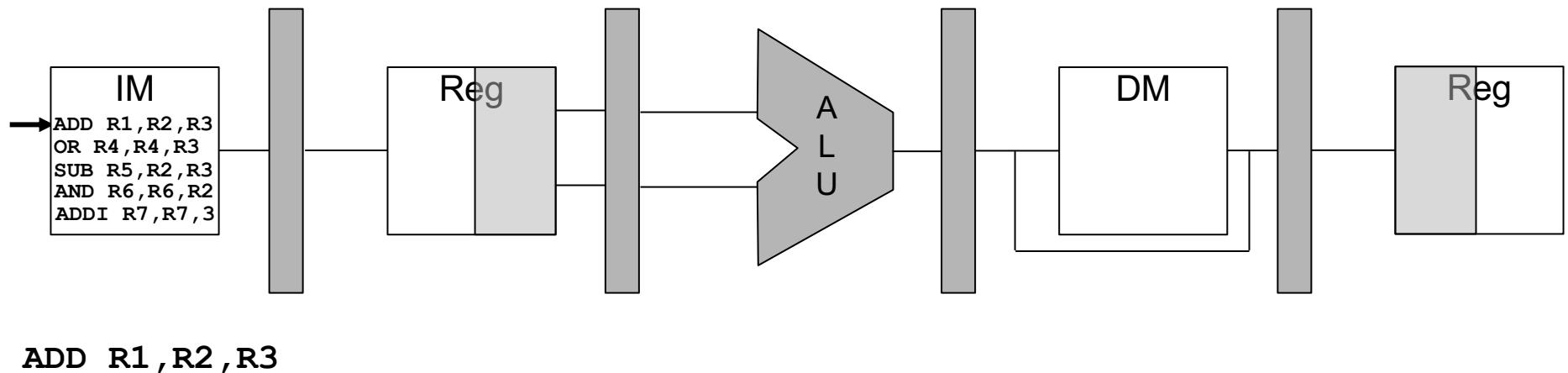


**ADD R1 ,R2 ,R3**

# Example Instruction Sequence

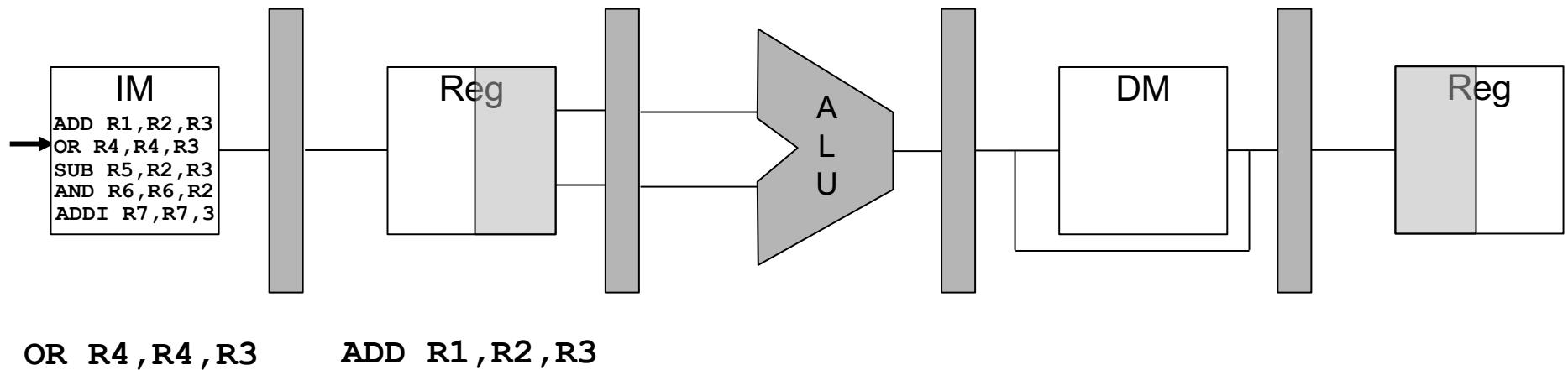

# Example Instruction Sequence

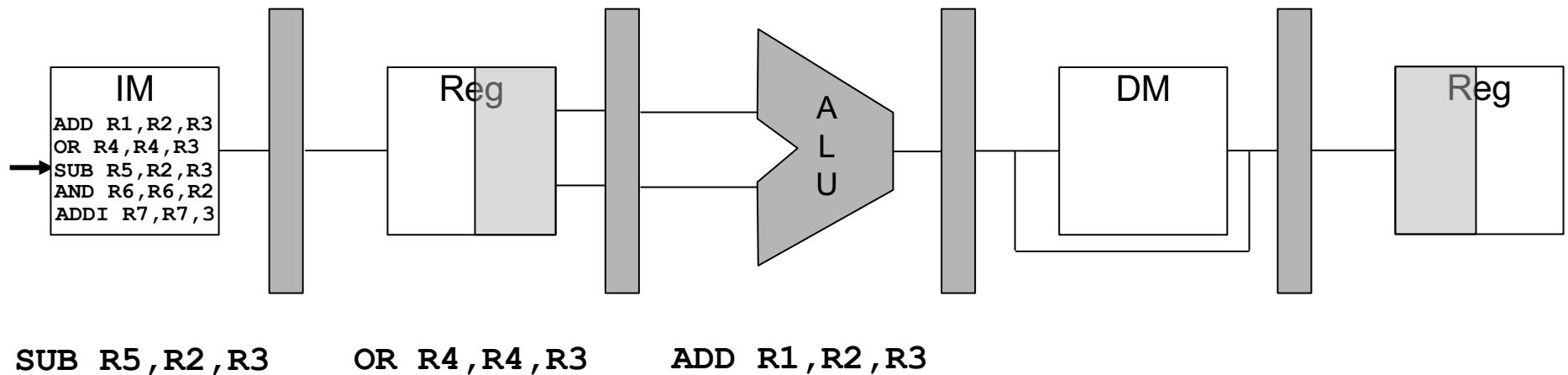


SUB R5 ,R2 ,R3


OR R4 ,R4 ,R3

ADD R1 ,R2 ,R3


# Example Instruction Sequence

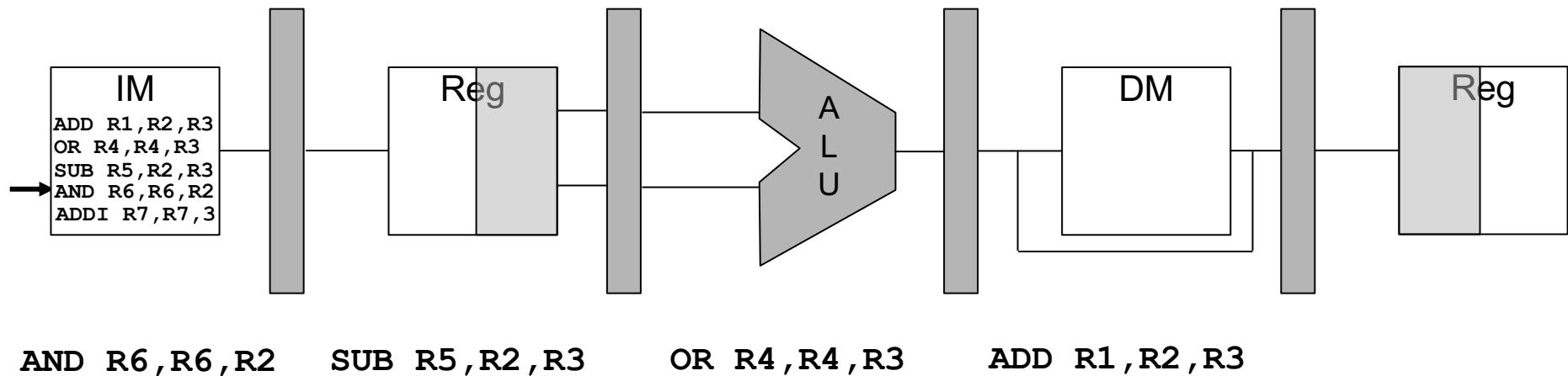


# Example Instruction Sequence

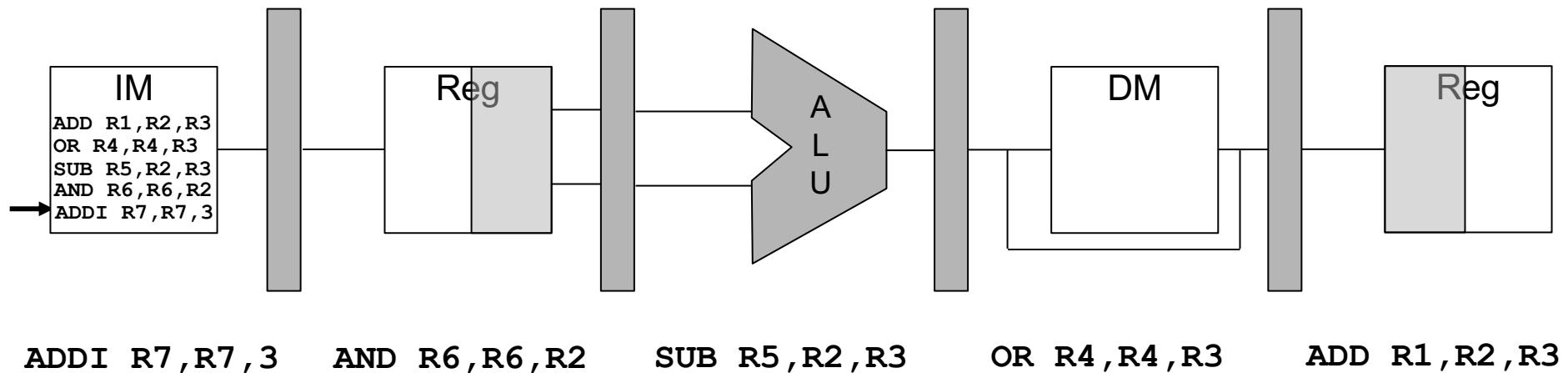


# Example Instruction Sequence

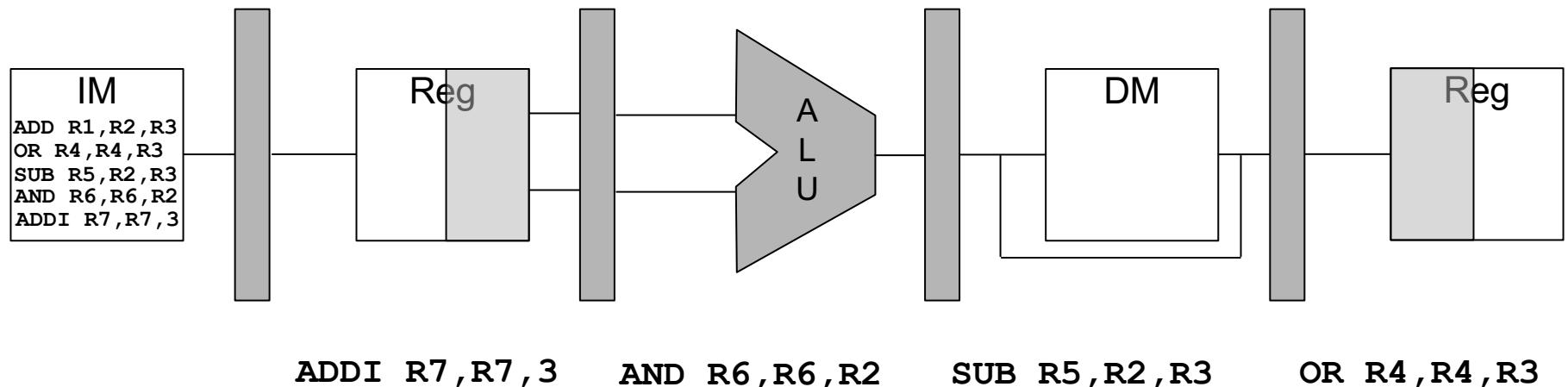


# Example Instruction Sequence

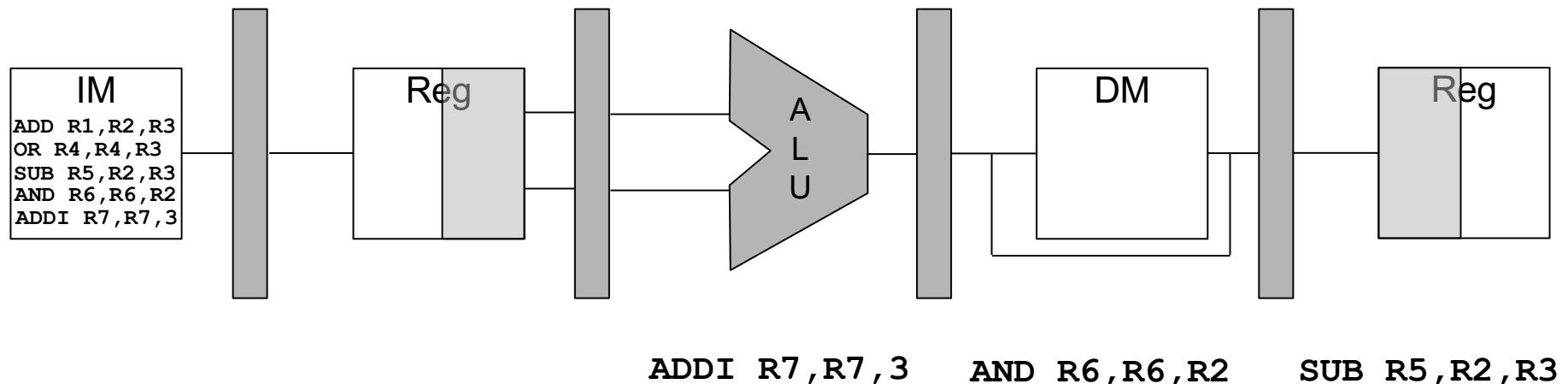

# Example Instruction Sequence

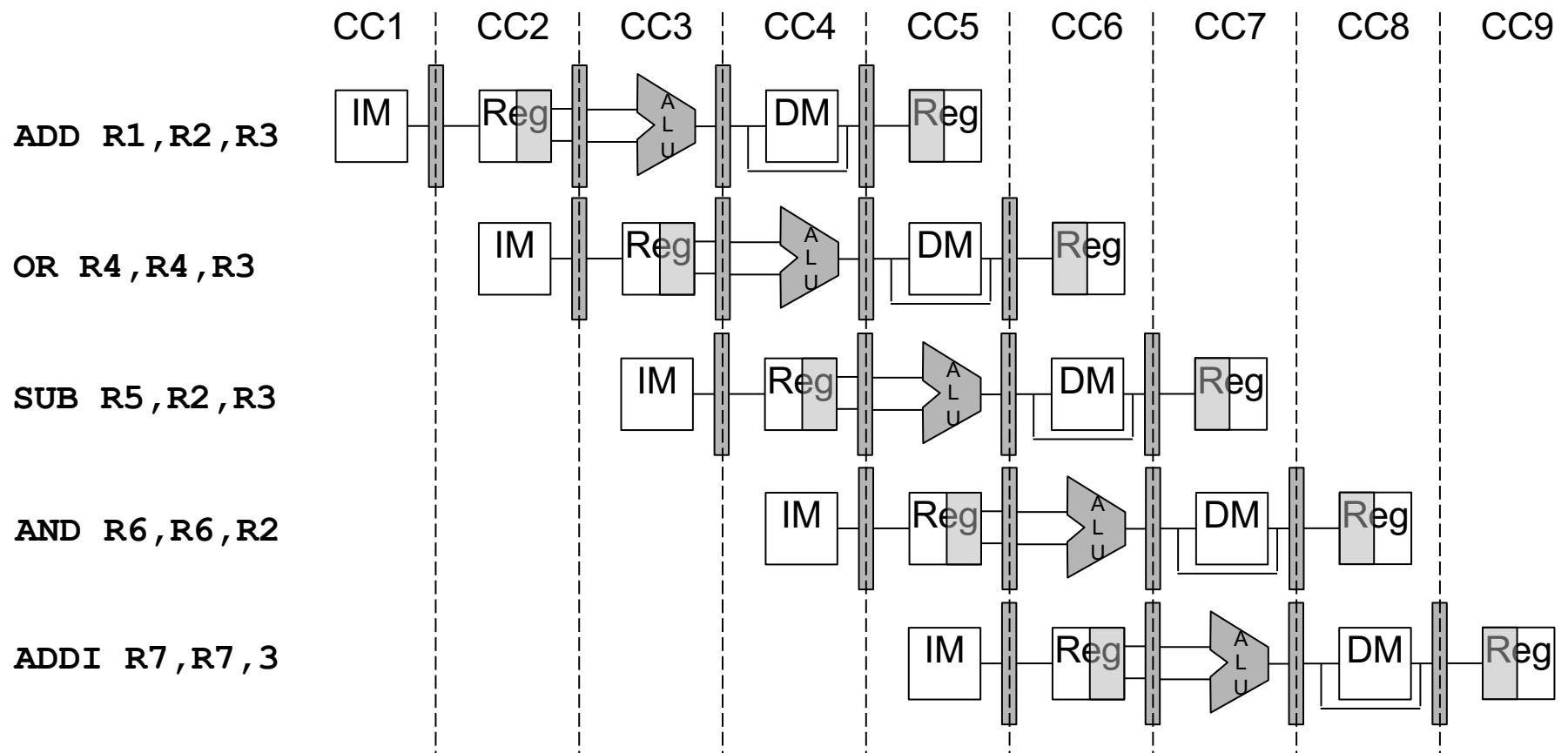

# What About This Sequence?

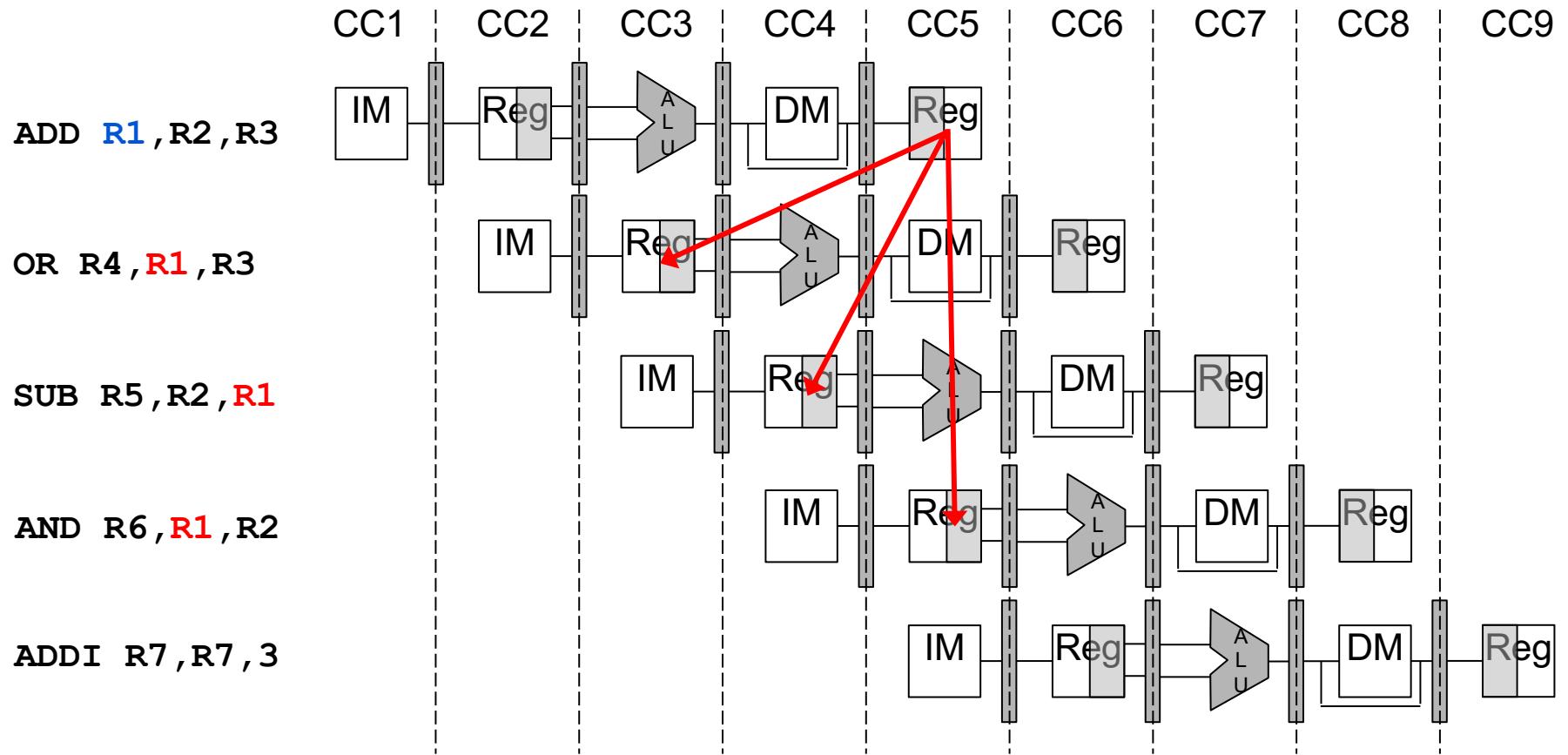

**The OR, SUB, and AND instructions are  
data dependent on the ADD instruction**

# Next Class

**More Pipelined Microprocessor  
(H&H 7.5.3-7.5.4)**