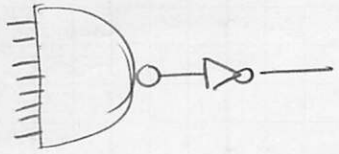


Result AND gate

$$\log_4(40) = 2.66$$



$$G = \frac{10}{3} \times 1$$

$$F = G \cdot H \cdot B = \frac{10}{3} \cdot 12 = 40$$


$$H = 12$$

$$F^{\frac{1}{2}} = 6.325$$

$$B = 1$$

$$\hat{D} = 2 \times 6.325 + 9 = 21.65$$


$$P = 8 + 1$$

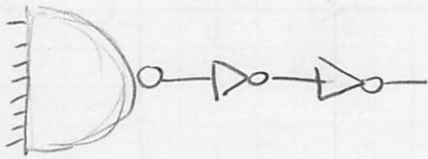

$$F = 40 \quad P = 10$$

$$F^{\frac{1}{3}} = 3.42$$

$$\hat{D} = 3 \times 3.42 + 10 = 20.26$$

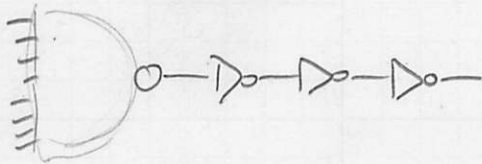

$$F = 40 \quad P = 11$$

$$F^{\frac{1}{4}} = 2.51$$

$$\hat{D} = 4 \times 2.51 + 11 = 21.06$$

Problem 1

$$A) \quad G = 1 \times 2 \times 1 = 2$$

$$H = (32 \times 3) / 10 = 9.6$$


$$B = 8$$

$$F = G \cdot H \cdot B = 2 \times 9.6 \times 8 = 153.6$$

$$f = \sqrt[3]{153.6} = 5.36$$

$$\hat{D} = 3 \times 5.36 + (1 + 4 + 1)$$

$$= 16.08 + 6 = 22.08$$

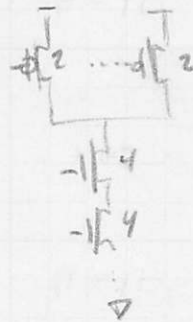

$$g = \frac{6}{3} = 2$$

$$p = \frac{2 \times 4 + 4}{3} = 4$$

B)

$$C_{w,1} = \frac{9}{f} C_{out}$$

$$C_{w,2} = \frac{1}{5.36} (32 \times 3) = 17.91$$

$$C_{w,T} = \frac{2}{5.36} (17.91) = 6.68$$

$$C_{w,x} = \frac{1}{5.36} (6.68 \times 8) = 9.97$$

↑ BRANCHING EFFORT

$$C) \log_4 (153.6) = \frac{\log_{10}(153.6)}{\log_{10}(4)} = \frac{2.186}{0.602} = \underline{\underline{3.6}}$$

D) 8 INPUT INVERTERS

$$C_g = 8 \times 10 = 80C$$

$$C_d = 8 \times 10 = 80C$$

$$C_{TOT} = 160C$$

16 OUTPUT INVERTERS

$$C_g = 16 \times 17.9 = 286C$$

$$C_d = 16 \times 17.9 = 286C$$

$$C_{TOT} = 572C$$


16 NAND GATES 4 INPUTS

$$C_g = 4 \times 16 \times 6.68 = 427C$$

$$C_d = 16 \times (4 \times 2.23 + 4.45) = 214C$$

$$C_{TOT} = 640C$$

$$C_{SW} = 160 + 572 + 640 + (16 \times 96) = \underline{\underline{2,908C}}$$

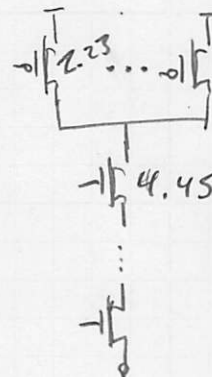

Problem 2

$$A) \quad G = 1 \times 1 \times 2 \times 1$$

$$H = (32 \times 3) / 10 = 9.6$$

$$B = 8$$

$$F = GHB = 153.6$$

$$\hat{f} = \sqrt[4]{153.6} = 3.52$$

$$\hat{D} = 4 \times 3.52 + (1 + 1 + 4 + 1)$$

$$= 14.08 + 7 = 21.08$$

} SAME AS BEFORE

$$\frac{21.08}{22.08} = 0.954 \quad \text{so } 4.59\% \text{ faster}$$

$$B) \quad C_{H,7} = \frac{1}{3.52} (32 \times 3) = 27.2$$

$$C_{H,7} = \frac{2}{3.52} (27.2) = 15.5$$

$$C_{W,8} = \frac{1}{3.52} (8 \times 15.5) = 35.23$$

$$C_{W,8} = \frac{1}{3.52} (35.23) = 10$$


NOTE: VERY DIFFERENT SIZING FOR GATES

AND OVERALL  $C_{SW}$  IS MUCH HIGHER

SINCE PERFORMANCE BENEFIT IS MUCH AND AREA/ENERGY IS SO MUCH HIGHER, PROBABLY BETTER OFF USING THE THREE STAGE DESIGN

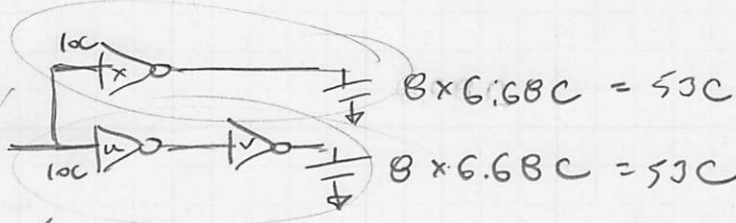Problem 3

Focus on just the fork, optimally size each path



$$G = 1$$

$$H = \frac{50C}{100C} = 5.3C$$

$$B = 1$$

$$F = GH B = 5.3$$

$$f = \sqrt{5.3} = 2.3$$

$$D = 2 \times 2.3 + 2 = 6.6 \tau$$

$$C_{in} = \frac{q}{f} C_{out} = \frac{1}{2.3} 53 = 23C$$

$$d = gh + p$$

$$d = 1 \cdot \frac{53C}{100C} + 1 = 6.3 \tau$$

2 inverter branch is a bit slower

Overall Delay through 2 inverter branch is

$$d_u = 1 \cdot \frac{23}{10} + 1 = 2.3 + 1 = 3.3$$

$$d_v = 1 \cdot \frac{53}{23} + 1 = 2.3 + 1 = 3.3$$

$$d_y = 2 \cdot \frac{17.91}{6.68} + 4 = 5.36 + 4 = 9.36$$

$$d_z = 1 \cdot \frac{96}{17.91} + 1 = 5.36 + 1 = 6.36$$

22.32

22.32 is pretty close to 22.08