

# **ECE 6745 Complex Digital ASIC Design**


## **Topic 4: Full-Custom Design Methodology**

Christopher Batten

School of Electrical and Computer Engineering  
Cornell University

<http://www.csl.cornell.edu/courses/ece6745>

# Part 1: ASIC Design Overview

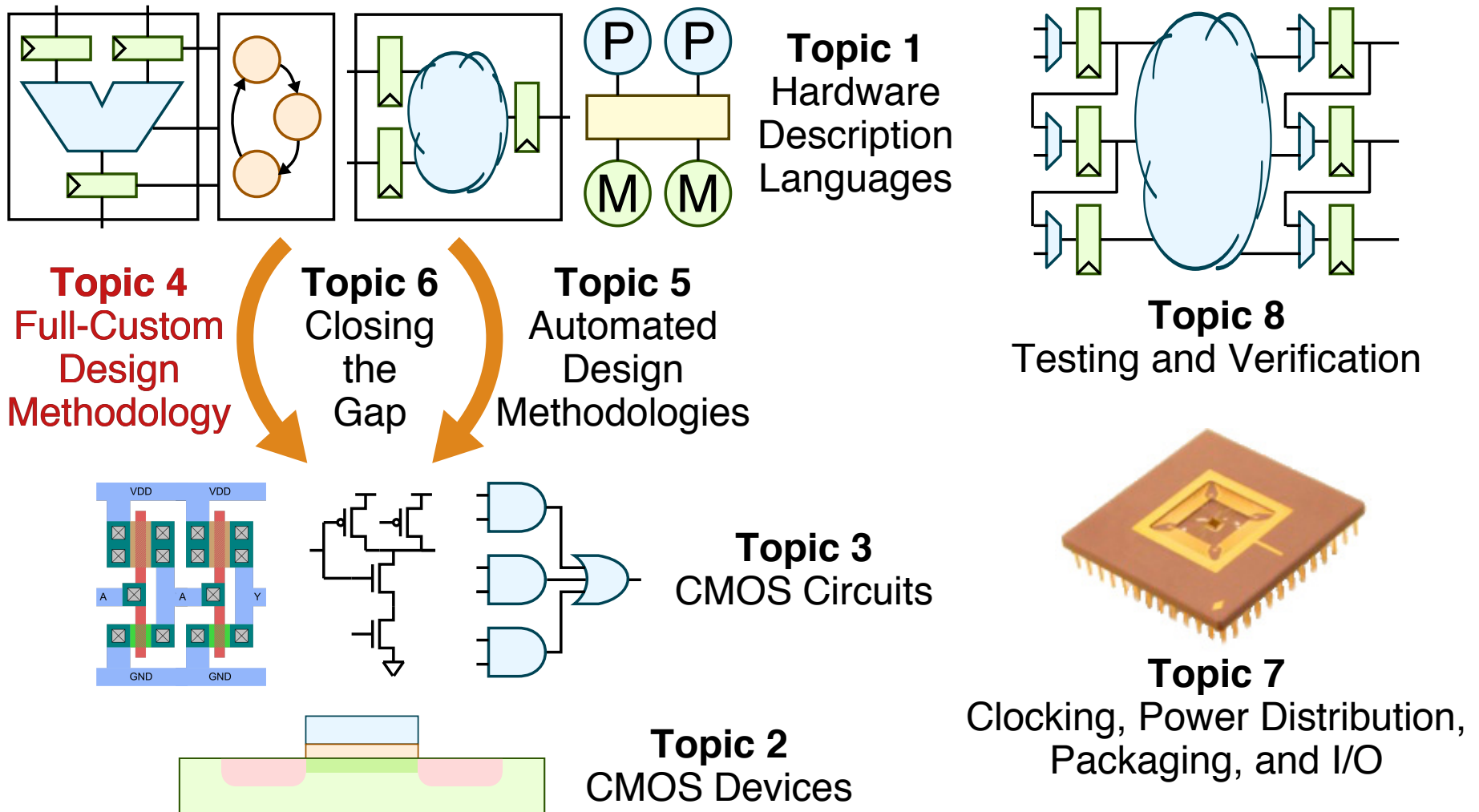

# Agenda

---

## Design Domains, Abstractions, and Principles

Modularity

Hierarchy


Encapsulation

Regularity

Extensibility

## Full-Custom Design

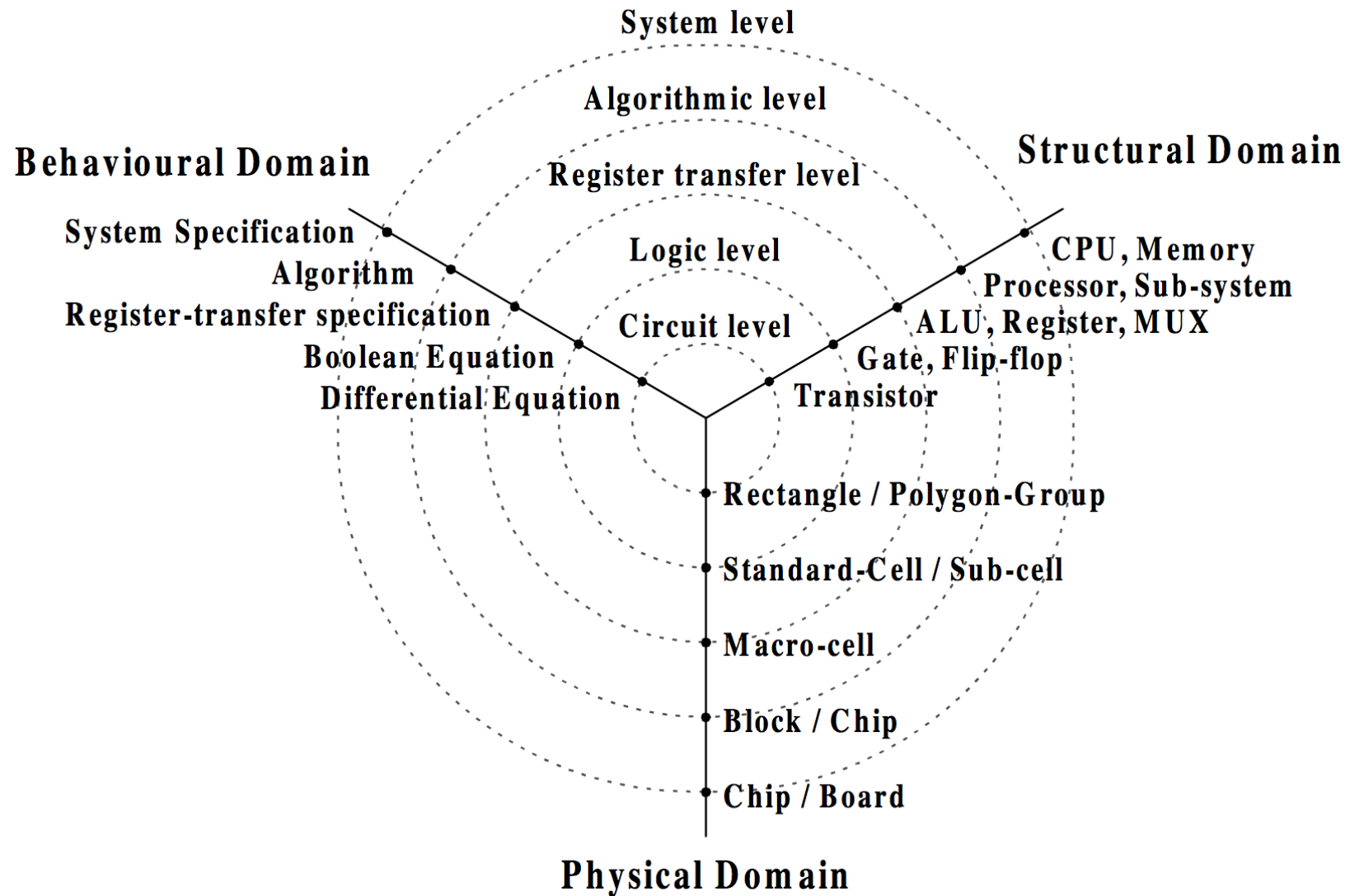
# Behavioral, Structural, and Physical Abstractions



Adapted from [Ellervee'04]



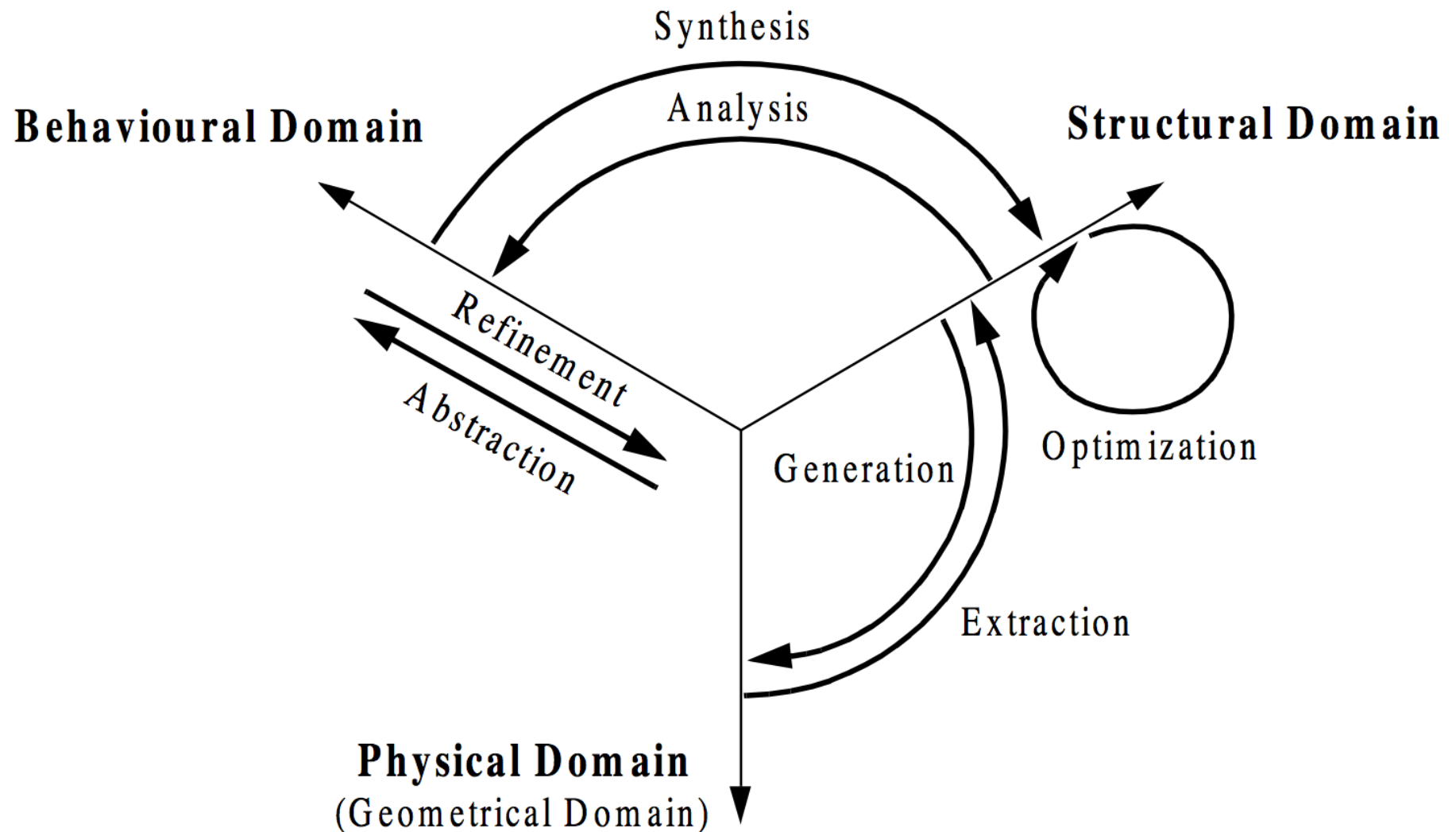
# Behavioral, Structural, and Physical Abstractions



Adapted from [Ellervee'04]
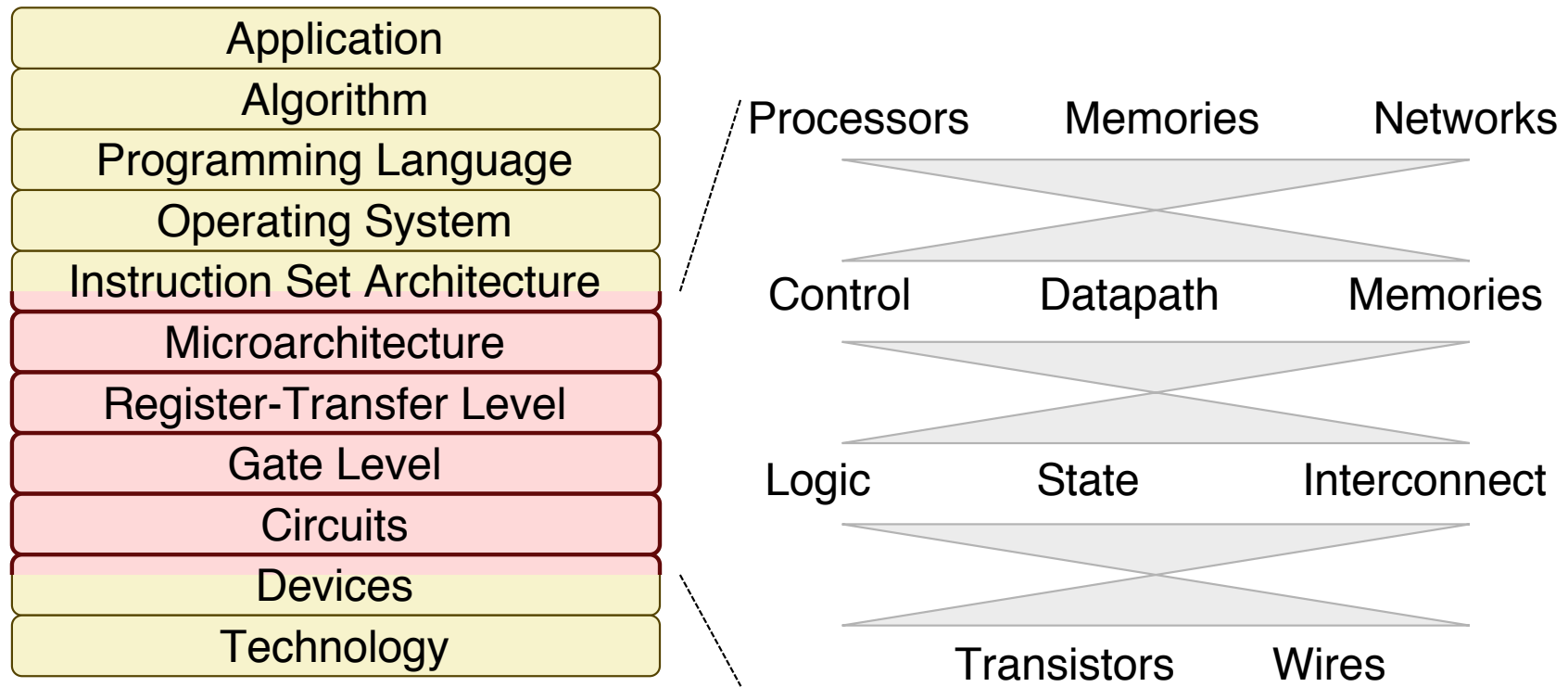
# Computer Engineering Stack Abstractions





# Design Principles in VLSI Design

---

- ▶ **Modularity** – Decompose into components with well-defined interfaces
- ▶ **Hierarchy** – Recursively apply modularity principle
- ▶ **Encapsulation** – Hide implementation details from interfaces
- ▶ **Regularity** – Leverage structure at various levels of abstraction
- ▶ **Extensibility** – Include mechanisms/hooks to simplify future changes

# Design Principle: Modularity

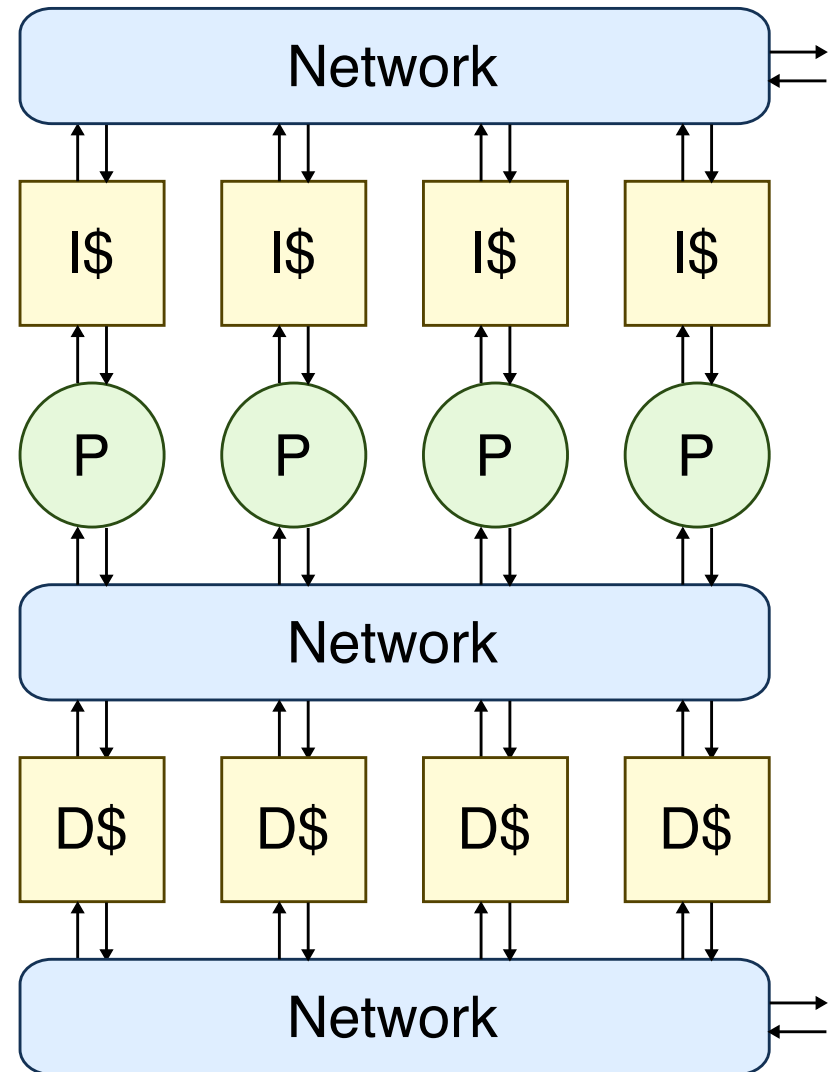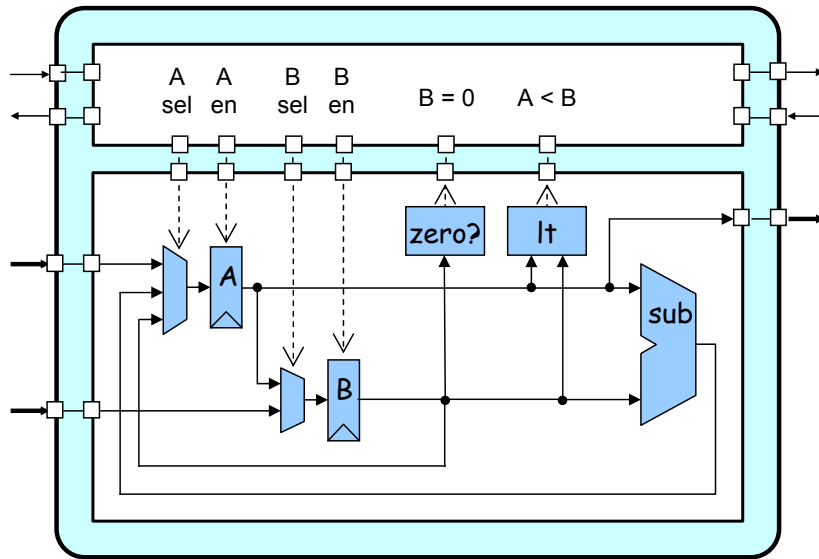


- ▶ Separate design into components w/ well-defined interfaces
- ▶ Reason, design, and test components in isolation
- ▶ Interface may or may not encapsulate implementation

# Design Principle: Modularity


Modularity can also impact electrical and physical characteristics

## Electrical Modularity

 

What happens if we cascade many of these transmission gate multiplexers?



## Physical Modularity

 

pwr/gnd rails & wells in fixed locations so they connect via abutment



Adapted from [Weste'11]

# Design Principle: Hierarchy

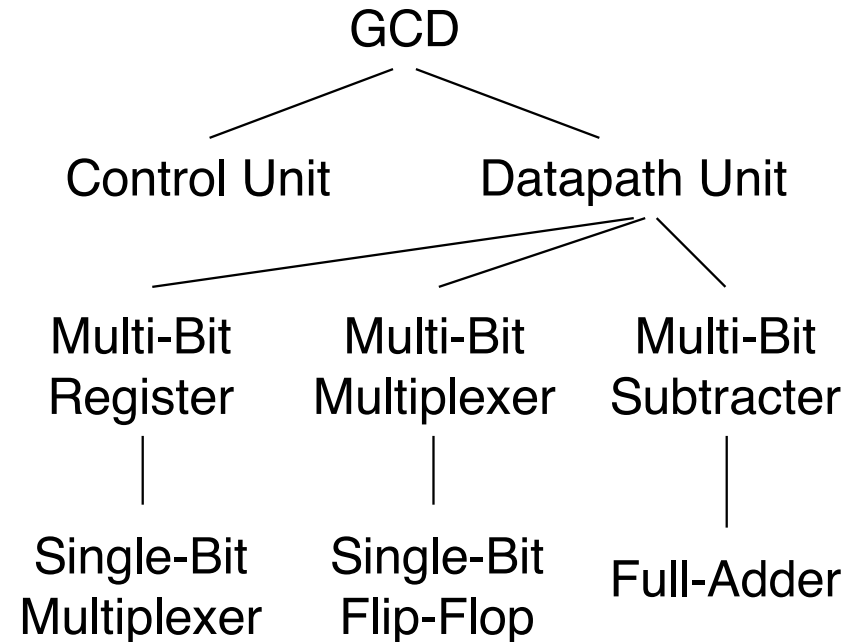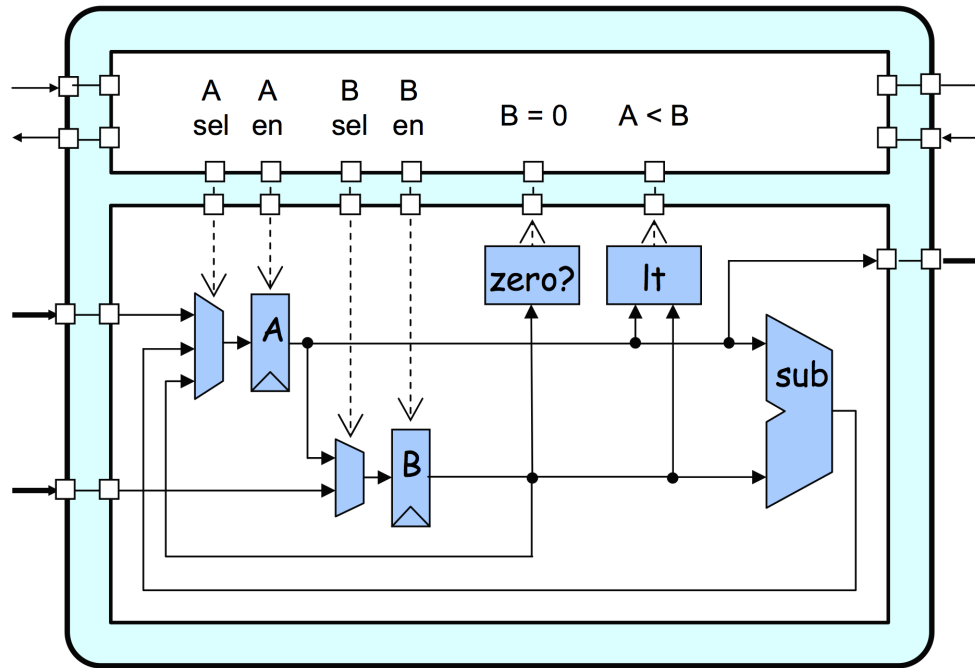

Recursively apply modularity principle until complexity of submodules is manageable

# Design Principle: Hierarchy

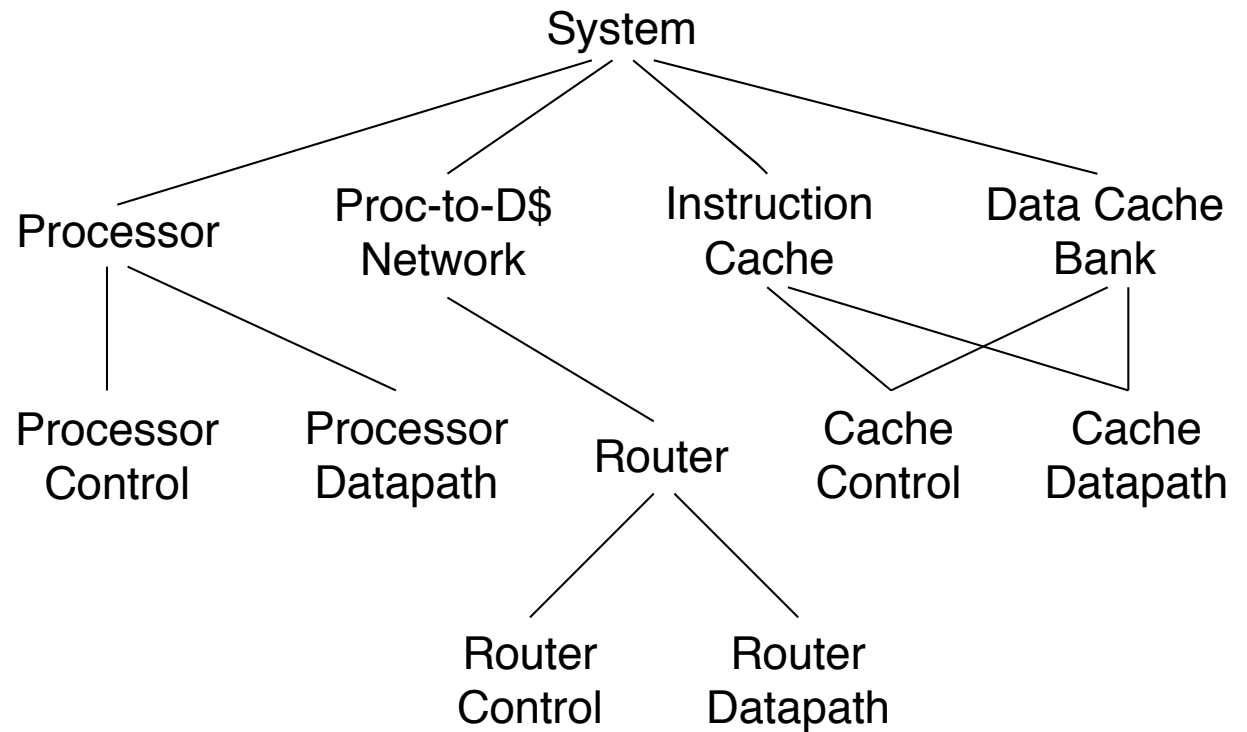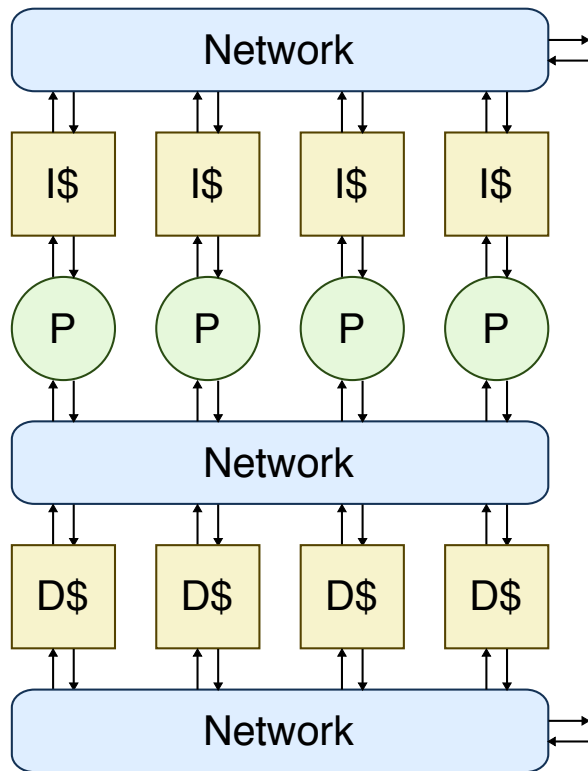


# Design Principle: Encapsulation

---

- ▶ Modularity requires well-defined interfaces, but these interfaces might still expose significant implementation details (e.g., interface in control/datapath split reveals many details of the implementation)
- ▶ Choose interfaces that hide implementation details where possible to enable more robust composition
- ▶ Lab 1 multipliers all use a latency-insensitive val/rdy message interface to hide timing details, any one of these can be swapped into a processor and should work without modification
  - ▷ Fixed-latency iterative multiplier
  - ▷ Variable-latency iterative multiplier
  - ▷ Pipelined multiplier




# Design Principle: Regularity

 


- ▶ Modularity, hierarchy, and encapsulation can still lead to many different kinds of modules which can increase design complexity
- ▶ Choose a hierarchical decomposition to leverage structure and thus facilitate reuse and reduce complexity
- ▶ Both structural and physical regularity can be exploited

# Design Principle: Regularity

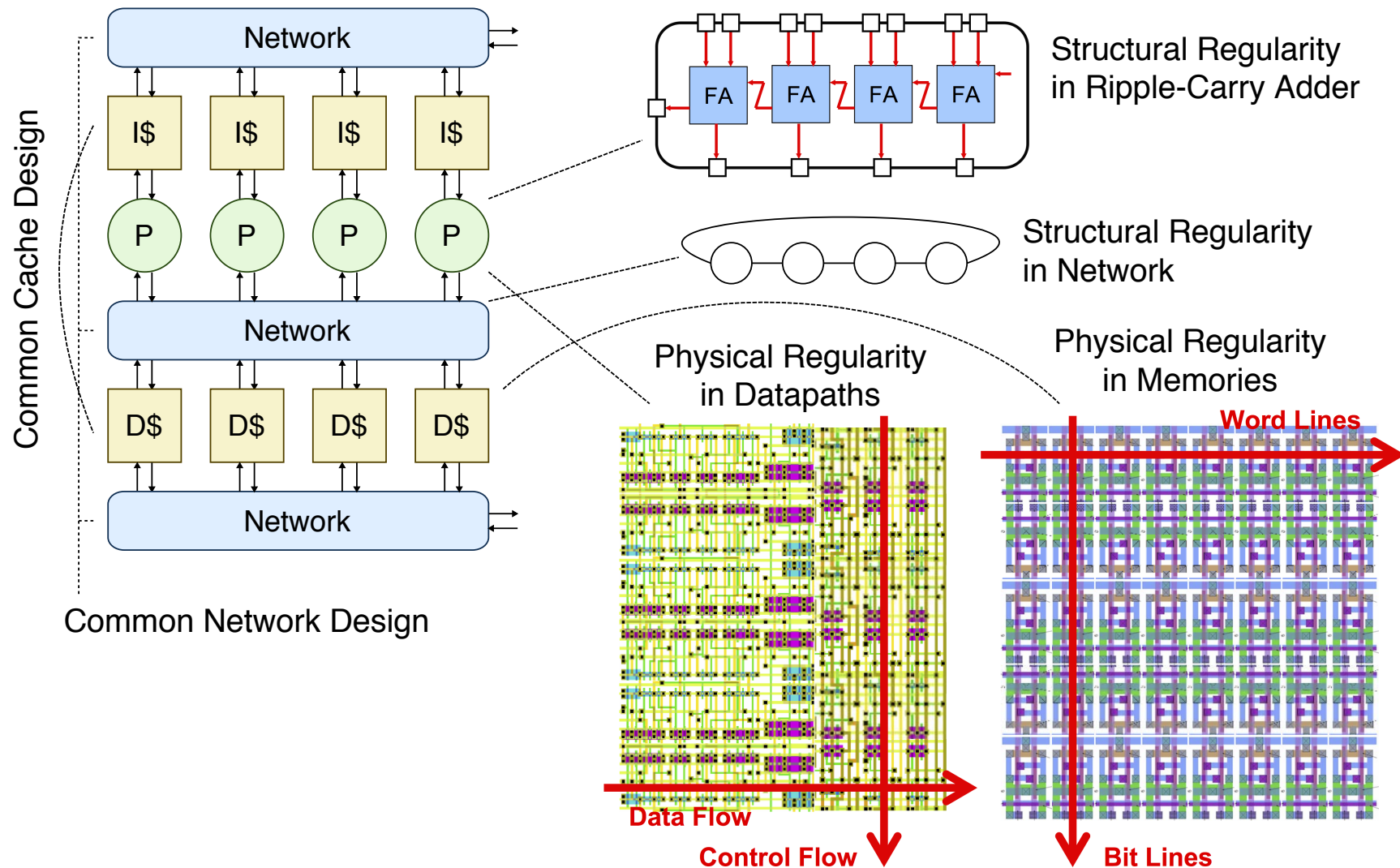


## Design Principle: Extensibility

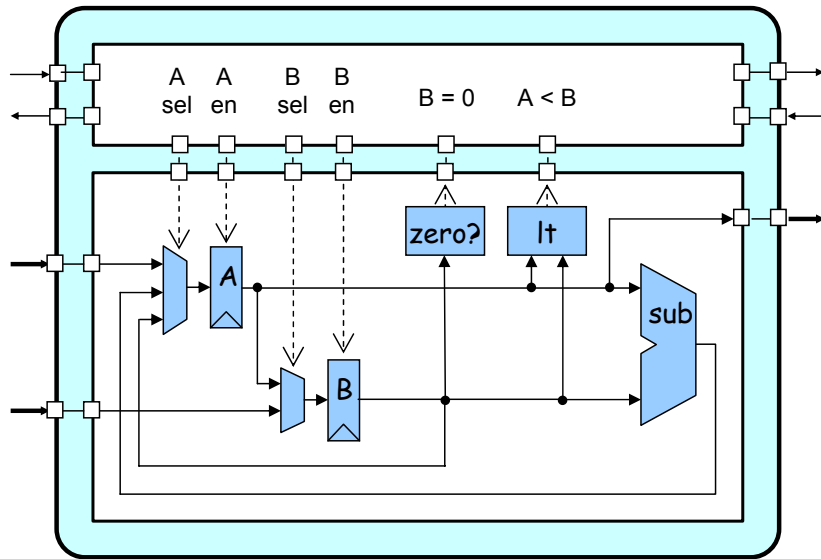

Simple form of polymorphism  
enables varying bitwidth of  
operands
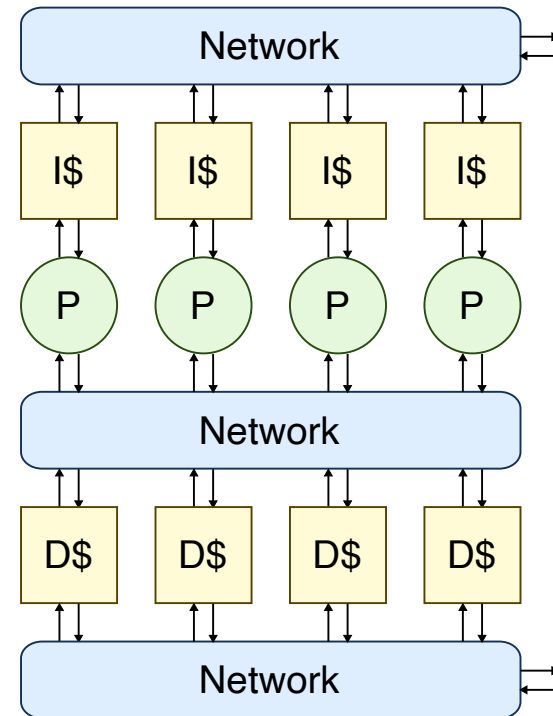
## Difficult with full-custom design methodology!



Parameterization of network and caches enables reuse; static elaboration could enable varying the number of cores and the types of components

# Agenda

---

Design Domains, Abstractions, and Principles

Full-Custom Design


Cells

Datapaths


Memories

Control

# Full Custom Design

 


Intel 4004

 

Key is that all circuits and transistors are optimized for specific context

 
# Overview of Full Custom Design Methodology



Adapted from [Weste'11]
 
# Custom Cells: Lambda-Based Design Rules



One lambda = one half of the “minimum” mask dimension, typically the length of a transistor channel. Usually all edges must be “on grid”, e.g., in the MOSIS scalable rules, all edges must be on a lambda grid.



Adapted from [Terman'02]



# Custom Cells: Sample “Lambda” Layout

  

Adapted from [Terman'02]




# Custom Cells: Lambda vs. Micron Rules

Lambda-based design rules are based on the assumption that one can scale a design to the appropriate size before manufacture. The assumption is that **all manufacturing dimensions scale equally**, an assumption that “works” only over some modest span of time. For example: if a design is completed with a poly width of  $2\lambda$  and a metal width of  $3\lambda$  then minimum width metal wires will always be 50% wider than minimum width poly wires.

Consider the following data from Weste, Table 3.2:

 contacted metal pitch  
 $1/2 * \text{contact size}$   
 contact surround  
 metal-to-metal spacing  
 contact surround  
 $1/2 * \text{contact size}$




lambda rule	lambda = 0.5u	micron rule
$1\lambda$	$0.5\mu$	$0.375\mu$
$1\lambda$	$0.5\mu$	$0.5\mu$
$3\lambda$	$1.5\mu$	$1.0\mu$
$1\lambda$	$0.5\mu$	$0.5\mu$
$1\lambda$	$0.5\mu$	$0.375\mu$
$7\lambda$	$3.5\mu$	$2.75\mu$


Scaled design is legal but much larger than it needs to be!

Adapted from [Terman'02]


# Custom Cells: Sticks and Compaction

 


Stick diagram

 

 
Horizontal constraints  
for compaction in X



Compact X then Y

 


Compact Y then X

 


Compact X with jog  
insertion, then Y

Adapted from [Terman'02]


# Custom Cells: Example Stick Diagram

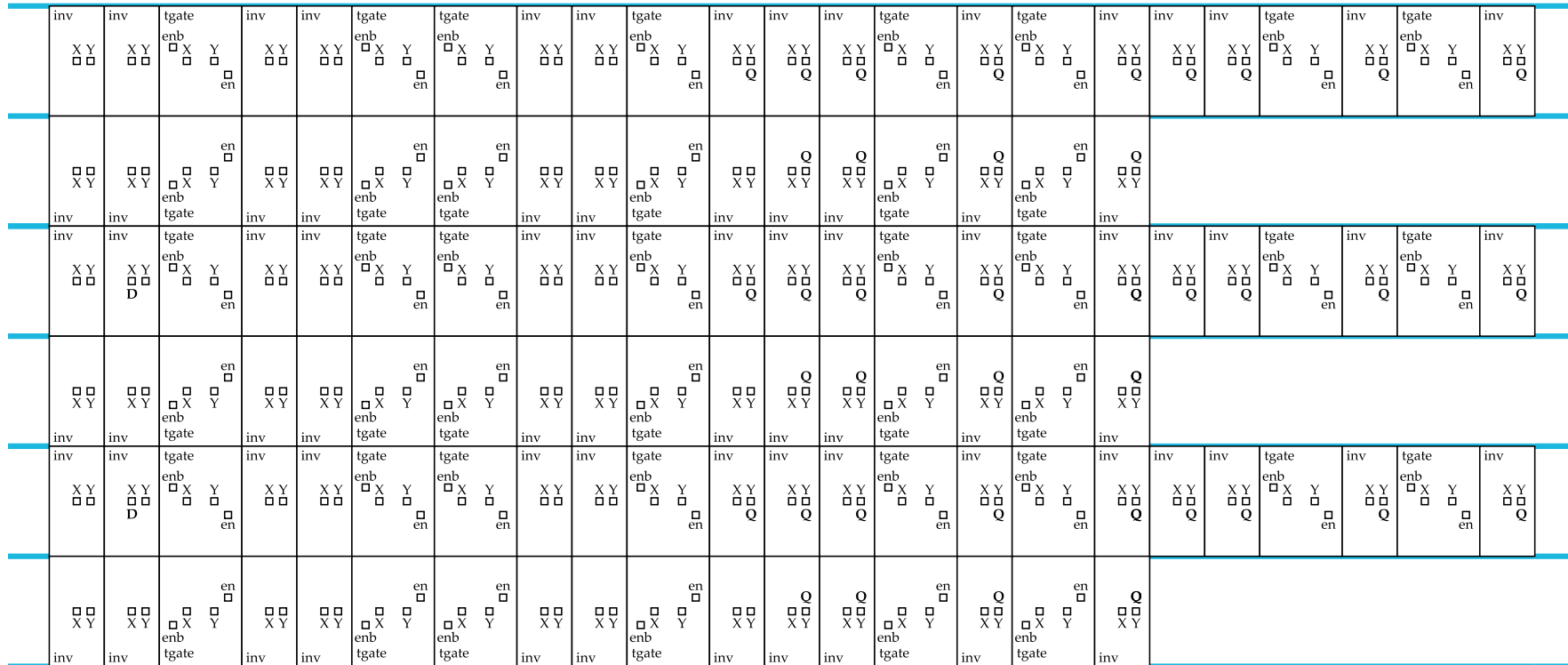

# Custom Cells: Example Stick Diagram

 


# Custom Cells: Cell “Styles”

 

Vertical Gates

 Good for circuits where fets sizes are similar and each gate has limited fanout. Best choice for multiple input static gates and for datapaths.



Horizontal Gates


Good for circuits where long and short fets are needed or where nodes must control many fets. Often used in multiple-output complex gates (e.g, sum/carry circuits).

What about routing signals between gates? Note that both layouts block metal/poly routing inside the cell. Choices: metal2 routing over the cell or routing above/below the cell.

- ♦ avoid long (> 50 squares) poly runs
- ♦ don't “capture” white space in a cell
- ♦ don't obsess over the layout, instead make a second pass, **optimizing where it counts**

Adapted from [Terman'02]

# Custom Cells: Optimizing Connections

 


Which does this gate do?


Which is better considering node capacitances?

Adapted from [Terman'02]

 
# Custom Cells: Optimizing Large Transistors



area = 928

 

area = 1008




 


area = 1080

Which is better considering wire resistances?  
Which is better considering node capacitances?

Adapted from [Terman'02]

    
# Custom Cells: Optimizing Diffusion Sharing



Adapted from [Terman'02]



# Custom Cells: Optimizing Across Cells

 


What does this cell do?

What if we want to replicate this cell vertically to process many bits in parallel?



Adapted from [Terman'02]

# Custom Cells: Optimizing Across Cells

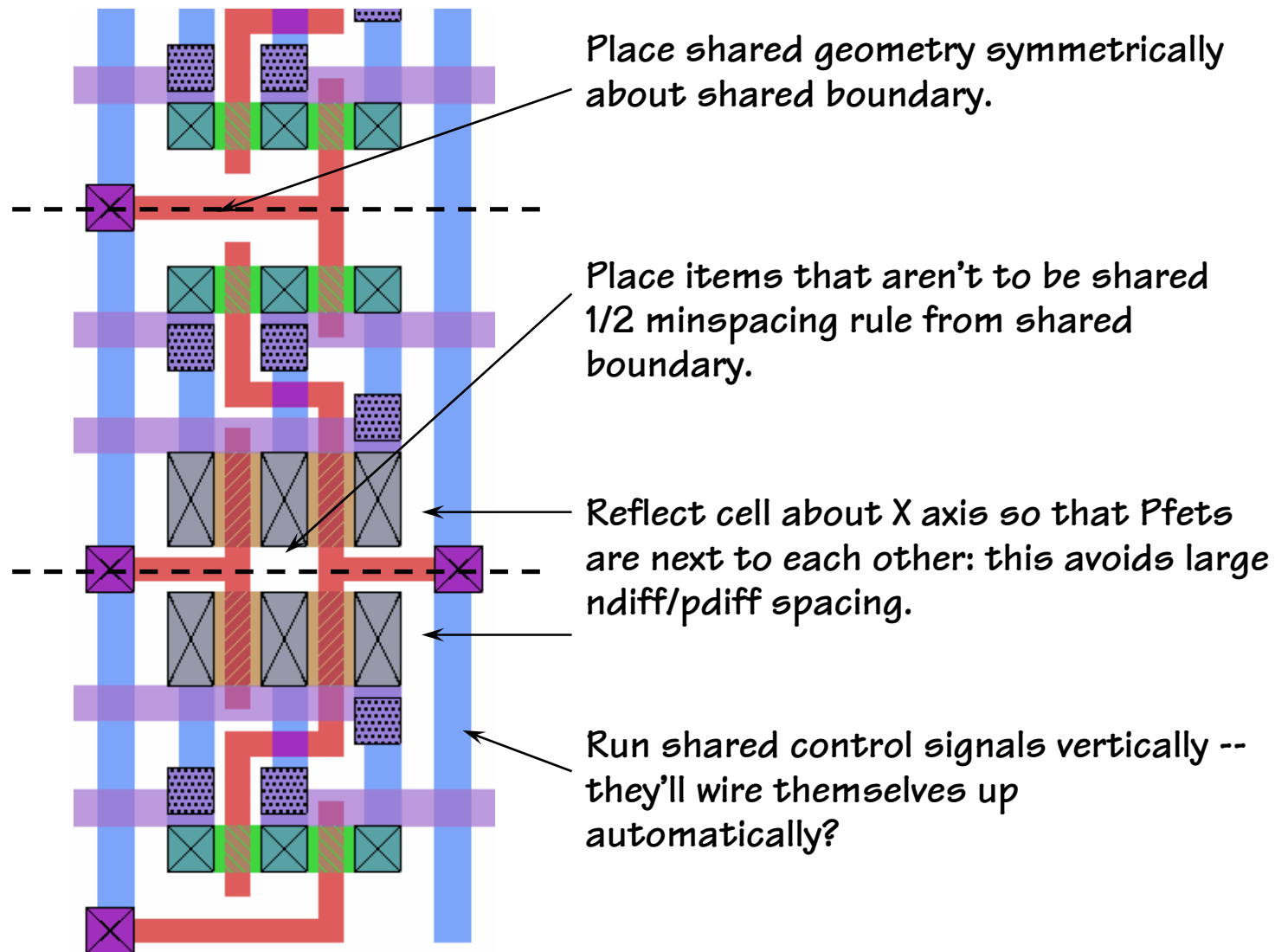

Adapted from [Terman'02]


# Custom Cells: Merging Simple Cells

 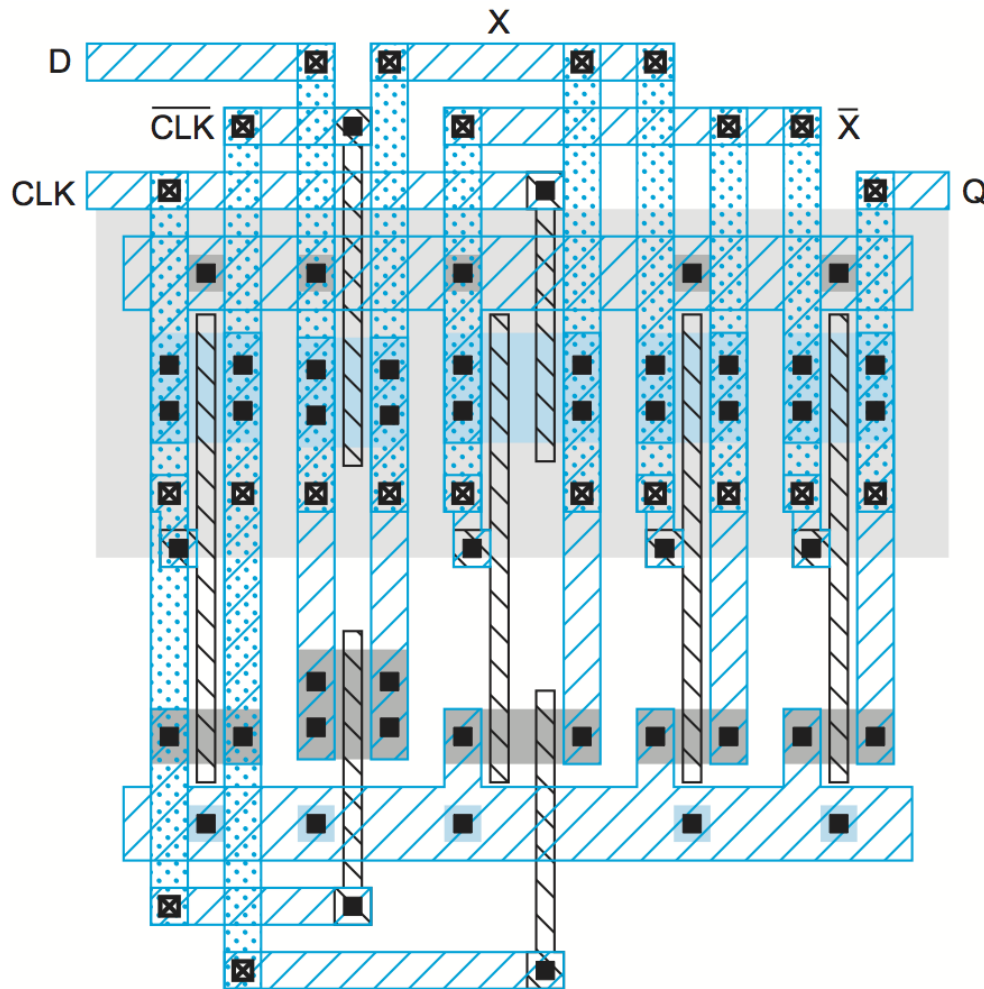


Two latch implementations: Left implementation composes primitive gates, while right implementation uses single tightly integrated gate

Adapted from [Weste'11]

# Custom Datapaths, Memories, Control

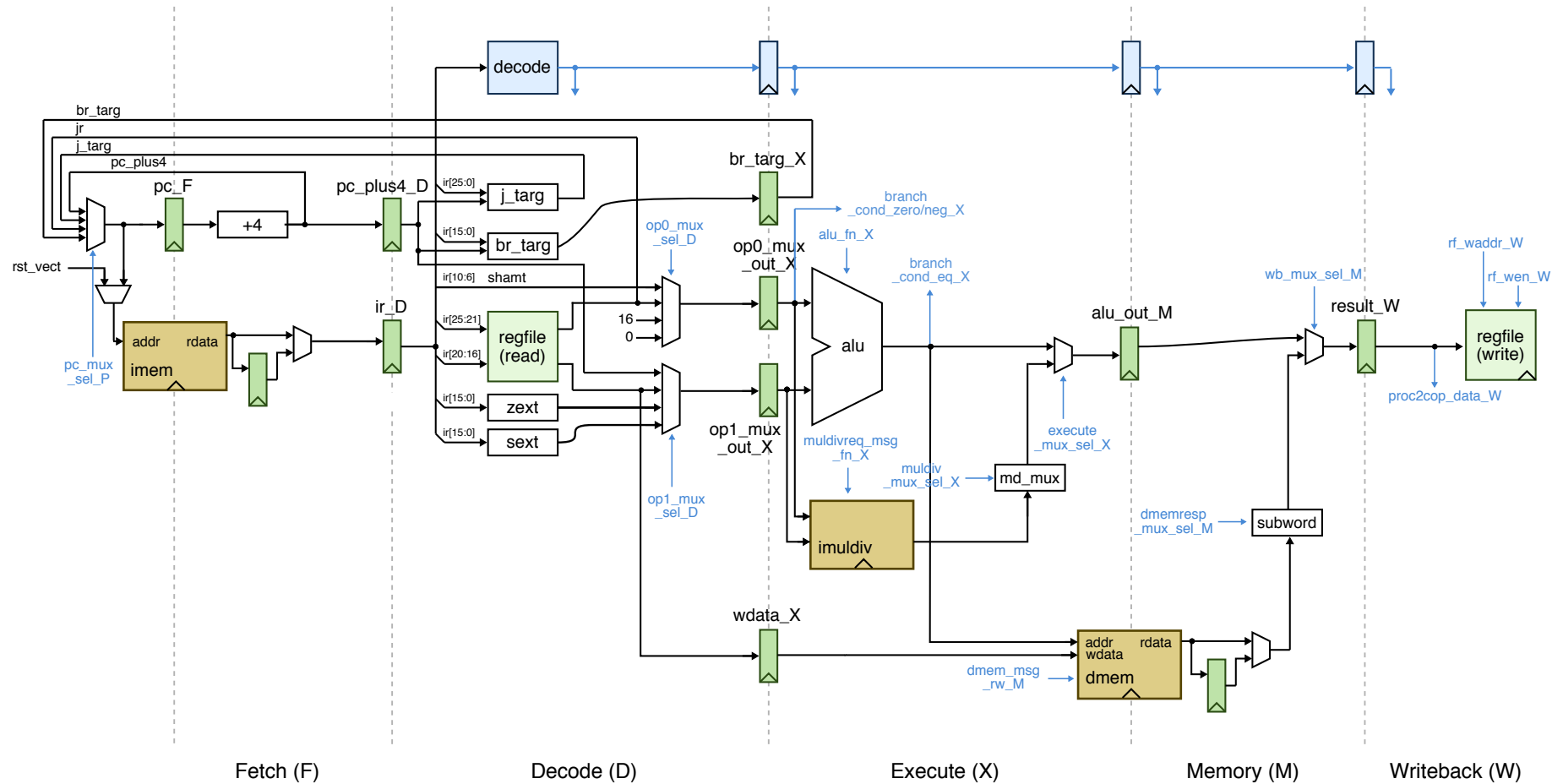


# Custom Datapaths, Memories, Control

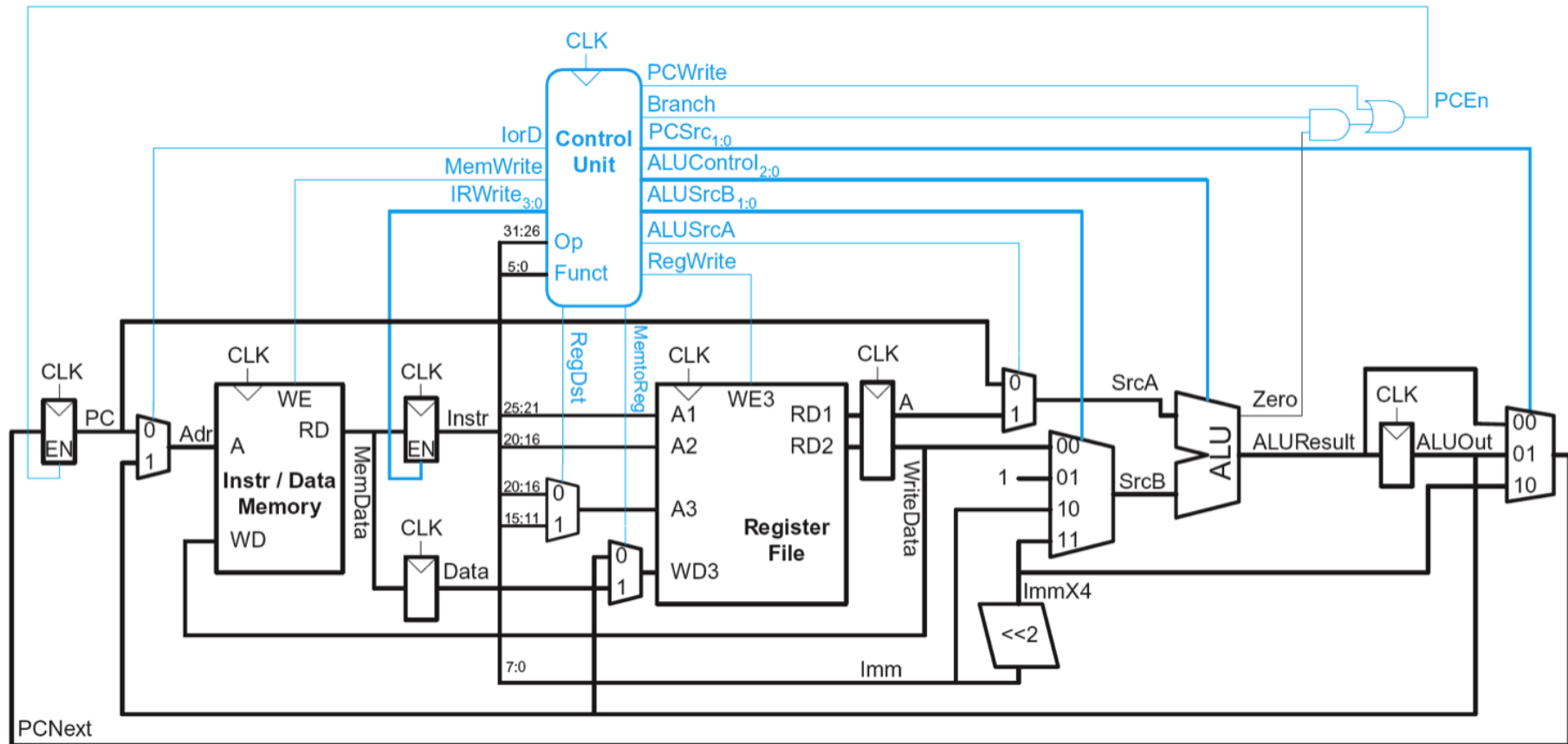

Adapted from [Weste'11]

# Custom Datapaths: PC Generation Unit

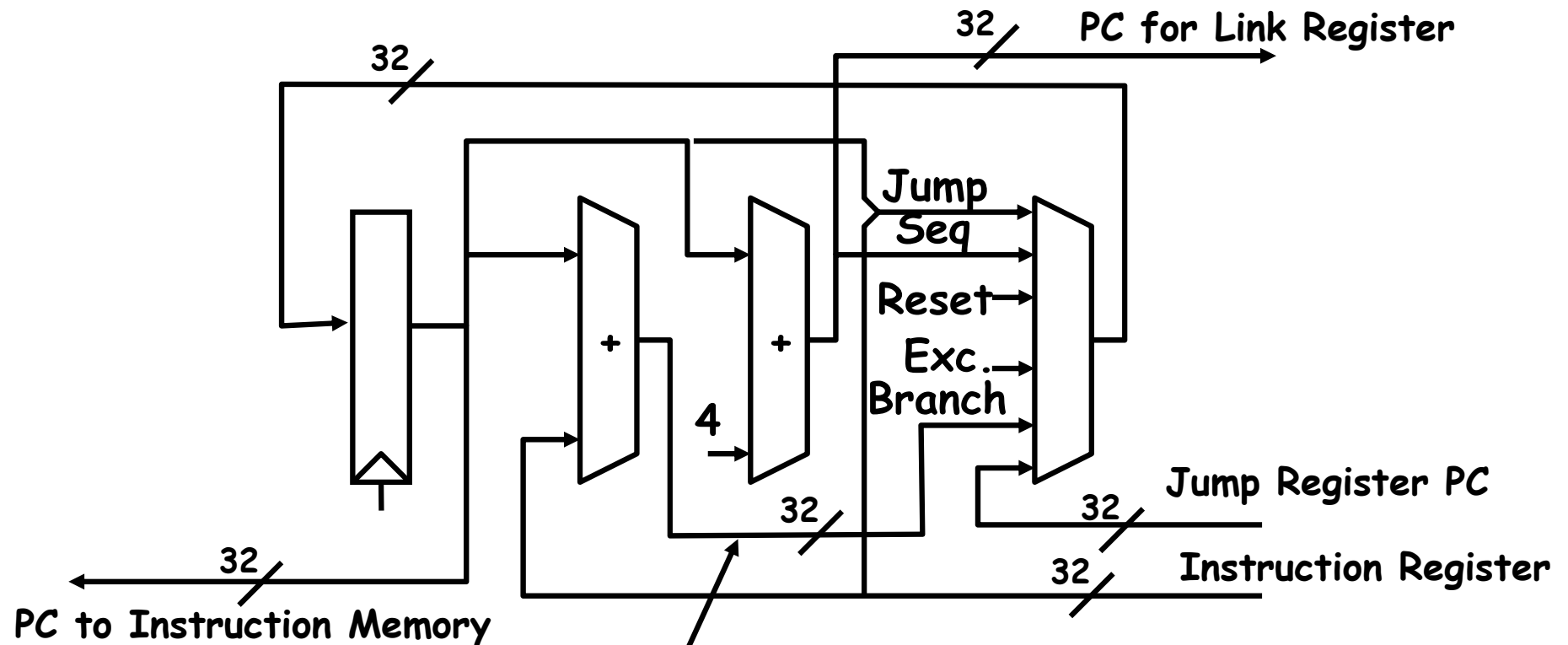


Routing every path as a separate 32-bit bus would take a large area

Adapted from [Terman'02]
 
# Custom Datapaths: Bitslices

- Implement datapath as single bit slices, contain one bit from each functional unit
- Route each bus bit position within bitslice




Adapted from [Terman'02]

 
# Custom Datapaths: Bit Pitch

- Height of each bit slice depends on:
  - height of tallest cell in entire bitslice
  - maximum number of buses running through any cell in bitslice

Two layers  
metal, buses  
run by side  
of cells



 
Three+ layers  
metal, buses run  
over cells



Adapted from [Terman'02]




# Custom Datapaths: PC Gen Example

 

Adapted from [Terman'02]
 
# Custom Datapaths: Datapath Library Cells


- Have to choose maximum datapath cell height
  - Too high, wastes area in simple cells
  - Too small, squeezes complex cells. Grow superlinearly in length dimension, so also wastes area.
- Compromise, around 8-12 metal tracks works OK





Adapted from [Terman'02]
 
# Custom Datapaths: Optimizing Datapath Layout

Reduce congestion by rearranging datapath components to minimize required number of vertical tracks per bitslice



 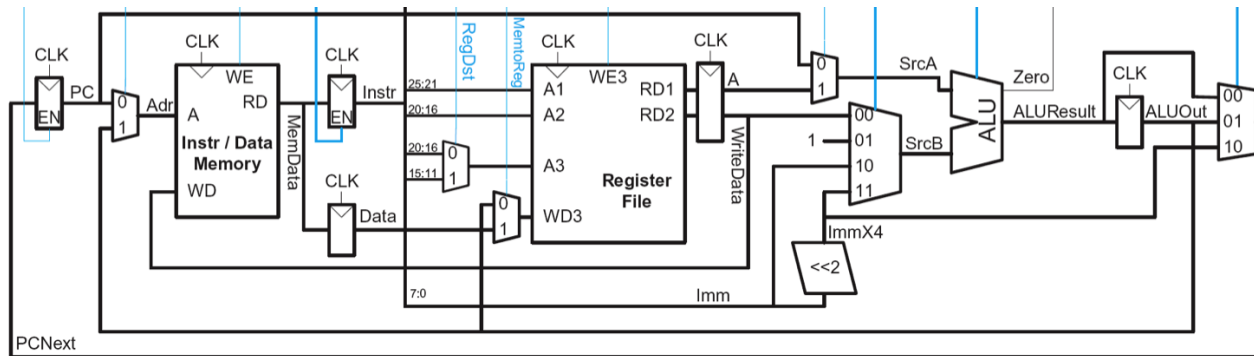
# Custom Datapaths: MIPS Datapath Track Allocation



Adapted from [Weste'11]




 
# Custom Datapaths: MIPS Datapath Example (1)




Adapted from [Weste'11]
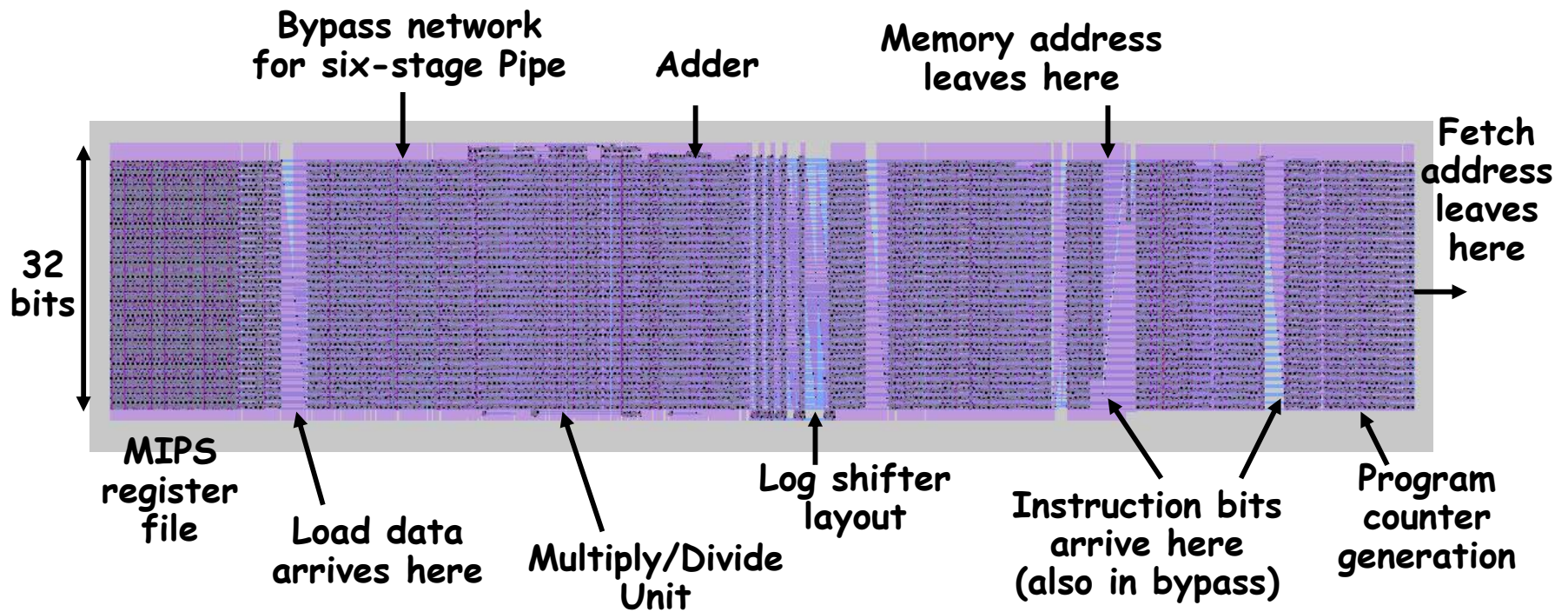 
# Custom Datapaths: MIPS Datapath Example (2)




Adapted from [Terman'02]

# Custom Memories: Array Structure

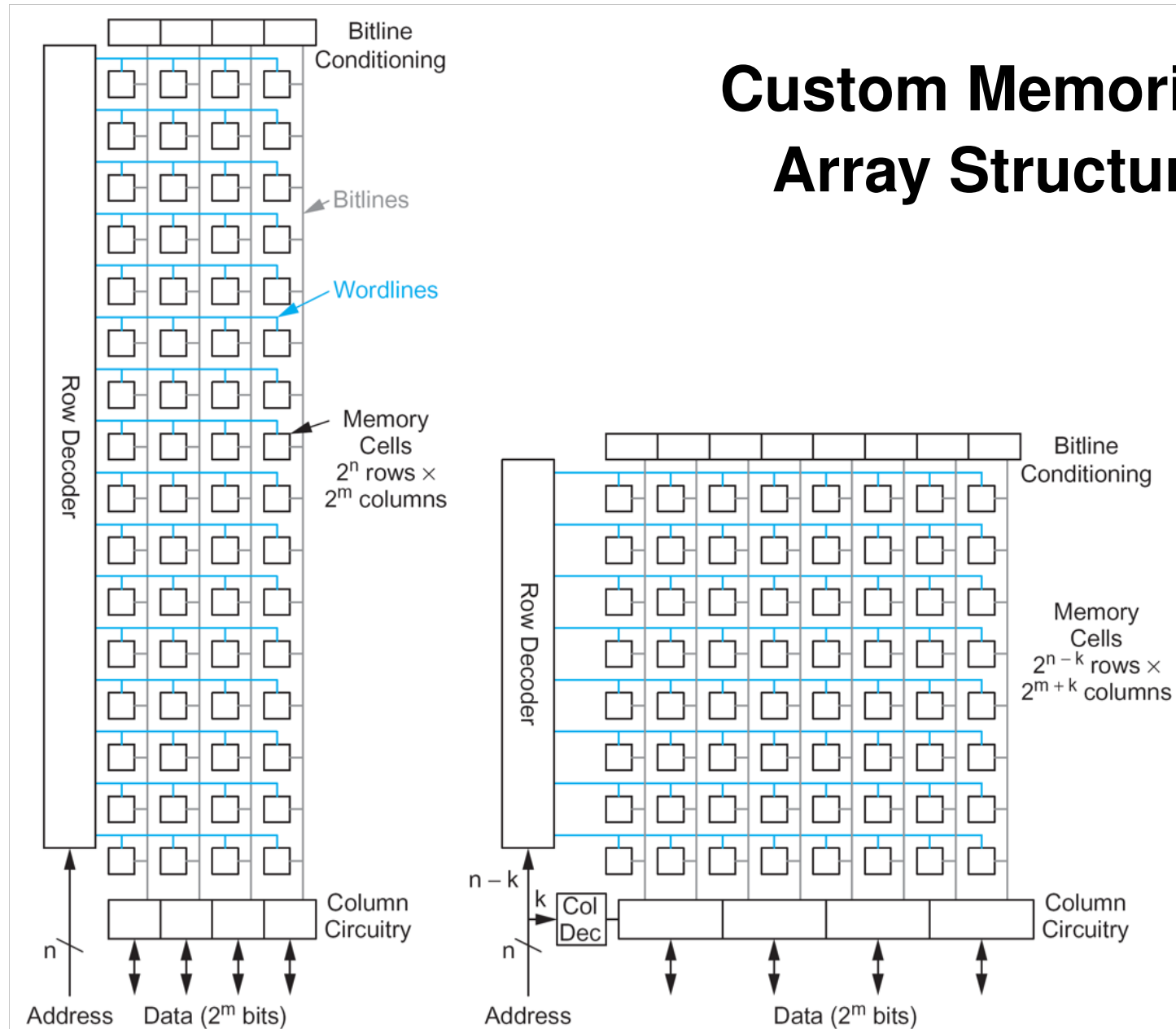

Adapted from [Weste'11]

 
# Custom Memories: Register File Circuits



Adapted from [Weste'11]



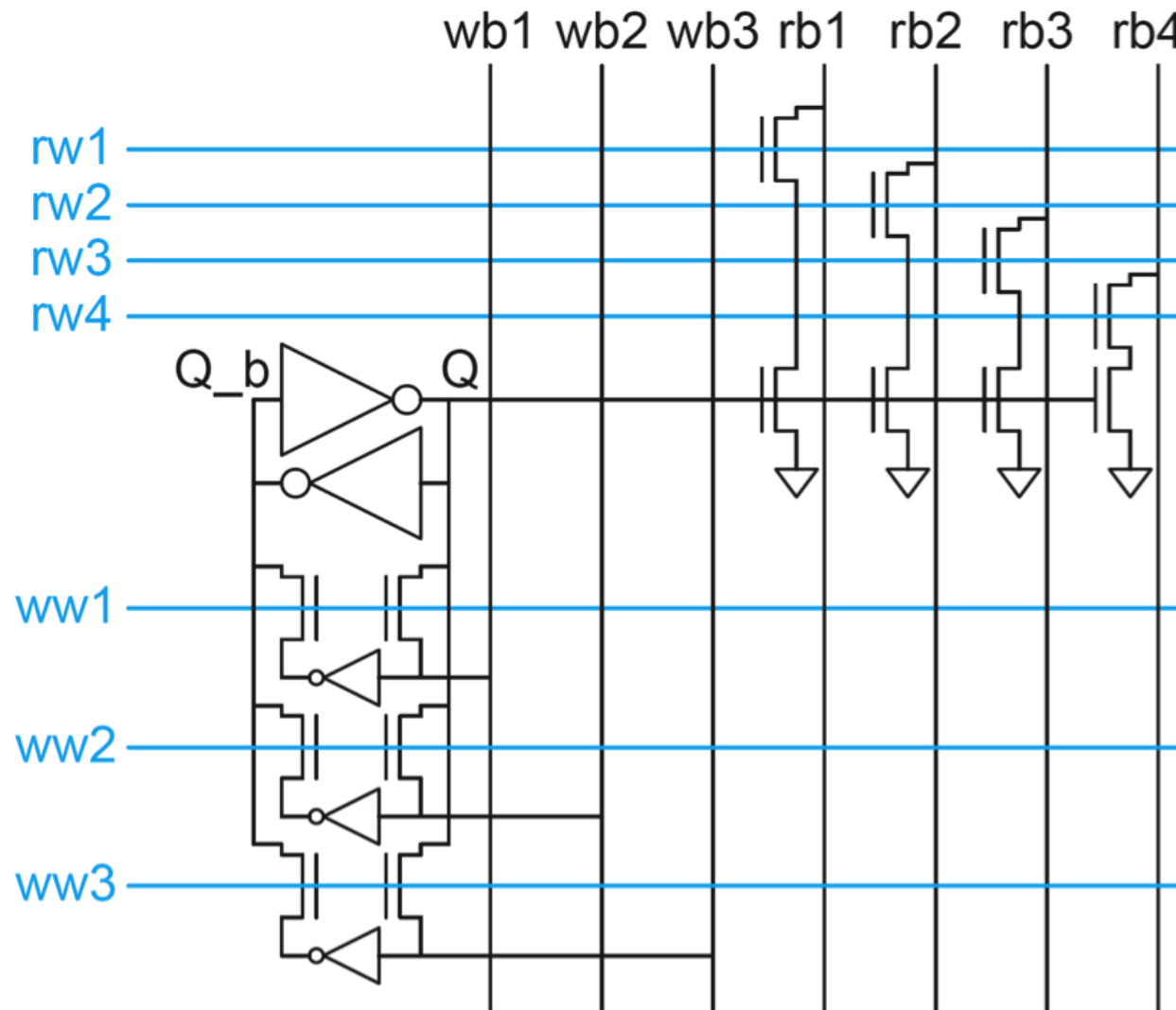
# Custom Memories: Register File Circuits




Adapted from [Weste'11]

# Custom Memories: SRAM Circuits

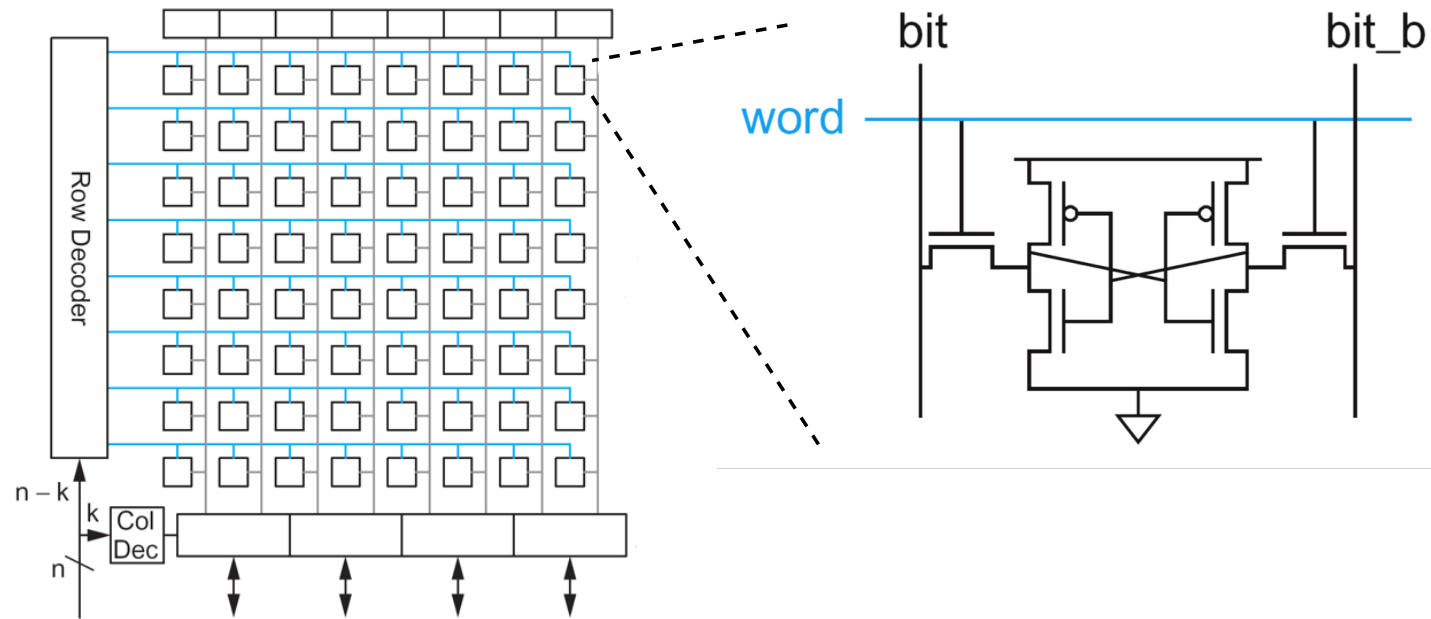

Adapted from [Weste'11]


# Custom Memories: SRAM Layout

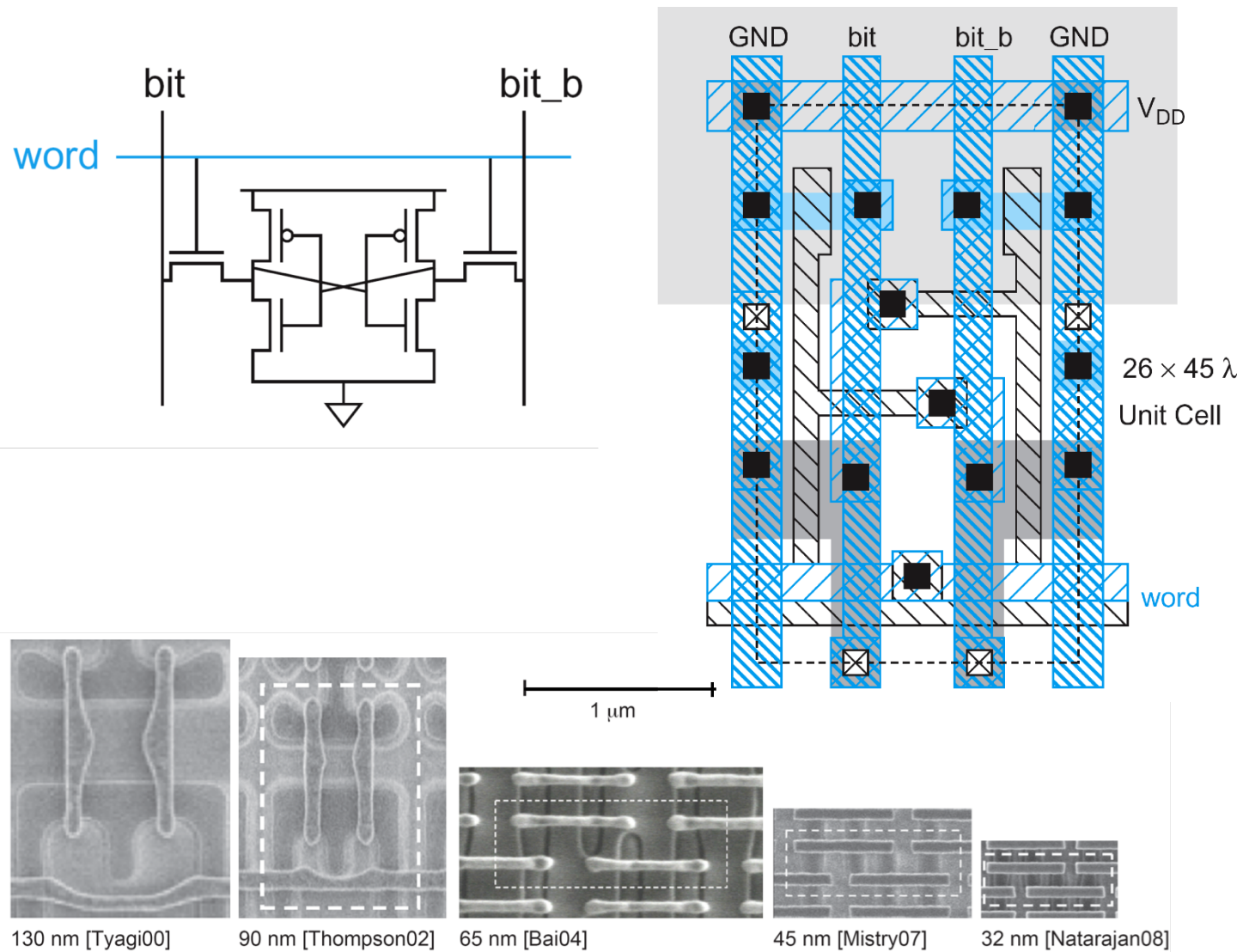

Adapted from [Weste'11]

 
# Custom Memories: SRAM

- Regular arrays built with cells that abut in two dimensions
  - Have to pitch match in both dimensions





Adapted from [Terman'02]

# Finite-State-Machine Control Unit

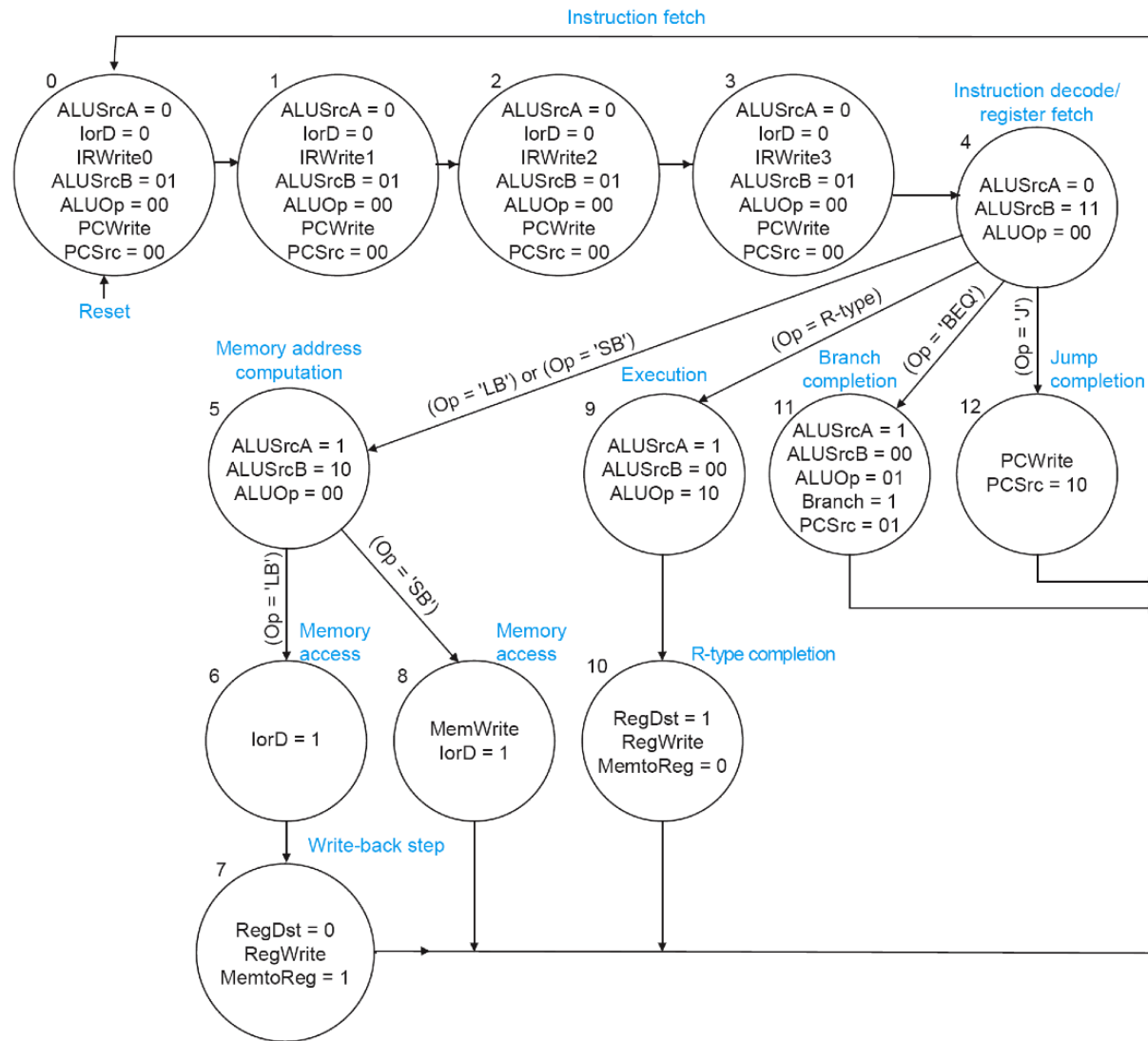

Adapted from [Weste'11]


# Full Custom Control Logic with PLA

 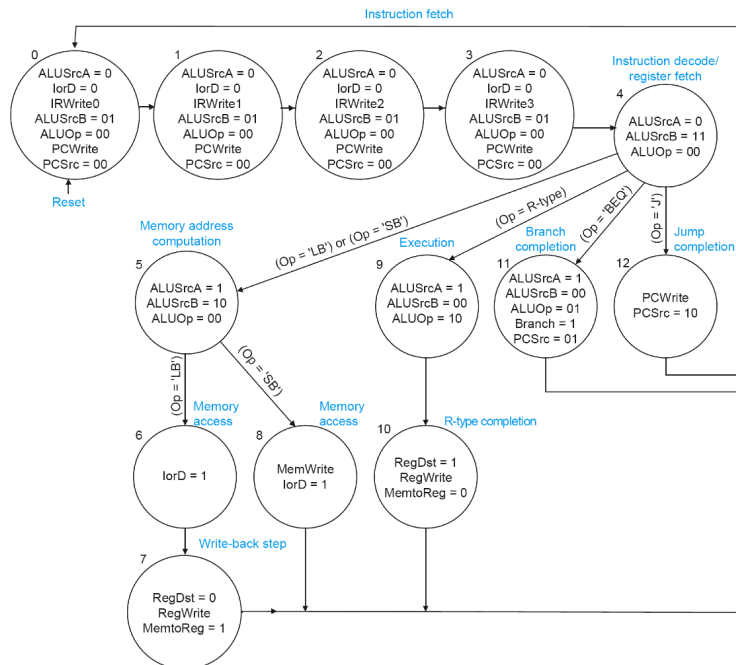

Adapted from [Weste'11]





# Top-Level Chip Floorplan

 

Adapted from [Weste'11]

# Final Full-Custom MIPS Processor

  

Adapted from [Weste'11]



# Acknowledgments

---

- ▶ [Weste'11] N. Weste and D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective," 4th ed, Addison Wesley, 2011.
- ▶ [Terman'02] C. Terman and K. Asanović, MIT 6.371 Introduction to VLSI Systems, Lecture Slides, 2002.
- ▶ [Ellervee'04] P. Ellervee, IAY3714 VLSI Synthesis and HDLs, Lecture Slides, 2004.