

ECE 6745 Complex Digital ASIC Design

Topic 9: CMOS Combinational Logic


School of Electrical and Computer Engineering
Cornell University

revision: 2025-02-13-11-19

1	RC Modeling	3
2	Delay	5
2.1.	RC Delay of Inverter	5
2.2.	RC Delay of 2-Input NAND Gate	6
2.3.	Equal Rise/Fall Times	9
2.4.	Equal Drive Strength	10
2.5.	Larger Gates	11
2.6.	Larger Loads	12
2.7.	Comparison of Inverter, NAND, NOR Gates	13
2.8.	Logical Effort: Single Stage	16
2.9.	Logical Effort: Multiple Stages	22
3	Energy	37
4	Area	44

Copyright © 2025 Christopher Batten. All rights reserved. This handout was prepared by Prof. Christopher Batten at Cornell University for ECE 6745 Complex Digital ASIC Design. Download and use of this handout is permitted for individual educational non-commercial purposes only. Redistribution either in part or in whole via both commercial or non-commercial means requires written permission.


1. RC Modeling

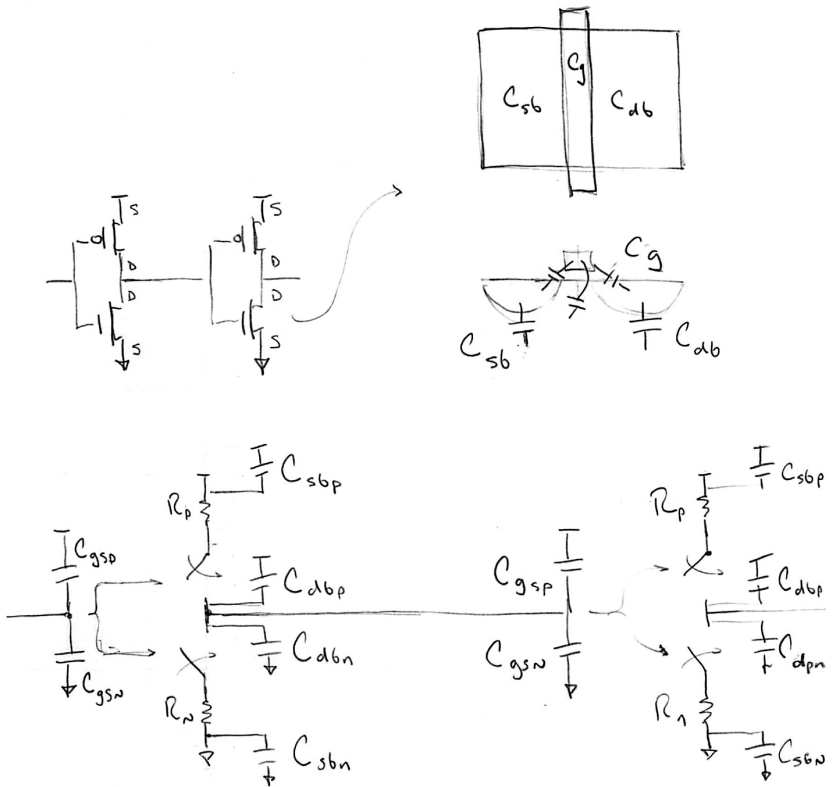




- C_{sb} capacitors do not actually switch, so ignore
- Lump $C_{dbp} + C_{dbn}$ since both tied to constant nodes
- Lump $C_{gsn} + C_{gsn}$ since both tied to constant nodes
- Assume PMOS mobility is $2\times$ worse than NMOS mobility

 1. RC Modeling

- Let C be the gate capacitance of minimum sized NMOS
- Let R be the effective resistance of a minimum sized NMOS
- Let k be width of a transistor relative to minimum sized NMOS



2-Input NAND Gate

  
 


Draw and label the parasitic capacitances.

2. Delay

- We will initially use RC modeling to estimate delay
- We will then use RC modeling to derive logical effort (LE)
- LE is a fast way to estimate delay for simple static CMOS circuits
- Often need to use a mix of RC modeling and LE

2.1. RC Delay of Inverter

  

- Let t_{pd} be the propagation delay, time until $V_{out} = V_{dd}/2$

$$V_{out} = V_{dd} e^{-t/\tau}$$

$$\frac{V_{dd}}{2} = V_{dd} e^{-t/\tau}$$

$$\frac{1}{V_{dd}} \frac{V_{dd}}{2} = e^{-t/\tau}$$

$$\ln\left(\frac{1}{2}\right) = \frac{-t}{\tau}$$


$$-\tau \ln\left(\frac{1}{2}\right) = t$$

$$t = \tau \ln(2)$$

- So $t_{pd} = \ln(2) \cdot RC_1$
- Let $R' = \ln(2) \cdot R$, so $t_{pd} = R'C_1$
- For inverter on previous page, $t_{pd} = 2R'C$
- We usually just assume effective resistance is scaled by $\ln(2)$
- So propagation delay of inverter on previous page:

$t_{pd} = 2RC$

2.2. RC Delay of 2-Input NAND Gate

 



- Requires complicated 2nd order model
- We can use a simple approximation

$$\begin{aligned} \tau &= \tau_1 + \tau_2 = RC_1 + (R + R)C_2 \\ &= RC + (2R)(3C) \\ &= RC + 6RC = 7RC \quad (3.5\times \text{ slower than inverter}) \end{aligned}$$

- Best when one τ much larger than the other τ
- Even if $\tau_1 = \tau_2$, error is $< 15\%$

Generalized Elmore Delay
  
$$t_{pd} = \sum_{i \text{ all nodes}} R_{ij} C_i$$



Assume all resistances are R and all capacitances are C

- Delay of path from x to y is impacted by branch to z
- Delay of path from x to z is impacted by branch to y
- For path x to y , lump $C_2 + C_3$ and use shared resistance $R_0 + R_1$
- For path x to z , lump C_1 and use shared resistance $R_0 + R_1$
- This extra term estimates impact of delay due to “branch”

$$\begin{aligned} T_{pd,xy} &= R_0 C_0 + (R_0 + R_1 + R_2) C_1 + (R_0 + R_1) (C_2 + C_3) \\ &= RC + 3RC + 4RC = 8RC \end{aligned}$$

$$\begin{aligned} T_{pd,xz} &= R_0 C_0 + (R_0 + R_1 + R_3) C_2 + (R_0 + R_1 + R_3 + R_4) C_3 + (R_0 + R_1) C_1 \\ &= RC + 3RC + 4RC + 2RC = 10RC \end{aligned}$$

Use Elmore Delay to Estimate Rise/Fall Times for 2-Input NAND Gate

$$t_{pd,1 \rightarrow 0}$$

$$A = 1$$

$$B = 0 \rightarrow 1$$

$$t_{pd,1 \rightarrow 0}$$

$$A = 0 \rightarrow 1$$

$$B = 1$$

$$t_{pd,0 \rightarrow 1}$$

$$A = 1 \rightarrow 0$$

$$B = 1 \rightarrow 0$$

$$t_{pd,0 \rightarrow 1}$$

$$A = 1$$


$$B = 1 \rightarrow 0$$

$$t_{pd,0 \rightarrow 1}$$

$$A = 1 \rightarrow 0$$

$$B = 1$$



2.3. Equal Rise/Fall Times

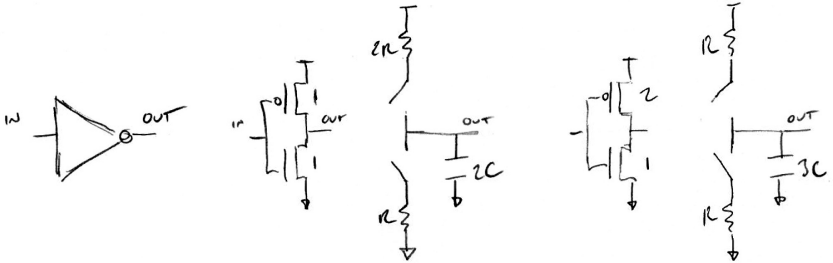
 $t_{pd,1 \rightarrow 0}$
 $\text{in} = 0 \rightarrow 1$
 $t_{pd,0 \rightarrow 1}$
 $\text{in} = 1 \rightarrow 0$

- For equal rise/fall times, the effective resistance of pullup must equal effective resistance of pulldown
- If we assume PMOS mobility $2\times$ worse than NMOS, then PMOS must be $2\times$ size of NMOS in an inverter for equal rise/fall times

  2.4. Equal Drive Strength

- Size transistors so worst case effective resistance is equal in both the pullup and pulldown networks.



$t_{pd,1 \rightarrow 0}$	$t_{pd,0 \rightarrow 1}$
worst	best
best	worst

inverter

2-input NAND w/o internal cap


2-input NAND w/ internal cap

- Is this a fair comparison? No, we are not normalizing anything across these gates. We need to either normalize:
 - Input gate gap (i.e., load on previous gate)
 - Drive strength (i.e., effective resistance)
-


- All three gates with equal rise/fall times *and* equal drive strengths


 
$$\begin{aligned} R_{EFF} &= R \\ C_{in} &= 3C \\ C_P &= 3C \end{aligned}$$



 
$$\begin{aligned} R & \\ C_{in} &= 4C \\ C_P &= 6C \end{aligned}$$




$$\begin{aligned} R & \\ C_{in} &= 5C \\ C_P &= 6C \end{aligned}$$

2.5. Larger Gates

 



$$t_{pd,1 \rightarrow 0} =$$

 

$$t_{pd,0 \rightarrow 1} =$$

- This is the **parasitic delay**, independent of size (k)

2.6. Larger Loads

 
 


$$t_{pd,1 \rightarrow 0} =$$

2.7. Comparison of Inverter, NAND, NOR Gates

- Complete a fair comparison assuming equal rise/fall times, equal drive strength, only parasitic delay

		$t_{pd,1 \rightarrow 0}$		$t_{pd,0 \rightarrow 1}$	
		worst	best	worst	best
inverter					
2-input NAND	w/o internal cap				
2-input NAND	w/ internal cap				
2-input NOR	w/o internal cap				
2-input NOR	w/ internal cap				

  

Use Elmore Delay to Estimate Rise/Fall Times for 2-Input NOR Gate

$$t_{pd,1 \rightarrow 0}$$

$$A = 0 \rightarrow 1$$

$$B = 0 \rightarrow 1$$

$$t_{pd,1 \rightarrow 0}$$

$$A = 0$$

$$B = 0 \rightarrow 1$$

$$t_{pd,1 \rightarrow 0}$$

$$A = 0 \rightarrow 1$$

$$B = 0$$

$$t_{pd,0 \rightarrow 1}$$

$$A = 0$$

$$B = 1 \rightarrow 0$$

$$t_{pd,0 \rightarrow 1}$$

$$A = 1 \rightarrow 0$$


$$B = 0$$

Use RC Modeling to Estimate Delay of 2-Input NAND and NOR Gates

- Ignore internal capacitance
- Assume worst case delay
- Assume an output load of $15C$

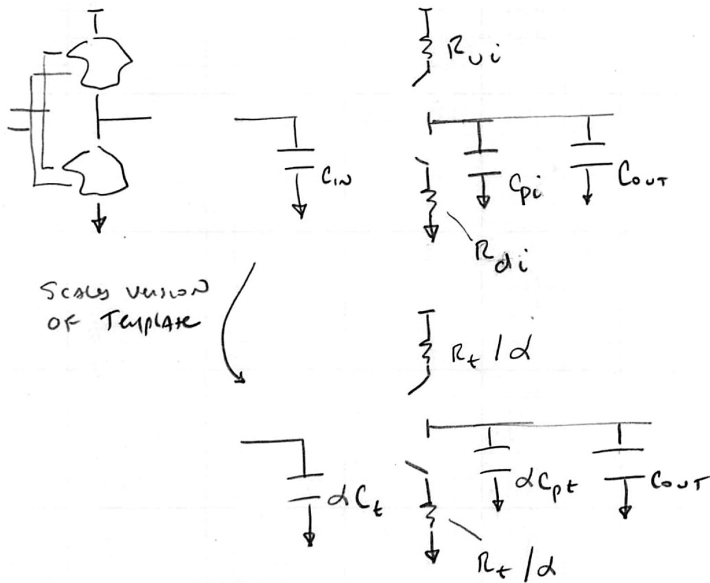2.8. Logical Effort: Single Stage

- Logic effort (LE) is just an abstraction over RC modeling
- Logic effort (LE) is a *linear delay model*
- Useful for building intuition for static CMOS modeling
- Keep in mind often need to use a mix of RC modeling and LE



$$C_{in} = \alpha C_t$$

$$R_i = R_{ui} = R_{di} = R_t / \alpha$$

$$C_{pi} = \alpha C_{pt}$$

- We know the propagation delay of the gate instance is:

$$t_{pd} = R_i(C_{out} + C_{pi})$$

- Let's rewrite this in terms of the template

$$C_{in} = \alpha C_t$$

$$R_i = R_{ui} = R_{di} = R_t / \alpha$$

$$C_{pi} = \alpha C_{pt}$$

$$\begin{aligned} t_{pd} &= R_i(C_{out} + C_{pi}) \\ &= R_i C_{out} + R_i C_{pi} \\ &= \frac{R_t}{\alpha} C_{out} + \frac{R_t}{\alpha} C_{pi} \\ &= \frac{R_t}{\alpha} C_{out} + \frac{R_t}{\alpha} (\alpha C_{pt}) \\ &= \frac{R_t}{\alpha} \left(\frac{C_{in}}{C_{in}} \right) C_{out} + \frac{R_t}{\alpha} (\alpha C_{pt}) \\ &= \frac{R_t}{\alpha} \alpha C_t \left(\frac{C_{out}}{C_{in}} \right) + \frac{R_t}{\alpha} (\alpha C_{pt}) \\ &= R_t C_t \left(\frac{C_{out}}{C_{in}} \right) + R_t C_{pt} \end{aligned}$$

- We don't want to deal with absolute delay
- Let's rewrite our propagation delay equation to be a "relative" delay
- Relative to the delay of a single unloaded minimal inverter
- Let's start by defining some new parameters

$$\tau = R_{inv}C_{inv} \quad \text{"relative delay units"}$$

$$g = R_t C_t / R_{inv} C_{inv} \quad \text{logical effort}$$

$$h = C_{out} / C_{in} \quad \text{electrical effort}$$

$$p = R_t C_{pt} / R_{inv} C_{inv} \quad \text{parasitic delay}$$

- Let's rewrite our propagation delay equation in terms of τ

$$\tau = R_{inv}C_{inv} \quad \text{"relative delay units"}$$

$$g = R_t C_t / R_{inv} C_{inv} \quad \text{logical effort}$$

$$h = C_{out} / C_{in} \quad \text{electrical effort}$$



$$p = R_t C_{pt} / R_{inv} C_{inv} \quad \text{parasitic delay}$$

$$\begin{aligned} t_{pd} = d_{abs} &= R_t C_t \left(\frac{C_{out}}{C_{in}} \right) + R_t C_{pt} \\ &= \left(\frac{R_{inv} C_{inv}}{R_{inv} C_{inv}} \right) R_t C_t \left(\frac{C_{out}}{C_{in}} \right) + \left(\frac{R_{inv} C_{inv}}{R_{inv} C_{inv}} \right) R_t C_{pt} \\ &= R_{inv} C_{inv} \left(\frac{R_t C_t}{R_{inv} C_{inv}} \right) \left(\frac{C_{out}}{C_{in}} \right) + R_{inv} C_{inv} \left(\frac{R_t C_{pt}}{R_{inv} C_{inv}} \right) \\ &= \tau g h + \tau p \\ &= \tau (g h + p) \end{aligned}$$

$$d_{abs} = \tau (g h + p)$$


- Let d be the delay in units of τ (i.e., $d = g h + p$)

Templates for Inverter, NAND, NOR Gates

  

R_{Eff}	R	R	R
C_{in}	$3C$	$4C$	$5C$
$\frac{R_{\text{eff}} C_{\text{in}}}{R_{\text{inv}} C_{\text{inv}}}$	$\frac{R 3C}{R 3C}$	$\frac{R 4C}{R 3C}$	$\frac{R 5C}{R 3C}$
g	1	$4/3$	$5/3$
$\frac{R_{\text{eff}} C_{\text{out}}}{R_{\text{inv}} C_{\text{inv}}}$	1	$\frac{G}{g} = 2$	$\frac{G}{g} = 2$

 RECALL $d = gh + p$ (LINEAR DELAY MODEL)
 PLOT d AS A FUNCTION OF h



$$\text{NOR } d = \frac{5}{3}h + 2$$

$$\text{NAND } d = \frac{4}{3}h + 2$$

$$\text{INV } d = h + 1$$

Why we prefer NAND vs. NOR? NOR has higher delay for same electrical effort

Use LE to Estimate Delay of 2-Input NAND and NOR Gates


- Assume an output load of $15C$

Let's list the many approximations we have made

2.9. Logical Effort: Multiple Stages

- **Path delay** is the sum of the delay of each stage

$$D = \sum d_i = \sum (g_i h_i + p_i)$$

 

- Calculate path delay assuming canonical sized gates


g_i	1	5/3	4/3	1
h_i	5/3	4/5	3/4	40/3
$g_i \cdot h_i$	5/3	4/3	1	40/3
p_i	1	2	2	1
d_i	2.67	3.33	3	14.33
D				23.33

- Calculate path delay assuming final gate is X16

g_i	1	5/3	4/3	1
h_i	5/3	4/5	48/4	40/48
$g_i \cdot h_i$	5/3	4/3	16	40/48
p_i	1	2	2	1
d_i	2.67	3.33	18	1.83
D				25.83

 Q1: How should we size gates to minimize total delay?

- Independent variables are h_i (i.e., internal gate sizing)
- We want to choose h_i to minimize D
- Take the partial derivative of D with respect to h_i , set to zero, and solve for optimum h_i



$$D = (g_1 h_1 + p_1) + (g_2 h_2 + p_2)$$

- Note that h_1 and h_2 are constrained since C_1 and C_3 are given and input cap of gate 2 is output cap for gate 1

$$h_1 = \frac{C_2}{C_1} \quad h_2 = \frac{C_3}{C_2} \quad h_1 h_2 = \frac{C_2}{C_1} \frac{C_3}{C_2} = \frac{C_3}{C_1}$$

- Let $H = h_1 h_2 = C_3 / C_1$, H is a constant since C_1 and C_3 are given
- Let's rework D to get it in terms of just one variable

$$D = (g_1 h_1 + p_1) + (g_2 h_2 + p_2)$$

$$D = g_1 h_1 + g_2 h_2 + (p_1 + p_2)$$

$$= g_1 h_1 + g_2 \frac{H}{h_1} + (p_1 + p_2)$$

$$= g_1 h_1 + g_2 H h_1^{-1} + (p_1 + p_2)$$

- Take partial derivative with respect to the only variable h_1

$$\begin{aligned}
 D &= g_1 h_1 + g_2 H h_1^{-1} + (p_1 + p_2) \\
 \frac{\partial D}{\partial h_1} &= g_1 - g_2 H h_1^{-2} + 0 \\
 &= g_1 - \frac{g_2 H}{h_1^2}
 \end{aligned}$$

- Set partial derivative to zero and solve for h_1

$$\begin{aligned}
 \frac{\partial D}{\partial h_1} &= g_1 - \frac{g_2 H}{h_1^2} = 0 \\
 g_1 &= \frac{g_2 H}{h_1^2} \\
 g_1 h_1^2 &= g_2 H \\
 h_1^2 &= \frac{g_2}{g_1} H \\
 h_1 &= \sqrt{\frac{g_2}{g_1} H}
 \end{aligned}$$

- Can use similar approach to find optimal h_i for more than 2 stages
- However, there is actually a much more interesting result!

$$\begin{aligned}
 g_1 h_1^2 &= g_2 H \\
 g_1 h_1^2 &= g_2 h_1 h_2 \\
 g_1 h_1 &= g_2 h_2 \\
 f_1 &= f_2
 \end{aligned}$$

- Delay is minimized when stage effort (f_i) is the same in both stages!
- Let \hat{f} be the optimal stage effort (i.e., $\hat{f} = f_1 = f_2$)
- We can use a trick to quickly calculate \hat{f}

$$\begin{aligned}\hat{f} &= \sqrt{\hat{f}^2} = \sqrt{\hat{f} \hat{f}} = \sqrt{f_1 f_2} \\ &= \sqrt{(g_1 h_1)(g_2 h_2)} \\ &= \sqrt{(g_1 g_2)(h_1 h_2)}\end{aligned}$$

- Let $G = g_1 g_2$, this is the **path logical effort**
- Let $H = h_1 h_2 = C_{out}/C_{in}$, this is the **path electrical effort**
- Let $F = GH$, this is the **path effort**

$$\begin{aligned}\hat{f} &= \sqrt{(g_1 g_2)(h_1 h_2)} \\ &= \sqrt{GH} \\ &= \sqrt{F}\end{aligned}$$

- We can calculate \hat{f} without finding the optimal size of each gate!
- Minimal delay with optimal sizing can be quickly calculated using:

$$\hat{D} = 2\hat{f} + (p_1 + p_2)$$

- This generalizes to paths with any number of stages

$$G = \prod g_i \quad \text{path logical effort}$$

$$H = \prod h_i = \frac{C_{out}}{C_{in}} \quad \text{path electrical effort}$$

$$F = GH \quad \text{path effort}$$

$$\hat{f} = F^{1/N} \quad \text{optimal stage effort}$$


$$P = \sum p_i \quad \text{path parasitic delay}$$

$$\hat{D} = N\hat{f} + P \quad \text{min delay with opt sizing}$$

Method for optimal sizing

1. Calculate path effort ($F = GH$)
2. Calculate effort for each stage ($\hat{f} = F^{1/N}$)
3. Estimate minimum delay with optimal sizing ($\hat{D} = N\hat{f} + P$)
4. Starting with last stage, work backwards sizing each gate


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}} \quad C_{in} = \frac{g}{\hat{f}} C_{out}$$

 Revisit earlier example

g_i	1	5/3	4/3	1
p_i	1	2	2	1

Optimal sizing with standard cells

 - This assumes we can size gates arbitrarily using full custom design
- What about if we are using a standard cell library?
- Assume we have a standard cell library with the following cells
 - INVX1, INVX2, INVX4, INVX8
 - NANDX1, NANDX2, NANDX4
 - NORX1, NORX2, NORX4



- Assume we have determined optimal sizing in C_{in}
- How do we figure out which standard cell to use?

- Given optimum C_{in} from before, what is α ?

C_{in}	g	$C_{in}/(g \times 3C)$	$= \alpha$	gate
17.17C	1	$17.17C/(1 \times 3C)$	$= 5.72$	INVX4
9.83C	4/3	$9.83C/((4/3) \times 3C)$	$= 2.45$	NANDX2
7.03C	5/3	$7.03C/((5/3) \times 3C)$	$= 1.41$	NORX1
3.02C	1	$3.02C/(1 \times 3C)$	$= 1.00$	INVX1

- Recalculate actual delay given these gates
- First calculate actual C_{in} for each standard cell gate

gate	α	g	$\alpha \times g \times 3C$	$= C_{in}$
INVX4	4	1	$4 \times 1 \times 3C$	$= 12C$
NANDX2	2	4/3	$2 \times 4/3 \times 3C$	$= 8C$
NORX1	1	5/3	$1 \times 5/3 \times 3C$	$= 5C$
INVX1	1	1	$1 \times 1 \times 3C$	$= 3C$


- Now use path delay equation

$$\begin{aligned}
 D &= \sum gh + \sum p \\
 &= (1 \times \frac{40}{12}) + (\frac{4}{3} \times \frac{12}{8}) + (\frac{5}{3} \times \frac{8}{5}) + (1 \times \frac{5}{3}) + (1 + 2 + 2 + 1) \\
 &= 3.33 + 2 + 2.67 + 1.67 + 6 = 9.67 + 6 = 15.67
 \end{aligned}$$

- Compare with optimal delay which is 15.32, off by 2.3%

What about branching?

- Consider the following simple example

 

$$G = 1 \times 1 = 1$$

$$H = 90C/5C = 18$$

$$F = GH = 18$$

$$F = \prod g_i h_i \\ = (1 \times 6) \times (1 \times 6) = 36$$

- So in this example $F = 2GH$
- The factor of two is called the **branching effort**
- Key Idea: some drive current is directed off path we are analyzing
- Similar to Elmore delay for trees

$$b = \frac{C_{\text{onpath}} + C_{\text{offpath}}}{C_{\text{onpath}}} \quad \text{stage branching effort}$$

$$B = \prod b_i \quad \text{path branching effort}$$


- So our new path effort equation is now:

$$F = \prod f_i = GBH$$


- Note that path effort depends on circuit topology and loading of entire path, but *not* size of transistors in network
- Note that path effort does not change if we add or remove inverters!

 Q2: How should we change topology to minimize delay?

- Assume we want to implement an eight input AND gate
- Calculate min delay assuming optimal sizing for three topologies
- First assume $H = 1$, then assume $H = 12$



Topology	$H = 1$			$H = 12$		
	$NF^{1/N}$	P	\hat{D}	$NF^{1/N}$	P	\hat{D}
NAND8						
NAND4						
NAND2						

 Determine optimal number of stages for chain of inverters

$$\hat{D} = NF^{1/N} + NP_{inv}$$

$$\frac{\partial \hat{D}}{\partial N} = F^{1/N} - F^{1/N} \ln(F^{1/N}) + P_{inv} = 0$$

- If $P_{inv} = 0$

$$\frac{\partial \hat{D}}{\partial N} = F^{1/N} - F^{1/N} \ln(F^{1/N}) = 0$$

$$\ln(F^{1/N}) = 1$$

$$F^{1/N} = e$$

$$\hat{f} = e$$

- So if we assume $P_{inv} = 0$, then the optimal number of stages results in a stage effort of e (i.e., 2.718) for every stage
- Since $G = 1$ for an inverter, this means $h = 2.718$ for every stage

- If $P_{inv} = 1$, then we need to solve this nonlinear equation:

$$F^{1/N} - F^{1/N} \ln(F^{1/N}) + 1 = 0$$

- Let $\rho = F^{1/\hat{N}}$ where \hat{N} is optimal number of stages

$$1 + \rho(1 - \ln(\rho)) = 0$$

- We can solve this numerically to find that $\rho \approx 3.59$
- So if we assume $P_{inv} = 1$, then the optimal number of stages results in a stage effort of 3.59 for every stage
- Since $G = 1$ for an inverter, this means $h = 3.59$ for every stage
- We can roughly approximate 3.59 to be 4
- Let's solve for \hat{N} as a function of F

$$F^{1/\hat{N}} = 4$$

$$\log(F^{1/\hat{N}}) = \log(4)$$

$$\frac{1}{\hat{N}} \log(F) = \log(4)$$


$$\hat{N} = \frac{\log(F)}{\log(4)} = \log_4(F)$$

- This is actually a pretty good estimate even for a path of gates which are not inverters!

Logical effort can help give us intuition on how to size gates + choose a topology to minimize delay but it has many limitations.

to deal with more complicated scenarios we can also write the delay equations for each gate in system and minimize the latest arrival time.

EXAMPLE

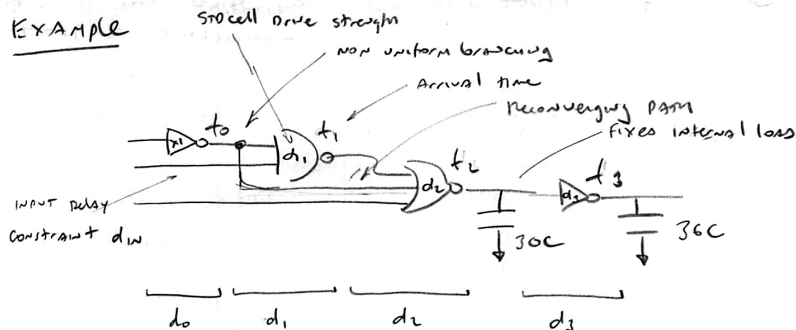

Let's write our linear delay equation as a function of α

$$d = gh + p$$

$$g = \frac{R_T C_T}{R_{inv} C_{inv}}$$

$$C_W = \alpha C_+ \quad C_+ = \frac{C_{in}}{\alpha}$$

$$d = \frac{C_{in}}{\alpha C_{inv}} \cdot \frac{C_{out}}{C_{inv}} + p$$

$$g = \frac{C_W}{\alpha C_{inv}}$$

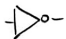
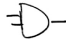

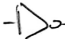
- 3C

$$d = \frac{C_{out}}{3\alpha} + p$$

Delay as function of α (500cell drive)

recall $C_W = 3g\alpha$

Now write delay equations for each stage

	d_0	d_1	d_2	d_3
				
α	1	α_1	α_2	α_3
g	1	$4/3$	$7/3$	1
$C_{in} = 3gd$	3	$4\alpha_1$	$7\alpha_2$	$3\alpha_3$
p	1	2	3	1

$$d_0 = \frac{(4\alpha_1 + 7\alpha_2)}{3 \cdot 1} + 1 = \frac{4}{3}\alpha_1 + \frac{7}{3}\alpha_2 + 1$$

$$d_1 = \frac{(7\alpha_2)}{3 \cdot \alpha_1} + 2 = \frac{7}{3} \frac{\alpha_2}{\alpha_1} + 2$$

$$d_2 = \frac{(30 + 3\alpha_3)}{3\alpha_2} + 3 = \frac{10}{\alpha_2} + \frac{\alpha_3}{\alpha_2} + 3$$

$$d_3 = \frac{(36)}{3\alpha_3} + 1 = \frac{12}{\alpha_3} + 1$$

Arrival Times

$$t_0 = d_0$$

$$t_1 = \max(t_0, d_{1w}) + d_1$$

$$t_2 = \max(t_0, t_1) + d_2$$

$$t_3 = t_2 + d_3$$

$$t_3 = \max(t_0, t_1) + d_2 + d_3$$

$$= \max(d_0, \max(d_0, d_{1w}) + d_1) + d_2 + d_3$$

$$t_3 = \max(d_0, \max(d_0, d_{in}) + d_1) + d_2 + d_3$$

Minimize t_3 subject to above constraints with d_1, d_2, d_3 as the independent variables

Actually in synthesis we really want to minimize AREA (or energy) subject to constraint on t_3 .


So we could craft optimization problem to be minimize sum of d_1, d_2, d_3 (proxy for area) subject to constraint:

$$t_{\text{clk period}} > \max(d_0, \max(d_0, d_{in}) + d_{1,2}) + d_2 + d_3$$


↳ clock period constraint

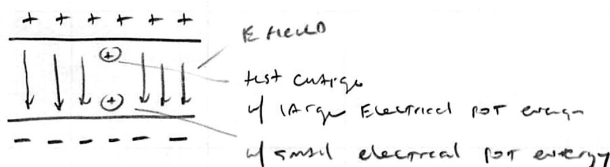3. Energy

- Energy is a measure of work
- Power is the rate at which work is done




Electric Potential Energy	Capacity for doing work which arises from position of a charge in an electric field	Joules
Electric Potential	Electric potential energy of a position per unit charge	Volts $1V = 1J/C$ $\Delta V = \Delta E/Q$
Current	Rate at which charge flows past position	Amps $1A = 1C/S$ $I = Q/\Delta t$
Power	Rate at which electric energy is supplied or consumed	Watts $1W = 1J/S$ $P = \Delta E/\Delta t = \frac{\Delta V \cdot Q}{Q/\Delta t} = VI$

 

$$E = \int_0^T P(t) dt$$


Energy Stored on a Capacitor

 

$$\begin{aligned}
 E_C &= \int_0^\infty P(t)dt = \int_0^\infty V(t)I(t)dt \\
 &= \int_0^\infty V(t) \frac{dQ}{dt} dt = \int_0^\infty V(t) \frac{Cdv}{dt} dt \\
 &= C \int_0^{V_{DD}} V(t)dV = \frac{1}{2} CV_{DD}^2
 \end{aligned}$$

- So on $1 \rightarrow 0$ input transition, $\frac{1}{2} CV_{DD}^2$ is stored on capacitor
- This energy is released on $0 \rightarrow 1$ input transition

Energy Delivered From Power Supply

 

$$\begin{aligned}
 E_{\text{supply}} &= \int_0^\infty P(t)dt = \int_0^\infty V_{DD}I(t)dt \\
 &= V_{DD} \int_0^\infty \frac{dQ}{dt} dt = V_{DD} \int_0^\infty \frac{Cdv}{dt} dt \\
 &= CV_{DD} \int_0^{V_{DD}} dV = CV_{DD}^2
 \end{aligned}$$

- $0 \rightarrow 1$ output transition
 - CV_{DD}^2 energy is delivered from power supply
 - half this energy dissipated as heat in PMOS
 - half this energy is stored on the capacitor
- $1 \rightarrow 0$ output transition
 - no energy is delivered from power supply
 - remaining energy on capacitor dissipated as heat in NMOS

- On average, each bit transition requires $\frac{1}{2}CV_{DD}^2$
- Let α be the **activity factor**, probability of a bit transitions per cycle

$$E_{\text{node}} = \alpha \frac{1}{2} CV_{DD}^2$$


Power Consumption

$$\begin{aligned} P_{\text{tot}} &= P_{\text{switching}} + P_{\text{static}} \\ &= \alpha f \frac{1}{2} CV_{DD}^2 + V_{DD} I_{\text{off}} \end{aligned}$$

- Sometimes engineers will assume α is the probability of just a $0 \rightarrow 1$ output transition instead of the probability of any transition
 - α = probability of any transition
 - α' = probability of a $0 \rightarrow 1$ transition only
- If you use α' then do not include the factor of $1/2$
- Note that book uses α but it is really α' in our notation!

Comparing Energy

 - Calculate the total switched cap in worst case




g	10/3	1
p	8	1
G	10/3	
H	1	
B	1	
F	10/3	
\hat{f}	1.8	

$$C_{\text{inv},g} = \frac{1}{1.8} \times 10 = 5.6$$

$$C_{\text{nand},g} = \frac{10/3}{1.8} \times 5.6 = 10.4$$
 
$$\begin{aligned} C_{\text{tot},g} &= C_{\text{inv},g} + 8C_{\text{nand},g} \\ &= 88.8C \end{aligned}$$



g	2	5/3
p	4	2
G	10/3	
H	1	
B	1	
F	10/3	
\hat{f}	1.8	

$$C_{\text{nor},g} = \frac{5/3}{1.8} \times 10 = 9.3$$


$$C_{\text{nand},g} = \frac{2}{1.8} \times 9.3 = 10.3$$

$$\begin{aligned} C_{\text{tot},g} &= 2C_{\text{nor},g} + 8C_{\text{nand},g} \\ &= 101C \end{aligned}$$


- To determine parasitic cap need to understand how gate cap is distributed across transistors

3. Energy


inverter

 


8 input NAND gate

 

2 input NOR gate

 

4 input NAND gate

 

$$E_{\text{node}} = \alpha \frac{1}{2} C V_{DD}^2$$

- Assume $\alpha = 0.1$ and $V_{DD} = 1\text{V}$ for both
- Only difference is amount of switched cap
- For 8-input NAND topology

$$C_{\text{tot}} = C_{\text{tot},g} + C_{\text{tot},p} = 88.8 + (5.6 + 24.96) = 119.36\text{C}$$

- For 4-input NAND topology

$$C_{\text{tot}} = C_{\text{tot},g} + C_{\text{tot},p} = 101 + (11.16 + 2 \times 20.58) = 153.32\text{C}$$


- So second topology requires $\approx 30\%$ more energy in the *worst* case
- Worst case is when all capacitance is switched
- This ignores the energy for switching the output load
- Let's assume $C = 0.5\text{ fF}$ (see extra notes)
- Assume clock frequency is 500 MHz

$$E = \alpha \frac{1}{2} C V_{DD}^2 = 0.1 \times \frac{1}{2} \times 120\text{C} \times \frac{0.5\text{fF}}{C} \times (1\text{V})^2 = 3\text{fJ}$$

$$P = \alpha f \frac{1}{2} C V_{DD}^2 = (0.5 \times 10^9)(30 \times 10^{-15}) = 1.5\mu\text{W}$$

Activity Factors

 - Previous example used fixed $\alpha = 0.1$ for all nodes
- Can improve accuracy by:
 - Propagate activity factor of inputs to internal nodes
 - Use RTL to calculate activity of inputs, then propagate
 - Use gate-level simulation to find activity of each node



P_i = probability node is one on cycle i

$\bar{P}_i = 1 - P_i$ = probability node is zero on cycle i

$$\alpha = P_{i-1}\bar{P}_i + \bar{P}_{i-1}P_i$$

$$\alpha' = \bar{P}_{i-1}P_i$$

- Assuming inputs have uncorrelated random data
- Each of these is equally likely: $0 \rightarrow 0$, $0 \rightarrow 1$, $1 \rightarrow 0$, $1 \rightarrow 1$

$$\alpha = P_{i-1}\bar{P}_i + \bar{P}_{i-1}P_i = 0.5$$

$$\alpha' = \bar{P}_{i-1}P_i = 0.25$$


$$\alpha' = \frac{1}{2}\alpha$$

Output Activity Factor of NAND2

- Calculate output activity factor of a NAND2 gate
- Assume inputs are uncorrelated random data
- Output of NAND2 is zero if both inputs one, otherwise output is one

$$\begin{aligned}\alpha'_{out} &= \overline{P}_{out,i-1} P_{out,i} \\ &= (P_A P_B)(1 - P_A P_B) \\ &= (0.5 \times 0.5)(1 - 0.5 \times 0.5) \\ &= (0.25)(1 - 0.25) \\ &= 0.1875\end{aligned}$$

Output Activity Factor of NAND8

 

4. Area

- Sum the transistor widths across all transistors in design
- Use standard cell footprints