ECE 6745 Complex Digital ASIC Design Topic 12: Synthesis Algorithms

Christopher Batten

School of Electrical and Computer Engineering Cornell University

http://www.csl.cornell.edu/courses/ece6745

Technology-Dependent Synthesis

Course Structure



Part 3: CAD Algorithms



Step 1: Single Assignment Form

```
// 1b inputs: y, z, a, q
// 2b inputs: f
// 3b inputs: q, c, b, e
wire x = y \& \& z;
wire [2:0] b
  = (a) ? {2'b0,x} : c;
wire [2:0] d, h;
always @(*) begin
  d = b + e;
  if (q) d = 3'b101;
  if (f)
  h = 3' b0;
  else
   h = q << 1;
```

For each output, create exactly one assignment that is a function only of the inputs

```
wire x = y && z;
wire [2:0] b
= (a) ? {2'b0,x} : c;
wire [2:0] d
= (q) ? 3'b101
      : ((a) ? {2'b0,x} : c)
      + e;
wire [2:0] h
= (f) ? 3'b0 : ( q << 1 );</pre>
```

end

Step 2: Bit Blast Outputs

```
// 1b inputs: y, z, a, q Generate separate assignment for each
// 2b inputs: f
// 3b inputs: g, c, b, e
wire x = y \& \& z;
wire [2:0] b
  = (a) ? \{2'b0,x\} : c;
wire [2:0] h
 = (f) ? 3'b0
```

: (q << 1);

```
bit, removes arithmetic operators leaving
only boolean operators (assume ternary
operator is short hand for equivalent
boolean operator)
```

wire x = y & & z;wire b[0] = (a) ? x : c[0];

wire b[1] = (a) ? 1'b0 : c[1]; wire b[2] = (a) ? 1'b0 : c[2];wire h[0] = (f[0]|f[1]) ? 1'b0 : 1'b0;wire h[1] = (f[0]|f[1]) ? 1'b0 : q[0];

wire h[2] = (f[0]|f[1]) ? 1'b0 : q[1];

RTL to Logic Synthesis

Technology-Independent Synthesis

Technology-Dependent Synthesis

RTL Datapath Synthesis

wire [15:0] a= b + c;



Ripple-Carry



Carry Lookahead



(c) Kogge-Stone

(f) Ladner-Fischer

Parallel-Prefix Tree-Based

Adapted from [Weste'11]

DWBB Quick Reference

DW01_add

Adder

DW01_add

Adder

- Parameterized word length
- Carry-in and carry-out signals



Building Block

Table 1-1Pin Description

Pin Name	Width	Direction	Function
А	width bit(s)	Input	Input data
В	width bit(s)	Input	Input data
CI	1 bit	Input	Carry-in
SUM	width bit(s)	Output	Sum of (A + B + CI)
СО	1 bit	Output	Carry-out

Table 1-2 Parameter Description

Parameter	Values	Description
width	≥1	Word length of A, B, and SUM

Table 1-3 Synthesis Implementations^a

Implementation	Function	License Feature Required
rpl	Ripple-carry synthesis model	none
cla	Carry-look-ahead synthesis model	none
pparch	Delay-optimized flexible parallel-prefix	DesignWare

a. During synthesis, Design Compiler will select the appropriate architecture for your constraints. However, you may force Design Compiler to use one of the architectures described in this table. For more details, please refer to the DesignWare Building Block IP User Guide.

Example from Synopsys DesignWare

RTL Datapath Synthesis directly transforms arithmetic operators into technology independent optimized gate-level netlists

Adapted from [Synopsys'11]

Technology-Dependent Synthesis

Part 3: CAD Algorithms



- Two-level boolean minimization based on assumption that reducing the number of product terms in an equation and reducing the size of each product term will result in a smaller/faster implementation
- Optimizing finite-state machines look for equivalent FSMs (i.e., FSMs that produce the same outputs give the same sequence of inputs) that have fewer states
- FSM state encodings minimize implementation area (= size of state storage + size of logic to implement next state and output functions).

Note that none of these optimizations are completely isolated from the target technology, but experience has shown that it's advantageous to reduce the size of the problem as much as possible before starting the technology-dependent optimizations.

Karnaugh Map Method Review

- 1. Choose an element of ON-set not already covered by an implicant
- 2. Find "maximal" groups of 1's and X's adjacent to that element. Remember to consider top/bottom row, left/right column, and corner adjacencies. This forms prime implicants.
- Repeat steps 1 and 2 to find all prime implicants
- S. Revise the 1's elements in the K-map. If covered by single prime implicant, it is *essential*, and participates in the final cover. The 1's it covers do not need to be revisited.
- 4. If there remain 1's not covered by essential prime implicants, then select the smallest number of prime implicants that cover the remaining 1's

Technology-Dependent Synthesis

Karnaugh Map Method Example







Primes around A B C' D Primes around A B' C' D' Essential Primes with Min Cover

Quine-McCluskey (QM) Method

- Quine-McCluskey method is an exact alogorithm which finds a minimum-cost sum-of-products implementation of a boolean function
- Four main steps
 - 1. Generate prime implicants
 - 2. Construct prime implicant table
 - ▷ 3. Reduce prime implicant table
 - a. Remove essential prime implicants
 - b. Row dominance
 - c. Column dominance
 - d. Iterate at this step until no further reductions
 - ▷ 4. Solve prime implicant table

RTL to Logic Synthesis

Technology-Independent Synthesis

Technology-Dependent Synthesis

QM Example #1 – Step 1

Start by expressing your Boolean function using O-	W	X	Y	Z	label
	0	0	0	0	0
terms (product terms with no don't care care entries).	0	1	0	1	5
For compactness the table for example 4-input, 1-	0	1	1	1	7
output function E(w x y z) chown to the right includes	1	0	0	0	8
ourpur runction i (w,x,y,z) shown to the right includes	1	0	0	1	9
only entries where the output of the function is 1 and	1	0	1	0	10
we've labeled each entry with it's decimal equivalent	1	0	1	1	11
we ve labeled each entry with he decimal equivalent.	1	1	1	0	14
	1	1	1	1	15

Look for pairs of O-terms that differ in only one bit position and merge them in a 1-term (i.e., a term that has exactly one '-' entry). Next 1-terms are examined in pairs to see if the can be merged into 2-terms, etc. Mark k-terms that get merged into (k+1) terms so we can discard them later.

1-terms	0,8	-000 [A]	2-terms:	8. 9.10.11	10[D]
	5,7	01-1 <mark>[B]</mark>		10,11,14,15	1-1-[E]
	7,15	-111 [C]		,,	
	8, 9	100-	_		
	8,10	10-0	3-terms:	none!	
	9,11	10-1			
	10,11	101-	Label	unmerged te	rms:
Example due to	10,14	1-10	these	e terms are pr	rimel
Srini Devadas	11,15	1-11	011000		
	14.15	111-			

Adapted from [Terman'02]

QM Example #1 – Step 2, Step 3a

An "X" in the prime term table in row R and column C signifies that the Oterm corresponding to row R is contained by the prime corresponding to column C.

Goal: select the minimum set of primes (columns) such that there is at least one "X" in every row. This is the classical minimum covering problem.

	Α	в	С	D	Ε	
0000	Х	•	•	•	•	→ A is essential
0101	•	Х	•	•	•	→B is essential
0111	•	х	х	•	•	
1000	Х	•	•	х	•	
1001	•	•	•	х	•	→ D is essential
1010	•	•	•	х	х	
1011	•	•	•	х	Х	
1110	•	•	•	•	х	→ E is essential
1111	•	•	х	•	Х	

Each row with a single X signifies an essential prime term since any prime implementation will have to include that prime term because the corresponding O-term is not contained in any other prime.

In this example the essential primes "cover" all the O-terms.

Adapted from [Terman'02]

Technology-Dependent Synthesis

Column Dominance

- 5 prime implicants, each covers 2 ON-set minterms
- A'C'D' and ACD are essential prime implicants, must be in final cover
- Pick min subset of remaining 3 prime implicants which covers ON-set



Karnaugh map with set of prime implicants: illustrating "column dominance"

Adapted from [Nowick'12]

Column Dominance

- Cross out columns A'C'D' and ACD since they are essential
- Each row intersected by one of the essential prime columns is also crossed out because that minterm is already covered

	A'C'D'	A'BC'	BC'D	ABD	ACD
	(0,4)	(4,5)	(5,13)	(13,15)	(11,15)
0	Х				
4	Х	Х			
5		Х	Х		
11					Х
13			Х	Х	
15				Х	Х

- BC'D covers minterm 5 and 13, but A'BC' only covers minterm 5 and ABD only covers minterm 13
- BC'D column dominates A'BC' and ABD, dominated prime implicants can be crossed out
- Only column BC'D remains

Adapted from [Nowick'12]

Row Dominance

- 4 prime implicants, no essential prime implicants
- Pick min subset of the 4 prime implicants to cover the 5 ON-set minterms



Row Dominance

- Row 3 is contained in 3 columns: A'B', A'D, and A'C
- Row 2 is covered by two of these three columns, so any prime implicant which contains row 2 also contains row 3

	A'B'	C'D	A'D	A'C
	(1,2,3)	(1,5)	(1,3,5,7)	(2,3,7)
1	Х	Х	Х	
2	Х			Х
3	Х		X	Х
5		X	Х	
7			X	Х

- Row 7 is covered by two of these three columns, so any prime implicant which contains row 7 also contains row 3
- Thus we can ignore row 3, it will always be covered as long as cover row 2 or row 7
- Cross out row 3, similarly row 1 dominates row 5 so cross out row 1

Adapted from [Nowick'12]

RTL to Logic Synthesis

Technology-Independent Synthesis

QM Example #2 – Step 1

(Column	Ι	Coli	umn II	Column III
0	0000		(0,2)	00-0	 (0,2,8,10) -0-0
2	0010		(0,8)	-000	 (0,8,2,10) -0-0
8	1000		(2,6)	0-10	 (2,6,10,14) -10
5	0101		(2,10)	-010	 (2,10,6,14) -10
6	0110		(8,10)	10-0	 (8,10,12,14) 1–0
10	1010		(8,12)	1-00	 (8,12,10,14) 1–0
12	1100		(5,7)	01-1	 (5,7,13,15) -1-1
7	0111		(5,13)	-101	 (5,13,7,15) -1-1
13	1101		(6,7)	011-	 (6,7,14,15) -11-
14	1110		(6,14)	-110	 (6,14,7,15) -11-
15	1111		(10, 14)	1-10	 (12,13,14,15) 11–
			(12,13)	110-	 (12,14,13,15) 11–
			(12, 14)	11-0	
			(7,15)	-111	 Eliminate redundant
			(13,15)	11-1	 entries in table
			(14,15)	111-	

Adapted from [Nowick'12]

RTL to Logic Synthesis			sis • Techn	ology-Independer	t Synthesis •	Technology-Dependent Synthesis			
	QM Example #2 – Step 2, Step 3a								
		B'D'(*) (0,2,8,10)	<i>CD'</i> (2,6,10,14)	<i>BD</i> (*) (5,7,13,15)	<i>BC</i> (6,7,14,15)	<i>AD'</i> (8,10,12,14)	<i>AB</i> (12,13,14,15)		
	(0)0	X							
	2	Х	Х						
	(0)5			Х					
	6		Х		Х				
	7			Х	Х				
	8	Х				Х			
	10	Х	Х			Х			
	12					Х	Х		
	13			Х			Х		
	14		Х		Х	Х	Х		
	15			Х	Х		Х		

* indicates an essential prime implicant

• indicates a distinguished row, i.e. a row covered by only 1 prime implicant

Technology-Dependent Synthesis

QM Example #2 – Step 3b, 3c, 3a

	CD'	BC	AD'	AB
	(2,6,10,14)	(6,7,14,15)	(8,10,12,14)	(12,13,14,15)
6	X	Х		
12			Х	Х
14	X	Х	Х	Х
		BC	/ 0/	A B
	(261014)	DC	AD (8 10 12 14)	AD (12.12.14.15)
	(2,0,10,14) V	(0,7,14,13) V	(8,10,12,14)	(12,13,14,13)
12	Λ	Λ	v	v
12			Λ	Λ
		CD'(**) (2,6,10,14	AD'(**) (8,10,12,14	-)
	(0)			
	(0)]	2	Х	

3.b Row Dominance – row 14 dominates both row 6 and 12; remove row 14 since if some product covers row 6, row 14 is guaranteed to be covered

3.c Column Dominance – column CD' dominates column BC (actually they co-dominate each other); remove column BC since it is redundant with column CD'

3.a Remove Essential Prime Implicants – second iteration of step 3, both remaining prime implicants are essential

 $\mathsf{F} = \mathsf{B'D'} + \mathsf{BD} + \mathsf{CD'} + \mathsf{AD'}$

Adapted from [Nowick'12]

ECE 6745

Technology-Independent Synthesis

QM Example #3 – Step 2

 $F(A, B, C, D) = \Sigma m(0, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13)$

	A'D'	B'D'	C'D'	A'C	B'C	A'B	BC'	AB'	AC'
0	X	Х	Х						
2	X	Х		X	Χ				
3				Х	Х				
4	X		Х			Х	Х		
5						Х	Х		
6	X			Х		Х			
7				Х		Х			
8		Х	Х					X	Х
9								Х	Х
10		Х			Х			Х	
11					Х			X	
12			Х				Х		Х
13							Х		Х
									Adapted from [Nowicl
			T1	2: Synthes	sis Algorith	ms			22

QM Example #3 – Step 3a, 3b, 3c, 3a

- 3a. No essential prime implicants
- 3b. Row dominance: 2>3, 4>5, 6>7, 8>9, 10>11, 12>13

	A'D'	B'D'	C'I	D' A'	C B'	C \Box	A'B	BC'	AB'	-
0	Х	Х	Х							
3				Х	х х	K				
5							Х	Х		
7				Х	K		Х			
9									Х	
11					Х	K			Х	
13								Х		
(0)0	A'D'	'(**) K	A'C	B'C	A'B	BC	"	AB'	AC'	
(o)0 3	A'D' X	(**) K	<i>A'C</i> X	<i>B'C</i> X	A'B	BC	11 <u>-</u>	1 <i>B'</i>	AC'	
(0)0 3 5	A'D' X	<u>'(**)</u> K	A'C X	B'C X	A'B X	BC X	<u>"</u>	1 <i>B'</i>	AC'	
(0)0 3 5 7	A'D'	'(**) K	A'C X X	<i>B'C</i> X	A'B X X	BC X	, <u>,</u>	1 <i>B'</i>	AC'	
(o)0 3 5 7 9	A'D'	'(**) K	A'C X X	<i>B'C</i> X	A'B X X	BC X	!!' <u></u>	А <i>В'</i> Х	<u>AC'</u> X	
(0)0 3 5 7 9 11	A'D' X	'(**) K	A'C X X	B'C X X	A'B X X	BC X	11 <u>-</u>	AB' X X	<u>AC'</u> X	

** indicates a secondary essential prime implicant

• indicates a distinguished row

3.c Column Dominance – column A'D', B'D', and C'D' dominate each other; remove any two of them

3.a Remove Essential Prime Implicants – second iteration of step 3, remove A'D'

ECE 6745

Adapted from [Nowick'12]

RTL to Logic Synthesi	is • T	Technology-Independent Synthesis				Technology-Dependent Synthesis		
	QM	Exar	nple #	#3 – S	Step 4			
	A'C	B'C	A'B	BC'	AR'	AC'		
3	Image: Non-State V	$\frac{D C}{\mathbf{V}}$						
5		7	Х	Х				
7	X		Х					
9					Х	Х		
11		X			Х			
13				Х		Х		

No essential prime implicants; no row dominance; no column dominance Cyclic covering problem – can be solved using a branch-and-bound search technique (see notes for details)

Adapted from [Nowick'12]

Heuristic Espresso Method

Quine-McCluskey

- Number of prime implicants grows rapidly with number of inputs
- ▷ Finding a minimum cover is NP-complete (i.e., computationally expensive)

Espresso

- Don't generate all prime implicants (i.e., QM step 1)
- Carefully select a subset of primes that still covers ON-set
- Heuristically explore space of covers
- Similar in spirit (but more structured) to finding primes in K-map

Redundancy in Boolean Space

- Every point in boolean space is an assignment of values to variables
- Redundancy involves inclusion or covering in boolean space
- Irredundant cover has no redundancy



Irredundant Covers vs. Minimal Covers

- Irredundant cover is not necessarily a minimal cover
- Can use reduce, expand, remove redundancy operations to explore space of irredundant covers



Espresso Algorithm

- 1. EXPAND implicants (choice of which implicants requires heuristic)
- 2. REMOVE-REDUNDANCY
- 3. REDUCE implicants (choice of which implicants requires heuristic)
- 4. EXPAND implicants (choice of which implicants requires heuristic)
- 5. REMOVE-REDUNDANCY
- 6. Goto step 3

Technology-Dependent Synthesis

Espresso Example



Initial Set of Primes found by Steps1 and 2 of the Espresso Method

4 primes, irredundant cover, but not a minimal cover!



Result of REDUCE: Shrink primes while still covering the ON-set

Choice of order in which to perform shrink is important

Technology-Dependent Synthesis

А

10

0

1

1

D

11

0

1

1

1

01

1

1

0

1

Espresso Example

AB

00

01

11

10

С

CD

00

1

1

0

1



Second EXPAND generates a different set of prime implicants

REMOVE-REDUNDANCY generates only three prime implicants!

В

Two-Level Logic vs. Multi-Level Logic

2-Level:

 $f_1 = AB + AC + AD$ $f_2 = \overline{AB} + \overline{AC} + \overline{AE}$

6 product terms which cannot be shared. 24 transistors in static CMOS

Multi-level:

Note that B + C is a common term in f_1 and f_2

K = B + C	3 Levels
$f_1 = AK + AD$	20 transistors in static CMOS
$f_2 = \overline{A}K + \overline{A}E$	not counting inverters

Adapted from [Devadas'06]

Two-Level Logic vs. Multi-Level Logic

Two-Level Logic

- At most two gates between primary input and primary output
- Real life circuits: programmable logic arrays
- Exact optimization methods: well-developed, feasible
- Heuristic methods also possible

Multi-Level Logic

- Any number of gates between primary input and primary output
- Most circuits in real life are multi-level
- ▷ Smaller, less power, and (in many cases) faster
- Exact optimization methods: few, high complexity, impractical
- Heuristic methods pretty much required

Part 3: CAD Algorithms



ECE 6745

Technology Mapping

- Once minimized logic equations, next step is to map each equation to the gates in the target standard cell library
- Classic approach uses DAG covering (K. Keutzer)
 - "Normal Form": use basic gates (e.g., 2-input NAND gates, inverters)
 - Represent logic equations as input netlist in normal form (subjective DAG) \triangleright
 - Represent each library gate in normal form (primitive DAG)
 - GOAL: Find a min cost covering of subjective DAG by primitive DAGs
- Sound algorithmic approach, but is NP-hard optimization problem



Tree Heuristic Transformation

If subject and primitive DAGs are trees, efficient algorithm can find optimum cover in linear time via dynamic programming, so use tree covering heuristic approach by partitioning graph into subtrees



ECE 6745

35 / 43

Technology Mapping Example

Problem statement: find an "optimal" mapping of this circuit:



36 / 43

Primitive DAGs for Standard-Cell Library Gates



Possible Covers





1 INV	= 2
1 NAND2	= 3
2 NAND3	= 8
1 AOI21	= _4
Area	Cost 17

Hmmm. Seems promising but is there a systematic and efficient way to arrive at the optimal answer?

Adapted from [Terman'02,Devadas'06]

Use Dynamic Programming!

Principle of optimality: Optimal cover for a tree consists of a best match at the root of the tree plus the optimal cover for the sub-trees starting at each input of the match.



Adapted from [Terman'02,Devadas'06]

Optimal Tree Covering Example



Optimal Tree Covering Example



Optimal Tree Covering Example





This matches our earlier intuitive cover, but accomplished systematically.

Refinements: timing optimization incorporating load-dependent delays, optimization for low power.

Adapted from [Terman'02, Devadas'06]

Acknowledgments

- [Weste'11] N. Weste and D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective," 4th ed, Addison Wesley, 2011.
- [Synopsys'11] "DesignWare Datapath and Building Block IP: Quick Reference," Synopsys, 2011.
- [Zhou'02] H. Zhou, Northwestern ECE 303 Advanced Digital Design, Lecture Slides, 2002.
- [Terman'02] C. Terman and K. Asanović, MIT 6.371 Introduction to VLSI Systems, Lecture Slides, 2002.
- [Nowick'12] S. Nowick, "The Quine-McCluskey Method," Columbia CSEE E6861y Computer-Aided Design of Digital Systems, Handout, 2012.
- [Devadas'06] S. Devadas, "VLSI CAD Flow: Logic Synthesis, Placement, and Routing," MIT 6.375 Complex Digital Systems Guest Lecture Slides, 2006.