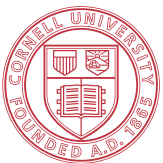


ECE 6775  
High-Level Digital Design Automation  
Fall 2023

# Field-Programmable Gate Arrays (FPGAs)




Cornell University



# Agenda


- ▶ FPGA introduction
  - Basic building blocks
  - Classical homogeneous FPGA architectures
  - Modern heterogeneous FPGA architectures

# Recap: Roofline Model

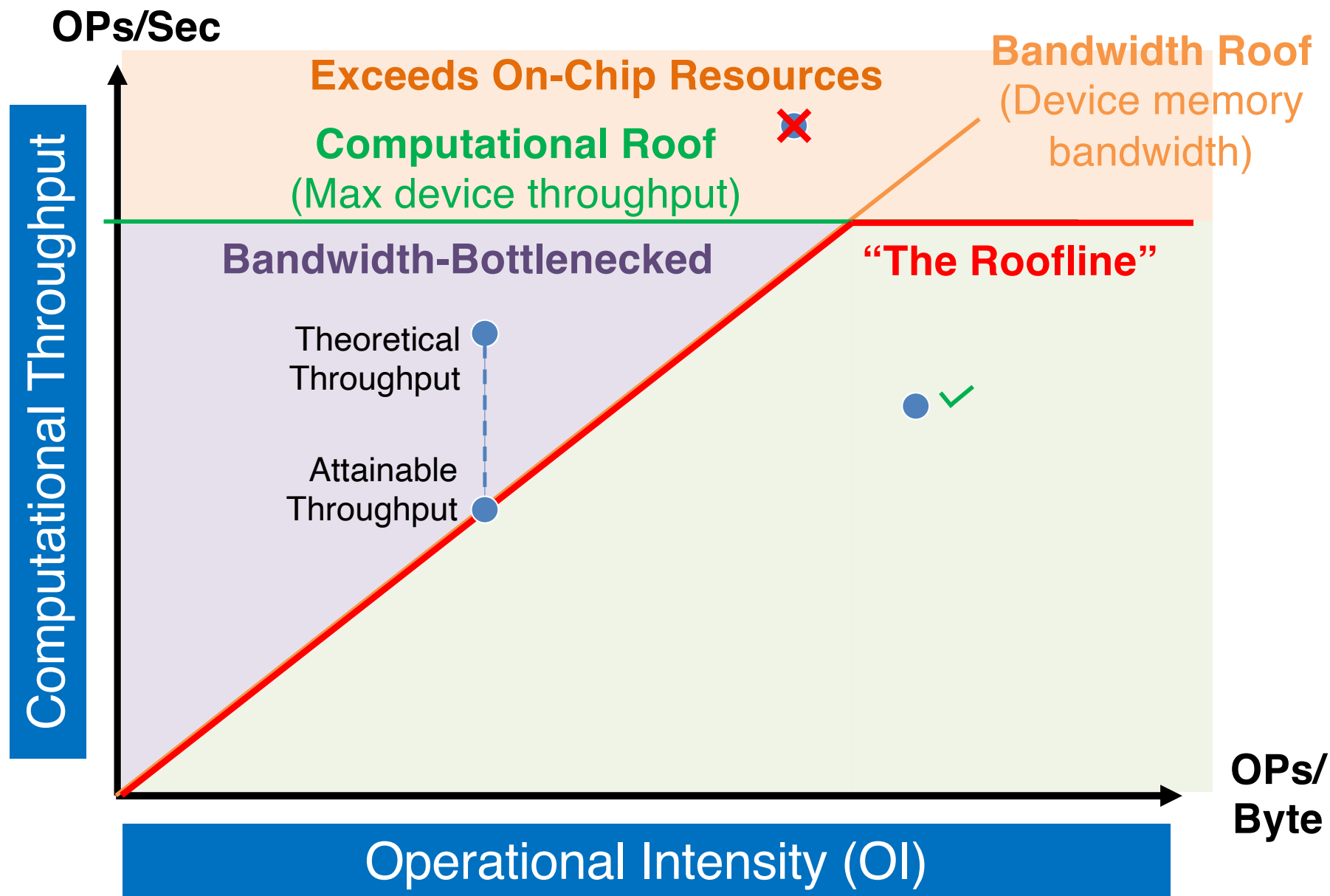

[1] S. Williams, A. Waterman, and D. Patterson, Roofline: an insightful visual performance model for multicore architectures, CACM, 2009.

 
# Exercise: OI Analysis of 2D Convolution



```
for (r = 1; r < H; r++)
  for (c = 1; c < W; c++)
    for (i = 0; i < 3; i++)
      for (j = 0; j < 3; j++)
        out[r][c] += img[r+i-1][c+j-1] * f[i][j];
```

- ▶ OI without line buffer, i.e., no data reuse
  - Number of operations =  $W \cdot H \cdot 9 \cdot 2$   
(1 mult + 1 add per pixel)
  - External memory accesses =  $W \cdot H \cdot 9$  bytes  
(assuming 1 byte per pixel in grayscale)
- ▶ OI with line buffer
  - Number of operations = ??
  - External memory accesses = ??
 
# Tradeoff between Compute Efficiency and Flexibility



# What Are FPGAs


- ▶ Field-programmable gate array
  - Can be configured to act like any circuit after manufacturing
  - Can do many things – we focus on computation acceleration




# FPGAs Come In Many Forms



PCIe-Attached

 

In-Storage

 




CPU Integrated



In-Network
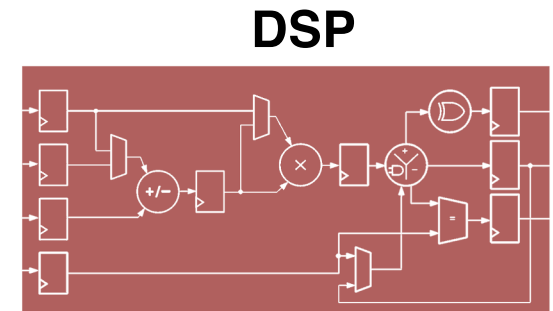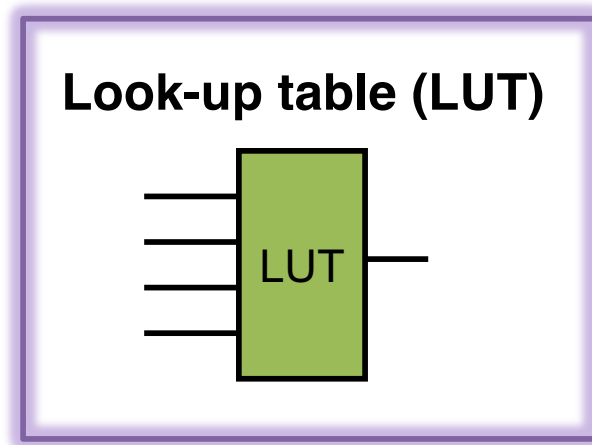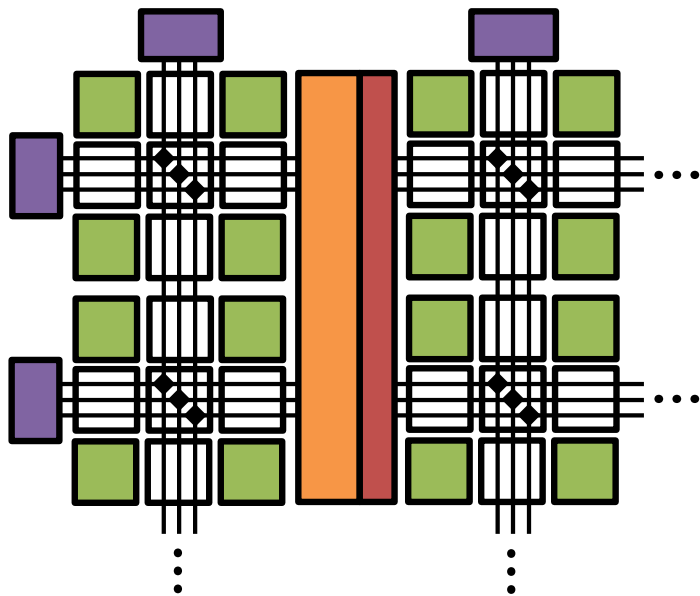
# Building Blocks of Modern FPGA Architectures

- ▶ A programmable array of logic blocks (LUT, FF), interconnects, I/Os, and dedicated blocks (BRAM, DSP)







# Counting Boolean Functions

- ▶ How many distinct 2-input 1-output Boolean functions exist?
  
- ▶ What about  $K$  inputs?

# Multiplexer as a Universal Gate


- ▶ Any function of  $k$  variables can be implemented with a  $2^k:1$  multiplexer

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

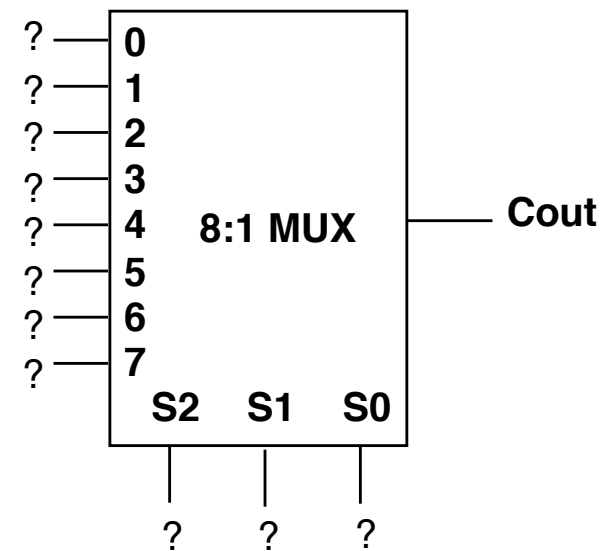 
 
# Look-Up Table (LUT)



- A k-input LUT (k-LUT) can be configured to implement any k-input 1-output combinational logic
  - $2^k$  SRAM bits
  - Delay is independent of logic function



A 3-input LUT
  
## Exercise: Implementing Logic with LUTs


- ▶ Implement a 2:1 MUX using a network of 2-input LUTs. Use the minimum number of LUTs



Building block:  
2-input LUT

 
# A Logic Element

- ▶ A k-input LUT is usually followed by a flip-flop (FF) that can be bypassed
- ▶ The LUT and FF combined form a logic element



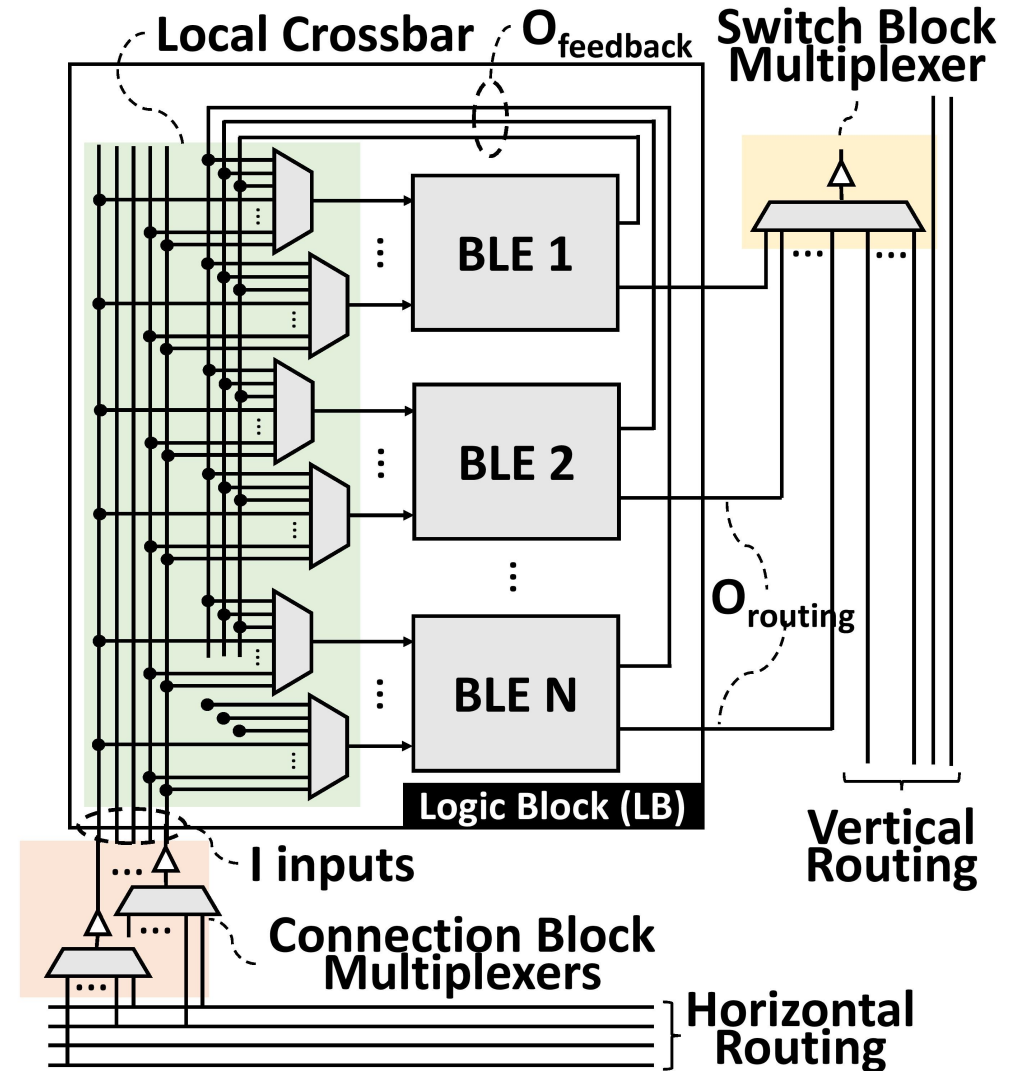
# A Logic Block


- ▶ A logic block clusters multiple logic elements



# Arithmetic Circuitry in Logic Block

 


Xilinx (now AMD)

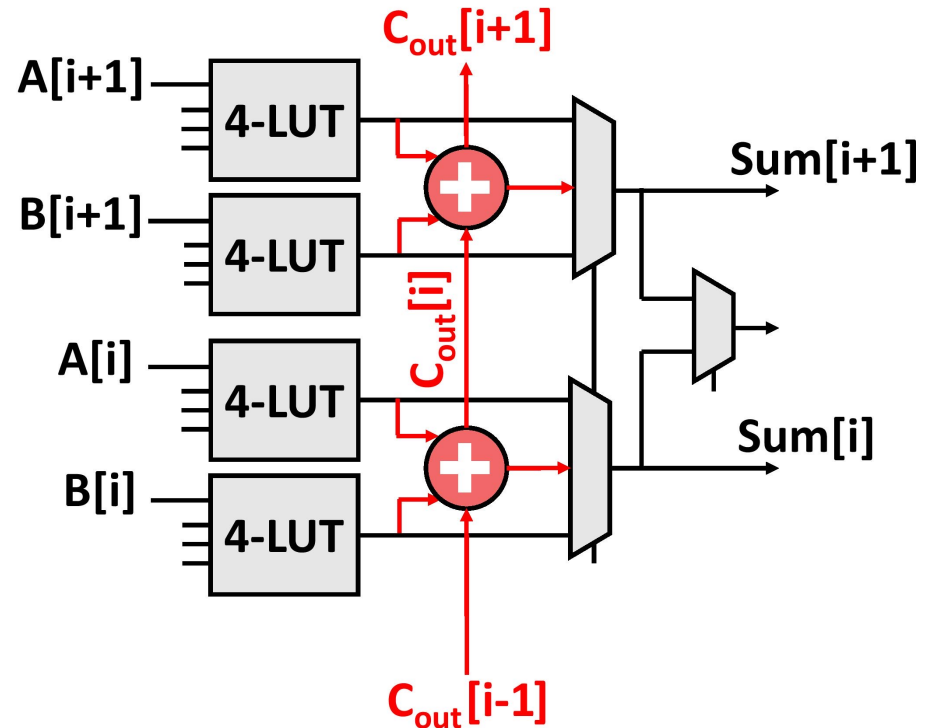


Altera (now Intel)

# Routing Architecture

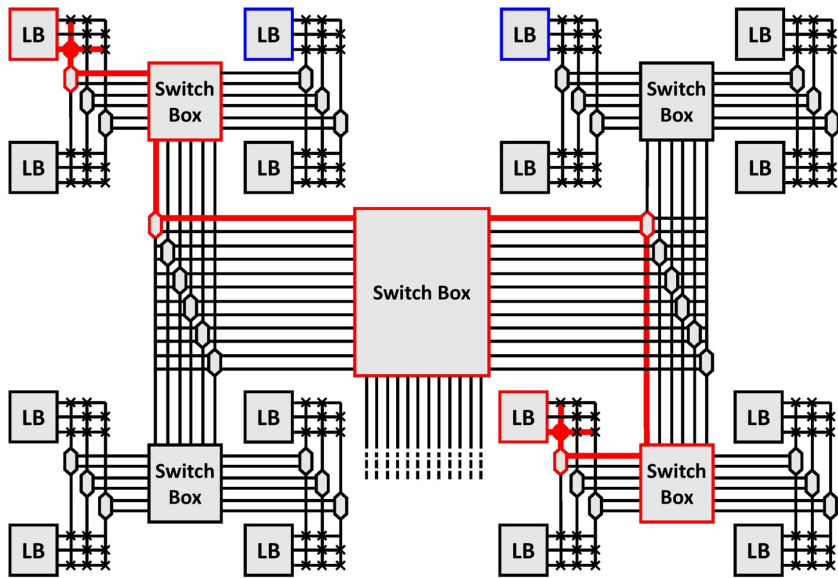

Hierarchical routing architecture


VS.

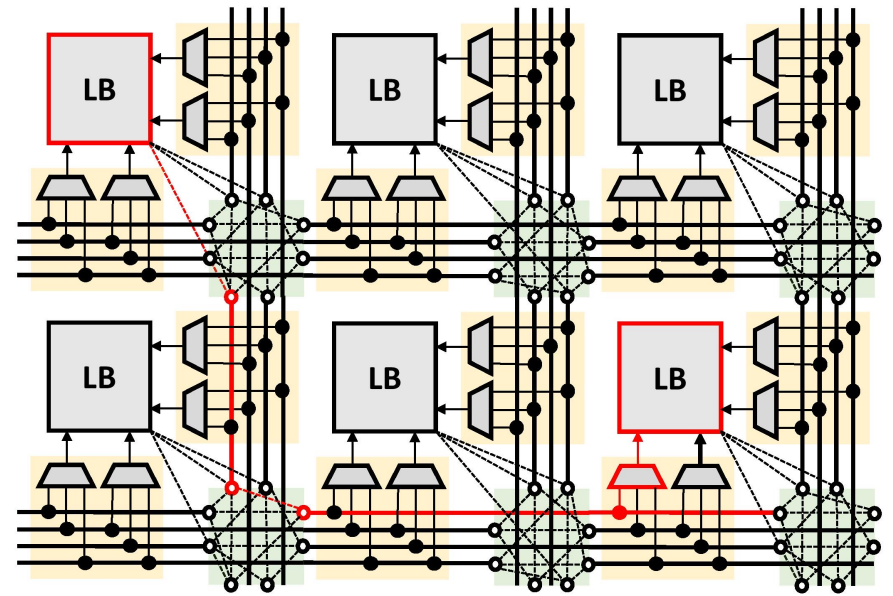

Island-style routing architecture



 
# Traditional Homogeneous FPGA Architecture


 
# Modern Heterogeneous Field-Programmable System-on-Chip (SoC)

- ▶ Island-style configurable mesh routing
- ▶ Lots of dedicated components
  - Memories/multipliers, I/Os, processors
  - Specialization leads to higher performance and lower power




[Figure credit: embeddedrelated.com]

## Dedicated DSP Blocks

- ▶ Built-in components for fast arithmetic operation optimized for DSP applications
  - Essentially a multiply-accumulate core with many other features
  - Fixed logic and connections, functionality may be configured using control signals at run time
  - Much faster than LUT-based implementation (ASIC vs. LUT)

# Example: Xilinx DSP48E Slice

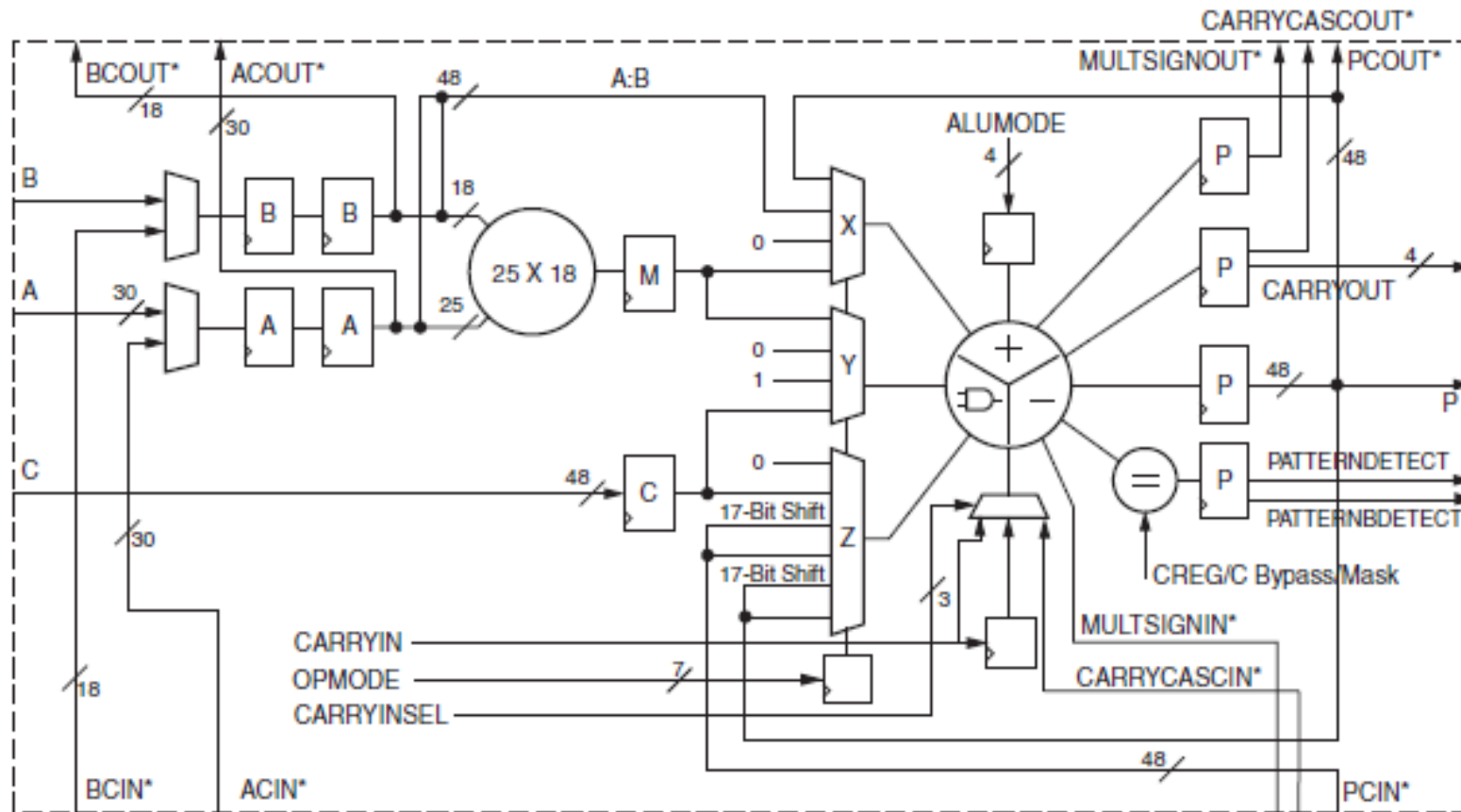


\*These signals are dedicated routing paths internal to the DSP48E column. They are not available to other DSP48E slices.

- 25x18 signed multiplier
- 48-bit add/subtract/accumulate
- 48-bit logic operations
- SIMD operations (12/24 bit)
- Pipeline registers for high speed
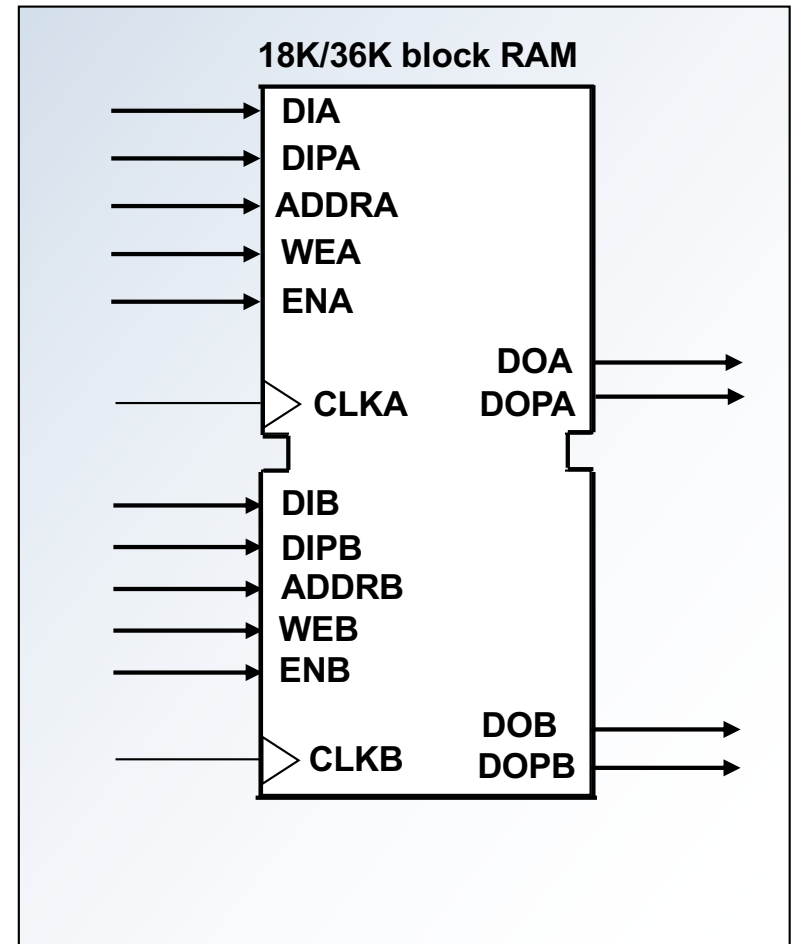
# Dedicated Block RAMs (BRAMs)


- ▶ Example: Xilinx 18K/36K block RAMs
  - 32k x 1 to 512 x 72 in one 36K block
  - Simple dual-port and true dual-port configurations
  - Built-in FIFO logic
  - 64-bit error correction coding per 36K block


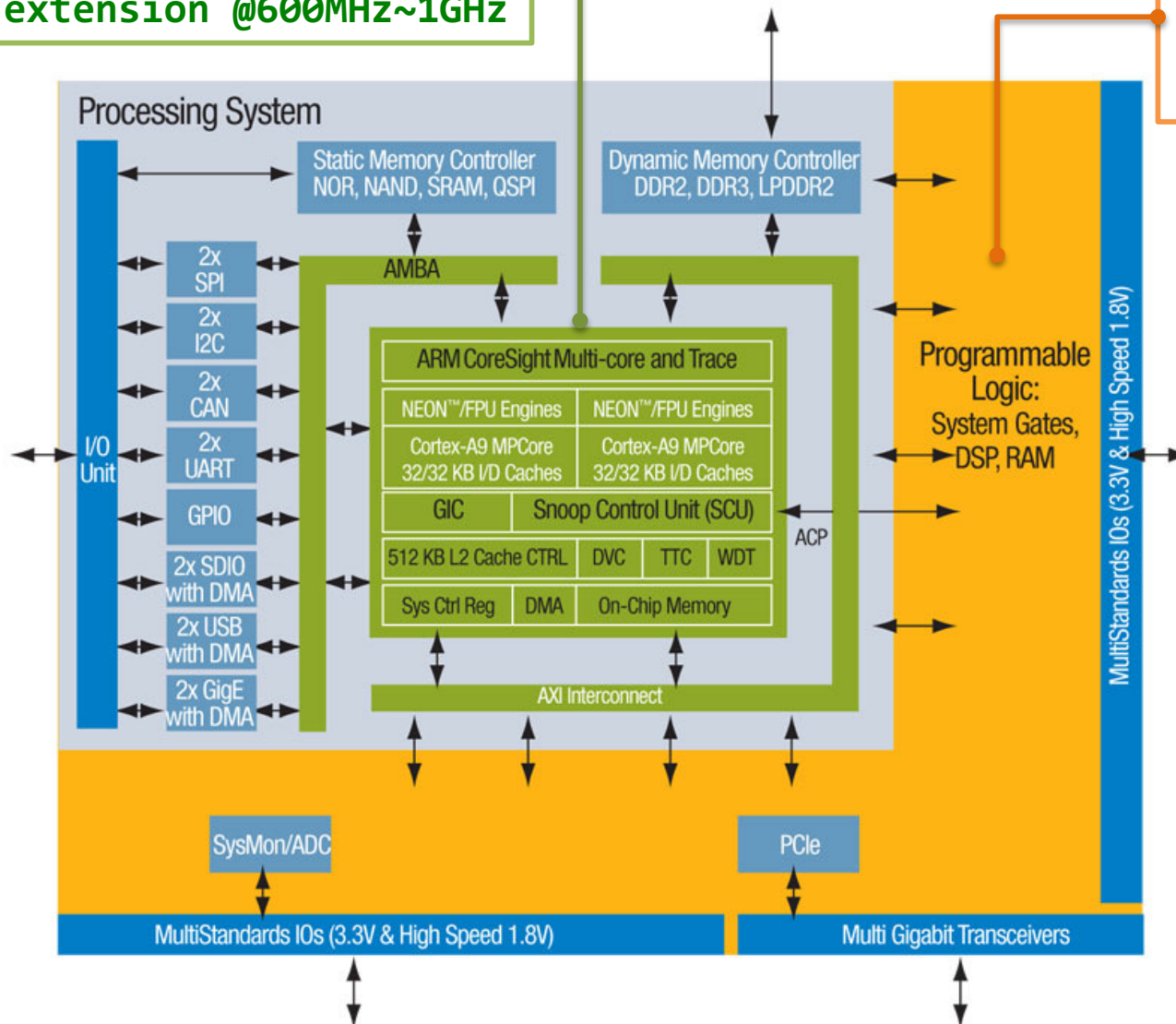
# An Embedded FPGA SoC


Dual ARM Cortex-A9 + NEON  
SIMD extension @600MHz~1GHz

Up to  
350K logic cells  
2MB Block RAM  
900 DSP48s



**Xilinx Zynq All Programmable System-on-Chip**  
[Source: AMD Xilinx]


# A Cloud FPGA Instance

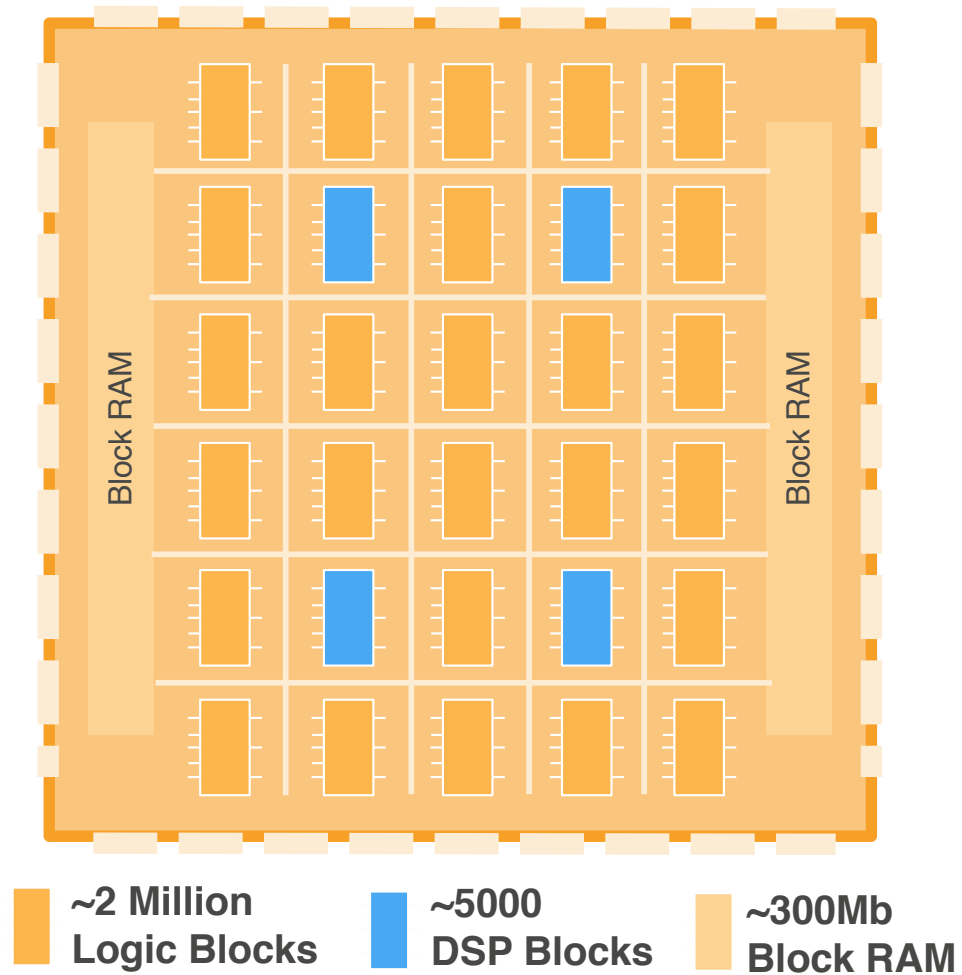

AWS F1 instance: AMD Xilinx UltraScale+ VU9P  
[Figure source: David Pellerin, AWS]

# An Even More Heterogeneous (FPGA) Accelerator

## AMD Xilinx Versal Architecture

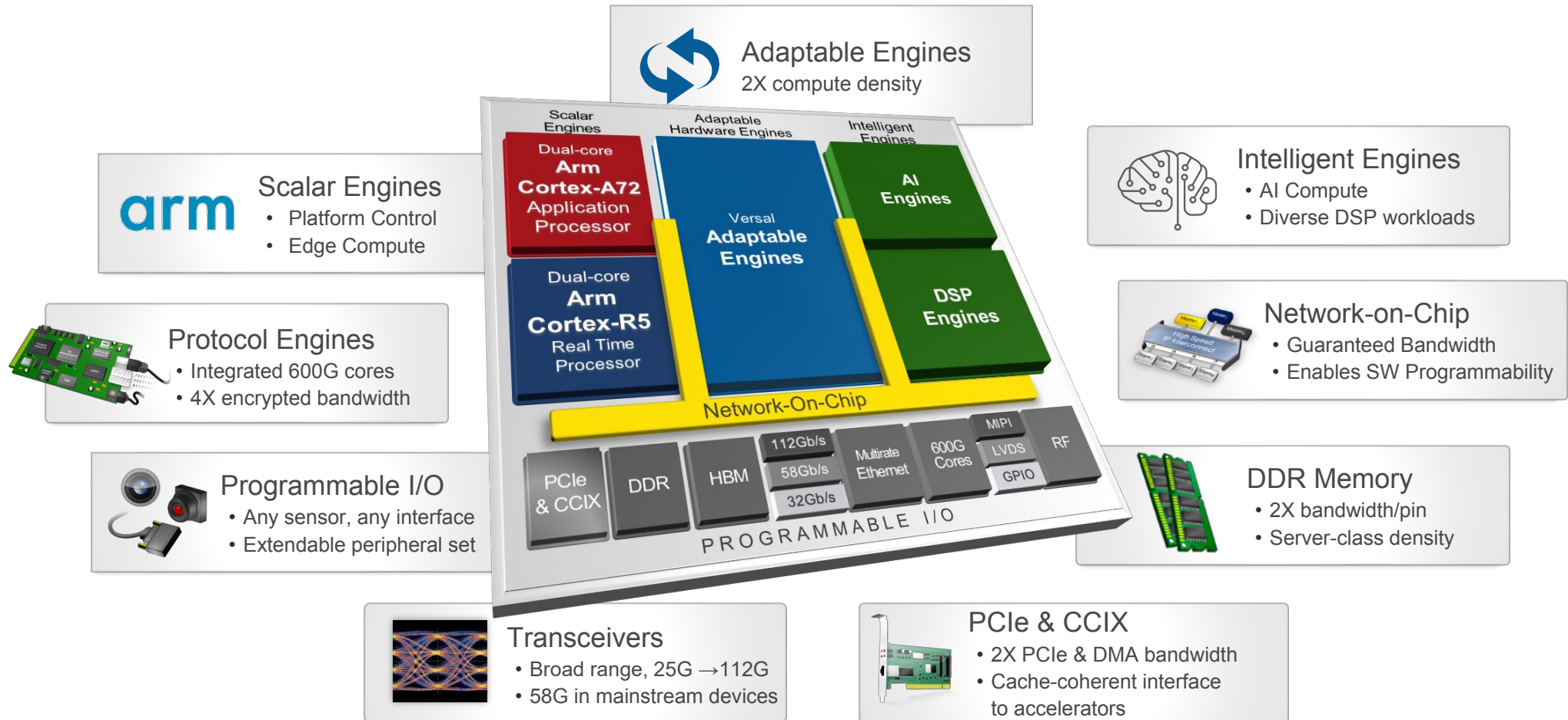



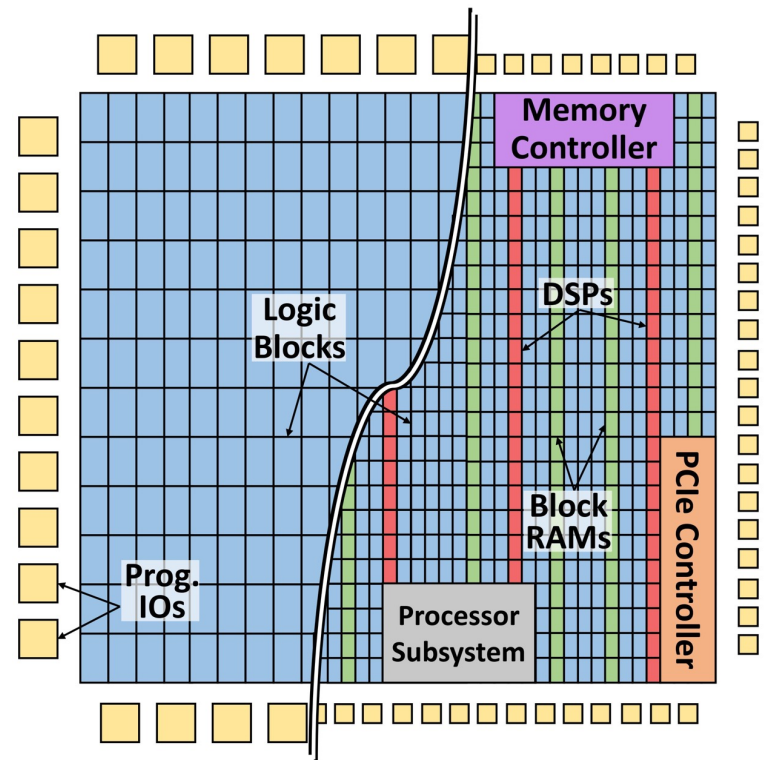
# Key Advantages of FPGA-Based Computing

- ▶ **Massive amount of fine-grained parallelism**
  - Highly parallel and/or deeply pipelined architecture
- ▶ **Silicon (re)configurable to fit the application**
  - Compute at desired numerical accuracy
  - Customized memory hierarchy

⇒ low (and often predictable) latency  
⇒ higher energy efficiency



# Next Lecture

- ▶ Analysis of Algorithms

# Acknowledgements

- ▶ These slides contain/adapt materials developed by
  - Prof. Jason Cong (UCLA)
  - Andrew Boutros and Prof. Vaughn Betz (Univ. of Toronto)
  - UCI CS295 by Prof. Sang-Woo Jun