

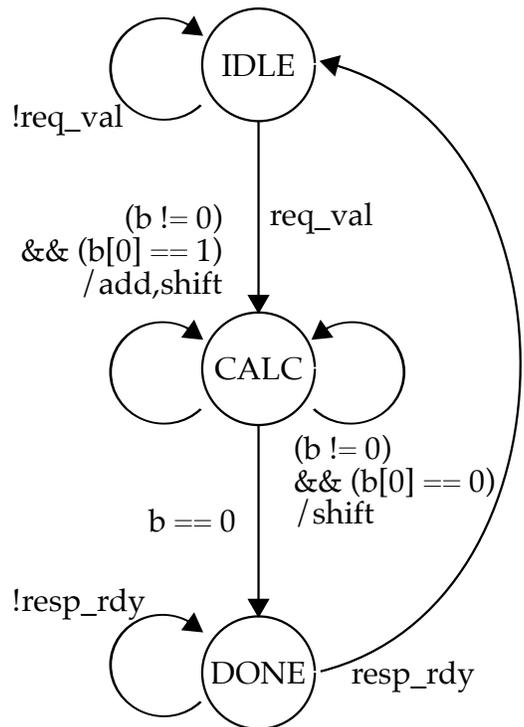
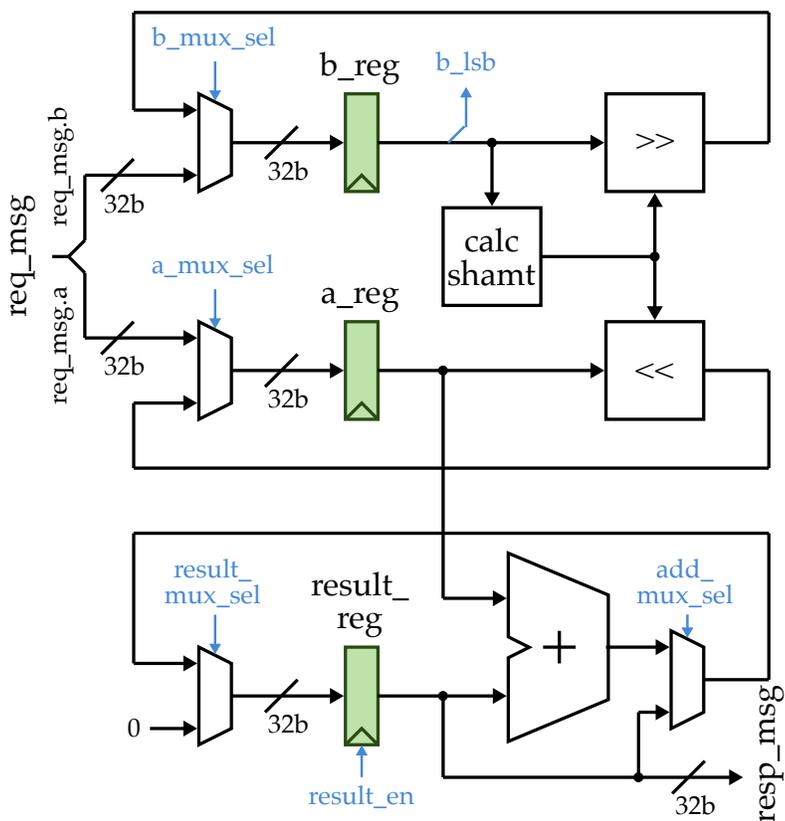


# ECE 4750 Computer Architecture

## Section 7: Open-Source Hardware

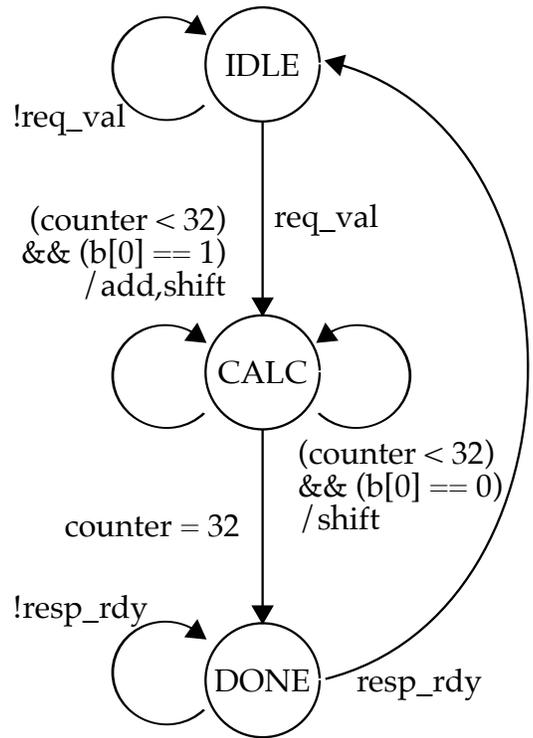

	Baseline Design	Alternative Design
<b>Total Area (um<sup>2</sup>)</b>		
- Counter		
- Left Shifter		
- Right Shifter		
- ResetReg		
- EnReg		
- Mux2		
- Reg		
- SimpleAdder		
- ZeroComparator		
- CalcShamt		
<b>Cycles/Transaction</b>		
<b>Cycle Time (ns)</b>		
<b>Time/Transaction (ns)</b>		
<b>Power (mW)</b>		
<b>Energy/Transaction (pJ)</b>		

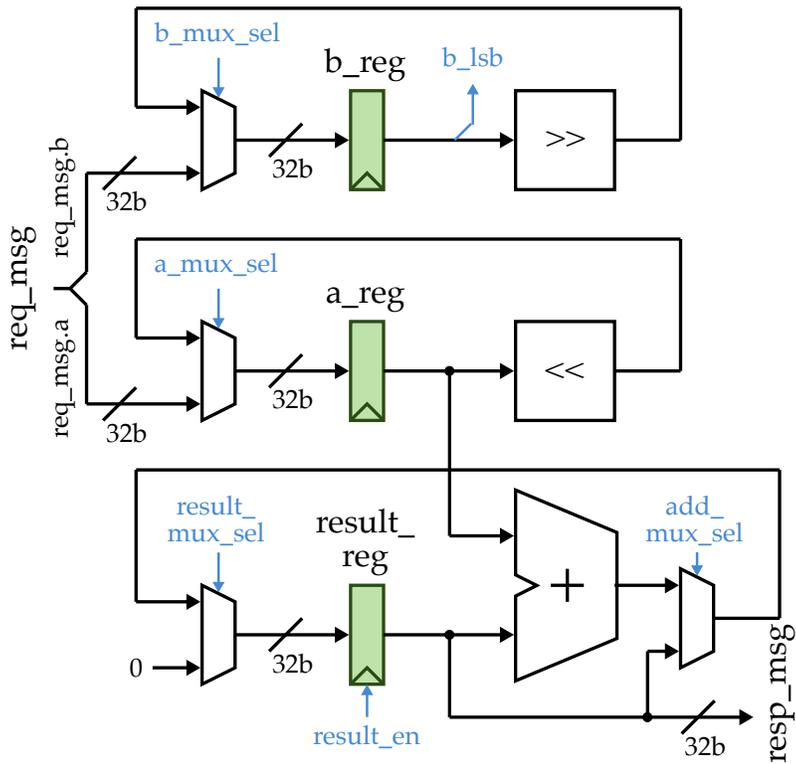